


# Lecture 12: Time and Glitches

CSE 370, Autumn 2007  
Benjamin Ylvisaker


## Where We Are

- Last lecture: Multi-Level Logic
- This lecture: Circuit Delay and Timing
- Next lecture: Adders, Comparators, ALUs
- Exam 1 on Wednesday
- Homework 4 in progress
- Lab 4 this week


## Sometimes Time Matters

 


# Glitches and Hazards

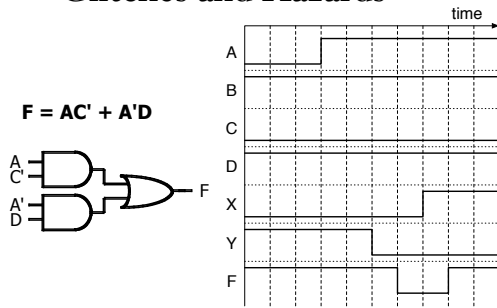

## Where Glitches Come From


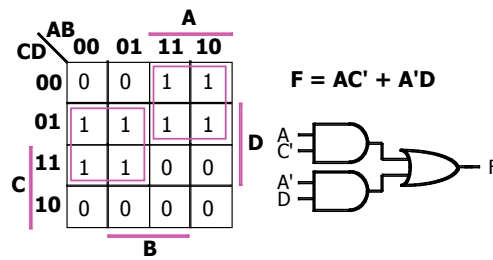


## Avoiding Glitches in 2-Level Circuits

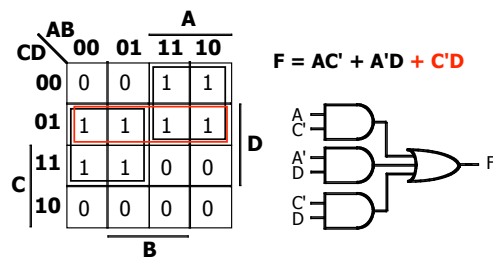

## Additional Gate Prevents Glitches

$$F = AC' + A'D + C'D$$

  

## Terminology of Hazards


- Static 1-Hazard




- Static 0-Hazard



- Dynamic Hazards

 

## A Dynamic Hazard

 

# Avoiding Dynamic Hazards

- Very hard
- Automated tools can help
- In practice, use 2-level circuits if you must avoid hazards at all costs

## Now You Try

- $F(A,B,C,D) = \neg AB + A\neg CD + \neg BCD$
- Draw waves that illustrate one input pattern/transition that can cause a glitch, and identify which gates would have to be slow or fast
- Change the circuit to make it hazard-free and draw the resulting circuit

## Thank You for Your Attention

- Read lab 4
- Study for the exam
- Continue working on homework 4
- Continue reading the book