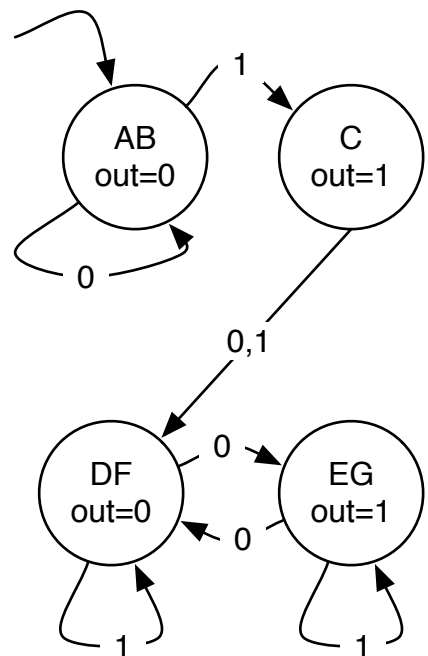


Row-matching method


Current State	Next State		output
	in=0	in=1	
A	B	C	0
B	B	C	0
C	D	F	1
D	E	D	0
E	D	E	1
F	G	F	0
G	F	G	1

merge

Result of the implication chart method (next page):



Implication chart method

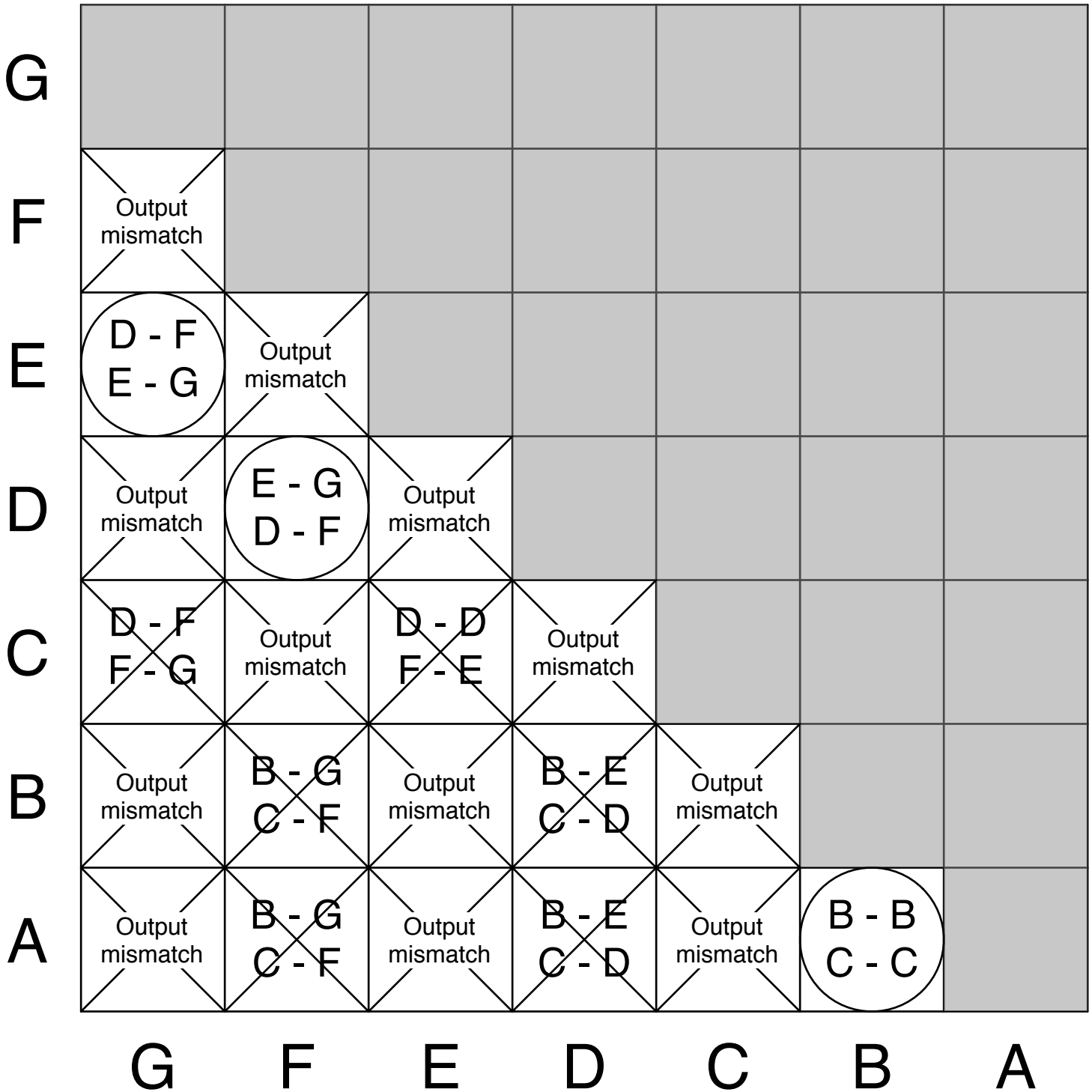

Merge: A and B, D and F, E and G