

Overview


- ◆ Last lecture
 - Finished counter design
 - ↳ Design example
 - ↳ Self-starting counters
- ◆ Today
 - Introduction to finite-state machines
 - ↳ Moore versus Mealy machines
 - ↳ Synchronous Mealy machines
 - ↳ Example: A parity checker

Finite state machines


- ◆ FSM: A system that visits a **finite** number of logically distinct states
- ◆ Counters are simple FSMs
 - Outputs and states are identical
 - Visit states in a fixed sequence
- ◆ FSMs are more complex than counting
 - Outputs can depend on current state and on inputs
 - State sequencing depends on current state and on inputs

Generalized FSM model

 - ◆ State variables (state vector) holds circuit state
 - Stored in registers
- ◆ Combinational logic computes next state and outputs
 - Next state is a function of current state and inputs
 - Outputs are functions of
 - ↳ Current state (**Moore** machine)
 - ↳ Current state and inputs (**Mealy** machine)




Moore versus Mealy machines

 

Moore machine
Outputs are a function of current state

 Outputs change synchronously with state changes




Mealy machine
Outputs depend on state and on inputs

Input changes can cause immediate output changes (**asynchronous**)

 
Example: Moore versus Mealy

- ◆ Circuits recognize $AB=10$ followed by $AB=01$
 - What kinds of machines are they?



Specifying outputs for a Moore machine

 
- ◆ Output is a function of state only
 - Specify output in the state bubble
 - Example: Detector for 01 or 10



| reset | input | current state | next state | current output |
|-------|-------|---------------|------------|----------------|
| 1 | — | — | A | 0 |
| 0 | 0 | A | B | 0 |
| 0 | 1 | A | C | 0 |
| 0 | 0 | B | B | 0 |
| 0 | 1 | B | D | 0 |
| 0 | 0 | C | E | 0 |
| 0 | 1 | C | C | 0 |
| 0 | 0 | D | E | 1 |
| 0 | 1 | D | C | 1 |
| 0 | 0 | E | B | 1 |
| 0 | 1 | E | D | 1 |

Specifying outputs for a Mealy machine

 - ◆ Output is a function of state and inputs
 - Specify outputs on transition arcs
 - Example: Detector for 01 or 10



| reset | input | current state | next state | current output |
|-------|-------|---------------|------------|----------------|
| 1 | - | - | A | 0 |
| 0 | 0 | A | B | 0 |
| 0 | 1 | A | C | 0 |
| 0 | 0 | B | B | 0 |
| 0 | 1 | B | C | 1 |
| 0 | 0 | C | B | 1 |
| 0 | 1 | C | C | 0 |

CSE370, Lecture 20

7

Comparing Moore and Mealy machines


- ◆ Moore machines
 - + Safer to use because outputs change at clock edge
 - May take additional logic to decode state into outputs
- ◆ Mealy machines
 - + Typically have fewer states
 - + React faster to inputs — don't wait for clock
 - Asynchronous outputs can be dangerous
- ◆ We will often design synchronous Mealy machines
 - Design a Mealy machine
 - Then register the outputs

CSE370, Lecture 20

8

Synchronous (registered) Mealy machine

 - ◆ Registered state and registered outputs
 - No glitches on outputs
 - No race conditions between communicating machines



CSE370, Lecture 20

9

FSM design

- ◆ Generalized counter design
 - Counter-design procedure
 1. State diagram
 2. State-transition table
 3. Next-state logic minimization
 4. Implement the design
 - FSM-design procedure
 1. State diagram and state-transition table
 2. State minimization
 3. State assignment (or state encoding)
 4. Next-state logic minimization
 5. Implement the design


CSE370, Lecture 20

10

Example: A parity checker

- ◆ Serial input string
 - OUT=1 if odd # of 1s in input
 - OUT=0 if even # of 1s in input

 1. State diagram and state-transition table



Moore-machine state diagram

| Present State | Input | Next State | Present Output |
|---------------|-------|------------|----------------|
| Even | 0 | Even | 0 |
| Even | 1 | Odd | 0 |
| Odd | 0 | Odd | 1 |
| Odd | 1 | Even | 1 |

CSE370, Lecture 20

11

Parity checker (con't)

2. State minimization: Already minimized
 - Need both states (even and odd)
 - Use one flip-flop
3. State assignment (or state encoding)

| Present State | Input | Next State | Present Output |
|---------------|-------|------------|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

Assignment
Even = 0
Odd = 1

CSE370, Lecture 20


12

Parity checker (con't)

4. Next-state logic minimization


- Assume D flip-flops
- Next state = (present state) XOR (present input)
- Present output = present state

5. Implement the design

 

Implementation

 - ◆ Can map FSMs to programmable logic devices
- Macro-cell = DFF + two-level logic



- ◆ Other options: Gate arrays, semicustom ICs, etc.