

Lecture 15

◆ Logistics

- HW6 is out, due Wednesday

◆ Last lecture

- Continuing on basic building blocks for sequential logic
 - ✦ Latches and flip-flops
 - ✦ Clear/Preset
 - ✦ State Diagram
 - ✦ Asynchronous inputs

◆ Today

- Continue more on building blocks for sequential logic
 - ✦ Timing issues with asynchronous inputs and some solutions
 - ✦ Registers
 - ✦ Summary of sequential logic building blocks

Asynchronous inputs

◆ Clocked circuits are **synchronous**



◆ Unclocked circuits or signals are **asynchronous**

◆ Synchronous circuits have asynchronous inputs

- Reset signal, memory wait, user input, etc.
- Inputs can change at any time
 - ✦ We must **synchronize the input** to our clock
 - ✦ Inputs can violate flip-flop setup/hold times

Timing terminology and constraints

- **Setup time t_{su}** : Amount of time the input must be stable before the clock transitions high (or low for negative-edge triggered FF)
- **Hold time t_h** : Amount of time the input must be stable after the clock transitions high (or low for negative-edge triggered FF)
- **Clock width t_w** : Clock width that must be met
- **Propagation delays t_{plh} and t_{phi}** : Propagation delay (high to low, low to high)

 
 


CSE370, Lecture 15

3

Synchronizer failure

  - ◆ Occurs when input changes near clock edge
 - Input is neither 1 or 0 when clock goes high
 - Output may be neither 0 or 1
 - ✦ May stay undefined for a long time
 - Undefined state is called **metastability**




CSE370, Lecture 15

4


Minimizing synchronizer failures

 - ◆ Failure probability can never be zero
 - Cascade two (or more) flip-flops
 - ↳ Effectively synchronizes twice
 - ↳ Both would have to fail for system to fail



Cascading flip-flops

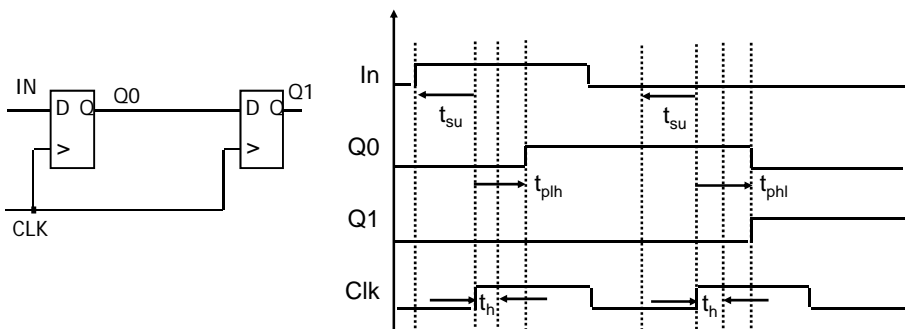
- ◆ Flip-flop propagation delays exceed hold times
 - Second stage commits its input before input changes



Side note: Clock skew

◆ Goal: Clock all flip-flops at the same time

 - Difficult to achieve in high-speed systems
 - ↳ Clock delays (wire, buffers) are comparable to logic delays
- Problem is called **clock skew**




Original state: IN = 0, Q0 = 1, Q1 = 1
 Next state: Q0 = 0, Q1 = 0 (should be Q1 = 1)

- Avoiding clock skew: design identical delays

Handling asynchronous inputs


◆ Never fan-out asynchronous inputs

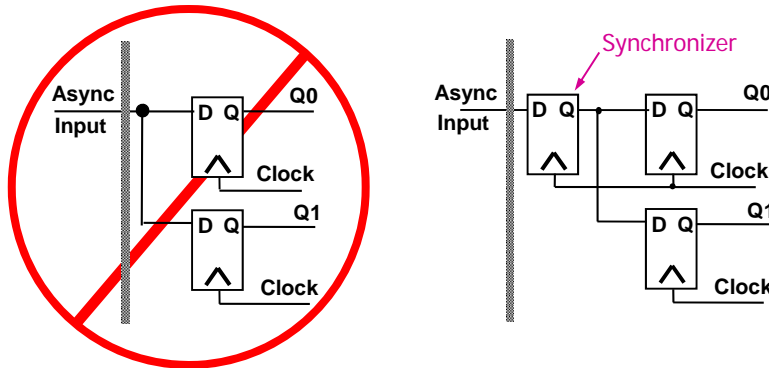- Synchronize at circuit boundary
- Fan-out synchronized signal



One more important concept: Debouncing

 - ◆ Switch inputs bounce
 - i. e. don't make clean transitions
- ◆ Can use SR latch for debouncing
 - Eliminates dynamic hazards
 - "Cleans-up" inputs



CSE370, Lecture 15

9

Summary:

Timing issues with asynchronous inputs

- ◆ For sequential logic circuits, timing issues have to be considered.
- ◆ Inputs are often asynchronous and can cause problems.
- ◆ Different amount of delay at different part of the circuit can cause problems also.
- ◆ Solutions:
 - Cascade flip flops in series
 - Incorporate RS latch for debouncing
 - Design to keep timing alignment in mind (length of cable, etc)

CSE370, Lecture 15


10

Registers

- ◆ Group of storage elements read/written as a unit.
 - Store related values (e.g. a binary word)
- ◆ Collection of flip-flops with common control
 - Share clock, reset, set lines
- ◆ Example:
 - Storage registers
 - Shift registers
 - Counters


Storage registers

 - ◆ Basic storage registers uses flip flops
- ◆ Example: 4 bit storage register




Shift registers

 - ◆ Hold successively sampled input values
 - Delays values in time
 - Example: 4-bit shift register
 - ✦ Stores 4 input values in sequence




Shift-register applications

 - ◆ Parallel-to-serial conversion for signal transmission




 - ◆ Pattern recognition (circuit recognizes 1001)




Counters

 - ◆ Ring counter: Sequence is 1000, 0100, 0010, 0001
 - Assuming one of these patterns is the starting state




 - ◆ Johnson counter: Sequence is 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000



A binary counter

- ◆ Has logic between flip-flops

 

Summary: Sequential-logic building blocks

- ◆ Know latches and flip-flops
- ◆ Know clocks, timing, timing diagrams
- ◆ Understand asynchronous inputs
- ◆ Know basic registers