

# Lecture 8

## ◆ Logistics

- HW2 due Friday
- Shorter HW3 posted--- due Monday (materials covered in midterm1) sol'n out on Monday, late assignment not accepted
- Verilog tutorial (overview + handout): provided with Lab 4
- Schedule shift: adjustment on the web
- Midterm 1: Wednesday in class --- materials up to Lecture 9
- Review session on Tuesday? Time?

## ◆ Last lecture

- K-maps, don't cares, POS K-maps

## ◆ Today

- K-maps 5, 6 dimensions
- "Switching-network" logic blocks (multiplexers/demultiplexers)
- Programmable logic devices (PLDs) --- sneak peak

# Karnaugh Maps, 6 dimensions

K-maps become 3D for 5 & 6 variables

		CD			
	EF	00	01	11	10
AB = 00	00	0	0	0	0
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	0	0

		CD			
	EF	00	01	11	10
AB = 01	00	1	0	0	0
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	0	0


OUTPUT =  
 $A'BC'D'F' +$   
 $CF + BC'D'E$

		CD			
	EF	00	01	11	10
AB = 11	00	0	0	0	0
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	0	0

		CD			
	EF	00	01	11	10
AB = 10	00	0	0	0	0
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	0	0
 
## Switching-network logic blocks


- ◆ Multiplexer (MUX)
  - Routes one of many inputs to a single output
  - Also called a *selector*
- ◆ Demultiplexer (DEMUX)
  - Routes a single input to one of many outputs
  - Also called a *decoder*



We construct these devices from:  
(1) logic gates  
(2) networks of transistor switches
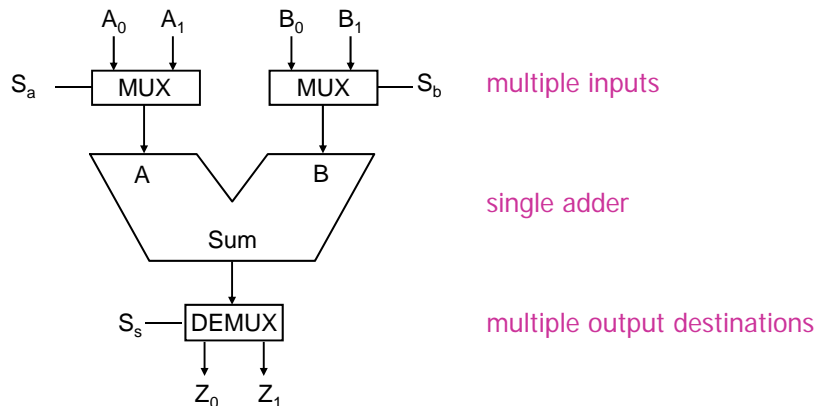
## Rationale: Sharing complex logic functions

- ◆ Share an adder: Select inputs; route sum



# Multiplexers

## ◆ Basic concept


- $2^n$  data inputs;  $n$  control inputs ("selects"); 1 output
- Connects one of  $2^n$  inputs to the output
- "Selects" decide which input connects to output
- Two alternative truth-tables: **Functional** and **Logical**

Example: A 2:1 Mux

**Functional** truth table

**Logical** truth table

$$Z = SIn_1 + S'In_0$$

 


S	Z
0	$In_0$
1	$In_1$


$In_1$	$In_0$	S	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Logic-gate implementation of multiplexers

2:1 mux

 


4:1 mux

 

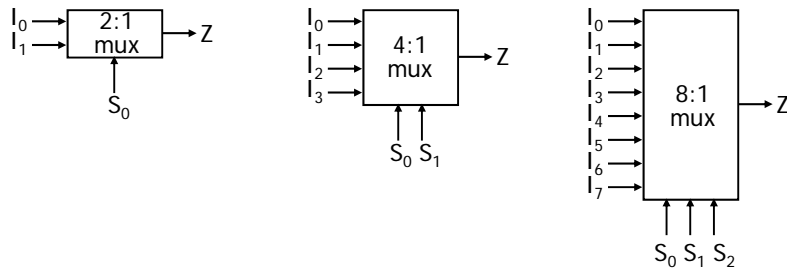
## Multiplexers (con't)

- ◆ 2:1 mux:  $Z = S'In_0 + SIn_1$
- ◆ 4:1 mux:  $Z = S_0'S_1'In_0 + S_0'S_1In_1 + S_0S_1'In_2 + S_0S_1In_3$
- ◆ 8:1 mux:  $Z = S_0'S_1'S_2'In_0 + S_0'S_1S_2In_1 + \dots$


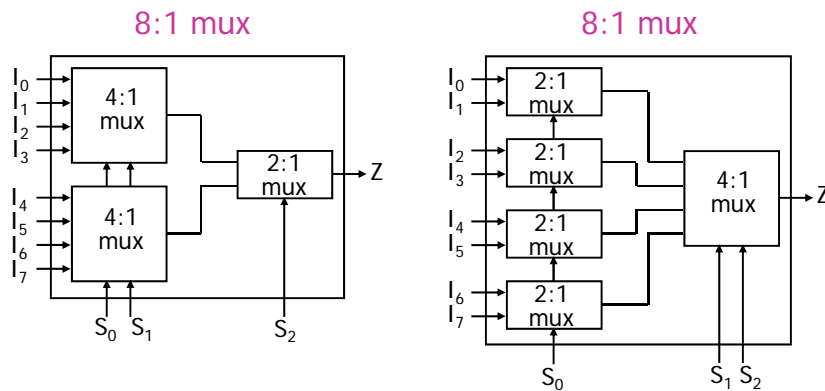
## Cascading multiplexers

- ◆ Can form large multiplexers from smaller ones
  - Many implementation options





## Multiplexers as general-purpose logic

- ◆ A  $2^n:1$  mux can implement any function of  $n$  variables
  - A lookup table
  - A  $2^{n-1}:1$  mux also can implement any function of  $n$  variables
- ◆ Example:  $F(A,B,C) = m_0 + m_2 + m_6 + m_7$ 

$$= A'B'C' + A'BC' + ABC' + ABC$$

$$= A'B'(C') + A'B(C') + AB(0) + AB(1)$$

A	B	C	F
0	0	0	1 C'
0	0	1	0
0	1	0	1 C'
0	1	1	0
1	0	0	0 0
1	0	1	0
1	1	0	1 1
1	1	1	1

  


## Multiplexers as general-purpose logic

- ◆ Implementing a  $2^{n-1}:1$  mux as a function of  $n$  variables
  - $(n-1)$  mux control variables  $S_0 - S_{n-1}$
  - One data variable  $S_n$
  - Four possible values for each data input:  $0, 1, S_n, S_n'$
  - Example:  $F(A,B,C,D)$  implemented using an  $8:1$  mux

CD		AB				D
		00	01	11	10	
C	00	1	0	1	1	}
	01	1	0	0	0	
	11	1	1	0	1	
	10	0	1	1	0	
		B		A		

 Choose A,B,C as control variables  
Choose D as a data variable



$$F = A'B'C'(1) + A'B'C(D) + A'BC'(0) + A'BC(1) + AB'C'(D) + AB'C(D) + ABC'(D') + ABC(D')$$

$$F = A'B'C' + A'CD + B'CD + AC'D' + BCD'$$

## Demultiplexers (DEMUX)

### ◆ Basic concept

- Single data input; n control inputs ("selects");  $2^n$  outputs
- Single input connects to one of  $2^n$  outputs
- "Selects" decide which output is connected to the input
- When used as a decoder, the input is called an "enable" (G)

#### 1:2 Decoder:

$$\text{Out0} = G \bullet S'$$

$$\text{Out1} = G \bullet S$$

#### 2:4 Decoder:

$$\text{Out0} = G \bullet S1' \bullet S0'$$

$$\text{Out1} = G \bullet S1' \bullet S0$$

$$\text{Out2} = G \bullet S1 \bullet S0'$$

$$\text{Out3} = G \bullet S1 \bullet S0$$

#### 3:8 Decoder:

$$\text{Out0} = G \bullet S2' \bullet S1' \bullet S0'$$

$$\text{Out1} = G \bullet S2' \bullet S1' \bullet S0$$

$$\text{Out2} = G \bullet S2' \bullet S1 \bullet S0'$$

$$\text{Out3} = G \bullet S2' \bullet S1 \bullet S0$$

$$\text{Out4} = G \bullet S2 \bullet S1' \bullet S0'$$


$$\text{Out5} = G \bullet S2 \bullet S1' \bullet S0$$

$$\text{Out6} = G \bullet S2 \bullet S1 \bullet S0'$$


$$\text{Out7} = G \bullet S2 \bullet S1 \bullet S0$$

## Logic-gate implementation of demultiplexers

### 1:2 demux

 


### 2:4 demux

 
 
## Demultiplexers as general-purpose logic

- ◆ A  $n:2^n$  demux can implement any function of  $n$  variables
  - DEMUX as logic building block
  - Use variables as select inputs
  - Tie enable input to logic 1
  - Sum the appropriate minterms (extra OR gate)



demultiplexer "decodes" appropriate minterms from the control signals


## Demultiplexers as general-purpose logic

### Example

$$F1 = A'BC'D + A'B'CD + ABCD$$


$$F2 = ABC'D' + ABC$$

$$F3 = (A' + B' + C' + D')$$

 

## Cascading demultiplexers


### ◆ 5:32 demux

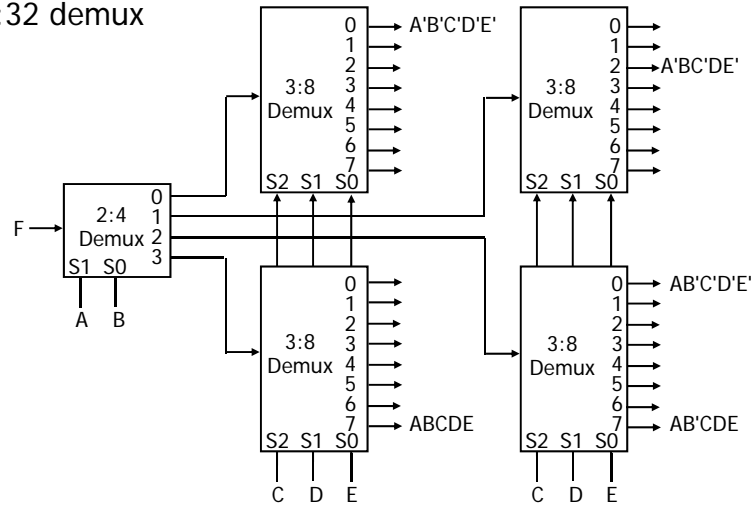

## Programmable logic (PLAs & PALs)
 
### ◆ Concept: Large array of uncommitted AND/OR gates

- Actually NAND/NOR gates
- You program the array by making or breaking connections
  - ✦ Programmable block for sum-of-products logic






## All two-level logic functions are available

---

- ◆ You "program" the wire connections

 

A 3-input, 5-term,  
4-function PLA