

CSE 370 – Winter 2008

Homework 3 – Solutions

Grading Breakdown:

- | | |
|---|---|
| 1. CLD-II, Chapter 2, problem 2.31, parts a and b
($\frac{1}{2}$ point for each SOP and POS Expression) | 3 |
| 2. CLD-II, Chapter 2, problem 2.35.
(1.5 points for each correct expression) | 3 |
| 3. CLD-II, Chapter 2, problem 2.44.
(Truth table: $\frac{1}{2}$ point, Expressions: 4points, Conclusion $\frac{1}{2}$ point) | 6 |
| 4. CLD-II, Chapter 3, problem 3.3, part a,b,c.
(1 point per part) | 3 |
| 5. Design Problem | 5 |

Total	20
--------------	-----------

Additional Grading details:

Penalties:

-2 for non standard k-maps

Bonuses:

+2 for word processed and printed work

+1 for very neat handwritten work

+2 for deep insight shown on problems

+2 for a solution to a design or optimization problem that is 50% better than the average

Note: All bonuses and penalties are subject to a maximum score of 20 points and a minimum score of 0.

$$1) \quad W(A, B, C) = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C$$

--- A ---

	0	2	6	4
C	0	1	0	1
	1	3	7	5
	--- B ---			

SoP: $W = \overline{A}B + A\overline{B}$

PoS: $W = (A+B)(\overline{A}+\overline{B})$

$$X(A, B, C) = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

--- A ---

	0	2	6	4
C	1	0	0	1
	1	3	7	5
	--- B ---			

SoP: $X = \overline{B}\overline{C} + BC$

PoS: $X = (\overline{B}+C)(B+\overline{C})$

$$Y(A, B, C, D) = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

--- A ---

	0	4	12	8
	1	0	0	1
	1	5	13	9
D	1	0	0	0
	3	7	15	11
C	1	0	0	0
	2	6	14	10
	--- B ---			

SoP: $X = \overline{A}\overline{B} + \overline{B}\overline{D}$

PoS: $X = (\overline{B})(\overline{A}+\overline{D})$

2) See truth table on page 17

d30

		--- m ₃ ---		
	X ₀	1 ₄	0 ₁₂	0 ₈
	0 ₁	0 ₅	X ₁₃	1 ₉
	0 ₃	0 ₇	X ₁₅	1 ₁₁
	0 ₂	1 ₆	X ₁₄	0 ₁₀
		--- m ₂ ---		

| m₀
|

| m₁
|

$$d30 = m_3 m_0 + \bar{m}_3 m_2 \bar{m}_0$$

d31

		--- m ₃ ---		
	X ₀	0 ₄	1 ₁₂	1 ₈
	1 ₁	1 ₅	X ₁₃	0 ₉
	1 ₃	1 ₇	X ₁₅	0 ₁₁
	0 ₂	0 ₆	X ₁₄	1 ₁₀
		--- m ₂ ---		

| m₀
|


| m₁
|

$$d31 = \bar{m}_3 m_0 + m_3 \bar{m}_0$$

3) Truth table for increment-by-one


I_3	I_2	I_1	I_0	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
I_3	I_2	I_1	I_0	O_3	O_2	O_1	O_0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

b) O3:

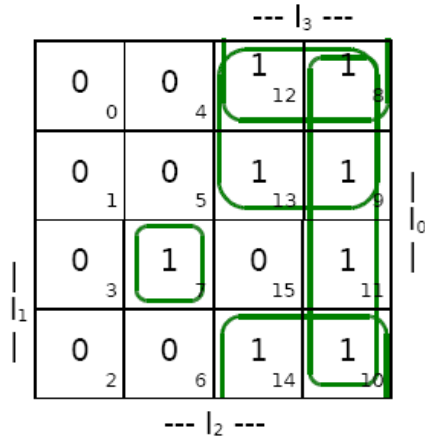


$$O_3 = I_3 \bar{I}_2 + I_3 \bar{I}_1 + I_3 \bar{I}_0 + \bar{I}_3 I_2 I_1 I_0$$

O2:

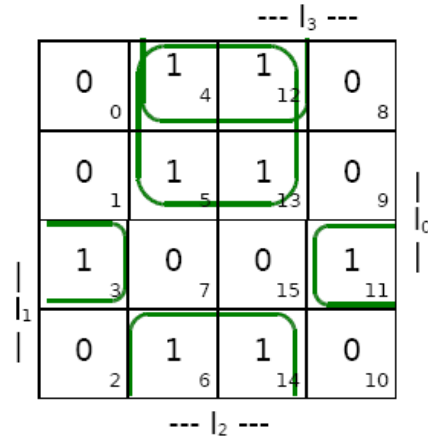


$$O_2 = I_2 \bar{I}_1 + I_2 \bar{I}_0 + \bar{I}_2 I_1 I_0$$

O1:

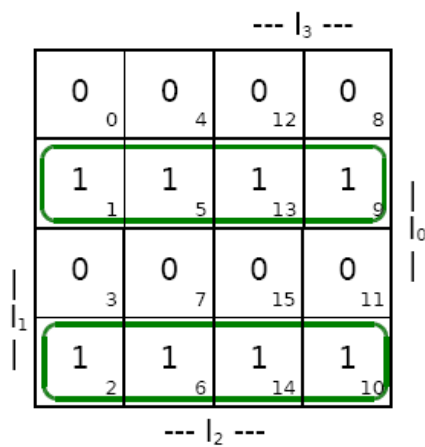


$$O_1 = I_1 \bar{I}_0 + \bar{I}_1 I_0$$

O0:

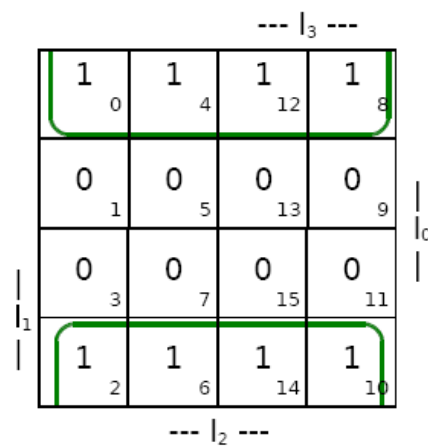

$$O_0 = \bar{I}_0$$

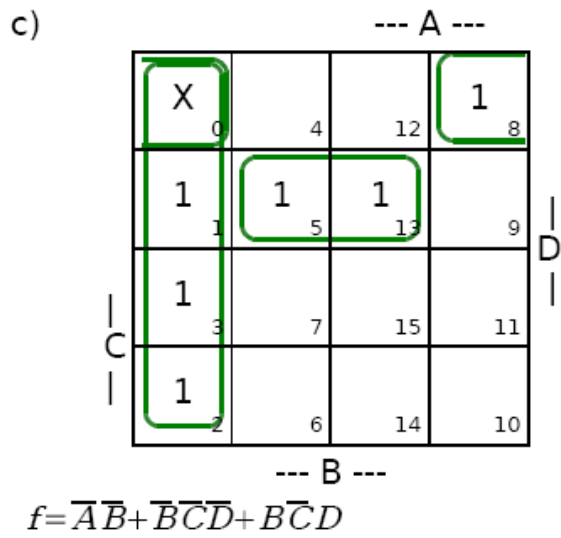

5. Design Problem

Truth Table	♣	β	N	Σ	F
Min-term Number					
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

♣ = A
 β = B
 N = C
 Σ = D

K-Map:

	A'B'	A'B	AB	AB'		
C'D'	0		4	12	8	
C'D	1		5		13	9
CD	3		7		15	11
CD'		2	6	14		10

Basic Function:

$$AB' + BD + B'CD'$$

Cost of basic implementation:

2 inverters + 2 2i/p and gates + 1 3i/p And gate + 2 OR Gates

$$\text{Cost: } 4 + 30 + 35 + 30 = 99\$$$

$$\text{Power: } 8 + 20 + 15 + 20 = 63 \text{ uW}$$

$$\text{Area: } 4 + 12 + 8 + 12 = 36 \text{ sq generic units}$$

Make 2 of the above. Substitute with a 2i/p with 3i/p And gate.

Best Designs - For each metric

Lowest Cost											
Student	Company	Function implemented	Inverters	2 i/p and	3 i/p and	2 i/p or	xor	Cost	Power	Area	Product
Isac Myers	♣ - β	$(B'+D)[(A+B) + D'C]$	2	2	0	3	0	79	58	34	
	Σ	$(B'+D)[(A+B) + D'C]$	5	1	0	4	0	85	70	40	
								164	128	74	1553408
Lowest Power											
Student		Function implemented	Inverters	2 i/p and	3 i/p and	2 i/p or	xor	Cost	Power	Area	Product
Benjamin Lee	♣ - β	$(B'+D)[(A+B) + D'C]$	2	2	0	3	0	79	58	34	
	Σ	$(B'+D)[(A+B) + D'C]$	2	1	1	3	0	99	63	36	
	Total							178	121	70	1507660
Lowest Area											
Student		Function implemented	Inverters	2 i/p and	3 i/p and	2 i/p or	xor	Cost	Power	Area	Product
Benjamin Lee	♣ - β	$(B'+D)[(A+B) + D'C]$	2	2	0	3	0	79	58	34	
	Σ	$(B'+D)[(A+B) + D'C]$	2	1	1	3	0	99	63	36	
	Total							178	121	70	1507660
Best Balanced Design											
Student		Function implemented	Inverters	2 i/p and	3 i/p and	2 i/p or	xor	Cost	Power	Area	Product
Benjamin Lee	♣ - β	$(B'+D)[(A+B) + D'C]$	2	2	0	3	0	79	58	34	
	Σ	$(B'+D)[(A+B) + D'C]$	2	1	1	3	0	99	63	36	
	Total		4	3	1	6	0	178	121	70	1507660