

## Overview

- ◆ Last lecture
  - Latches
  - Flip-flops
    - ↳ Edge-triggered D
    - ↳ Master-slave
  - Timing diagrams
- ◆ Today
  - Sequential Verilog

## Variables

- ◆ wire
  - Connects components together
- ◆ reg
  - Saves a value
    - ↳ Part of a behavioral description
  - Does **NOT** necessarily become a register when you synthesize
    - ↳ May become a wire
- ◆ The rule
  - Declare a variable as reg if it is a target of an assignment statement
    - ↳ Continuous assign doesn't count

## Sequential Verilog

- ◆ Sequential circuits: Registers & combinational logic
  - Use positive edge-triggered registers
  - Avoid latches and negative edge-triggered registers
- ◆ Register is triggered by "posedge clk"

```
module register(Q, D, clock);
  input  D, clock;
  output Q;
  reg   Q;

  always @(posedge clock) begin
    Q = D;
  end
endmodule
```

Example: A D flip-flop

A real register. Holds Q between clock edges

## always block

- ◆ A procedure that describes a circuit's function
  - Can contain multiple statements
  - Can contain *if*, *for*, *while*, *case*
  - Triggers at the specified conditions
  - *begin/end* groups statements within *always* block

```
module register(Q, D, clock);
  input  D, clock;
  output Q;
  reg   Q;

  always @(posedge clock) begin
    Q = D;
  end
endmodule
```

## always example

```
module and_gate(out, in1, in2);
  input  in1, in2;
  output out;
  reg   out;

  always @(in1 or in2) begin
    out = in1 & in2;
  end
endmodule
```

Not a real register!  
Holds assignment in  
always block

The compiler will not synthesize  
this code to a register, because  
*out* changes whenever *in1* or *in2*  
change. Can instead simply write  
`wire out, in1, in2;`  
`and (out, in1, in2);`

specifies when block is executed  
i.e. triggered by changes in *in1* or *in2*

## Incomplete trigger or incomplete assignment

- ◆ What if you omit an input trigger (e.g. *in2*)
  - Compiler will insert a register to hold the state
  - Becomes a sequential circuit — **NOT** what you want

```
module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  reg   out;

  always @(in1) begin
    out = in1 & in2;
  end
endmodule
```

A real register! Holds *out*  
because *in2* isn't specified  
in *always* trigger

### 2 rules:

- 1) Include all inputs in the trigger list
- 2) Use complete assignments
  - ⇒ Every path must lead to an assignment for *out*
  - ⇒ Otherwise *out* needs a state element

## Assignments

### ◆ Be careful with `always` assignments

- Which of these statements generate a latch?

```
always @(c or x) begin
  if (c) begin
    value = x;
  end
  y = value;
end
```

```
always @(c or x) begin
  value = x;
  if (c) begin
    value = 0;
  end
  y = value;
end
```

```
always @(c or x) begin
  if (c)
    value = 0;
  else if (x)
    value = 1;
end
```

```
always @(a or b)
  f = a & b & c;
end
```

## Another way: Use functions

### ◆ Functions for combinational logic

- Functions can't have state

```
module and_gate (out, in1, in2);
  input in1, in2;
  output out;

  assign out = myfunction(in1, in2);
  function myfunction;
    input in1, in2;
    begin
      myfunction = in1 & in2;
    end
  endfunction
endmodule
```

#### Benefits:

- Functions force a result
- ⇒ Compiler will fail if function does not generate a result
- ⇒ If you build a function wrong the circuit will not synthesize.
- If you build an `always` block wrong you get a register

## *if*

### ◆ Same as C *if* statement

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;
endmodule
```

- ⇒ Single *if* statements synthesize to multiplexers
- ⇒ Nested *if/else* statements usually synthesize to logic

## *if* (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel[0] == 0)
      if (sel[1] == 0) Y = A;
      else Y = B;
    else
      if (sel[1] == 0) Y = C;
      else Y = D;
endmodule
```

## *case*

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    case (sel)
      2'b00: Y = A;
      2'b01: Y = B;
      2'b10: Y = C;
      2'b11: Y = D;
    endcase
endmodule
```

- case* executes sequentially
- ⇒ First match executes
- ⇒ Don't need to break out of *case* statements synthesize to muxes

## *case* (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;

  assign out = mymux(sel, A, B, C, D);
  function mymux;
    input [1:0] sel, A, B, C, D;
    begin
      case (sel)
        2'b00: mymux = A;
        2'b01: mymux = B;
        2'b10: mymux = C;
        2'b11: mymux = D;
      endcase
    end
  endfunction
endmodule
```

- Note: You can define a function in a file
- Then *include* it into your Verilog module

## default case

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;          // 3-bit encoded output
reg    [2:0] Y;          // target of assignment

always @(A)
  case (A)
    8'b00000001: Y = 0;
    8'b00000010: Y = 1;
    8'b00000100: Y = 2;
    8'b00001000: Y = 3;
    8'b00010000: Y = 4;
    8'b00100000: Y = 5;
    8'b01000000: Y = 6;
    8'b10000000: Y = 7;
    default: Y = 3'bx; // Don't care about other cases
  endcase
endmodule
```

If you omit the *default*, the compiler will create a latch for Y  
 ⇒ Either list all 256 cases  
 ⇒ Or use a function (compiler will warn you of missing cases)

CSE370, Lecture 15

13

## case executes sequentially

```
// Priority encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;          // 3-bit encoded output
reg    [2:0] Y;          // target of assignment

always @(A)
  case (1'b1)
    A[0]: Y = 0;
    A[1]: Y = 1;
    A[2]: Y = 2;
    A[3]: Y = 3;
    A[4]: Y = 4;
    A[5]: Y = 5;
    A[6]: Y = 6;
    A[7]: Y = 7;
    default: Y = 3'bx; // Don't care when input is all 0's
  endcase
endmodule
```

Case statements execute sequentially  
 ⇒ Take the first alternative that matches

CSE370, Lecture 15

14

## for

```
// simple encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;          // 3-bit encoded output
reg    [2:0] Y;          // target of assignment
integer i;               // Temporary variables for program
reg    [7:0] test;

always @(A) begin
  test = 8b'00000001;
  Y = 3'bx;
  for (i = 0; i < 8; i = i + 1) begin
    if (A == test) Y = i;
    test = test << 1; // Shift left, pad with 0s
  end
end
endmodule
```

for statements synthesize as cascaded combinational logic  
 ⇒ Verilog unrolls the loop

CSE370, Lecture 15

15

## Verilog while/ repeat/ forever

- ◆ *while* (expression) statement
  - execute statement while expression is true
- ◆ *repeat* (expression) statement
  - execute statement a fixed number of times
- ◆ *forever* statement
  - execute statement forever

CSE370, Lecture 15

16

## Blocking and non-blocking assignments

- ◆ Blocking assignments ( $Q = A$ )
  - Variable is assigned immediately
  - New value is used by subsequent statements
- ◆ Non-blocking assignments ( $Q <= A$ )
  - Variable is assigned after all scheduled statements are executed
  - Value to be assigned is computed but saved for later
- ◆ Example: Swap

```
always @(posedge CLK)          always @(posedge CLK)
begin                          begin
  temp = B;                    A <= B;
  B = A;                       B <= A;
  A = temp;                    end
end
```

CSE370, Lecture 15

17

## Blocking and non-blocking assignments

```
reg B, C, D;                  reg B, C, D;
always @(posedge clk)        always @(posedge clk)
begin                          begin
  B = A;                      B <= A;
  C = B;                      C <= B;
  D = C;                      D <= C;
end                              end
```



CSE370, Lecture 15

18

## Swap

◆ The following code executes incorrectly

- One block executes first
- Loses previous value of variable

```

always @(posedge CLK)      always @(posedge CLK)
begin                      begin
  A = B;                  B = A;
end                        end
    
```

◆ Non-blocking assignment fixes this

- Both blocks are scheduled by posedge CLK

```

always @(posedge CLK)      always @(posedge CLK)
begin                      begin
  A <= B;                 B <= A;
end                        end
    
```


## Parallel versus serial execution

◆ **assign** statements are implicitly parallel

- "=" means continuous assignment
- Example
 

```

 assign E = A & D;
assign A = B & C;
            
```
- A and E change if B changes



◆ **always** blocks execute in parallel

- always @(posedge clock)

◆ Procedural block internals not necessarily parallel

- "=" is a blocking assignment (sequential)
- "<=" is a nonblocking assignment (parallel)
- Examples of procedures: **always**, **function**, etc.

## Synthesis examples

