

Lecture 25

- ◆ Logistics
 - HW8 due today
 - Ant extra credit due Friday
 - Final exam, Wednesday March 18, 2:30-4:20 pm here
 - ↳ Review session Monday, March 16, 4:30 pm, here
- ◆ Last lecture
 - Encoding & Partitioning examples
- ◆ Today
 - Pipelining & Retiming
 - Control vs Datapath in a simple computer design

Other sequential logic optimization techniques


- ◆ Pipelining --- allows faster clock speed
- ◆ Retiming --- can reduce registers or change delays

Pipelining related definitions

- ◆ Latency: Time to perform a computation
 - Data input to data output
- ◆ Throughput: Input or output data rate
 - Typically the clock rate
- ◆ Combinational delays drive performance
 - Define $d \equiv$ delay through slowest combinational stage
 - $n \equiv$ number of stages from input to output
 - Latency $\propto n * d$ (in sec)
 - Throughput $\propto 1/d$ (in Hz)


Pipelining

 - ◆ What?
 - Subdivide combinational logic
 - Add registers between logic
- ◆ Why?
 - Trade latency for throughput
 - ↳ Reduce logic delays
 - ↳ Increase clock speed
 - Increased throughput
 - Increased latency
 - ↳ Takes cycles to fill the pipe
 - Increase circuit utilization
 - ↳ Simultaneous computations




Pipelining

 - ◆ When?
 - Need throughput more than latency
 - ↳ Signal processing
 - Logic delays > setup/hold times
 - Acyclic logic
- ◆ Where?
 - At natural breaks in the combinational logic
 - Adding registers makes sense




Pipelining example

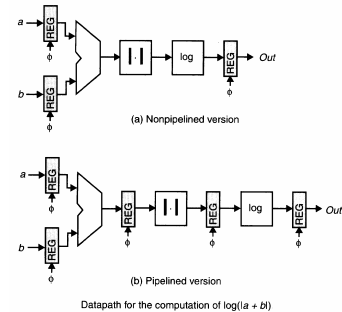

Pipelining and clock skew

- ◆ Which is faster?
- ◆ Which is safer?

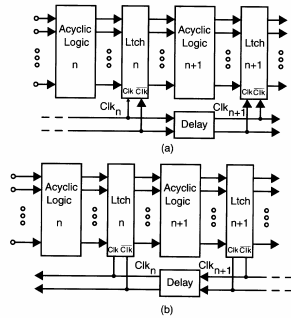

CSE370, Lecture 25

Retiming


- ◆ Pipelining adds registers
 - To increase the clock speed
- ◆ Retiming moves registers around
 - Reschedules computations to optimize performance
 - ↳ Minimize critical path
 - ↳ Optimize logic across register boundaries
 - ↳ Reduce register count
 - Without altering functionality

CSE370, Lecture 25

8

Retiming in a nutshell

 - ◆ Change position of FFs
 - For speed
 - To suit implementation target
- ◆ Retiming modifies state assignment
 - Preserves FSM functionality




CSE370, Lecture 25

9

Retiming ground rules

 - ◆ Rules:
 - Remove one register from each input and add one to each output
 - Remove one register from each output and add one to each input



CSE370, Lecture 25


10

Retiming examples

- ◆ Reduce register count



- ◆ Change output delays

 


CSE370, Lecture 25

11

Optimal pipelining

 - Add registers
- Use retiming to optimize location




CSE370, Lecture 25

12

 Example: Digital correlator

- ◆ $y_t = \delta(x_t, a_0) + \delta(x_{t-1}, a_1) + \delta(x_{t-2}, a_2) + \delta(x_{t-3}, a_3)$
 - δ is a comparator: $\delta(x, a) = 1$ if $x = a$; 0 otherwise
 - y_t is the number of matches between input and pattern $a_0 a_1 a_2 a_3$




CSE370, Lecture 25

13

Example: Digital correlator (cont'd)

- ◆ Delays: Comparator = 3; adder = 7

 


CSE370, Lecture 25

14

Data-path and control

 - ◆ Digital hardware systems = data-path + control
 - datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - control: FSM generating sequences of control signals that instructs datapath what to do next




CSE370, Lecture 25

15

Tri-state gates


- ◆ The third value
 - logic values: "0", "1"
 - don't care: "X" (must be 0 or 1 in real circuit!)
 - third value or state: "Z" — high impedance, infinite R, no connection
- ◆ Tri-state gates
 - additional input – output enable (OE)
 - output values are 0, 1, and Z
 - when OE is high, the gate functions normally
 - when OE is low, the gate is disconnected from wire at output
 - allows more than one gate to be connected to the same output wire
 - as long as only one has its output enabled at any one time (otherwise, sparks could fly)

 

CSE370, Lecture 25

Tri-state and multiplexing

 - ◆ When using tri-state logic
 - (1) make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
 - (2) make sure to only use value on wire when its being driven (using a floating value may cause failures)
- ◆ Using tri-state gates to implement an economical multiplexer




CSE370, Lecture 25

17

Open-collector gates and wired-AND

- ◆ Open collector: another way to connect gate outputs to the same wire
 - gate only has the ability to pull its output low
 - it cannot actively drive the wire high (default – pulled high through resistor)
- ◆ Wired-AND can be implemented with open collector logic
 - if A and B are "1", output is actively pulled low
 - if C and D are "1", output is actively pulled low
 - if one gate output is low and the other high, then low wins
 - if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - low to high transition usually slower than it would have been with a gate pulling high
 - hence, the two NAND functions are ANDed together

 


CSE370, Lecture 25

18

Structure of a computer

◆ Block diagram view

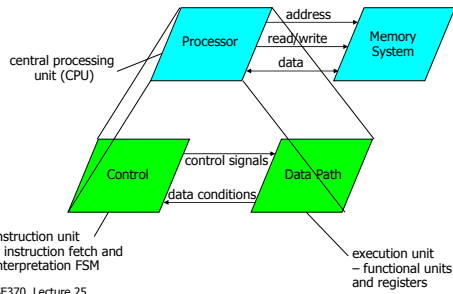

CSE370, Lecture 25


19

Registers

◆ Selectively loaded – EN or LD input

◆ Output enable – OE input

 ◆ Multiple registers – group 4 or 8 in parallel



OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs

CSE370, Lecture 25

20


Register files

◆ Collections of registers in one package

- two-dimensional array of FFs
- address used as index to a particular word
- can have separate read and write addresses so can do both at same time

◆ 4 by 4 register file

 - 16 D-FFs
- organized as four words of four bits each
- write-enable (load)
- read-enable (output enable)



CSE370, Lecture 25

21


Memories

◆ Larger collections of storage elements

- implemented not as FFs but as much more efficient latches
- high-density memories use 1 to 5 switches (transistors) per memory bit

◆ Static RAM – 1024 words each 4 bits wide

 - once written, memory holds forever (not true for denser dynamic RAM)
- address lines to select word
 - (10 lines for 1024 words)
- read enable
 - same as output enable
 - often called chip select
 - permits connection of many chips into larger array
- write enable (same as load enable)
- bi-directional data lines
 - output when reading, input when writing



CSE370, Lecture 25

22

Instruction sequencing

◆ Example – an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)

- Step 1:** get the ADD instruction from memory into an instruction register (IR)
- Step 2:** decode instruction
 - instruction in IR has the code of an ADD instruction
 - register indices used to generate output enables for registers Rx and Ry
 - register index used to generate load signal for register Rz
- Step 3:** execute instruction
 - enable Rx and Ry output and direct to ALU
 - setup ALU to perform ADD operation
 - direct result to Rz so that it can be loaded into register

CSE370, Lecture 25

23

Instruction types

◆ Data manipulation

- add, subtract
- increment, decrement
- multiply
- shift, rotate
- immediate operands

◆ Data staging

- load/store data to/from memory
- register-to-register move

◆ Control

- conditional/unconditional branches in program flow
- subroutine call and return

CSE370, Lecture 25

24

Elements of the control unit (aka instruction unit)

- ◆ Standard FSM elements
 - state register
 - next-state logic
 - output logic (datapath/control signalling)
 - Moore or synchronous Mealy machine to avoid loops unbroken by FF
- ◆ Plus additional "control" registers
 - instruction register (IR)
 - program counter (PC)
- ◆ Inputs/outputs
 - outputs control elements of data path
 - inputs from data path used to alter flow of program (test if zero)

CSE370, Lecture 25


25

Instruction execution

- ◆ Control state diagram (for each diagram)
 - reset
 - fetch instruction
 - decode
 - execute

- ◆ Instructions partitioned into three classes
 - branch
 - load/store
 - register-to-register

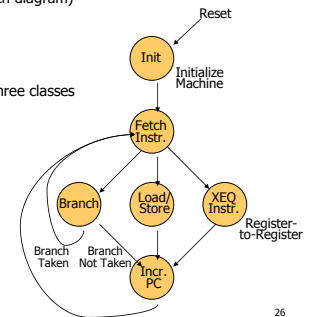- ◆ Different sequence through diagram for each instruction type




CSE370, Lecture 25

26

Data path (hierarchy)

 - ◆ Arithmetic circuits constructed in hierarchical and iterative fashion
 - each bit in datapath is functionally identical
 - 4-bit, 8-bit, 16-bit, 32-bit, 32-bit datapaths




CSE370, Lecture 25

27

Data path (ALU)

- ◆ ALU block diagram

 - input: data and operation to perform
- output: result of operation and status information




CSE370, Lecture 25

28

Data path (ALU + registers)

 - ◆ Accumulator
 - special register
 - one of the inputs to ALU
 - output of ALU stored back in accumulator
- ◆ One-address instructions
 - operation and address of one operand
 - other operand and destination is accumulator register
 - $AC \leftarrow AC \text{ op Mem}[\text{addr}]$
 - "single address instructions" (AC implicit operand)




CSE370, Lecture 25

29

Data path (bit-slice)

 - ◆ Bit-slice concept – iterate to build n-bit wide datapaths



CSE370, Lecture 25

30

