

Minimization of Boolean logic

- Minimization
 - uniting theorem
 - grouping of terms in Boolean functions
- Alternate representations of Boolean functions
 - cubes
 - Karnaugh maps

Simplification of two-level combinational logic

- Finding a minimal sum of products or product of sums realization
 - exploit don't care information in the process
- Algebraic simplification
 - not an algorithmic/systematic procedure
 - how do you know when the minimum realization has been found?
- Computer-aided design tools
 - precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - to understand automatic tools and their strengths and weaknesses
 - ability to check results (on small examples)

The uniting theorem

- Key tool to simplification: $A(B' + B) = A$
- Essence of simplification of two-level logic
 - find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$


A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

B has the same value in both on-set rows
 – B remains, actually B' because B is 0 in both cases

A has a different value in the two rows
 – A is eliminated

Boolean cubes

 
- Visual technique for indentifying when the uniting theorem can be applied
- n input variables = n-dimensional "cube"



Mapping truth tables onto Boolean cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 


ON-set = solid nodes
OFF-set = empty nodes
DC-set = x'd nodes

Three variable example

- Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$Cout = BCin + AB + ACin$$

Higher dimensional cubes

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2

*represents an expression in one variable
i.e., 3 dimensions - 2 dimensions*

A is asserted (true) and unchanged
B and C vary

This subcube represents the
literal A

m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
 - a 0-cube, i.e., a single node, yields a term in 3 literals
 - a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - an m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

Karnaugh maps

- Flat map of Boolean cube
 - wrap-around at edges
 - hard to draw and visualize for more than 4 dimensions
 - virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
 - guide to applying the uniting theorem
 - on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

	A	0	1
B	0	1	1
	1	0	0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

Karnaugh maps (cont'd)

- Numbering scheme based on Gray-code
 - e.g., 00, 01, 11, 10
 - only a single bit changes in code for adjacent map cells

	AB	00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5



	A	0	1
C	0	2	6
	1	3	7

	A	0	4	12	8
		1	5	13	9
		3	7	15	11
C		2	6	14	10

$$13 = 1101 = ABC'D$$




Adjacencies in Karnaugh maps

  - Wrap from first to last column
- Wrap top row to bottom row






Karnaugh map examples

   - $F =$
- $Cout =$
- $f(A,B,C) = \sum m(0,4,5,7)$





More Karnaugh map examples

   

Karnaugh map: 4-variable example

■ $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$

$F = C + A'BD + B'D'$

  

find the smallest number of the largest possible subcubes to cover the ON-set
 (fewer terms with fewer inputs per term)

Karnaugh maps: don't cares

- $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$
 - without don't cares
 - $f = A'D + B'C'D$

		A		
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
	B			
	D			

Karnaugh maps: don't cares (cont'd)

- $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$
 - $f = A'D + B'C'D$ without don't cares
 - $f = A'D + C'D$ with don't cares

		A		
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
	B			
	D			

by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s
depending on which is more
advantageous

Activity

- Minimize the function $F = \sum m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$

		A		
	1	0	X	1
	0	0	X	X
C	X	1	1	0
	1	X	1	0
		B		

Does $BC + A'B'D' + B'C'D' = A'C + AB + B'C'D'$?

- NO! Not in general, only if we ignore the cells with don't cares

		A		
	1	0	X	1
	0	0	X	X
C	X	1	1	0
	1	X	1	0
		B		

$$F_1 = BC + A'B'D' + B'C'D'$$

$$F_2 = A'C + AB + B'C'D'$$

$$F_1 \neq F_2$$

$$F_1 + d(3,6,9,12,13) = F_2 + d(3,6,9,12,13)$$

(don't cares all 1)

$$F_1 \cdot D(3,6,9,12,13) = F_2 \cdot D(3,6,9,12,13)$$

(don't cares all 0)

		A		
	1	0	0	1
	0	0	0	0
C	0	1	1	0
	1	1	1	0
		B		

		A		
	1	0	1	1
	0	0	1	0
C	1	1	1	0
	1	1	1	0
		B		

Combinational logic summary (so far)

- Logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Axioms and theorems of Boolean algebra
 - proofs by re-writing and perfect induction
- Gate logic
 - networks of Boolean functions and their time behavior
- Canonical forms
 - two-level and incompletely specified functions
- Simplification
 - a start at understanding two-level simplification