 


Combinational logic


- Switches
- Basic logic and truth tables
- Logic functions
- Boolean algebra
- Proofs by re-writing and by perfect induction

Switches: basic element of physical implementations

- Implementing a simple circuit (arrow shows action if wire changes to "1"):



 close switch (if A is "1" or asserted)
and turn on light bulb (Z)





open switch (if A is "0" or unasserted)
and turn off light bulb (Z)

$$Z \equiv A$$

Switches (cont'd)

  - Compose switches into more complex ones (Boolean functions):



Switching networks


- Switch settings
 - determine whether or not a conducting path exists to light the light bulb
- To build larger computations
 - use the light bulb (output of the network) to set other switches (inputs to another network)

Transistor networks


- Modern digital systems are designed in CMOS technology
 - MOS stands for Metal-Oxide on Semiconductor
 - C is for complementary because there are both normally-open and normally-closed switches
- MOS transistors act as voltage-controlled switches
 - similar, though easier to work with than relays.

MOS transistors

 - MOS transistors have three terminals: drain, gate, and source
 - they act as switches in the following way:
 - if the voltage on the gate terminal is (some amount) higher/lower than the source terminal then a conducting path will be established between the drain and source terminals




 n-channel
open when voltage at G is low
closes when:
 $\text{voltage}(G) > \text{voltage}(S) + \epsilon$



p-channel
closed when voltage at G is low
opens when:
 $\text{voltage}(G) < \text{voltage}(S) - \epsilon$

Most digital logic is CMOS


 


Mark Bohr Intel



0V ≡ Logic 0
1.8V ≡ Logic 1

X	Y
0V	1.8V
1.8V	0V

  


Multi-input logic gates



- CMOS logic gates are inverting
 - Easy to implement NAND, NOR, NOT while AND, OR, and Buffer are harder



Claude Shannon – 1938

 


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

  

Possible logic functions of two variables

 - There are 16 possible functions of 2 input variables:
 - in general, there are 2^{2^n} functions of n inputs



X	Y	16 possible functions (F_0 - F_{15})															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	0	0
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Labels for functions (circled in original):

- F_0 : X and Y
- F_1 : X
- F_2 : Y
- F_3 : X xor Y
- F_4 : X or Y
- F_5 : X nor Y
- F_6 : not (X or Y)
- F_7 : X = Y
- F_8 : not Y
- F_9 : not X
- F_{10} : X nand Y
- F_{11} : not (X and Y)

Minimal set of functions


- Can we implement all logic functions from NOT, NOR, and NAND?
 - For example, implementing X and Y is the same as implementing not (X nand Y)
- In fact, we can do it with only NOR or only NAND
 - NOT is just a NAND or a NOR with both inputs tied together

X	Y	X nor Y	X nand Y
0	0	1	1
1	1	0	0

- and NAND and NOR are "duals", that is, its easy to implement one using the other

$$\begin{aligned}
 X \text{ nand } Y & \equiv \text{not} ((\text{not } X) \text{ nor } (\text{not } Y)) \\
 X \text{ nor } Y & \equiv \text{not} ((\text{not } X) \text{ nand } (\text{not } Y))
 \end{aligned}$$

Boolean algebra

 

George Boole – 1854

- An algebraic structure consists of
 - a set of elements B
 - binary operations $\{ +, \cdot \}$
 - and a unary operation $\{ ' \}$
 - such that the following axioms hold:

1. the set B contains at least two elements: a, b
2. closure: $a + b$ is in B $a \cdot b$ is in B
3. commutativity: $a + b = b + a$ $a \cdot b = b \cdot a$
4. associativity: $a + (b + c) = (a + b) + c$ $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
5. identity: $a + 0 = a$ $a \cdot 1 = a$
6. distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c)$ $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
7. complementarity: $a + a' = 1$ $a \cdot a' = 0$

Logic functions and Boolean algebra

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: $'$, $+$, and \cdot

X, Y are Boolean algebra variables

X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X'	$X' \cdot Y$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

X	Y	X'	Y'	$X \cdot Y$	$X' \cdot Y'$	$(X \cdot Y) + (X' \cdot Y')$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \cdot Y) + (X' \cdot Y') \rightarrow X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

Axioms and theorems of Boolean algebra

- identity
 1. $X + 0 = X$
 - 1D. $X \cdot 1 = X$
- null
 2. $X + 1 = 1$
 - 2D. $X \cdot 0 = 0$
- idempotency:
 3. $X + X = X$
 - 3D. $X \cdot X = X$
- involution:
 4. $(X')' = X$
- complementarity:
 5. $X + X' = 1$
 - 5D. $X \cdot X' = 0$
- commutativity:
 6. $X + Y = Y + X$
 - 6D. $X \cdot Y = Y \cdot X$
- associativity:
 7. $(X + Y) + Z = X + (Y + Z)$
 - 7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
- distributivity:
 8. $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$
 - 8D. $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$

Axioms and theorems of Boolean algebra (cont'd)

- uniting:
 9. $X \cdot Y + X \cdot Y' = X$
 - 9D. $(X + Y) \cdot (X + Y') = X$
- absorption:
 10. $X + X \cdot Y = X$
 - 10D. $X \cdot (X + Y) = X$
 11. $(X + Y') \cdot Y = X \cdot Y$
 - 11D. $(X \cdot Y') + Y = X + Y$
- factoring:
 12. $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$
 - 12D. $X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$
- consensus:
 13. $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$
 - 13D. $(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$
- de Morgan's:
 14. $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$
 - 14D. $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$
- generalized de Morgan's:
 15. $f'(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$

Axioms and theorems of Boolean algebra (cont'd)

- Duality
 - a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
 - any theorem that can be proven is thus also proven for its dual!
 - a meta-theorem (a theorem about theorems)
- duality:
 - 16. $X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$
- generalized duality:
 - 17. $f(X_1, X_2, \dots, X_n, 0, 1, +, \bullet) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \bullet, +)$
- Different than deMorgan's Law
 - this is a statement about theorems
 - this is not a way to manipulate (re-write) expressions

Proving theorems (rewriting)

- Using the laws of Boolean algebra:
 - e.g., prove the theorem: $X \cdot Y + X \cdot Y' = X$
 - distributivity (8) $X \cdot Y + X \cdot Y' = X \cdot (Y + Y')$
 - complementarity (5) $X \cdot (Y + Y') = X \cdot (1)$
 - identity (1D) $X \cdot (1) = X$
 - e.g., prove the theorem: $X + X \cdot Y = X$
 - identity (1D) $X + X \cdot Y = X \cdot 1 + X \cdot Y$
 - distributivity (8) $X \cdot 1 + X \cdot Y = X \cdot (1 + Y)$
 - identity (2) $X \cdot (1 + Y) = X \cdot (1)$
 - identity (1D) $X \cdot (1) = X$

Activity

- Prove consensus theorem using the laws of Boolean algebra:

$$\square (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$$

	$(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z)$
identity	$(X \cdot Y) + (1) \cdot (Y \cdot Z) + (X' \cdot Z)$
complementarity	$(X \cdot Y) + (X' + X) \cdot (Y \cdot Z) + (X' \cdot Z)$
distributivity	$(X \cdot Y) + (X' \cdot Y \cdot Z) + (X \cdot Y \cdot Z) + (X' \cdot Z)$
commutativity	$(X \cdot Y) + (X \cdot Y \cdot Z) + (X' \cdot Y \cdot Z) + (X' \cdot Z)$
factoring	$(X \cdot Y) \cdot (1 + Z) + (X' \cdot Z) \cdot (1 + Y)$
null	$(X \cdot Y) \cdot (1) + (X' \cdot Z) \cdot (1)$
identity	$(X \cdot Y) + (X' \cdot Z)$

identity	1. $X + 0 = X$	1D. $X \cdot 1 = X$
null	2. $X + 1 = 1$	2D. $X \cdot 0 = 0$
complementarity:	5. $X + X' = 1$	5D. $X \cdot X' = 0$
commutativity:	6. $X + Y = Y + X$	6D. $X \cdot Y = Y \cdot X$
associativity:	7. $(X + Y) + Z = X + (Y + Z)$	7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
distributivity:	8. $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$	8D. $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$
factoring:	12. $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$	12D. $X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$

Proving theorems (perfect induction)

- Using perfect induction (complete truth table):

- e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented


X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

A simple example: 1-bit binary adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin}$$

$$\text{Cout} = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}$$