

## Combinational logic design case studies



- Arithmetic circuits
  - integer representations
  - addition/subtraction
  - arithmetic/logic units
- General design procedure
- Case studies
  - BCD to 7-segment display controller
  - Leap-year flag calculator

## General design procedure for combinational logic

- 1. Understand the problem
  - what is the circuit supposed to do?
  - write down inputs (data, control) and outputs
  - draw block diagram or other picture
- 2. Formulate the problem using a suitable design representation
  - truth table or waveform diagram are typical
  - may require encoding of symbolic inputs and outputs
- 3. Choose implementation target
  - programmable logic: FPGA, ROM, PAL, PLA
  - mux, decoder and OR-gate
  - discrete gates
- 4. Follow implementation procedure
  - HDL to be synthesized, K-maps for two-level logic, multi-level logic tools
  - design tools and hardware description language (e.g., Verilog) are crucial
  
## BCD to 7-segment display controller

- Understanding the problem
  - input is a 4 bit bcd digit (A, B, C, D)
  - output is the control signals for the display (7 outputs C0 – C6)
- Block diagram



## Formalize the problem

- Truth table
  - show don't cares
- Choose implementation target
  - if ROM, we are done
  - don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
  - minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

## Implementation as minimized sum-of-products

- 15 unique product terms when minimized individually

$C0 = A + B D + C + B' D'$   
 $C1 = C' D' + C D + B'$   
 $C2 = B + C' + D$   
 $C3 = B' D' + C D' + B C' D + B' C$   
 $C4 = B' D' + C D'$   
 $C5 = A + C' D' + B D' + B C'$   
 $C6 = A + C D' + B C' + B' C$


## Implementation as minimized S-o-P (cont'd)

- Can do better
  - 9 unique product terms (instead of 15)
  - share terms among outputs
  - each output not necessarily in minimized form

$C0 = A + B D + C + B' D'$   
 $C1 = C' D' + C D + B'$   
 $C2 = B + C' + D$   
 $C3 = B' D' + C D' + B C' D + B' C$   
 $C4 = B' D' + C D'$   
 $C5 = A + C' D' + B D' + B C'$   
 $C6 = A + C D' + B C' + B' C$

$C0 = B C' D + C D + B' D' + B C D' + A$   
 $C1 = B' D + C' D' + C D + B' D'$   
 $C2 = B' D + B C' D + C' D' + C D + B C D'$   
 $C3 = B C' D + B' D + B' D' + B C D'$   
 $C4 = B' D' + B C D'$   
 $C5 = B C' D + C' D' + A + B C D'$   
 $C6 = B' C + B C' + B C D' + A$

## PLA implementation

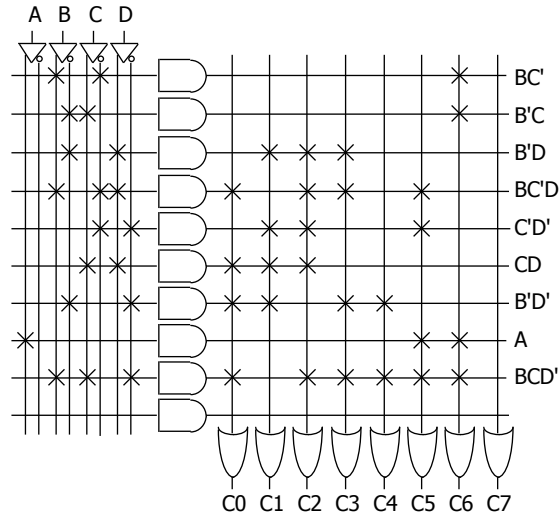

## PAL implementation vs. Discrete gate implementation

- Limit of 4 product terms per output
  - decomposition of functions with larger number of terms
  - do not generally share terms in PAL anyway (although there are exceptions)

$$C2 = B + C' + D$$

$$C2 = B'D + B'C'D + C'D' + CD + BCD'$$

$$C2 = B'D + B'C'D + C'D' + W \quad \leftarrow \text{need another input and another output}$$

$$W = CD + BCD' \quad \leftarrow$$

- decompose into multi-level logic (hopefully with CAD support)
  - find common sub-expressions among functions

$$C0 = C3 + A'B'X' + ADY$$

$$C1 = Y + A'C5' + C'D'C6$$

$$C2 = C5 + A'B'D + A'CD$$

$$C3 = C4 + BD C5 + A'B'X'$$

$$C4 = D'Y + A'CD'$$

$$C5 = C'C4 + AY + A'BX$$

$$C6 = AC4 + CC5 + C4'C5 + A'B'C$$

$$X = C' + D'$$

$$Y = B'C$$

## Activity: divisible-by-4 circuit

- BCD coded year (digits for thousands, hundreds, tens, and ones)
  - YM8 YM4 YM2 YM1 , YH8 YH4 YH2 YH1 , YT8 YT4 YT2 YT1 , YO8 YO4 YO2 YO1

## Activity: divisible-by-4 circuit

- BCD coded year (digits for thousands, hundreds, tens, and ones)
  - YM8 YM4 YM2 YM1 , YH8 YH4 YH2 YH1 , YT8 YT4 YT2 YT1 , YO8 YO4 YO2 YO1
- Only need to look at low-order two digits of the year  
all years ending in 00, 04, 08, 12, 16, 20, etc. are divisible by 4
  - if tens digit is even, then divisible by 4 if ones digit is 0, 4, or 8
  - if tens digit is odd, then divisible by 4 if the ones digit is 2 or 6
- Translates into the following Boolean expression:
  - $YT1' (YO8' YO4' YO2' YO1' + YO8' YO4 YO2' YO1' + YO8 YO4' YO2' YO1' )$   
+  $YT1 (YO8' YO4' YO2 YO1' + YO8' YO4 YO2 YO1' )$
- Digits with values from 10 to 15 will never occur, simplify further to yield:
  - $YT1' ( YO == 0 | YO == 4 | YO == 8 | YO == 12)$   
+  $YT1 (YO == 2 | YO == 6 | YO == 10 | YO == 14)$
  - $YT1' YO2' YO1' + YT1 YO2 YO1'$


## Divisible-by-100 and divisible-by-400 circuits

- Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:
  - $YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1'$
- Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits:
  - $(YM1' YH2' YH1' + YM1 YH2 YH1')$ 
    - $(YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1')$

## Combining to determine leap year flag

- Label outputs of the previous three circuits: D4, D100, and D400
  - $\text{leap\_year\_flag} = D4 \cdot D100' + D400$

## Implementation of leap year flag

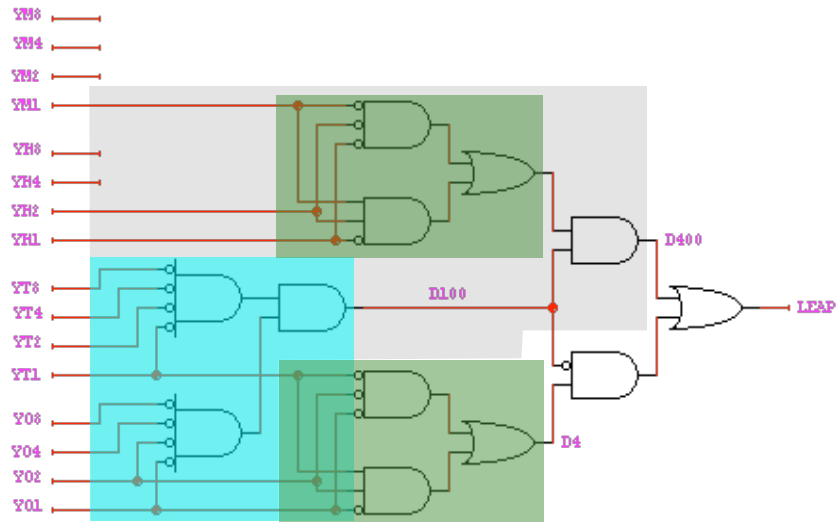


Autumn 2010

CSE370 - XII - Combinational Logic Case Studies

13

## Implementation of leap year flag in FPGA

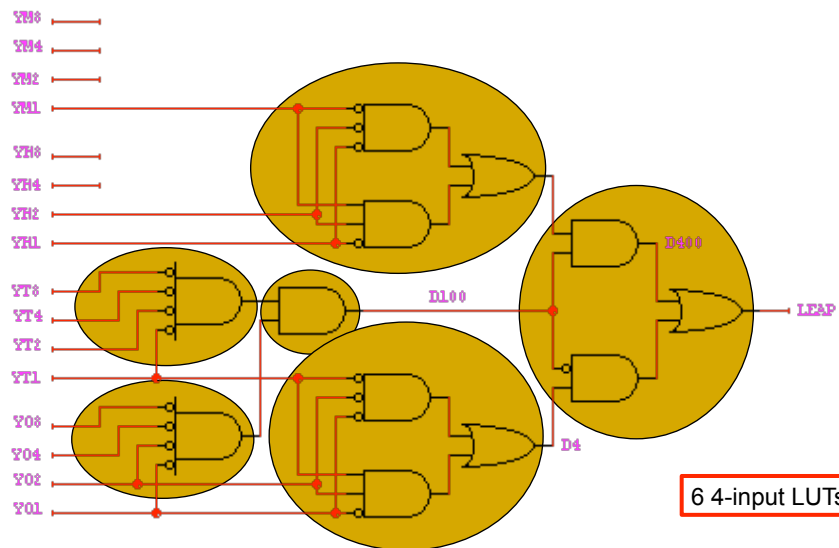

Autumn 2010

CSE370 - XII - Combinational Logic Case Studies

14

## Summary for examples of combinational logic

- Combinational logic design process
  - formalize problem: encodings, truth-table, equations
  - choose implementation technology (FPGA, ROM, PAL, PLA, discrete gates)
  - implement by following the design procedure for that technology
- Binary number representation
  - positive numbers the same
  - difference is in how negative numbers are represented
  - 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
  - basic half-adder and full-adder
  - carry lookahead logic
  - carry-select