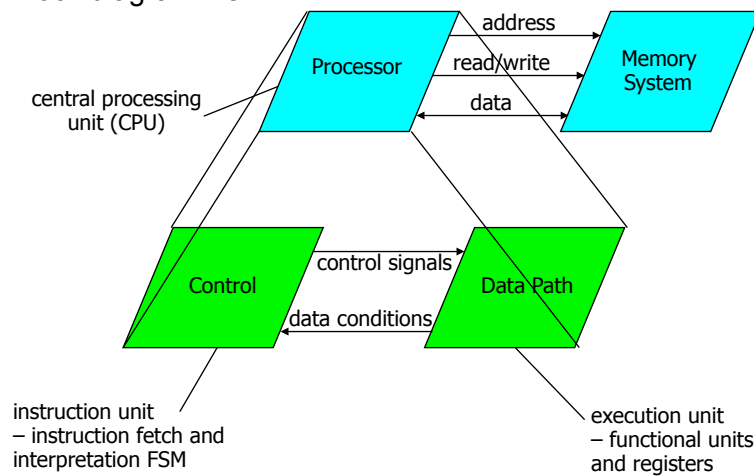


Computer organization

- Computer design – an application of digital logic design procedures
- Computer = processing unit + memory system
- Processing unit = control + datapath
- Control = finite state machine
 - inputs = machine instruction, datapath conditions
 - outputs = register transfer control signals, ALU operation codes
 - instruction interpretation = instruction fetch, decode, execute
- Datapath = functional units + registers
 - functional units = ALU, multipliers, dividers, etc.
 - registers = program counter, shifters, storage registers


Structure of a computer

- Block diagram view



Registers

 - Selectively loaded – EN or LD input
- Output enable – OE input
- Multiple registers – group 4 or 8 in parallel






OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs


Register transfer

   - Point-to-point connection
 - dedicated wires
 - muxes on inputs of each register
- Common input from multiplexer (input bus)
 - load enables for each register
 - control signals for multiplexer
- Common bus with output enables (input/output bus)
 - output enables and load enables for each register




Register files

 - Collections of registers in one package
 - two-dimensional array of FFs
 - address used as index to a particular word
 - can have separate read and write addresses so can do both at same time
- 4 by 4 register file
 - 16 D-FFs
 - organized as four words of four bits each
 - write-enable (load)
 - read-enable (output enable)



Memories

- Larger collections of storage elements
 - implemented not as FFs but as much more efficient latches
 - high-density memories use 1 to 5 switches (transistors) per memory bit
- Static RAM – 1024 words each 4 bits wide
 - once written, memory holds as long as there is power applied
 - not true for denser dynamic RAM – lose power, lose memory
 - address lines to select word (10 lines for 1024 words)
 - read enable
 - same as output enable
 - often called chip select (CS)
 - permits connection of many chips into larger array (tie multiple chips IO pins together)
 - write enable (same as load)
 - bi-directional data lines
 - output when reading, input when writing

 

Instruction sequencing

- Example – an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)
- Step 1: get ADD instruction from memory into instruction register (IR)
- Step 2: decode instruction
 - instruction in IR has “operation code” to identify it as an ADD instruction
 - register indices used to generate output enables for registers Rx and Ry
 - register index used to generate load signal for register Rz
- Step 3: execute instruction
 - enable Rx and Ry output and direct to ALU (possibly through busses/muxes)
 - set ALU to perform ADD operation
 - direct result (through busses/muxes) to Rz so that it can be loaded into register

Instruction types


- Data manipulation
 - add, subtract
 - increment, decrement
 - multiply
 - shift, rotate
 - immediate operands
- Data staging
 - load/store data to/from memory
 - register-to-register move
- Control
 - conditional/unconditional branches in program flow
 - subroutine call and return

Elements of the control unit (aka instruction unit)

- Standard FSM elements
 - state register
 - next-state logic
 - output logic (data-path/control signaling)
 - Moore or synchronous Mealy machine (to avoid loops unbroken by FF)
- Plus additional “control” registers
 - instruction register (IR)
 - program counter (PC)
- Inputs/outputs
 - outputs control elements of data path
 - inputs from data path used to alter flow of program (e.g., test if zero)


Instruction execution

 - Control state diagram (for each diagram)
 - reset
 - fetch instruction
 - decode
 - execute
- Instructions partitioned into three classes
 - branch
 - load/store
 - register-to-register
- Different sequence through diagram for each instruction type (may need more than one state)




Data path (hierarchy)

 - Arithmetic circuits constructed in hierarchical and modular fashion
 - each bit in datapath is functionally identical
 - 4-bit, 8-bit, 16-bit, 32-bit datapaths
 - may include carry-lookahead or carry-select capability




Data path (ALU)

 - ALU block diagram
 - input: data on which to operate and operation to perform
 - output: result of operation and status information




Data path (ALU + registers)

- Accumulator (common register construct)
 - special register
 - one of the inputs to ALU
 - output of ALU always stored back in accumulator
- One-address instructions
 - only need operation and address of one operand
 - other operand and destination is accumulator register
 - $AC \leftarrow AC \text{ <op> Mem[addr]}$
 - "single address instructions" (AC implicit operand)
- Multiple registers
 - part of instruction used to choose register operands

 

Data path (bit-slice)

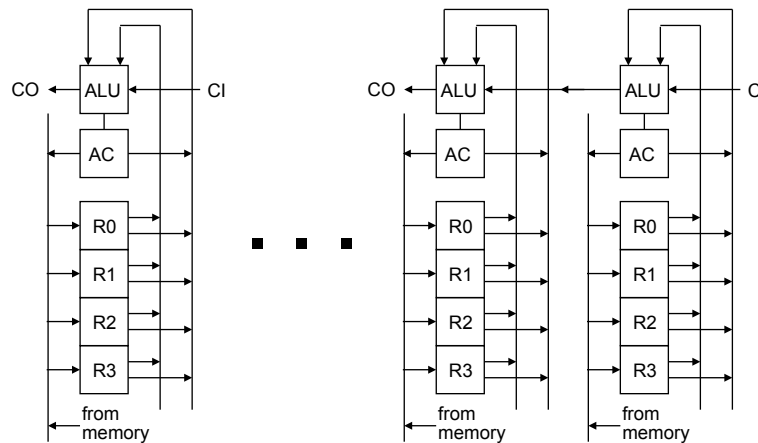- Bit-slice concept – replicate to build n-bit wide datapaths



Instruction path


- Program counter (PC)
 - keeps track of program execution
 - address of next instruction to read from memory
 - may have “auto-increment” feature or use ALU to “add 1”
- Instruction register (IR)
 - current instruction
 - includes ALU operation and address(es) of operand(s)
 - also holds target of jump instruction if branch instruction
 - immediate operands – value represented explicitly in instruction
- Relationship to data path
 - PC may be incremented through ALU
 - contents of IR may also be required as input to ALU – immediate operands

Data path (memory interface)

- Memory
 - separate data and instruction memory (Harvard architecture)
 - two address busses, two data busses
 - single combined memory (Princeton architecture)
 - single address bus, single data bus
- Separate memory
 - ALU output -> data memory input
 - instruction register -> data memory address
 - data memory output -> input to registers
 - program counter -> instruction memory address
 - instruction memory output -> instruction register
- Single memory
 - ALU output -> memory input
 - PC or IR -> address
 - memory output -> instruction or data registers

Block diagram of processor (Harvard)

- Register transfer view of Harvard architecture
 - black arrows represent data-flow between registers
 - blue arrows other are control signals from control FSM (also load control for each register, not shown)
 - 2 MARs (PC and IR)
 - MAR = memory address register
 - 3 MBRs (AC, REG and IR)
 - MBR = memory buffer register

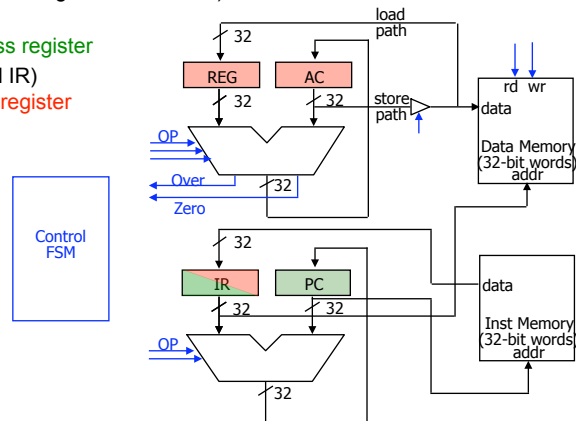


Autumn 2010

CSE370 - XIX - Computer Organization

17

Block diagram of processor (Princeton)

- Register transfer view of Princeton architecture
 - black arrows represent data-flow between registers
 - blue arrows other are control signals from control FSM (also load control and output enable for each register, not shown)
 - 2 MARs (PC and IR) multiplexed (3-state)
 - MAR = memory address register
 - 3 MBRs (AC, REG and IR)
 - MBR = memory buffer register

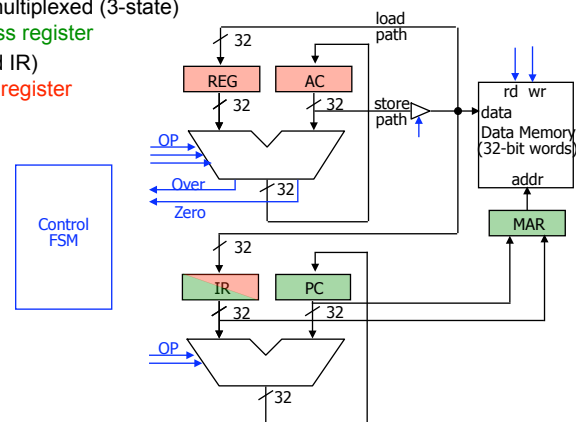

Autumn 2010

CSE370 - XIX - Computer Organization

18

A simplified processor data-path and memory

- Modeled after MIPS R2000
 - Used in 378 text by Patterson & Hennessy
 - Princeton architecture – shared data/instruction memory
 - 32-bit machine
 - 32 register file
 - PC incremented through ALU
 - Multi-cycle instructions in our implementation
 - single-cycle for real R2000, you'll see that in 378
 - Only a subset of the instructions are implemented
 - Synchronous Mealy (Moore) controller

Processor instructions


- Three principal types (32 bits in each instruction)

type	op	rs	rt	rd	shft	funct
R(egister)	6	5	5	5	5	6
I(mmediate)	6	5	5		16	
J(ump)	6			26		

- The instructions we will implement (only a small subset)

R	add	0	rs	rt	rd	0	32	rd = rs + rt	
	sub	0	rs	rt	rd	0	34	rd = rs - rt	
	and	0	rs	rt	rd	0	36	rd = rs & rt	
	or	0	rs	rt	rd	0	37	rd = rs rt	
	slt	0	rs	rt	rd	0	42	rd = (rs < rt)	
I	lw	35	rs	rt	offset			rt = mem[rs + offset]	
	sw	43	rs	rt	offset			mem[rs + offset] = rt	
	beq	4	rs	rt	offset			pc = pc + offset, if (rs == rt)	
J	addi	8	rs	rt	offset			rt = rs + offset	
	j	2	target address						pc = target address
	halt	63	-						stop execution until reset

Our R2000 implementation

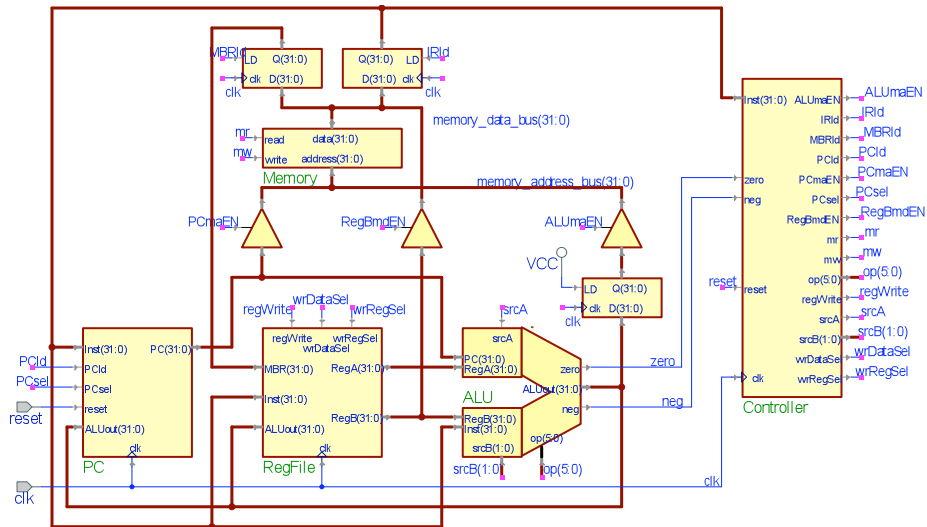

Autumn 2010

CSE370 - XIX - Computer Organization

21

Memory

```

module Memory(address, write, read, data);

    input  [31:0] address;
    input  write, read;
    inout  [31:0] data;

    reg    [31:0] memory[0:255];

    wire   delayed_write;

    assign #10 delayed_write = write;

    always @(posedge delayed_write) begin
        memory[address[7:0]] = data;
    end

    assign data = read ? memory[address[7:0]] : 32'hzzzzzzzz;

endmodule
    
```

Autumn 2010

CSE370 - XIX - Computer Organization

22

Program (compute n^{th} Fibonacci number)

Compiler

```

r0 = mem[254];
r1 = 0;
r2 = 1;

loop:
    if (r0 > 0) goto entry; else goto exit2;

entry:
    r1 = r1 + r2;
    r0 = r0 - 1;

    if (r0 == 0) goto exit1;
    r2 = r2 + r1;
    r0 = r0 - 1;
    if (r0 == 0) goto exit2; else goto loop;

exit1:
    r2 = r1;

exit2:
    mem[255] = r2;
    HALT
    
```

```

r1 = 0
r2 = 1
r0 = mem [ rz + 254 ]

r3 = ( rz < r0 )
if ( r3 == rz ) goto exit2
if ( rz == rz ) goto entry

loop:
    r1 = r1 + r2
    r0 = r0 + ( -1 )

entry:
    if ( r0 == rz ) goto exit1
    r2 = r2 + r1
    r0 = r0 + ( -1 )
    if ( r0 == rz ) goto exit2
    goto loop

exit1:
    r2 = r1 | rz

exit2:
    mem [ rz + 255 ] = r2
    halt
    
```

Memory – initial contents (test fixture)

```

parameter ALU      = 6'h00; // op = 0
parameter LW       = 6'h23; // op = 35
parameter SW       = 6'h2b; // op = 43
parameter BEQ      = 6'h04; // op = 4
parameter ADDI     = 6'h08; // op = 8
parameter J        = 6'h02; // op = 2
parameter HALT     = 6'h3f; // op = 63

parameter ADD      = 6'h20; // funct = 32
parameter SUB     = 6'h22; // funct = 34
parameter AND      = 6'h24; // funct = 36
parameter OR       = 6'h25; // funct = 37
parameter SLT     = 6'h2a; // funct = 42
    
```

```

parameter shftX    = 5'hxx;

parameter r0       = 5'h00;
parameter r1       = 5'h01;
parameter r2       = 5'h02;
parameter r3       = 5'h03;
parameter rz       = 5'h1f;
    
```

```

initial begin
    memory[8'h00] = {ADDI, rz, r1, 16'h0000}; // r1 = 0
    memory[8'h01] = {ADDI, rz, r2, 16'h0001}; // r2 = 1
    memory[8'h02] = {LW, rz, r0, 16'h00fe}; // r0 = mem [ rz + 254 ]
    memory[8'h03] = {ALU, rz, r0, r3, shftX, SLT}; // r3 = ( rz < r0 )
    memory[8'h04] = {BEQ, r3, rz, 16'h0009}; // if ( r3 == rz ) goto exit2
    memory[8'h05] = {BEQ, rz, rz, 16'h0002}; // if ( rz == rz ) goto entry /* goto entry
    memory[8'h06] = {ALU, r1, r2, r1, shftX, ADD}; // loop: r1 = r1 + r2
    memory[8'h07] = {ADDI, r0, r0, 16'hffff}; // r0 = r0 + ( -1 )
    memory[8'h08] = {BEQ, r0, rz, 16'h0004}; // entry: if ( r0 == rz ) goto exit1
    memory[8'h09] = {ALU, r2, r1, r2, shftX, ADD}; // r2 = r2 + r1
    memory[8'h0a] = {ADDI, r0, r0, 16'hffff}; // r0 = r0 + ( -1 )
    memory[8'h0b] = {BEQ, r0, rz, 16'h0002}; // if ( r0 == rz ) goto exit2
    memory[8'h0c] = {J, 26'h00000006}; // goto loop
    memory[8'h0d] = {ALU, r1, rz, r2, shftX, OR}; // exit1: r2 = r1 | rz /* r2 = r1
    memory[8'h0e] = {SW, rz, r2, 16'h00ff}; // exit2: mem [ rz + 255 ] = r2
    memory[8'h0f] = {HALT, 26'hxxxxxxx}; // halt

    memory[8'hfe] = 32'h00000004; // this is the input N
end
    
```

ALU

```
module ALU(RegA, PC, Inst, RegB, op, srcA, srcB, ALUout, zero, neg);

    input  [31:0] RegA;
    input  [31:0] PC;
    input  [31:0] Inst;
    input  [31:0] RegB;
    input  [5:0] op;
    input  srcA;
    input  [1:0] srcB;
    output [31:0] ALUout;
    output zero, neg;

    wire  [31:0] A;
    reg   [31:0] B;
    reg   [31:0] result;
    reg   zero;
    reg   neg;

    assign A = (srcA) ? PC : RegA;

    always @(Inst or RegB or srcB) begin
        case (srcB)
            2'b00: B = RegB;
            2'b01: B = 32'h00000000;
            2'b10: B = {Inst[15], Inst[15], Inst[15], Inst[15], Inst[15], Inst[15],
                Inst[15], Inst[15], Inst[15], Inst[15], Inst[15], Inst[15],
                Inst[15], Inst[15], Inst[15], Inst[15], Inst[15:0]};
            2'b11: B = 32'h00000001;
        endcase
    end

    always @(A or B or op) begin
        case (op)
            6'b000001: result = A + B;
            6'b000010: result = A - B;
            6'b000100: result = A & B;
            6'b001000: result = A | B;
            6'b010000: result = A;
            6'b100000: result = B;
            default: result = 32'hxxxxxxxx;
        endcase
        zero = (result == 32'h00000000);
        neg = result[31];
    end

    assign ALUout = result;
endmodule
```

Registers and 3-state drivers

```
module Reg32_LD(D, LD, Q, clk);

    input  [31:0] D;
    input  LD;
    output [31:0] Q;
    input  clk;

    reg   [31:0] Q;

    always @(posedge clk) begin
        if (LD) Q = D;
    end
endmodule

module Tri32(I, OE, O);

    input  [31:0] I;
    input  OE;
    output [31:0] O;

    assign O = (OE) ? I : 32'hzzzzzzzz;
endmodule
```

PC – a special register

```
module PC(ALUout, Inst, reset, PCsel, PCld, clk, PC);

    input  [31:0] ALUout;
    input  [31:0] Inst;
    input  reset, PCsel, PCld, clk;
    output [31:0] PC;

    reg    [31:0] PC;
    wire   [31:0] src;

    assign src = PCsel ? ALUout : {6'b000000, Inst[25:0]};

    always @(posedge clk) begin
        if (reset) PC = 32'h00000000;
        else
            if (PCld) PC = src;
        end
    end
endmodule
```

Register file

```
module RegFile(MBR, ALUout, Inst, regWrite, wrDataSel, wrRegSel, RegA, RegB, clk);

    input  [31:0] MBR;
    input  [31:0] ALUout;
    input  [31:0] Inst;
    input  regWrite, wrDataSel, wrRegSel;
    output [31:0] RegA;
    output [31:0] RegB;
    input  clk;

    wire   [4:0] rs, rt, rd, wrReg;
    wire   [31:0] wrData;

    reg    [31:0] RegFile[0:31];
    reg    [31:0] RegA, RegB;

    initial begin
        RegFile[31] = 0;
    end

    assign rs = Inst[25:21];
    assign rt = Inst[20:16];
    assign rd = Inst[15:11];

    assign wrReg = wrRegSel ? rd : rt;

    assign wrData = wrDataSel ? MBR : ALUout;

    always @(posedge clk) begin
        RegA = RegFile[rs];
        RegB = RegFile[rt];
        if (regWrite && (wrReg != 31)) begin
            RegFile[wrReg] = wrData;
        end
    end
endmodule
```

Tracing an instruction's execution


- Instruction: $r3 = r1 + r2$

R	0	rs=r1	rt=r2	rd=r3	shft=X	funct=32
---	---	-------	-------	-------	--------	----------

- instruction fetch
 - move instruction address from PC to memory address bus
 - assert memory read
 - move data from memory data bus into IR
 - configure ALU to add 1 to PC
 - configure PC to store new value from ALUout
- instruction decode
 - op-code bits of IR are input to control FSM
 - rest of IR bits encode the operand addresses (rs and rt) – these go to register file
- instruction execute
 - set up ALU inputs
 - configure ALU to perform ADD operation
 - configure register file to store ALU result (rd)


Tracing an instruction's execution (cont'd)

Step 1: $IR \leftarrow mem[PC];$

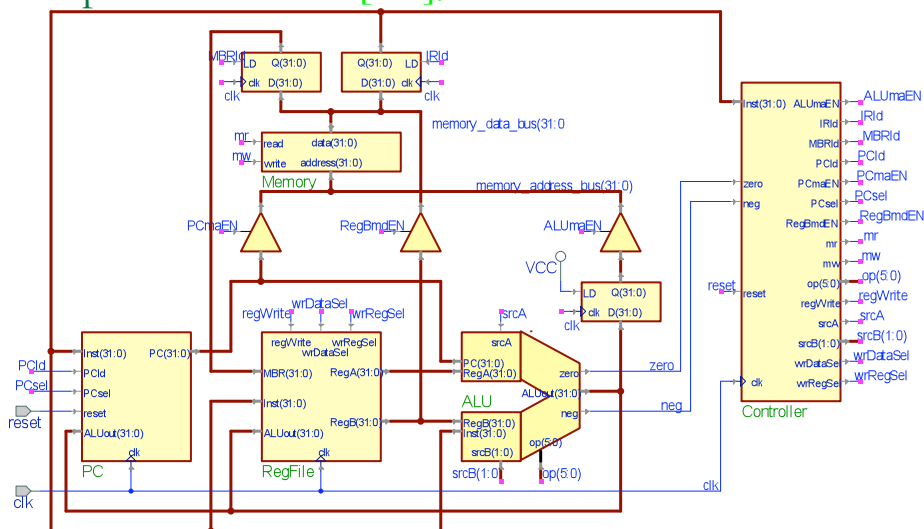


Tracing an instruction's execution (cont'd)

Step 1: $IR \leftarrow \text{mem}[PC];$

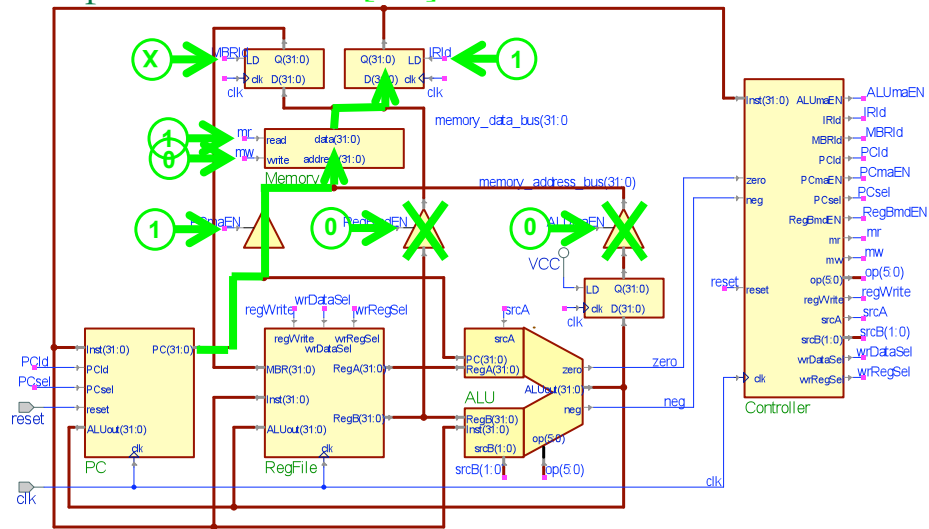

Tracing an instruction's execution (cont'd)

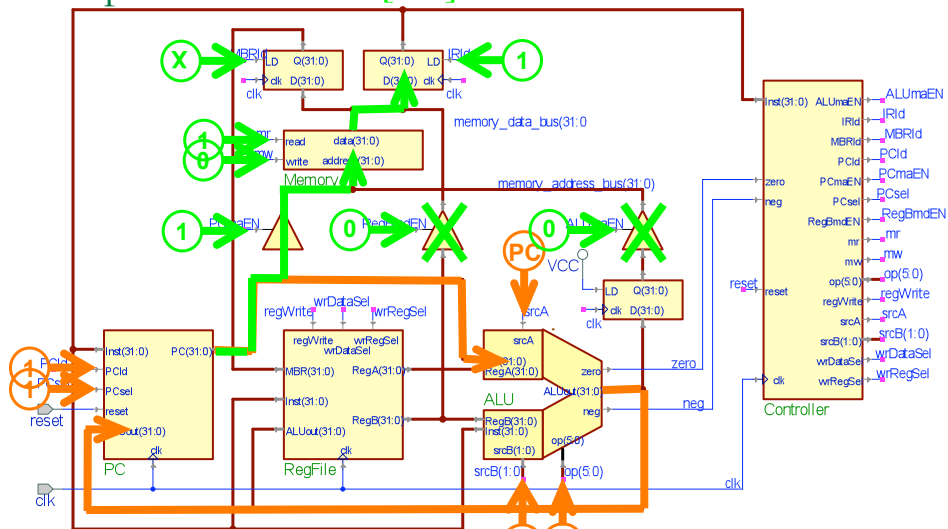Step 1: $IR \leftarrow \text{mem}[PC]; PC \leftarrow PC + 1;$




Tracing an instruction's execution (cont'd)

Step 1: $IR \leftarrow \text{mem}[PC]$; $PC \leftarrow PC + 1$;

- Control signals
 - $PCmaEN = 1$;
 - $mr = 1$;
 - $IRId = 1$;
 - $ALUmaEN = 0$;
 - $mw = 0$;
 - $RegBmdEN = 0$;
 - $srcA = "PC" = 1$;
 - $srcB = "1" = 2'b11$;
 - $op = "+" = 6'b000001$;
 - $PCId = 1$;
 - $PCsel = 1$;
- But, also . . .
 - $regWrite = 0$;
 - $wrDataSel = X$;
 - $wrRegSel = X$;
 - $MBRId = X$;
- At end of cycle, IR is loaded with instruction that will be seen by controller
 - But, control signals for instruction can't be output until next cycle
 - One cycle just for signals to propagate (Step 2)


Tracing an instruction's execution (cont'd)

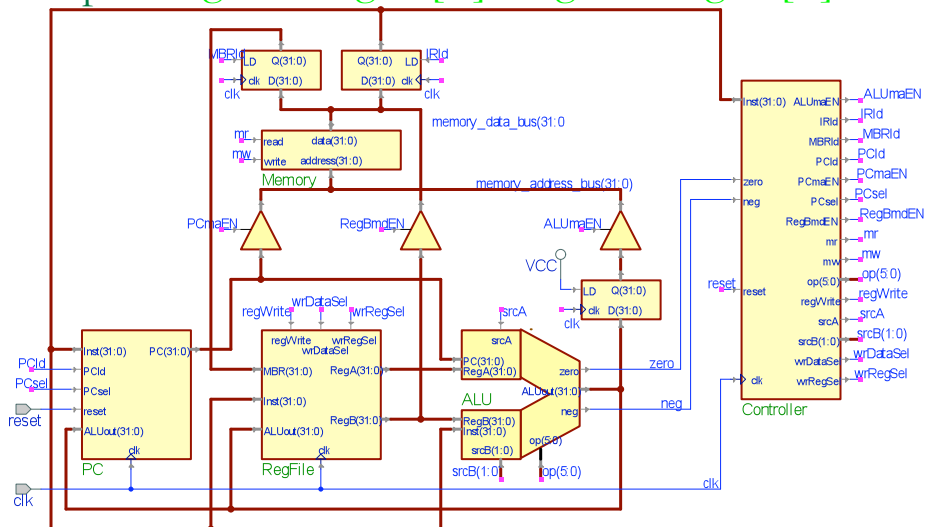Step 2: $RegA \leftarrow \text{regfile}[rs]$; $RegB \leftarrow \text{regfile}[rt]$;



Tracing an instruction's execution (cont'd)

Step 2: $\text{RegA} \leftarrow \text{regfile}[\text{rs}]; \text{RegB} \leftarrow \text{regfile}[\text{rt}];$

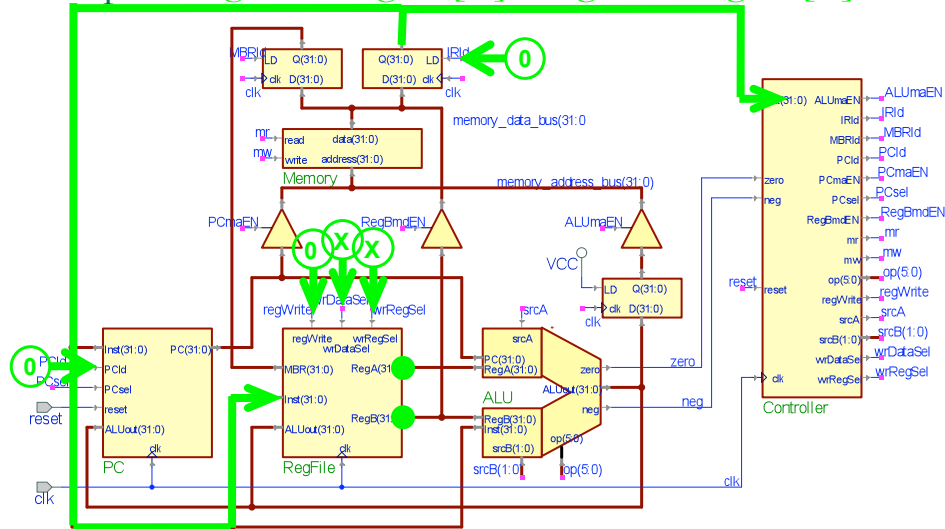

Autumn 2010

CSE370 - XIX - Computer Organization

35

Tracing an instruction's execution (cont'd)

Step 2: $\text{RegA} \leftarrow \text{regfile}[\text{rs}]; \text{RegB} \leftarrow \text{regfile}[\text{rt}];$

Control signals

- PCmaEN = 0;
- mr = X;
- IRld = 0;
- ALUaEN = 0;
- mw = 0;
- RegBmdEN = 0;
- regWrite = 0;
- PCld = 0;
- PCsel = X;

But, also . . .

- srcA = X;
- srcB = 2'bX;
- op = 6'bXXXXXX;
- wrDataSel = X;
- wrRegSel = X;
- MBRld = X;


Autumn 2010

CSE370 - XIX - Computer Organization

36


Tracing an instruction's execution (cont'd)

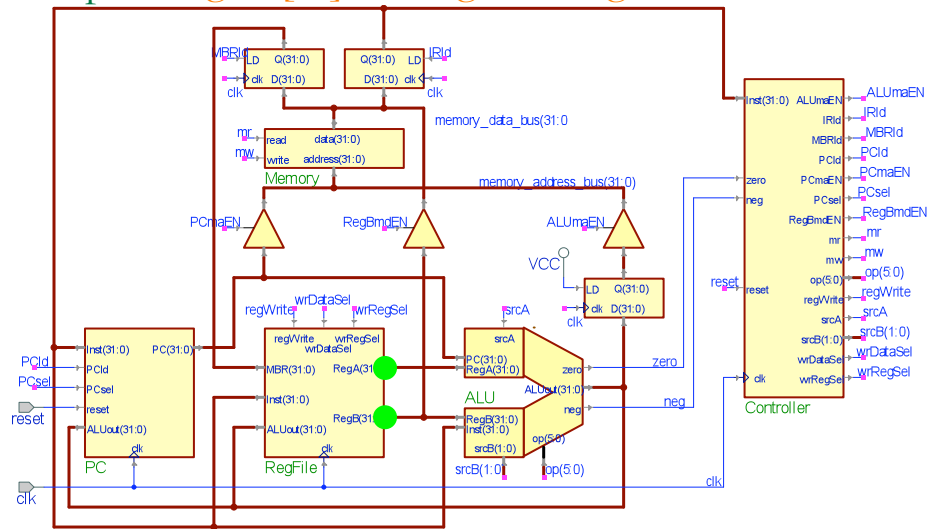Step 3: $\text{Regfile}[rd] \leftarrow \text{RegA} + \text{RegB};$



Tracing an instruction's execution (cont'd)

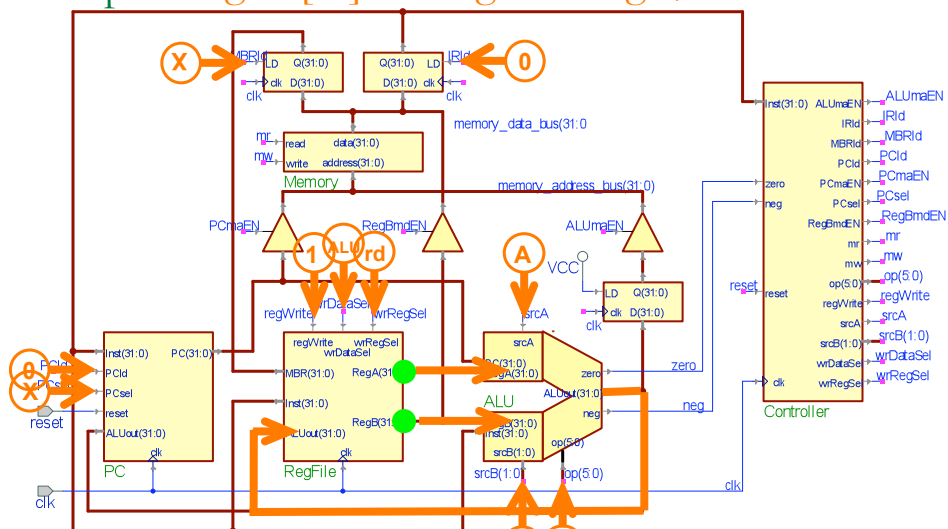Step 3: $\text{Regfile}[rd] \leftarrow \text{RegA} + \text{RegB};$



Tracing an instruction's execution (cont'd)

Step 3: $\text{Regfile}[\text{rd}] \leftarrow \text{RegA} + \text{RegB};$

■ Control signals

- $\text{PCmaEN} = 0;$
- $\text{mr} = X;$
- $\text{IRId} = 0;$
- $\text{ALUmaEN} = 0;$
- $\text{mw} = 0;$
- $\text{RegBmdEN} = 0;$
- $\text{srcA} = \text{"A"} = 0;$
- $\text{srcB} = \text{"B"} = 2'b00;$
- $\text{op} = \text{"+"} = 6'b000001;$
- $\text{regWrite} = 1;$
- $\text{wrDataSel} = \text{"ALU"} = 0;$
- $\text{wrRegSel} = \text{"rd"} = 1;$

■ But, also . . .

- $\text{PCId} = 0;$
- $\text{PCsel} = X;$
- $\text{MBRId} = X;$

Register-transfer-level description

■ Control

- transfer data between registers by asserting appropriate control signals


■ Register transfer notation - work from register to register

- instruction fetch:
 - $\text{mabus} \leftarrow \text{PC};$ – move PC to memory address bus (PCmaEN , ALUmaEN)
 - memory read; – assert memory read signal (mr)
 - $\text{IR} \leftarrow \text{memory};$ – load IR from memory data bus (IRId)
 - $\text{op} \leftarrow \text{add}$ – send PC into A input, 1 into B input, add ($\text{PC} + 1$)
(srcA , $\text{srcB}[1:0]$, op)
 - $\text{PC} \leftarrow \text{ALUout}$ – load result of incrementing in ALU into PC (PCId , PCsel)
- instruction decode:
 - IR to controller
 - values of A and B read from register file (rs , rt)
- instruction execution:
 - $\text{op} \leftarrow \text{add}$ – send regA into A input, regB into B input, add ($\text{A} + \text{B}$)
(srcA , $\text{srcB}[1:0]$, op)
 - $\text{rd} \leftarrow \text{ALUout}$ – store result of add into destination register
(regWrite , wrDataSel , wrRegSel)

Register-transfer-level description (cont'd)


- How many states are needed to accomplish these transfers?
 - data dependencies (where do values that are needed come from?)
 - resource conflicts (ALU, busses, etc.)
- In our case, it takes three cycles
 - one for each step
 - all operations within a cycle occur between rising edges of the clock
- How do we set all of the control signals to be output by the state machine?
 - depends on the type of machine (Mealy, Moore, synchronous Mealy)

Review of FSM timing

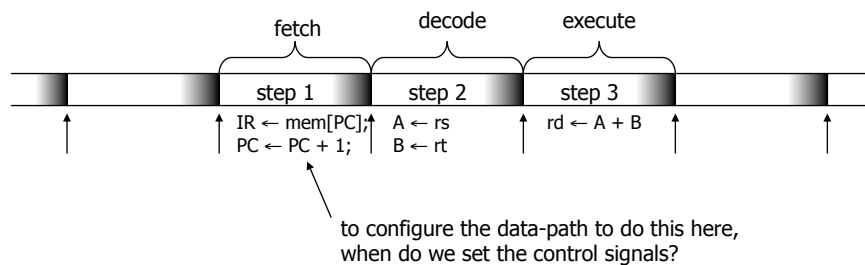

FSM controller for CPU (skeletal Moore FSM)

 
- First pass at deriving the state diagram (Moore machine)
 - these will be further refined into sub-states



FSM controller for CPU (reset and inst. fetch)


- Assume Moore machine
 - outputs associated with states rather than arcs
- Reset state and instruction fetch sequence
- On reset (go to Fetch state)
 - start fetching instructions
 - PC will set itself to zero

 $mabus \leftarrow PC;$
 $memory\ read;$
 $IR \leftarrow memory\ data\ bus;$
 $PC \leftarrow PC + 1;$




FSM controller for CPU (decode)

 - Operation decode state
 - next state branch based on operation code in instruction
 - read two operands out of register file
 - what if the instruction doesn't have two operands?




FSM controller for CPU (instruction execution)

 - For add instruction
 - configure ALU and store result in register
 - $rd \leftarrow A + B$
 - other instructions may require multiple cycles



FSM controller for CPU (add instruction)

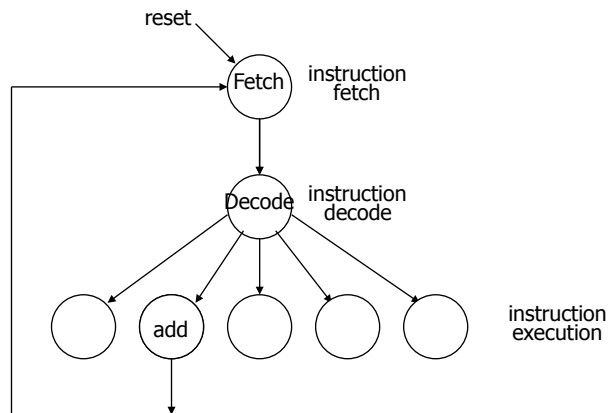- Putting it all together and closing the loop
 - the famous instruction fetch decode execute cycle




FSM controller for CPU

- Now we need to repeat this for all the instructions of our processor
 - fetch and decode states stay the same
 - different execution states for each instruction
 - some may require multiple states if available register transfer paths require sequencing of steps


Tracing an instruction's execution (LW)

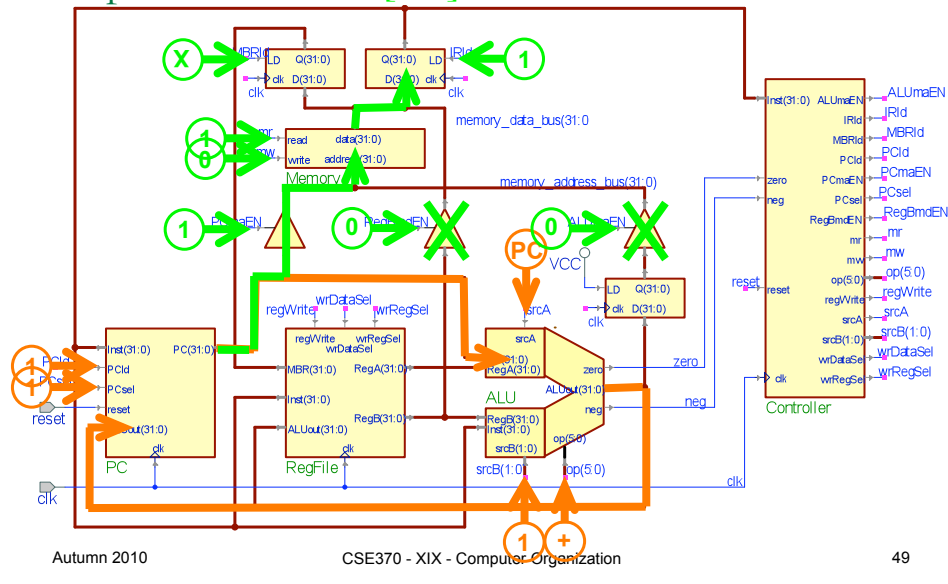Step 1: $IR \leftarrow \text{mem}[PC]; PC \leftarrow PC + 1;$




Tracing an instruction's execution (LW cont'd)

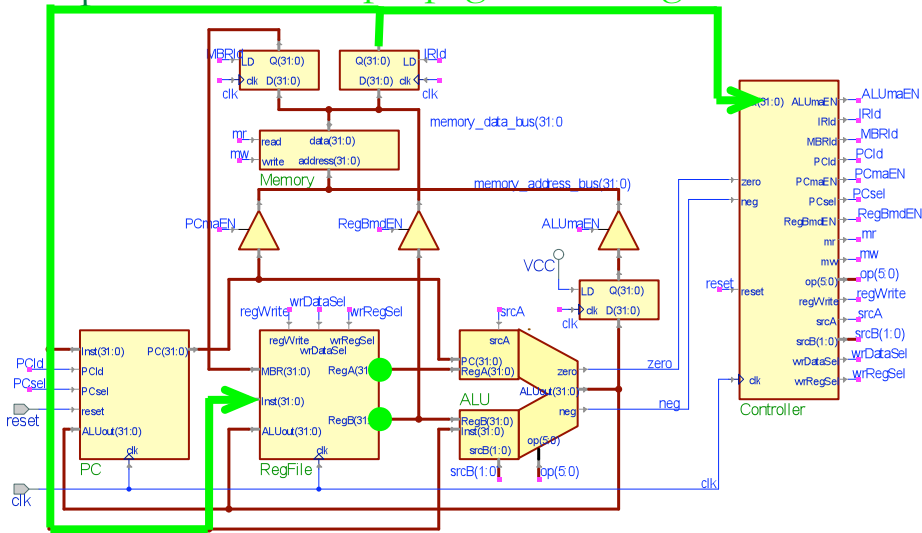Step 2: Instruction propagates through controller




Tracing an instruction's execution (LW cont'd)

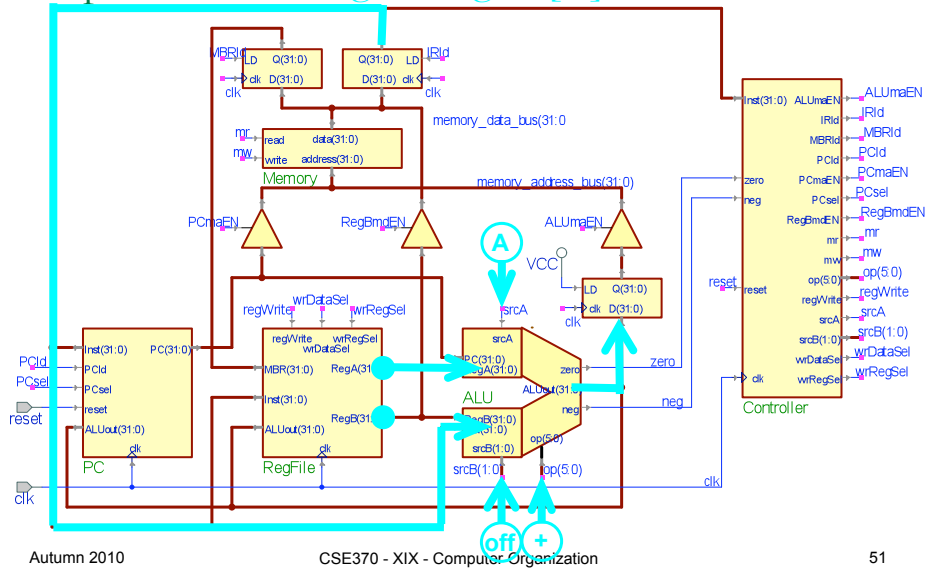Step 3: $ALUoutReg \leftarrow regfile[rs] + offset;$




Tracing an instruction's execution (LW cont'd)

Step 4: $MBR \leftarrow mem[ALUoutReg];$

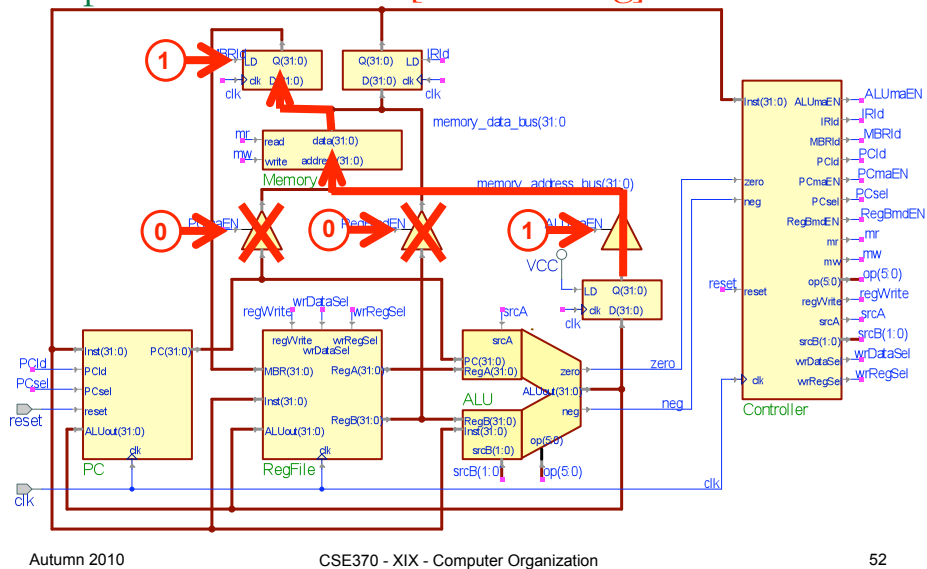

Tracing an instruction's execution (LW cont'd)

Step 5: $\text{regfile}[rt] \leftarrow \text{MBR};$

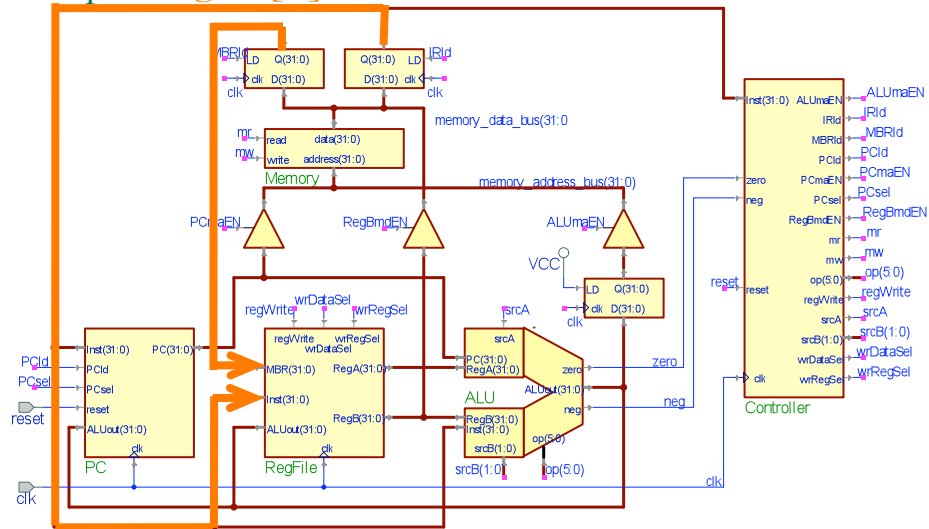

Autumn 2010

CSE370 - XIX - Computer Organization

53

Controller signals for all cycles (LW cont'd)


Control signals for:	Fetch	Decode	LW1	LW2	LW3
PCmaEN =	1	0			
ALUmaEN =	0	0			
RegBmdEN =	0	0			
mr =	1	X			
mw =	0	0			
IRld =	1	0			
MBRld =	X	X			
srcA =	"PC"	X			
srcB =	"4"	X			
op =	"+"	X			
regWrite =	0	0			
wrDataSel =	X	X			
wrRegSel =	X	X			
PCld =	1	0			
PCsel =	1	X			

Autumn 2010

CSE370 - XIX - Computer Organization

54

FSM controller (complete state diagram)

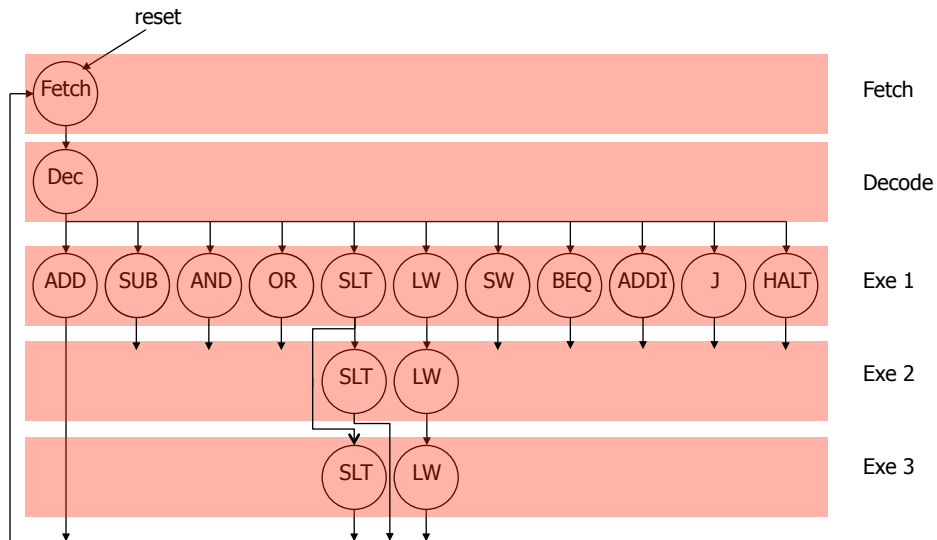

Autumn 2010

CSE370 - XIX - Computer Organization

55

Controller

```
module Controller(Inst, neg, zero, reset, clk,
  srcA, srcB, op, mr, mw, PCmaEN, ALUmaEN,
  RegBmdEN, MBRld, IRld, regWrite,
  wrDataSel, wrRegSel, PCsel, PClid);
```

```
input [31:0] Inst;
input neg, zero, reset, clk;

output srcA;
output [1:0] srcB;
output [5:0] op;
output MBRld, IRld, regWrite;
output wrDataSel, wrRegSel, PCsel, PClid;
output mr, mw, PCmaEN, ALUmaEN, RegBmdEN;
```

```
reg srcA;
reg MBRld, IRld, regWrite;
reg wrDataSel, wrRegSel, PCsel, PClid;
reg mr, mw, PCmaEN, ALUmaEN, RegBmdEN;
reg [5:0] op;
reg [1:0] srcB;

reg [2:0] state;

wire [5:0] instOp;
wire [5:0] instSubOp;
```

```
parameter ALU = 6'h00; // op = 0
parameter LW = 6'h23; // op = 35
parameter SW = 6'h2b; // op = 43
parameter BEQ = 6'h04; // op = 4
parameter ADDI = 6'h08; // op = 8
parameter J = 6'h02; // op = 2
parameter HALT = 6'h3f; // op = 63
parameter ADD = 6'h20; // funct = 32
parameter SUB = 6'h22; // funct = 34
parameter AND = 6'h24; // funct = 36
parameter OR = 6'h25; // funct = 37
parameter SLT = 6'h2a; // funct = 42
parameter DONTCARE = 6'hxx;
```

```
parameter fetch = 3'b000;
parameter decode = 3'b100;
parameter executel = 3'b001;
parameter execute2 = 3'b010;
parameter execute3 = 3'b011;
parameter BADSTATE = 3'bxxx;
```

```
parameter srcAreg = 1'b0;
parameter srcAPC = 1'b1;
parameter srcBreg = 2'b00;
parameter srcBzero = 2'b01;
parameter srcBimmed = 2'b10;
parameter srcBone = 2'b11;
parameter aluAdd = 6'b000001;
parameter aluSub = 6'b000010;
parameter aluAnd = 6'b000100;
parameter aluOr = 6'b001000;
parameter aluPassA = 6'b010000;
parameter aluPassB = 6'b100000;
parameter pcSelTarget = 1'b0;
parameter pcSelALU = 1'b1;
parameter regALU = 1'b0;
parameter regMBR = 1'b1;
parameter regRT = 1'b0;
parameter regRD = 1'b1;
```

Autumn 2010

CSE370 - XIX - Computer Organization

56

Controller

```
assign instOp = Inst[31:26];
assign instSubOp = Inst[5:0];

always @(posedge clk) begin
  if (reset) begin
    state = fetch; end
  else begin
    casex ({state, instOp, instSubOp})
      {fetch, DONTCARE, DONTCARE}: state = decode; // fetch cycle
      {decode, DONTCARE, DONTCARE}: state = execute1; // decode cycle
      {execute1, ALU, ADD}: state = fetch; // execute cycle for ALU-ADD
    // FILL IN REST OF STATES FOR SUB, AND, and OR
      {execute1, ALU, SLT}: state = (neg ? execute2 : execute3); // 1st execute cycle for ALU-SLT,
                                                                    // branch depending on comparison
      {execute2, ALU, SLT}: state = fetch; // 2nd execute cycle for ALU-SLT when rs < rt
      {execute3, ALU, SLT}: state = fetch; // 2nd execute cycle for ALU-SLT when rs >= rt
      {execute1, LW, DONTCARE}: state = execute2; // 1st execute cycle for LW
      {execute2, LW, DONTCARE}: state = execute3; // 2nd execute cycle for LW
      {execute3, LW, DONTCARE}: state = fetch; // 3rd execute cycle for LW
      {execute1, SW, DONTCARE}: state = execute2; // 1st execute cycle for SW
    // FILL IN REST OF STATES FOR SW, BEQ, ADDI, J, and HALT
      default: state = BADSTATE; // should never get here
    endcase
  end
end
```

Controller

```
always @(state) begin

  // Set defaults that may be overwritten in case statement, just to be safe
  IRld = 0; MBRld = 0; PCld = 0; regWrite = 0;
  mr = 0; mw = 0; ALUmaEN = 0; PCmaEN = 0; RegBmdEN = 0;

  casex ({state, instOp, instSubOp})

    {fetch, DONTCARE, DONTCARE}: begin
      // fetch the instruction and load it into instruction register
      PCmaEN = 1;
      mr = 1;
      IRld = 1;
      // increment PC
      srcA = srcAPC;
      srcB = srcBone;
      op = aluAdd;
      PCsel = pcSelALU;
      PCld = 1;
    end

    {decode, DONTCARE, DONTCARE}: begin
      // propagate signals into controller, nothing to do
    end

    {execute1, ALU, DONTCARE}: begin
      srcA = srcAreg;
      srcB = srcBreg;
      case (instSubOp)
        ADD: op = aluAdd;
        SUB: op = aluSub;
        AND: op = aluAnd;
        OR: op = aluOr;
        SLT: op = aluSub;
      endcase
      wrRegSel = regRD;
      wrDataSel = regALU;
      regWrite = 1;
    end
  end
```

Controller

```

{execute2, ALU,      SLT}: begin
    // rs < rt, load a one into rd
    srcB = srcBone;
    op = aluPassB;
    wrDataSel = regALU;
    wrRegSel = regRD;
    regWrite = 1;
end

{execute3, ALU,      SLT}: begin
    // rs > rt, load a zero into rd
    srcB = srcBzero;
    op = aluPassB;
    wrDataSel = regALU;
    wrRegSel = regRD;
    regWrite = 1;
end


{execute1, LW,       DONTCARE}: begin
    // compute address by adding rs + offset
// FILL IN OTHER STATES AND CONTROL SIGNALS FOR FIRST LW EXECUTE STATE
end

{execute2, LW,       DONTCARE}: begin
    // read from memory into MBR
// FILL IN OTHER STATES AND CONTROL SIGNALS FOR SECOND LW EXECUTE STATE
end

{execute3, LW,       DONTCARE}: begin
    // write MBR into register file's rt
// FILL IN OTHER STATES AND CONTROL SIGNALS FOR THIRD LW EXECUTE STATE
end

{execute1, SW,       DONTCARE}: begin
    // compute address by adding rs + offset
// FILL IN OTHER STATES AND CONTROL SIGNALS FOR FIRST SW EXECUTE STATE
end
// FILL IN OTHER STATES AND CONTROL SIGNALS FOR SW, BEQ, ADDI, J, and HALT
endcase
end
endmodule
    
```

Simulation of the processor

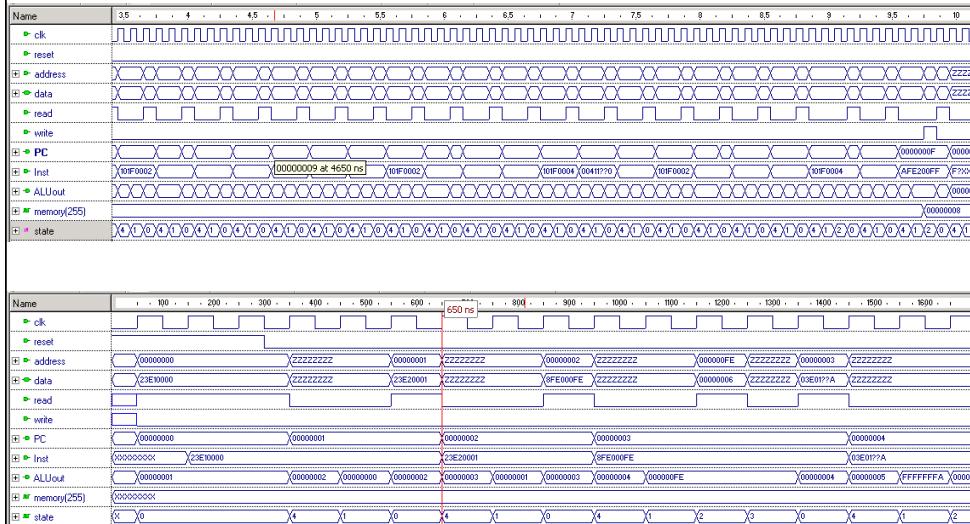

Estimating performance


- Recall basic constraint equations:

- $T_{\text{period}} > T_{\text{FFprop}} + T_{\text{delay}} + T_{\text{setup}}$
- $T_{\text{prop}} > T_{\text{hold}}$ (this is usually designed in to the FFs and is not our concern)

- Clock period is maximum of T_{period} along all possible paths in the circuit between flip-flops

- Clock period = 1/frequency = $\max(T_{\text{period}})$ over all paths
- Assuming all FFs are the same:

 
$$\max(T_{\text{period}}) = T_{\text{FFprop}} + \max(T_{\text{delay}}) + T_{\text{setup}}$$



Paths between FFs during “fetch” and “decode”


$$T_{\text{delay}} = T_{\text{3state}} + T_{\text{memoryread}} + T_{\text{wires}}$$

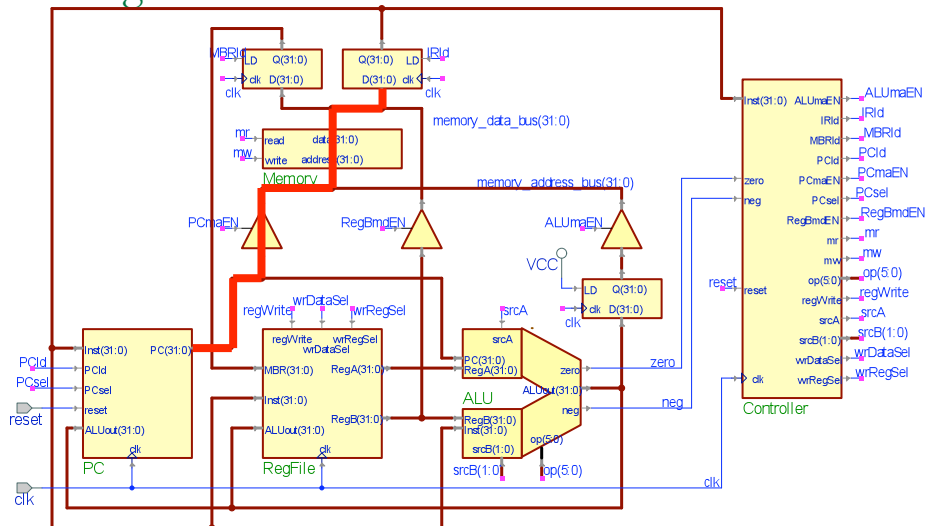Assume T_{wires} is small and can be ignored.
Note: this is **NOT TRUE** in modern chip design



Paths between FFs during “fetch” and “decode”

$$T_{\text{delay}} = T_{\text{Amux}} + T_{\text{ALU}} + T_{\text{PCmux}}$$

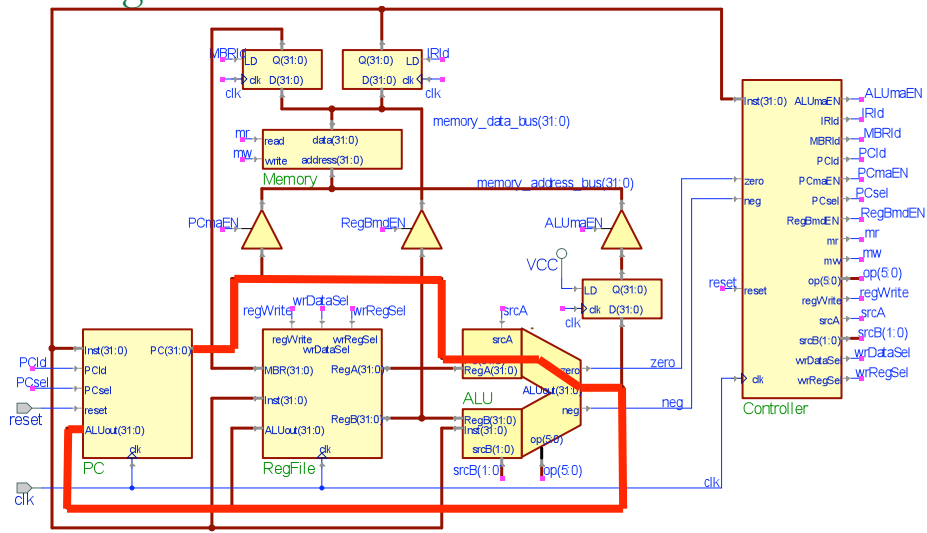


Autumn 2010

CSE370 - XIX - Computer Organization

63

Paths between FFs during “fetch” and “decode”

$$T_{\text{delay}} = T_{\text{RegFileRead}}$$

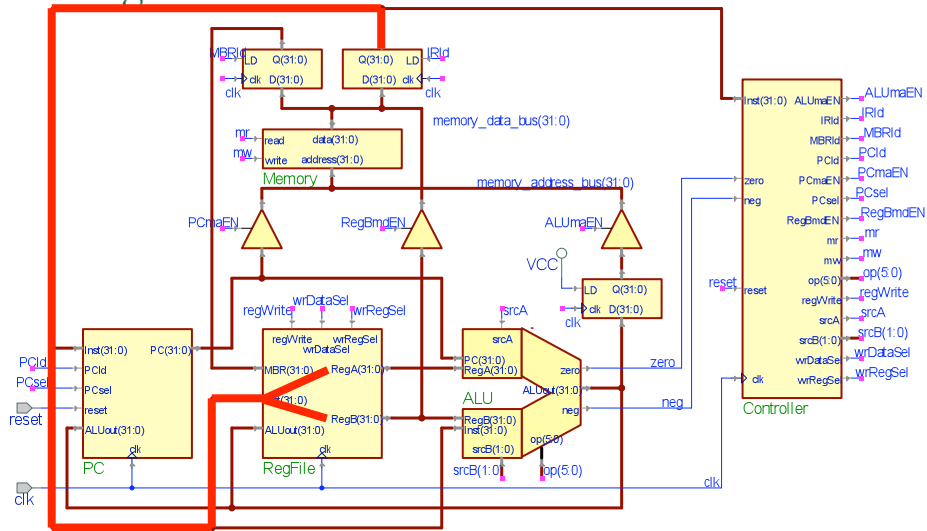


Autumn 2010

CSE370 - XIX - Computer Organization

64

Paths between FFs during “fetch” and “decode”

$$T_{\text{delay}} = T_{\text{Controller}}$$

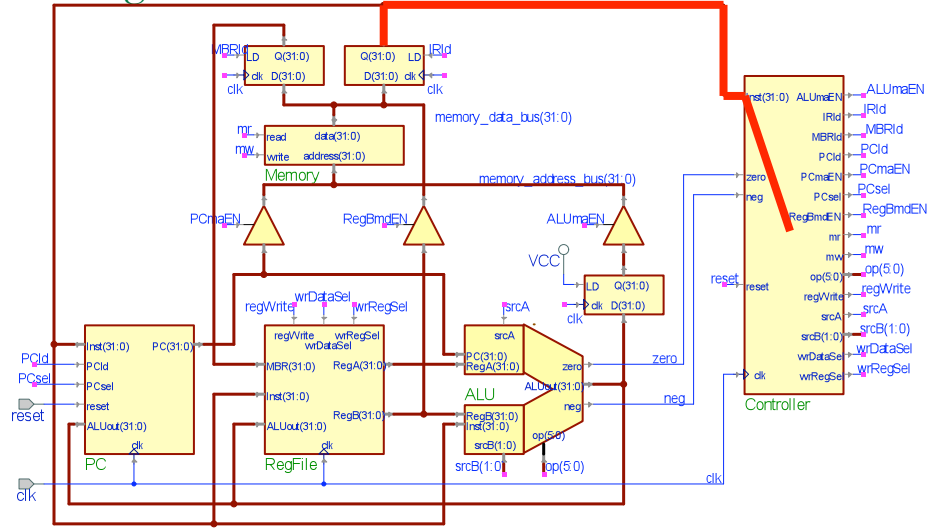

Autumn 2010

CSE370 - XIX - Computer Organization

65

Estimating performance for “fetch” and “decode” cycles

- $\text{Max}(T_{\text{delay}}) = \text{Max of the paths on previous four slides}$
 - $T_{3\text{state}} + T_{\text{memoryread}}$
 - $T_{\text{Amux}} + T_{\text{ALU}} + T_{\text{PCmux}}$
 - $T_{\text{RegFileRead}}$
 - $T_{\text{controller}}$
- Which is likely to be largest?
 - $T_{3\text{state}}$, T_{Amux} and T_{PCmux} are likely to be small
 - $T_{\text{RegFileRead}}$ is larger (32 register memory – large tri-state mux)
 - T_{ALU} is probably larger as it includes a 32-bit carry (lookahead?)
 - $T_{\text{memoryread}}$ is an even larger array (typically an important factor)
 - $T_{\text{controller}}$ is the wild card (depends on complexity of logic in FSM)


Autumn 2010

CSE370 - XIX - Computer Organization

66

Other paths between FFs during “execute” (only partial)

$$T_{\text{delay}} = T_{\text{3state}} + T_{\text{memorywrite}}$$

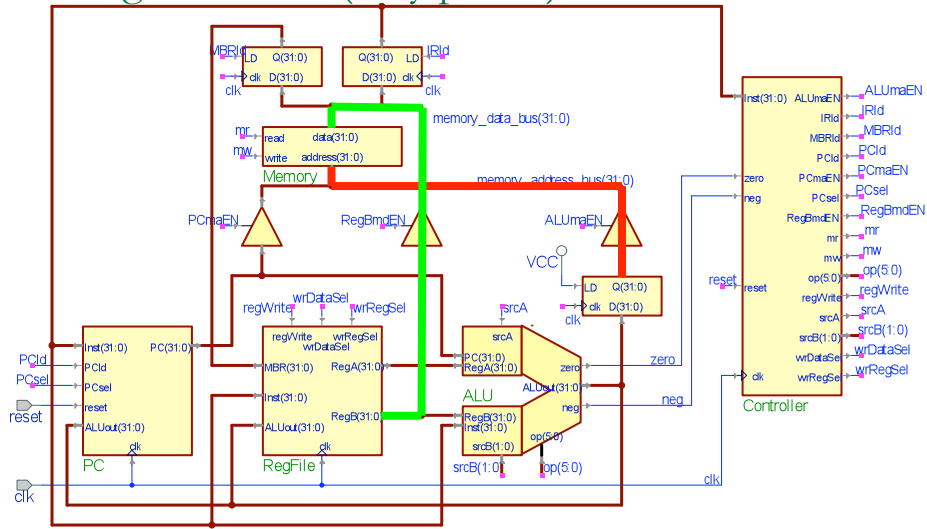


Autumn 2010

CSE370 - XIX - Computer Organization

67

Other paths between FFs during “execute” (only partial)

$$T_{\text{delay}} = T_{\text{Bmux}} + T_{\text{ALU}} + T_{\text{controller}}$$

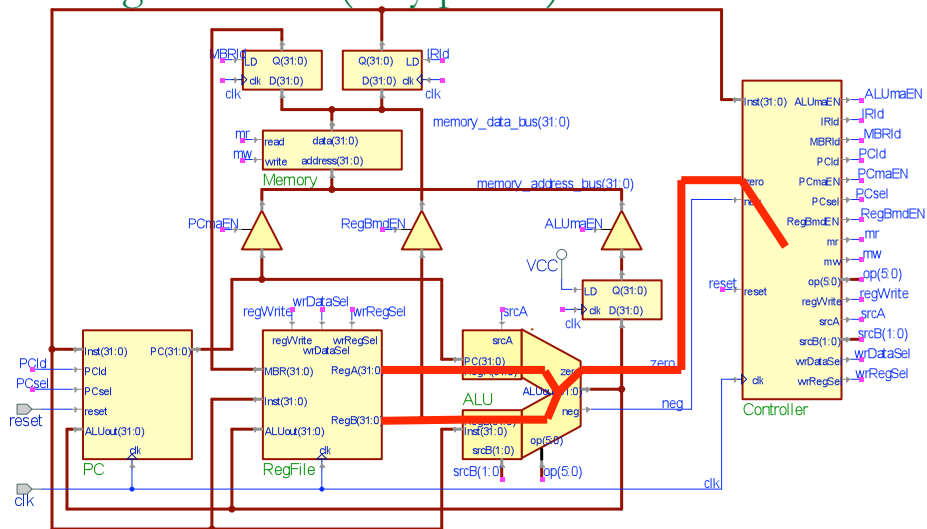

Autumn 2010

CSE370 - XIX - Computer Organization

68

Estimating performance for “execute” cycles

- $\text{Max}(T_{\text{delay}}) = \text{Max of previous as well as}$
 - $T_{\text{3state}} + T_{\text{memorywrite}}$
 - $T_{\text{Bmux}} + T_{\text{ALU}} + T_{\text{controller}}$
- Now T_{ALU} and $T_{\text{controller}}$ are added together
 - These are two of our potentially largest delays
 - Adding them together will almost surely be the maximum
 - How could this path be broken up so that we separate the ALU and controller's delays?

Other factors in estimating performance

- Off-chip communication is much slower than on-chip
 - T_{wires} can't always be ignored
 - Try to keep communicating elements on one chip
 - Separate onto separate chips at clock boundaries
- Add registers to data-path to separate long propagation delays into smaller pieces
 - Adds more cycles to operations
 - But each cycle is smaller
 - Which is better?
 - more numerous cycles of simple and fast operations
 - fewer cycles of complex and slow operations
- This is what computer architecture is about – see CSE 378