

Homework 6 solutions**The Table**

Opcode	X_i	Y_i	Z_i	C_0	F_i	C_{i+1}	N	C	Z	V
ADD	A_i	B_i	C_i	0	S_i	Z_{i+1}	F7	C8	nor (F0..F7)	$C8_{xorX7}$
INC	A_i	0	C_i	1	S_i	Z_{i+1}	F7	C8	nor (F0..F7)	$C8_{xorX7}$
DEC	A_i	1	C_i	0	S_i	Z_{i+1}	F7	C8	nor (F0..F7)	$C8_{xorX7}$
SUB	A_i	$\sim B_i$	C_i	1	S_i	Z_{i+1}	F7	C8	nor (F0..F7)	$C8_{xorX7}$
CMP	A_i	$\sim B_i$	C_i	1	S_i	Z_{i+1}	F7	C8	nor (F0..F7)	$C8_{xorX7}$
PASS	A_i	0	0	x	S_i	x	F7	C8/0	nor (F0..F7)	$C8_{xorX7}/0$
NEG	$\sim A_i$	0	C_i	1	S_i	Z_{i+1}	F7	x	nor (F0..F7)	$C8_{xorX7}$
XOR	A_i	B_i	0	x	S_i	x	F7	0	nor (F0..F7)	0
XNOR	A_i	$\sim B_i$	0	x	S_i	x	F7	0	nor (F0..F7)	0
NOT	$\sim A_i$	0	0	x	S_i	x	F7	0	nor (F0..F7)	0
AND	A_i	B_i	0	x	Z_{i+1}	x	F7	0	nor (F0..F7)	0
OR	A_i	B_i	1	x	Z_{i+1}	x	F7	0	nor (F0..F7)	0
SHL	x	x	x	x	A_{i-1}	x	F7	A7	nor (F0..F7)	0
SHR	x	x	x	x	A_{i+1}	x	F7	0	nor (F0..F7)	0


Design Notes


- Implement AND by setting C_i to 0 and selecting the result from Z_{i+1} (Carry out of the full adder). $Z_{i+1} = X_i Y_i + Z_i Y_i + Z_i X_i$. If we set X_i to 0, then $Z_{i+1} = X_i Y_i$
- Implement AND by setting X_i to 1 and selecting the result from Z_{i+1} . $Z_{i+1} = X_i Y_i + Z_i Y_i + Z_i X_i$. If we set X_i to 1, then $Z_{i+1} = X_i Y_i + (X_i + Y_i) = X_i + Y_i$.
- Note that PASS looks more like a logical operation than like an arithmetic operation. If we think of it this way, the control lines get a little easier to optimize. C and V for PASS will always be zero either way, so no need to worry about control lines for those cases
- I decided to implement SHL and SHR by bypassing the FA completely, using a 4:1 multiplexor on the output. This way, most of the control lines will be don't cares for these two instructions.
- Whenever Z_i is set to 1 or 0, C_{i+1} , Z_i , and C_0 are don't cares.

Control Line Definitions:

- s_0 controls X_i : $X_i = s_0 \text{ xor } A_i$ (conditionally invert A_i)
- s_1s_2 control Y_i : $Y_i = s_1's_2'Bi + s_1's_2Bi' + s_1s_2'(0) + s_1s_2(1)$ (4:1 mux on s_1,s_2). This simplifies to $s_1[s_2 \text{ xor } Bi] + s_1s_2$
- s_3s_4 control Z_i : $Z_i = s_3's_4'Ci + s_3's_4(0) + s_3s_4'(1) + s_3s_4(1)$ (4:1 mux on $C_i, 0, 1$). This simplifies to $s_3's_4'Ci + s_3$
- s_5s_6 control F_i : $F_i = 4:1$ mux on $S_i, Z_{i+1}, A_{i-1}, A_{i+1}$ selected by s_5s_6 .
- s_7 : Disables V and C in the case of logic operations: $V = s_7(C_8 \text{ xor } C_7)$, $C^* = s_7(C_8)$
- s_8 : Enables C in the case of SHL: $C = C^* + s_8A_7$
- s_9 : Determines value of C_0 , $C_0 = s_9$

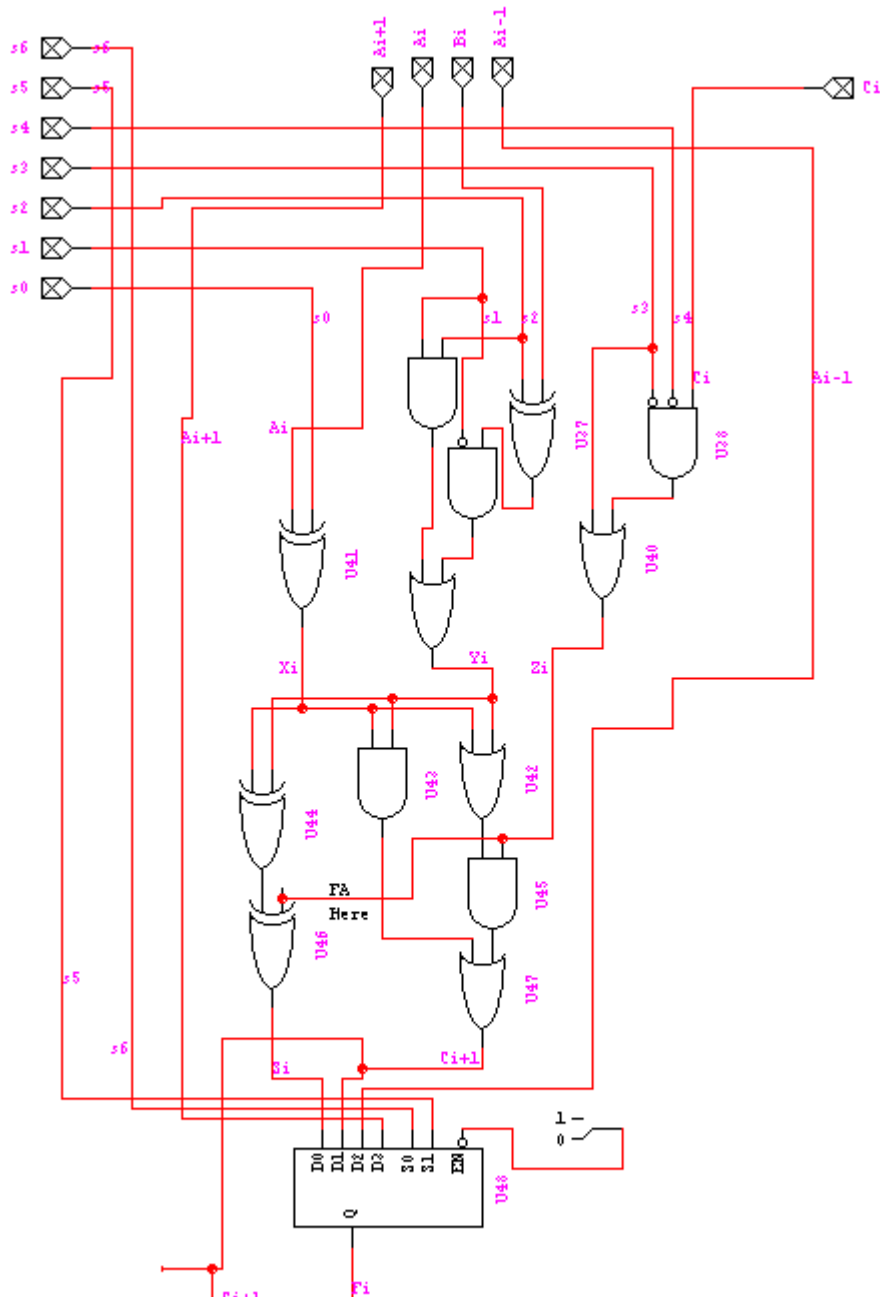Gate Level Implementation of an ALU BitSlice: Total Gates = 13 + (4:1mux) + Inverter-for-Bi = 18gates



 

Remainder of System:

Condition Codes

- V: 2 gates (C8xorC7)s7
- C: 3 gates (C8s7)+(A7s8)
- Z: 1 gate (8-input NOR)
- N: 0 gates (F7)

Control Logic: By inspecting the table above. The following control lines are asserted for the following instructions

- s0 = [NEG] + [NOT]
- s1 = [INC] + [DEC] + [PASS] + [NEG] + [NOT]
- s2 = [DEC] + [SUB] + [CMP] + [XNOR]
- s3 = [OR]
- s4 = [ARITHMETIC]'
- s5 = [SH(L/R)]
- s6 = [AND] + [OR] + [SHR]
- s7 = [ARITHMETIC]
- s8 = [SHL]
- s9 = ([ADD] + [DEC])'

Optimizing the Control Logic: Determine encoding by placing the the instructions in a K-MAP while trying to keep the groups together according to the above. For example, NEG and NOT are close together to make s0 simple, ADD and DEC are adjacent to make s9 simple, s1 and s2 are grouped as good as can be without violating the separation between logic and arithmetic functions, etc. This is probably not an optimal placement, but its not bad.

P3P2P1P0	00	01	11	10
00	OR	PASS	INC	x
01	AND	NOT	NEG	x
11	SHR	XNOR	DEC	ADD
10	SHL	XOR	CMP	SUB

Letting ARITHMETIC = P3, we organize the k-map so that all arithmetic functions are in the P3=1 region. According to the K-MAP we get the following logic functions. All but s1 and s2 can be implement with one gate or less.

- s0 = P2P1'P0
- s1 = P2P1' + P3P2P0

- $s_2 = P_2P_1P_0 + P_3P_2P_0'$
- $s_3 = P_2'P_1'P_0'$
- $s_4 = P_3'$
- $s_5 = P_3P_2P_1$
- $s_6 = P_3'P_2's_8'$
- $s_7 = P_3$
- $s_8 = P_3'P_2'P_1P_0'$
- $s_9 = (P_3P_1P_0)'$

$$\text{Decoder Gate Count} = 12 + (4 \text{ inversions}) = 16$$

$$\text{Total System} = (\text{BitSlice} * 8) + (\text{CC}) + (\text{Decoder}) + (2 \text{ control line inversions}) = 144 + 6 + 16 + 2 = 168 \text{ gates}$$

The critical delay is as follows:


- For bit 0, the critical path is from P3 to s2 to Yi to Ci+1: 11 gates
- For bits 1-6, the critical path is from Ci to Ci+1: 6 gates
- For bit 7, the critical path is from C7 to (C or F7): 6 gates

$$\text{The total delay} = 11 + (6 * 6) + 6 = 53 \text{ gate delays}$$

Here is the Verilog Model for the Controller:

```
module Decoder(P3, P2, P1, P0, s0, s1, s2, s3, s4, s5, s6, s7, s8, s9);
  input P3;
  input P2;
  input P1;
  input P0;
  output s0;
  output s1;
  output s2;
  output s3;
  output s4;
  output s5;
  output s6;
  output s7;
  output s8;
  output s9;
  assign s7 = P3;
  assign s8 = ~P3 & ~P2 & P1 & ~P0;
  assign s3 = ~P2 & ~P1 & ~P0;
  assign s9 = ~(P3 & P1 & P0);
  assign s4 = ~P3;
  assign s5 = ~P3 & ~P2 & P1;
  assign s6 = ~P3 & ~P2 & ~s8;
  assign s0 = P2 & ~P1 & P0;
  assign s1 = (P2 & ~P1) | (P3 & P2 & P0);
  assign s2 = (P2 & P1 & P0) | (P3 & P1 & ~P0);
endmodule
```

ALU Schematic

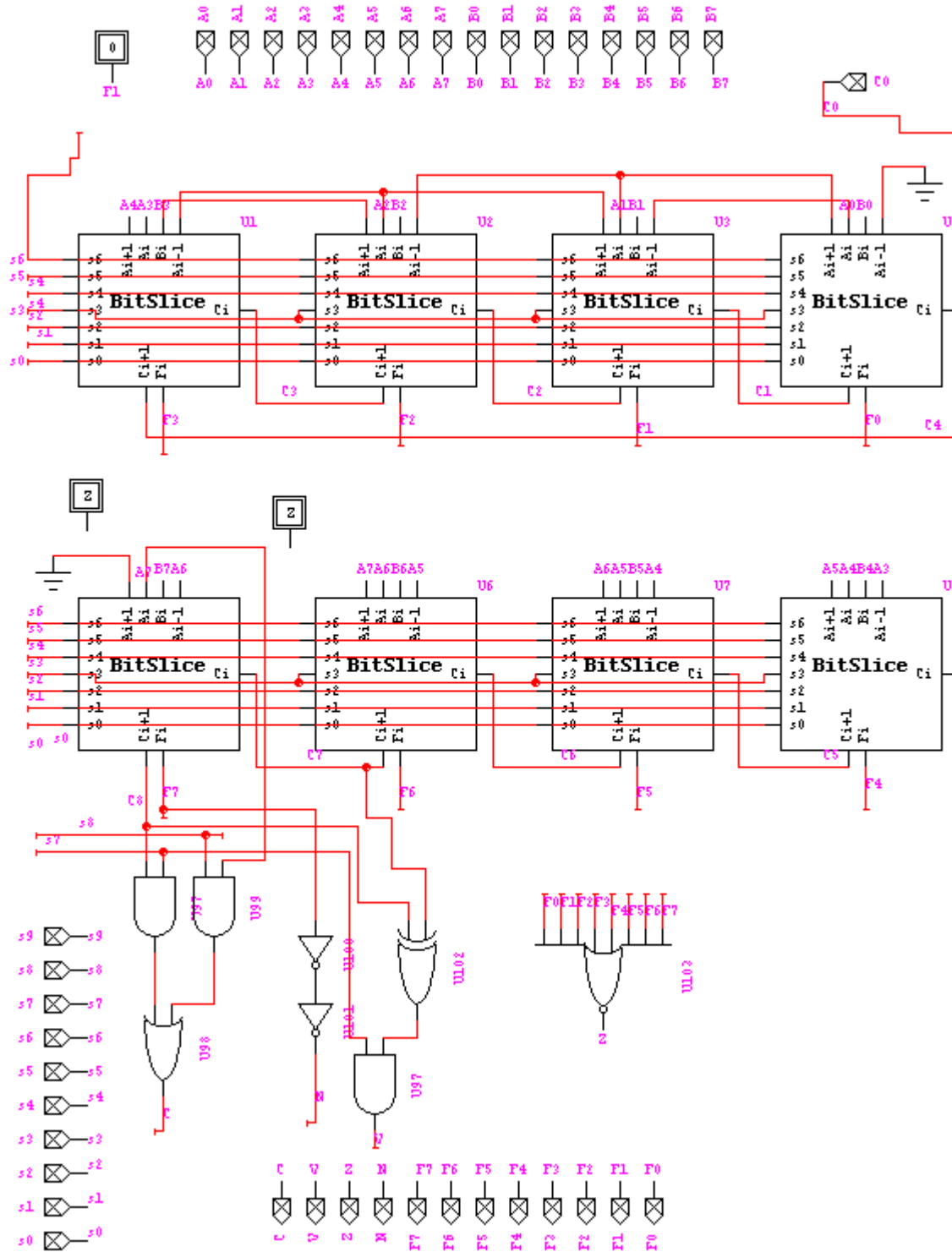

Test Vectors



Ready, Vectors Processed (17), NO ERRORS

	0	1	2	3	4	5	6	
0	\$TIME	\$I [P3..P0]	\$E Z	\$E V	\$E N	\$E C	\$E [F7..F0]	
1	\$D 50	0 "OR"	0	= 0	= 1	= 0	= F5	=
2	\$D 50	1 "AND"	0	= 0	= 0	= 0	= 05	=
3	\$D 50	2 "SHL"	0	= 0	= 0	= 1	= 4A	=
4	\$D 50	3 "SHR"	0	= 0	= 0	= 0	= 52	=
5	\$D 50	4 "PASS"	0	= 0	= 1	= 0	= A5	=
6	\$D 50	5 "NOT"	0	= 0	= 0	= 0	= 5A	=
7	\$D 50	6 "XOR"	0	= 0	= 1	= 0	= F0	=
8	\$D 50	7 "XNOR"	0	= 0	= 0	= 0	= 0F	=
9	\$D 50	A "SUB"	0	= 1	= 0	= 1	= 50	=
10	\$D 50	B "ADD"	0	= 0	= 1	= 0	= FA	=
11	\$D 50	C "INC"	0	= 0	= 1	= 0	= A6	=
12	\$D 50	D "NEG"	0	= 0	= 0	= 0	= 5B	=
13	\$D 50	E "CMP"	0	= 1	= 0	= 1	= 50	=
14	\$D 50	F "DEC"	0	= 0	= 1	= 1	= A4	=
15	\$STOP							
16	1451							

Top Level Schematic

