 


Arithmetic circuits

- ❑ Excellent examples of multi-level combinational logic design
- ❑ Time vs. space trade-offs
 - doing things fast may require more logic and thus more space
- ❑ Arithmetic and logic units
 - general-purpose building blocks
 - critical components of micro-processor
 - used within most computer instructions

Heart of a Computer



**ALU =
Arithmetic and
Logic Unit**


**ADD (A+B)
INC (A+1)
DEC (A+ -1)
SUB (A+ -B)
CMP (A+ -B)
COMP(0+ -A)
PASS (A + 0)**

**SHIFT
AND
OR
XOR**


Full adder implementations

- Standard approach
 - 6 gates
 - 2 XORs, 2 ANDs, 2 ORs
 
$$\text{Sum} = A \text{ xor } B \text{ xor } C$$




$$\text{Carry} = AB + \text{Cin}(A+B)$$

 

Adder/subtractor


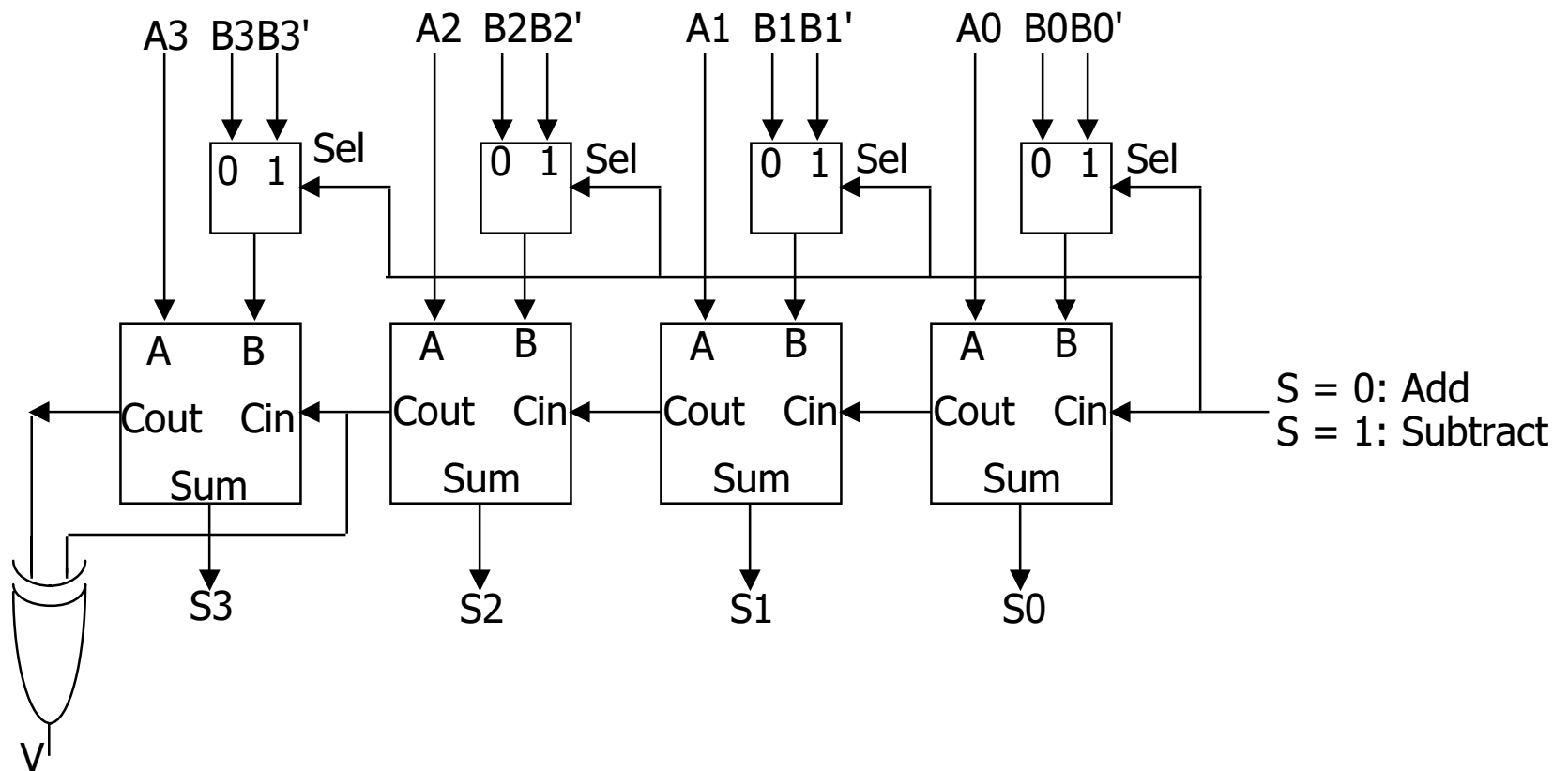
- Use an adder to do subtraction thanks to 2s complement representation
 - $A - B = A + (-B) = A + B' + 1$
 - Use function select (S) to choose add or subtract



Ripple-carry adders

❑ Critical delay

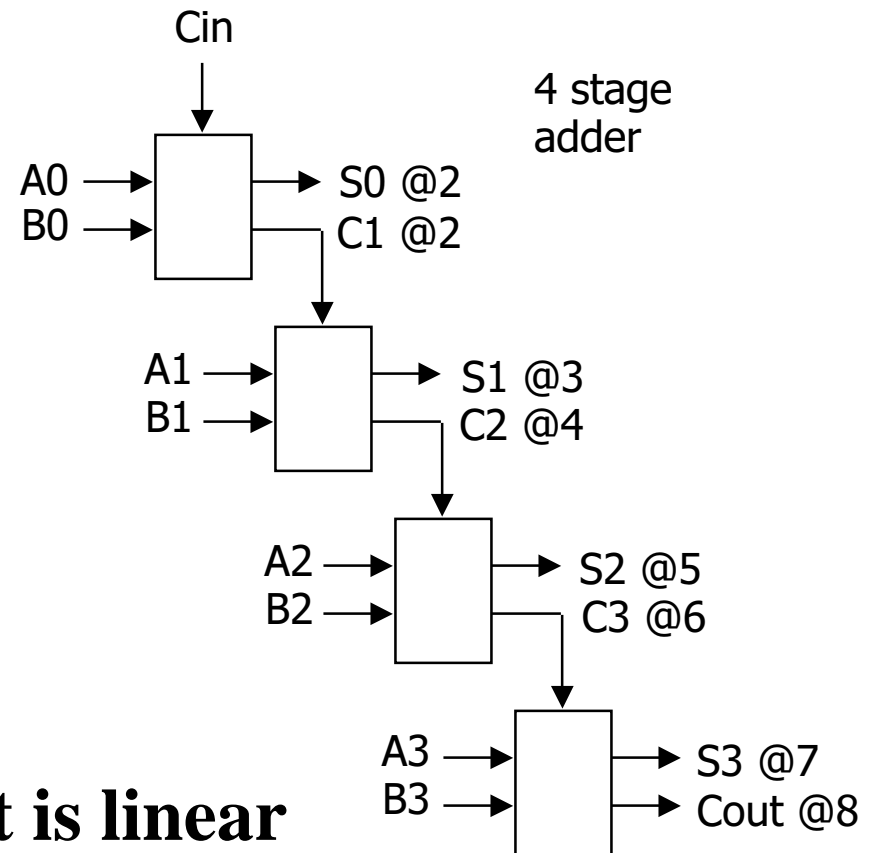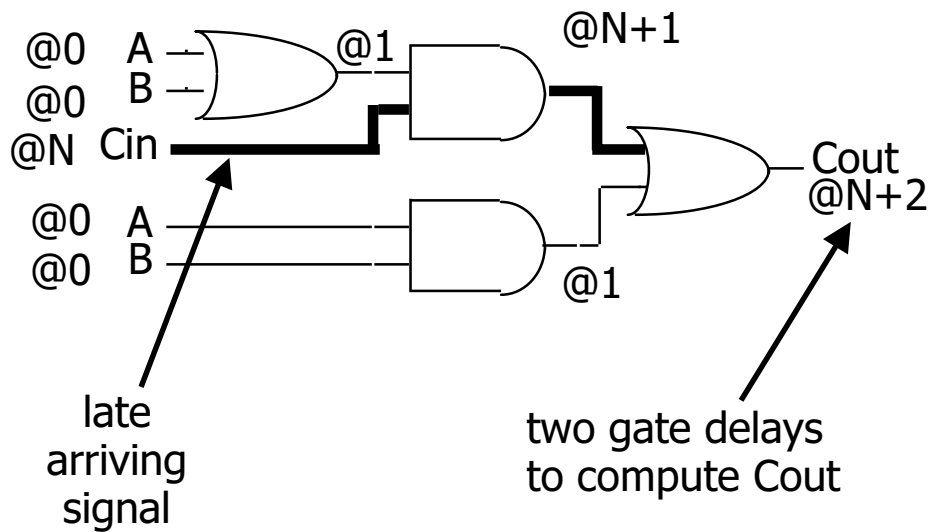
- the propagation of carry from low to high order stages



Delay is linear, Cost is linear


Ripple-carry adders (cont'd)

 - ❑ Critical delay
 - the propagation of carry from low to high order stages
 - 1111 + 0001 is the worst case addition
 - carry must propagate through all bits




Need a Fast Adder

Size is linear, speed is linear

 

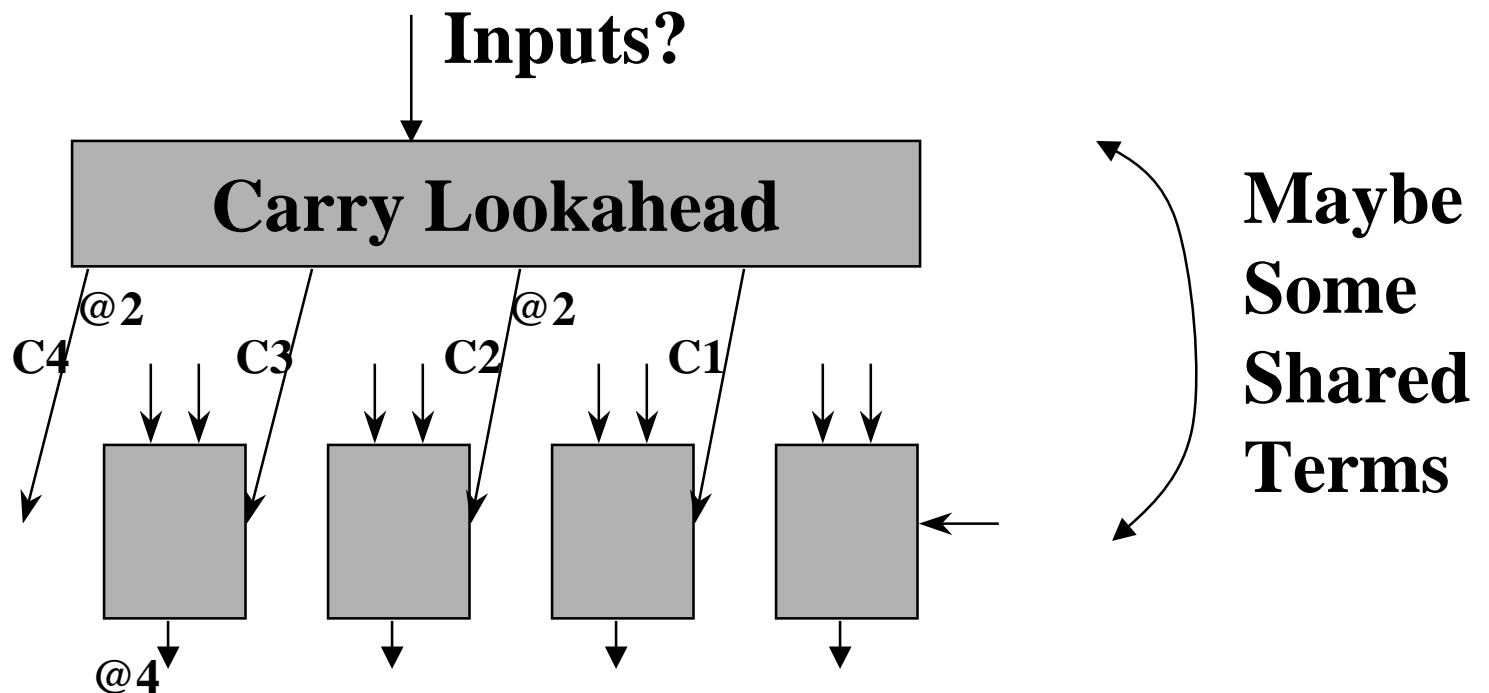Find a 2-level implementation for each carry



Carry-lookahead logic

- ❑ The key is the carry. Compute as much as possible about Carry out before you get the carry in.
- ❑ Intutively C_{i+1} is true if A_i and B_i generate and carry or if C_i is true and A_i and B_i propagate a carry
- ❑ Carry generate: $G_i = A_i B_i$
 - must generate carry when $A = B = 1$
- ❑ Carry propagate: $P_i = A_i \text{ xor } B_i$
 - carry-in will equal carry-out here
- ❑ Sum and Cout can be re-expressed in terms of generate/propagate:
 - $S_i = A_i \text{ xor } B_i \text{ xor } C_i$
 $= P_i \text{ xor } C_i$
 - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$
 $= A_i B_i + C_i (A_i + B_i)$
 $= A_i B_i + C_i (A_i \text{ xor } B_i)$
 $= G_i + C_i P_i$





Carry-lookahead logic (cont'd)

- Re-express the carry logic as follows:
 - $C_1 = G_0 + P_0 C_0$
 - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
 - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
 - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$


- Each of the carry equations can be implemented with two-level logic (in terms of P and G)
 - all inputs are now directly derived from data inputs and not from intermediate carries
 - this allows computation of all sum outputs to proceed in parallel

Carry-lookahead implementation

    - Adder with propagate and generate outputs




increasingly complex
logic for carries

 

Carry-lookahead implementation (cont'd)

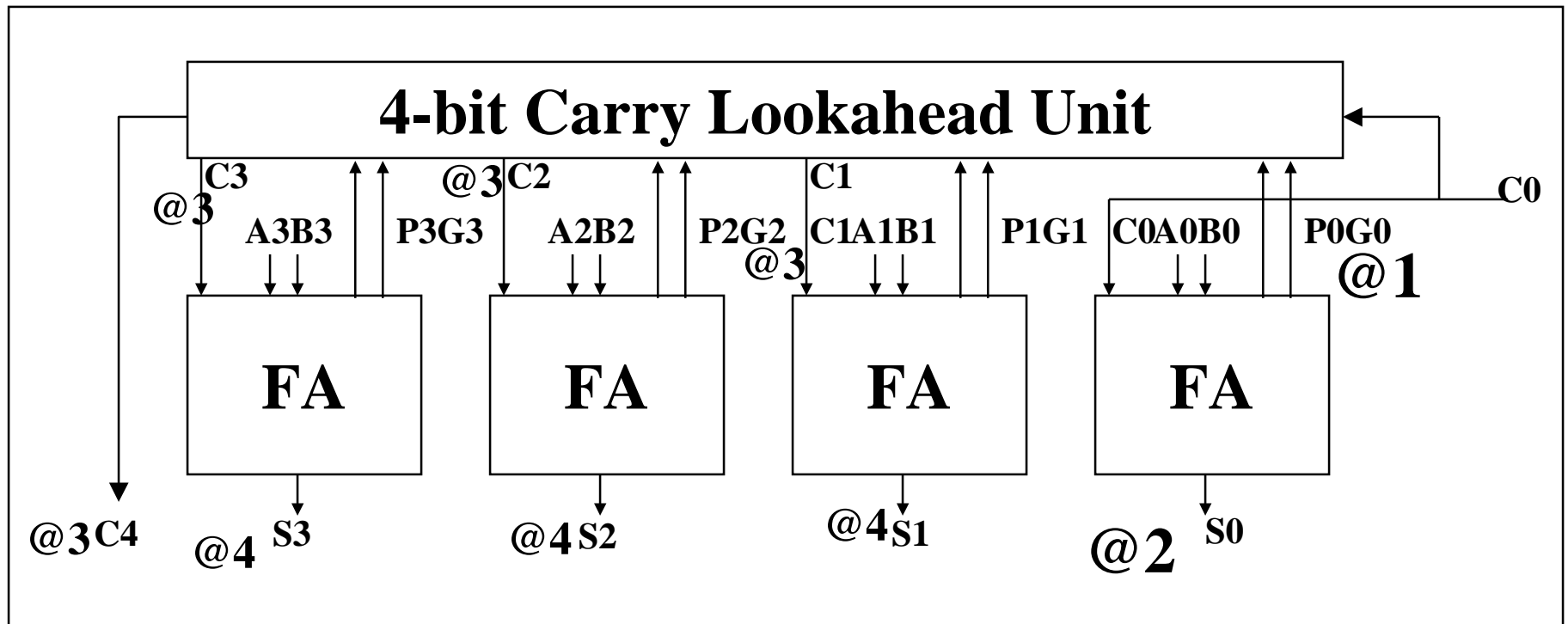- Carry-lookahead logic generates individual carries
 - sums computed much more quickly in parallel
 - however, cost of carry logic increases with more stages




$$G_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 \quad @3$$

$$P_4 = P_3P_2P_1P_0 \quad @2$$

PG


Carry-lookahead adder with cascaded carry-lookahead logic

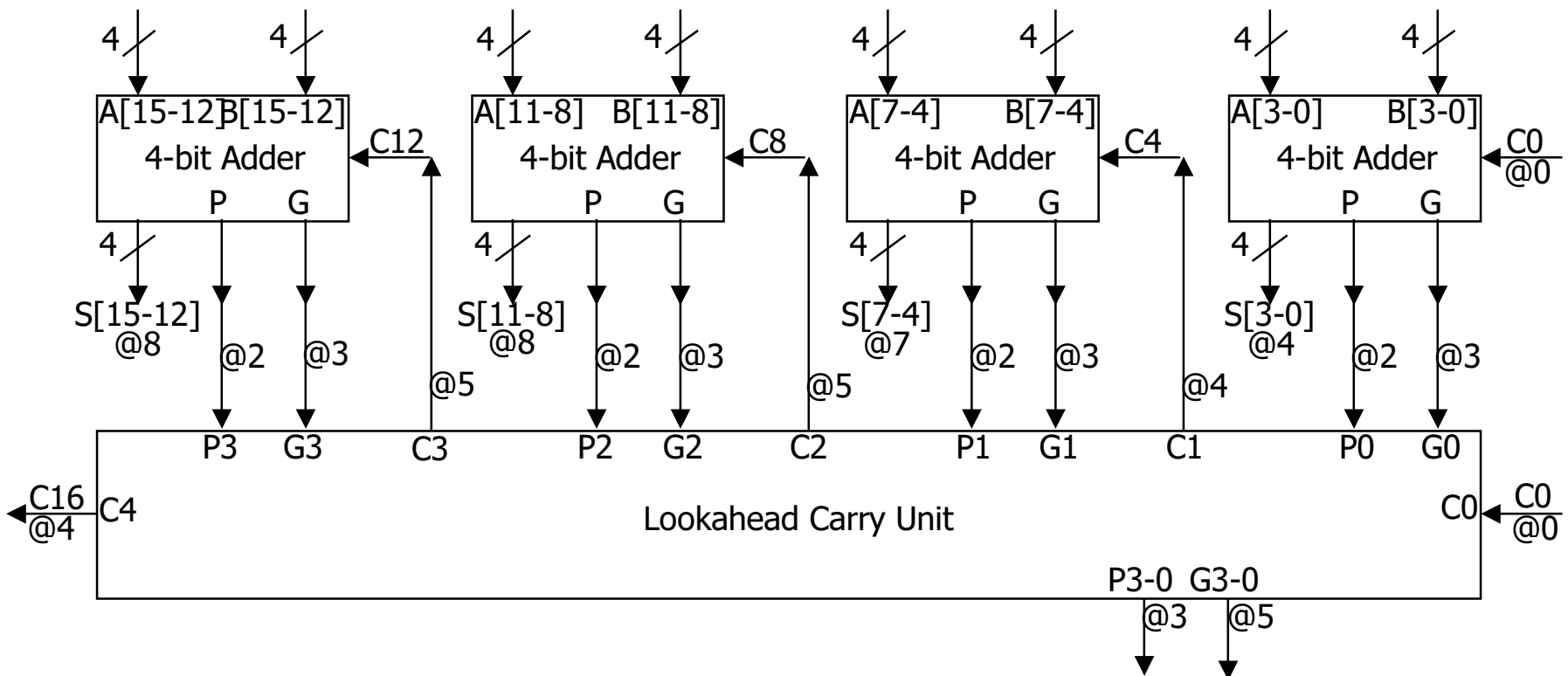- Carry-lookahead adder
 - 4 four-bit adders with internal carry lookahead
 - second level carry lookahead unit extends lookahead to 16 bits




Carry-select adder

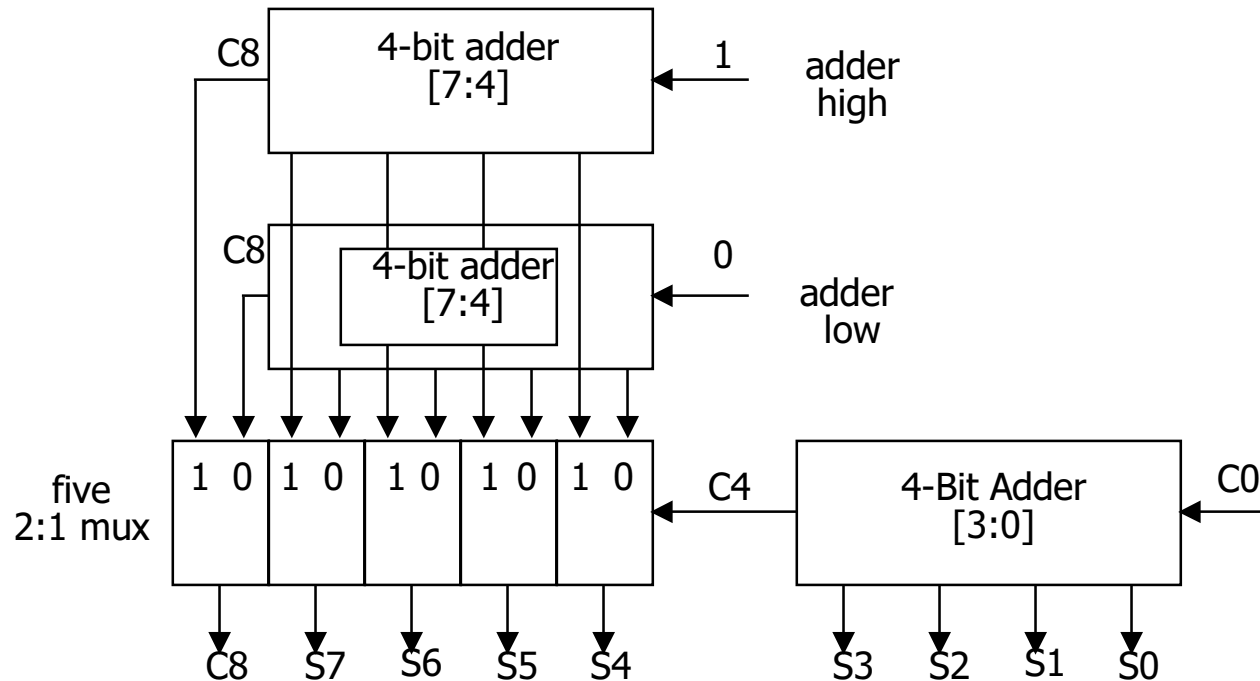- ❑ Redundant hardware to make carry calculation go faster
 - compute two high-order sums in parallel while waiting for carry-in
 - one assuming carry-in is 0 and another assuming carry-in is 1
 - select correct result once carry-in is finally computed



Heart of a Computer

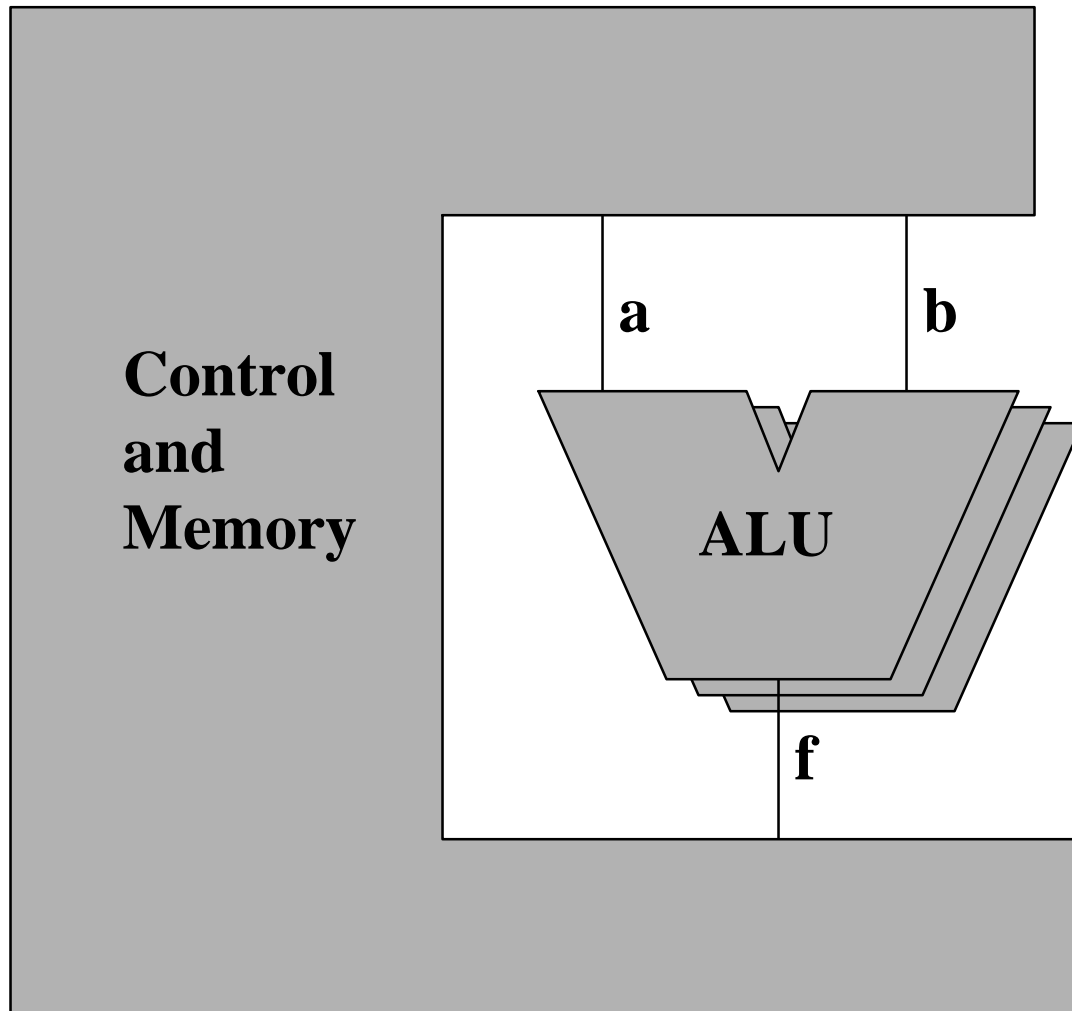

**ALU =
Arithmetic and
Logic Unit**

**ADD (A+B)
INC (A+1)
DEC (A+ -1)
SUB (A+ -B)
CMP (A+ -B)
COMP(0+ -A)
PASS (A + 0)**

**SHIFT
AND
OR
XOR**

Arithmetic logic unit design specification

M = 0, logical bitwise operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	input A_i transferred to output
0	1	$F_i = \text{not } A_i$	complement of A_i transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	compute XOR of A_i, B_i
1	1	$F_i = A_i \text{ xnor } B_i$	compute XNOR of A_i, B_i

M = 1, C0 = 0, arithmetic operations

0	0	$F = A$	input A passed to output
0	1	$F = \text{not } A$	complement of A passed to output
1	0	$F = A \text{ plus } B$	sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	sum of B and complement of A

M = 1, C0 = 1, arithmetic operations

0	0	$F = A \text{ plus } 1$	increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

logical and arithmetic operations
not all operations appear useful, but "fall out" of internal logic


Arithmetic logic unit design (cont'd)

□ Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1	
0	0	0	X	0	X	0	X	
			X	1	X	1	X	
			X	0	X	1	X	
	0	1	0	X	1	X	0	X
				X	0	X	1	X
				X	1	0	1	X
	1	0	0	X	0	0	0	X
				X	0	1	1	X
				X	1	0	1	X
	1	1	0	X	1	1	0	X
				X	0	0	1	X
				X	0	1	0	X
1	0	0	0	0	X	0	X	
			0	1	X	1	X	
			0	0	X	1	X	
	0	1	0	0	1	X	0	X
				0	0	X	1	X
				0	1	0	1	X
	1	0	0	0	0	0	0	0
				0	0	1	1	0
				0	1	0	1	0
	1	1	0	0	0	0	1	0
				0	0	1	0	1
				0	1	0	0	1
1	0	0	0	1	1	0	0	
			0	1	X	0	1	
			0	0	X	1	1	
	1	0	0	1	1	X	1	0
				1	0	X	1	0
				1	1	0	1	1
1	1	0	1	0	0	0	1	
			1	0	1	1	1	
			1	1	0	1	0	
1	0	1	1	0	1	1	1	
			1	1	0	1	1	
			1	0	1	1	0	
	1	1	1	1	0	1	1	1
				1	1	0	1	1
				1	1	1	0	1

Arithmetic logic unit design (cont'd)

 
- Sample ALU – multi-level discrete gate logic implementation



12 gates

Arithmetic logic unit design (cont'd)

 □ Sample ALU – clever multi-level implementation



first-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

other gates

for M=0 (logical operations, Ci is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1 S_0' (A_i) + S_1 S_0 (A_i') +$$

$$S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$


for M=1 (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci

8-Bit Bit-Sliced ALU

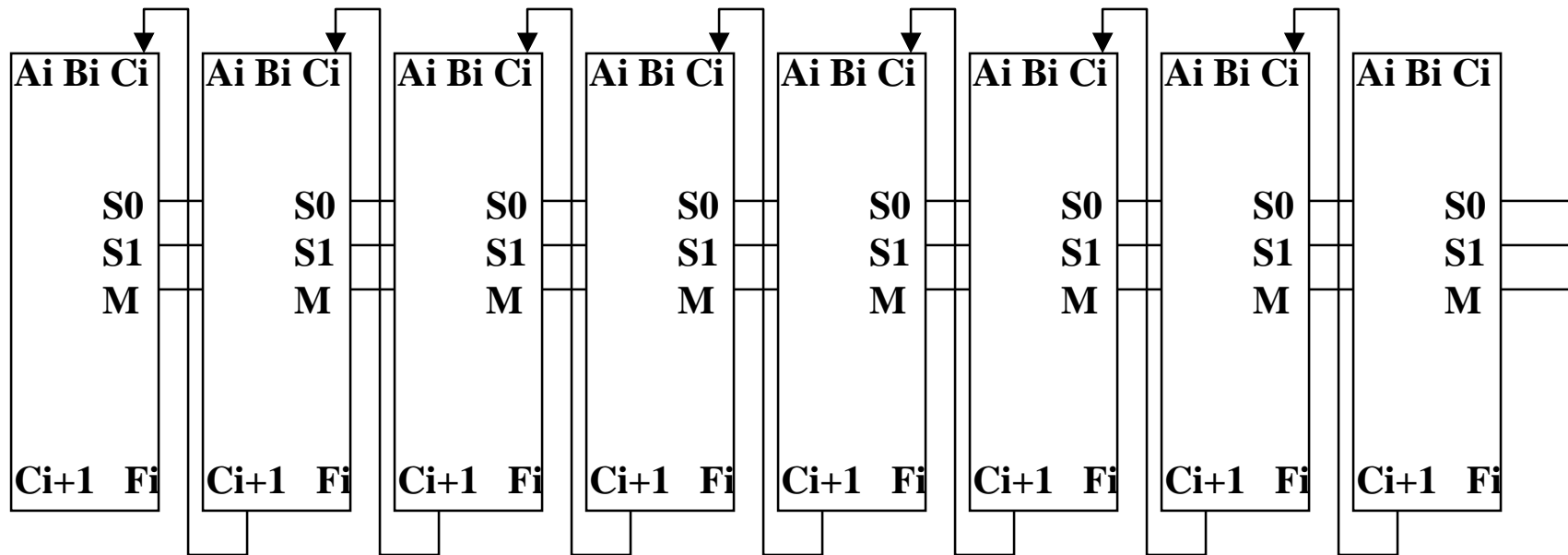

Carry lookahead techniques can be applied to this too

Summary for examples of Math Hardware

- ❑ Binary number representation
 - positive numbers the same
 - difference is in how negative numbers are represented
 - 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- ❑ Circuits for binary addition
 - basic half-adder and full-adder
 - carry lookahead logic
 - carry-select
- ❑ ALU Design
 - specification, implementation