

# Hardware description languages

---

- ❑ Describe hardware at varying levels of abstraction
- ❑ Structural description
  - textual replacement for schematic
  - hierarchical composition of modules from primitives
- ❑ Behavioral/functional description
  - describe what module does, not how
  - synthesis generates circuit for module
- ❑ Simulation semantics

# HDLs

---

- ❑ Abel (circa 1983) - developed by Data-I/O
  - targeted to programmable logic devices
  - not good for much more than state machines
- ❑ ISP (circa 1977) - research project at CMU
  - simulation, but no synthesis
- ❑ Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
  - similar to Pascal and C
  - delays is only interaction with simulator
  - fairly efficient and easy to write
  - IEEE standard
- ❑ VHDL (circa 1987) - DoD sponsored standard
  - similar to Ada (emphasis on re-use and maintainability)
  - simulation semantics visible
  - very general but verbose
  - IEEE standard

# Verilog

---

- ❑ Supports structural and behavioral descriptions
- ❑ Structural
  - explicit structure of the circuit
  - e.g., each logic gate instantiated and connected to others
- ❑ Behavioral
  - program describes input/output behavior of circuit
  - many structural implementations could have same behavior
  - e.g., different implementation of one Boolean function
- ❑ We'll only be using behavioral Verilog in DesignWorks
  - rely on schematic when we want structural descriptions

# Structural model

---

```
module xor_gate (out, a, b);
  input      a, b;
  output     out;
  wire      abar, bbar, t1, t2;

  inverter  invA (abar, a);
  inverter  invB (bbar, b);
  and_gate  and1 (t1, a, bbar);
  and_gate  and2 (t2, b, abar);
  or_gate   or1 (out, t1, t2);

endmodule
```

# Simple behavioral model

- Continuous assignment

```
module xor_gate (out, a, b);  
  input          a, b;  
  output         out;  
  reg            out;  
  
  assign #6 out = a ^ b;  
  
endmodule
```

simulation register -  
keeps track of  
value of signal

**delay from input change  
to output change**

# Simple behavioral model

- always block

```
module xor_gate (out, a, b);  
    input        a, b;  
    output       out;  
    reg          out;  
  
    always @(a or b) begin  
        #6 out = a ^ b;  
    end  
  
endmodule
```


specifies when block is executed  
ie. triggered by which signals

# Event Queue in Verilog


```
module xor_gate (w,x,y,z);  
  input  [7:0]  x, w;  
  output [7:0]  y, z;  
  reg    [7:0]  y, z;  
  
  always @(x) 1  
    y = x + 1;  
  always @(y or w) 2  
    z = y + w;  
endmodule
```

Initially  $y = 0$

Case 1: at time zero:  $w=1, x = 0$

 

Case 2: at time zero:  $x=0, w=1$

 

Good simulators will not execute this event

**Point: Simulation semantics are simulator/order independent**