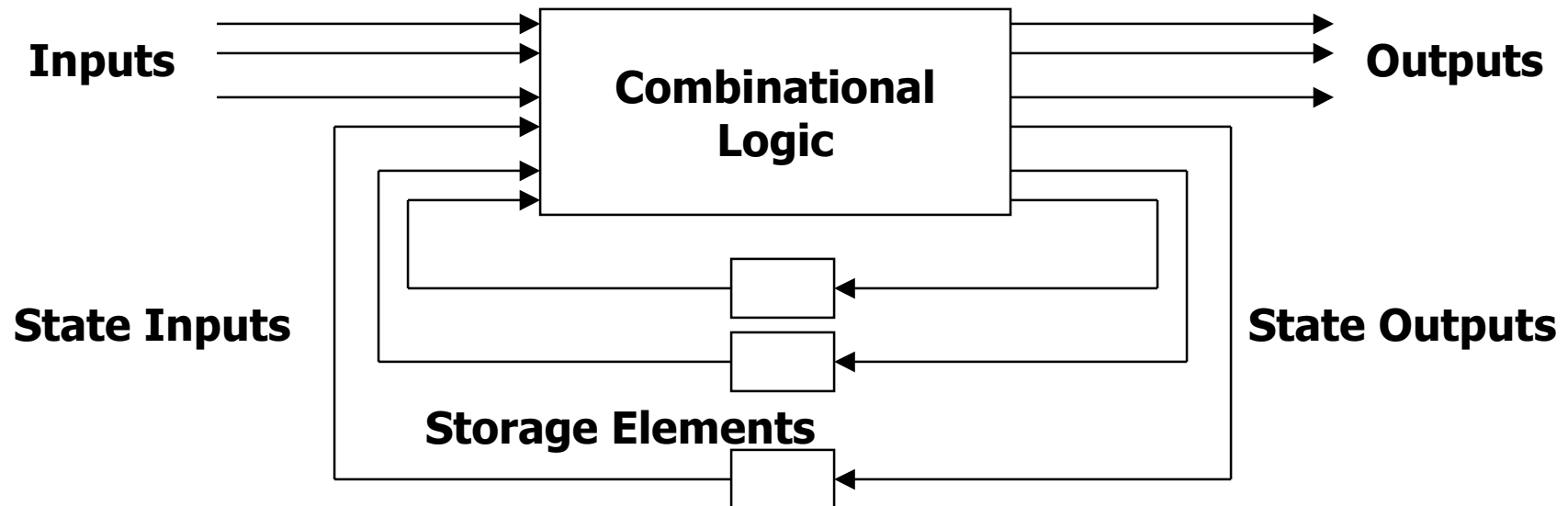


Sequential logic implementation

- ❑ Sequential systems
 - primitive sequential elements
 - combinational logic
- ❑ Models for representing sequential circuits
 - finite-state machines (Moore and Mealy)
 - representation of memory (states)
 - changes in state (transitions)
- ❑ Basic sequential circuits
 - shift registers
 - counters
- ❑ Design procedure
 - state diagrams
 - state transition table
 - next state functions


Abstraction of state elements

- ❑ Divide circuit into combinational logic and state
- ❑ Localize the feedback loops and make it easy to break cycles
- ❑ Implementation of storage elements leads to various forms of sequential logic



Forms of sequential logic

 
- ❑ Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- ❑ Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)



Finite state machine representations

- ❑ States: determined by possible values in sequential storage elements
- ❑ Transitions: change of state
- ❑ Clock: controls when state can change by controlling storage elements

 
- ❑ Sequential logic
 - sequences through a series of states
 - based on sequence of values on input signals
 - clock defines time divisions between states and input values



 Example finite state machine diagram



□ Mutex from Introduction

- Two inputs
- Three states, one for each possible output configuration
- Outputs a function of state only (Moore machine)




Shift Register Example

  - ❑ Complex State Diagram, Simple Logic
 - input value shown on transition arcs
 - State encoding = output encoding



Counters Example


 
- ❑ Counters
 - proceed through well-defined sequence of states in response to enable
- ❑ Many types of counters: binary, BCD, Gray-code
 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
 - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...



How do we turn a state diagram into logic?

❑ Counter

  - 3 flip-flops to hold state
- logic to compute next state
- clock signal controls when flip-flop memory can change
 - wait long enough for combinational logic to compute new value
 - don't wait too long as that is low performance





FSM design procedure

- ❑ Start with counters
 - simple because output is just state
 - simple because no choice of next state based on input
- ❑ State diagram to state transition table
 - tabular form of state diagram
 - like a truth-table
- ❑ State encoding
 - decide on representation of states
 - for counters it is simple: just its value
- ❑ Implementation
 - flip-flop for each state bit
 - combinational logic based on encoding

FSM design procedure: state diagram to encoded state transition table

 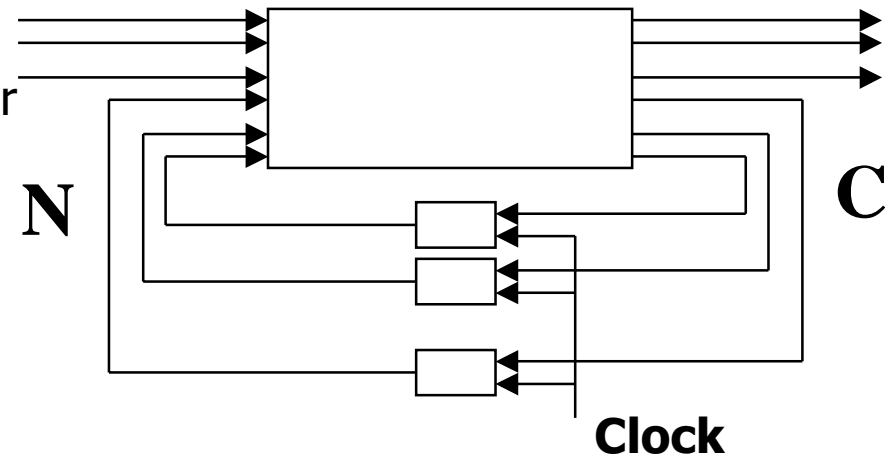- ❑ Tabular form of state diagram
- ❑ Like a truth-table (specify output for all input combinations)
- ❑ Encoding of states: easy for counters – just use value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0




Implementation

- ❑ D flip-flop for each state bit
- ❑ Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

notation to show function represent input to D-FF

   
$$\begin{aligned}
 N1 &:= C1' \\
 N2 &:= C1C2' + C1'C2 \\
 &:= C1 \text{ xor } C2 \\
 N3 &:= C1C2C3' + C1'C3 + C2'C3 \\
 &:= C1C2C3' + (C1' + C2')C3 \\
 &:= (C1C2) \text{ xor } C3
 \end{aligned}$$




Another example

- Shift register
 - input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


$N1 := In$
 $N2 := C1$
 $N3 := C2$

 

More complex counter example

 - ❑ Complex counter
 - repeats 5 states in sequence
 - not a binary number representation
- ❑ Step 1: derive the state transition diagram
 - count sequence: 000, 010, 011, 101, 110
- ❑ Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	x	x	x
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	x	x	x
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	x	x	x

note the don't care conditions that arise from the unused state codes

More complex counter example (cont'd)

- Step 3: K-maps for next state functions

C+	C			
	0	0	0	X
A	X	1	X	1
	B			


B+	C			
	1	1	0	X
A	X	0	X	1
	B			

A+	C			
	0	1	0	X
A	X	1	X	0
	B			

$$C+ := A$$

$$B+ := B' + A'C'$$

$$A+ := BC'$$

 

Self-starting counters (cont'd)


- Re-deriving state transition table from don't care assignment

C+	C		
	0	0	0
A	1	1	1
	B		

B+	C		
	1	1	0
A	1	0	0
	B		



A+	C		
	0	1	0
A	0	1	0
	B		

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 


Self-starting counters

  - ❑ Start-up states
 - at power-up, counter may be in an unused or invalid state
 - designer must guarantee that it (eventually) enters a valid state
- ❑ Self-starting solution
 - design counter so that invalid states eventually transition to a valid state
 - may limit exploitation of don't cares





State machine model

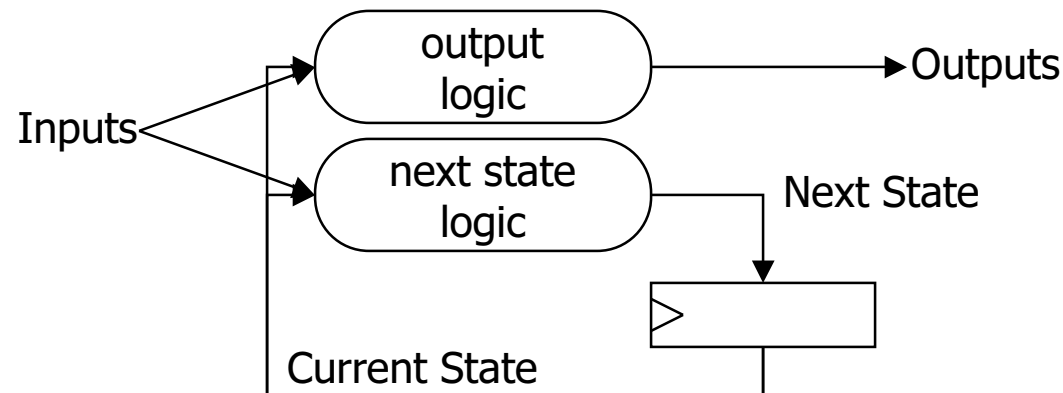- ❑ Values stored in registers represent the state of the circuit
- ❑ Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - function of current state and inputs (Mealy machine)
 - function of current state only (Moore machine)





State machine model (cont'd)

 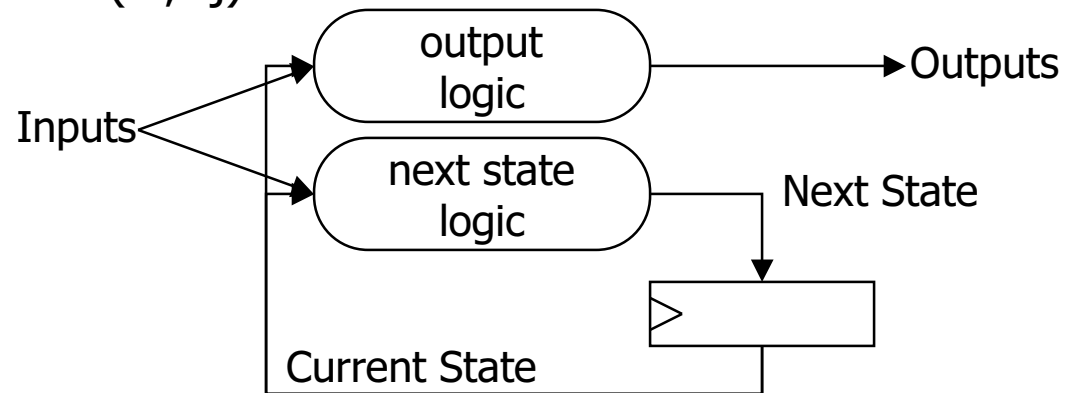- ❑ States: S_1, S_2, \dots, S_k
- ❑ Inputs: I_1, I_2, \dots, I_m
- ❑ Outputs: O_1, O_2, \dots, O_n
- ❑ Transition function: $F_s(S_i, I_j)$
- ❑ Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




  Example: ant brain (Ward, MIT)

- ❑ Sensors: L and R antennae, 1 if in touching wall
- ❑ Actuators: F - forward step, TL/TR - turn left/right slightly
- ❑ Goal: find way out of maze
- ❑ Strategy: keep the wall on the right




Ant behavior: And States of Mind

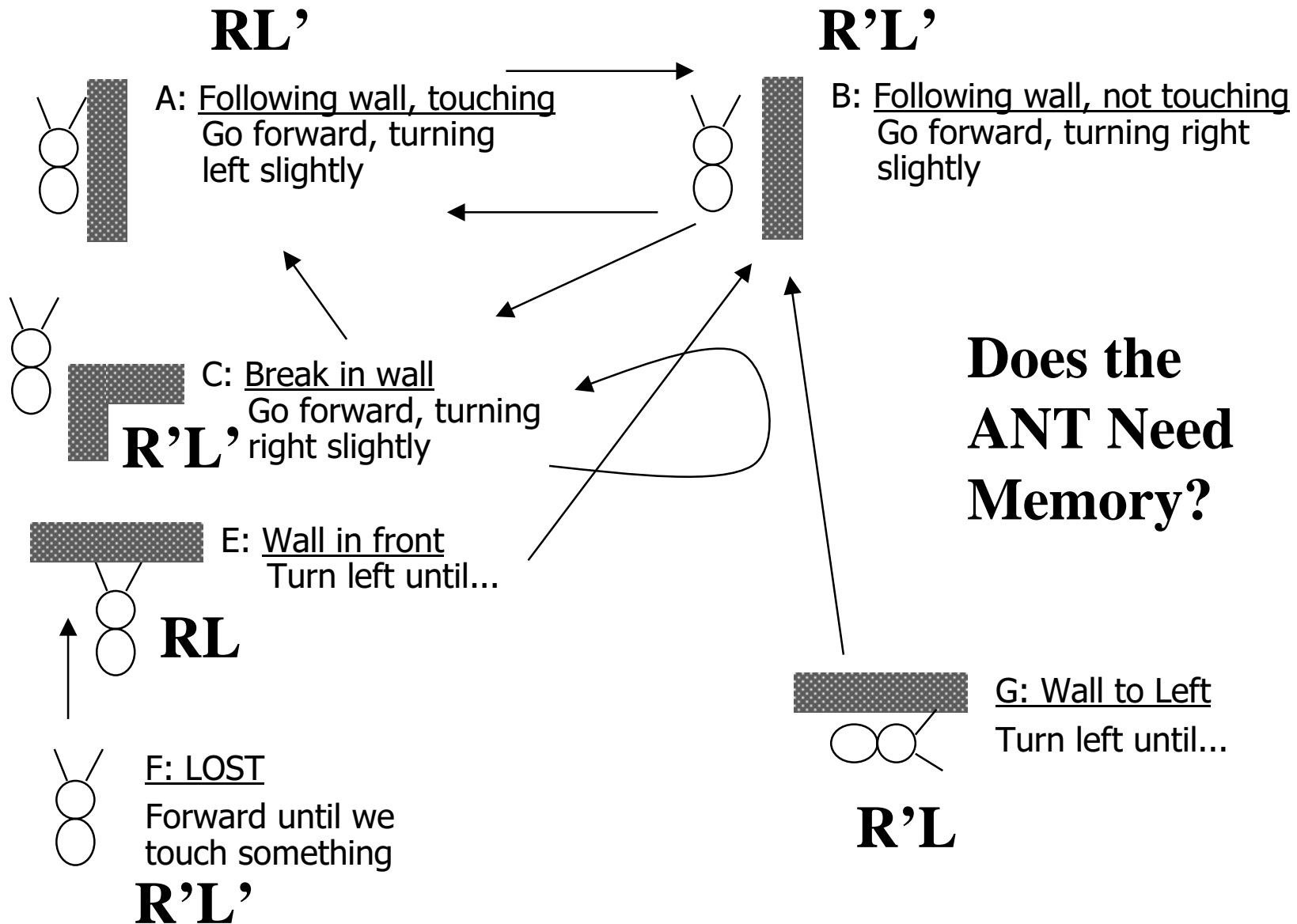

Designing an ant brain

□ State diagram

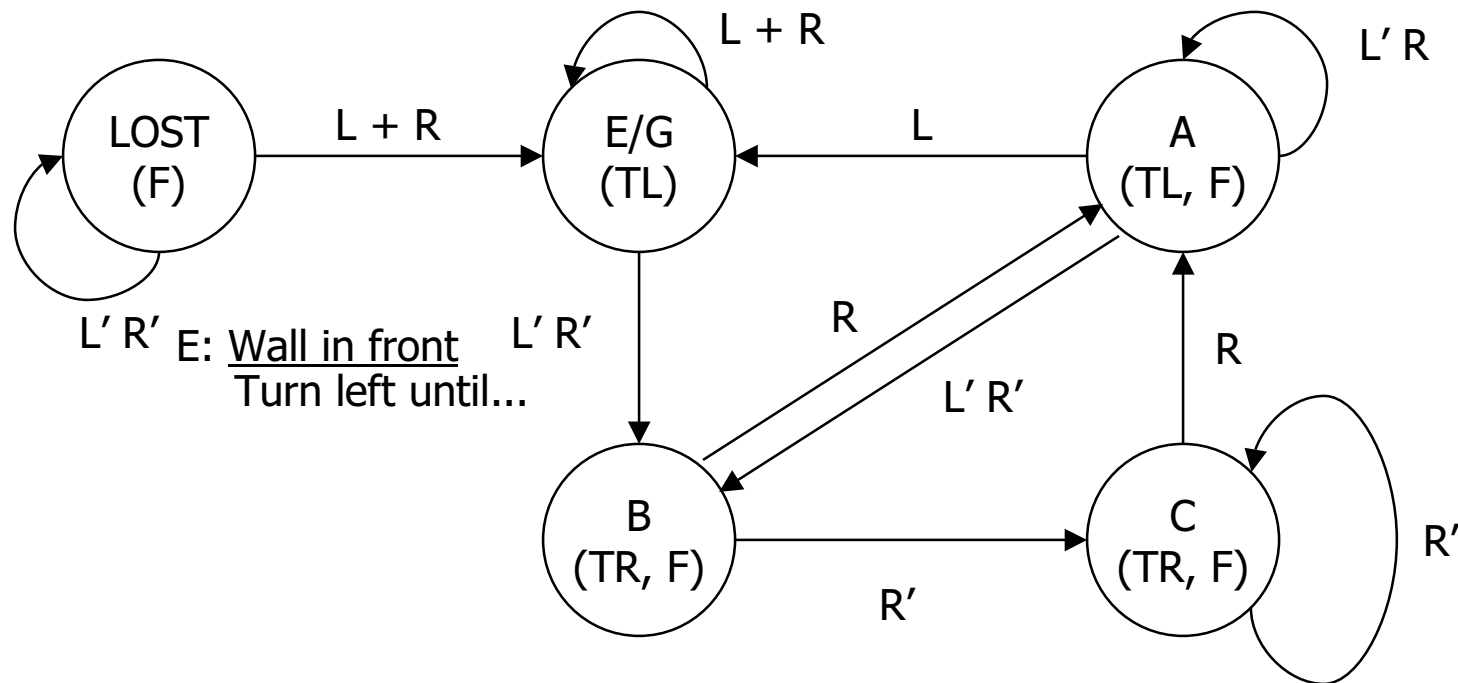A: Following wall, touching
B: Following wall, not touching
C: Break in wall, not touching
E: Wall in Front
G: Wall to Left
F: Lost




Synthesizing the ant brain circuit

- ❑ Encode states using a set of state variables
 - arbitrary choice - may affect cost, speed
- ❑ Use transition truth table
 - define next state function for each state variable
 - define output function for each output
- ❑ Implement next state and output functions using combinational logic
 - 2-level logic (ROM/PLA/PAL)
 - multi-level logic
 - next state and output functions can be optimized together

Transition truth table

- Using symbolic states and outputs

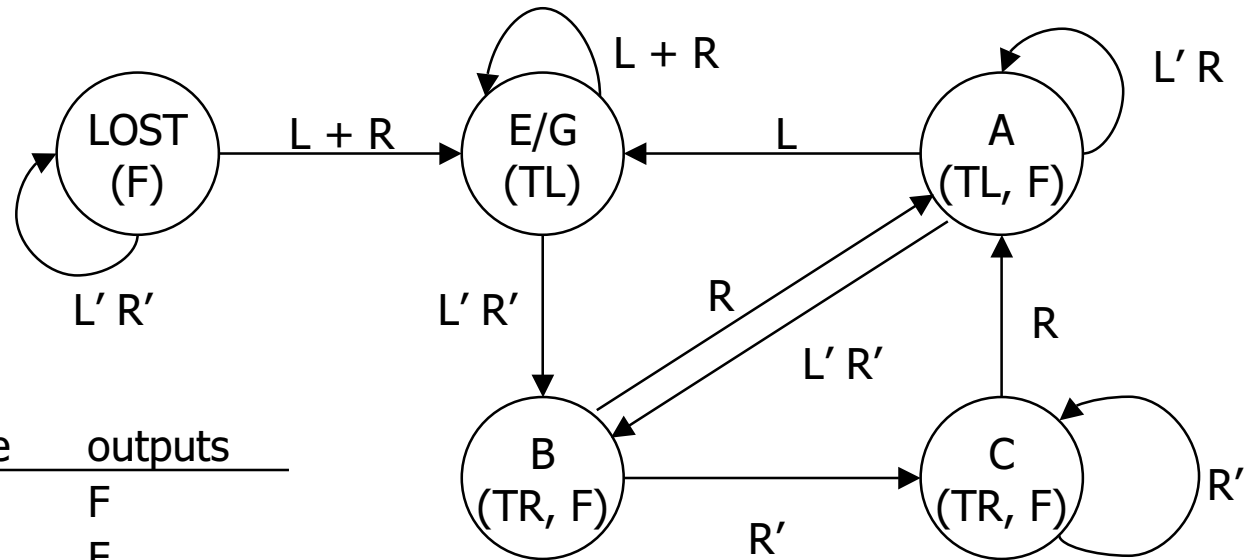

state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	-	1	E/G	F
LOST	1	-	E/G	F
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	-	E/G	TL, F
B	-	0	C	TR, F
B	-	1	A	TR, F
...

Synthesis

- 5 states : at least 3 state variables required (X, Y, Z)
 - state assignment (in this case, arbitrarily chosen)

LOST - 000
 E/G - 001
 A - 010
 B - 011
 C - 100

state X,Y,Z	L	R	next state X', Y', Z'	outputs F TR TL		
0 0 0	0	0	0 0 0	1	0	0
0 0 0	0	1	0 0 1	1	0	0
...
0 1 0	0	0	0 1 1	1	0	1
0 1 0	0	1	0 1 0	1	0	1
0 1 0	1	0	0 0 1	1	0	1
0 1 0	1	1	0 0 1	1	0	1
0 1 1	0	0	1 0 0	1	1	0
0 1 1	0	1	0 1 0	1	1	0
...

it now remains to synthesize these 6 functions


e.g.

$$TR = X + Y Z$$

$$X^+ = X R' + Y Z R' = R' TR$$


Circuit implementation

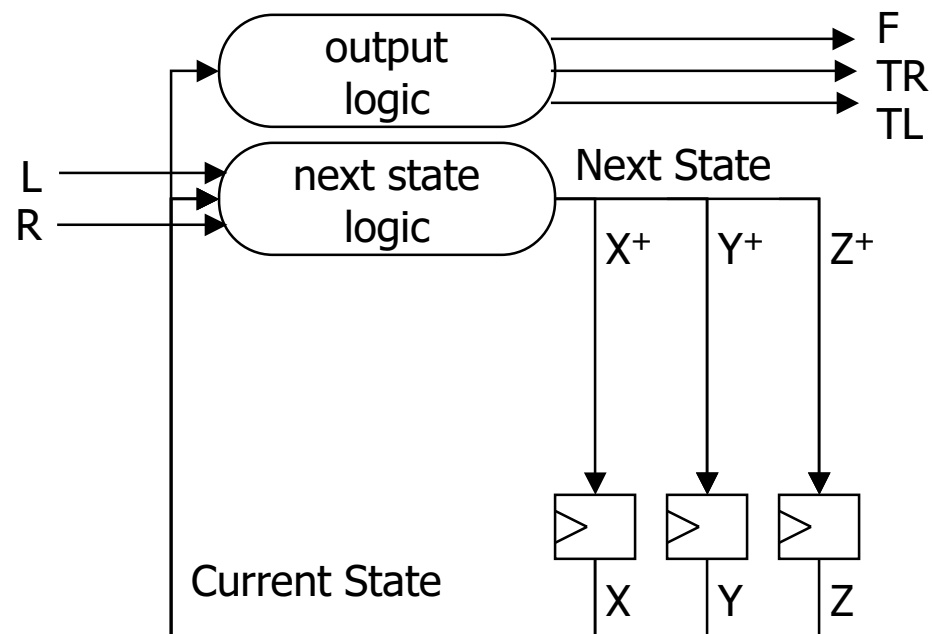- Outputs are a function of the current state only - Moore machine



Don't cares in FSM synthesis

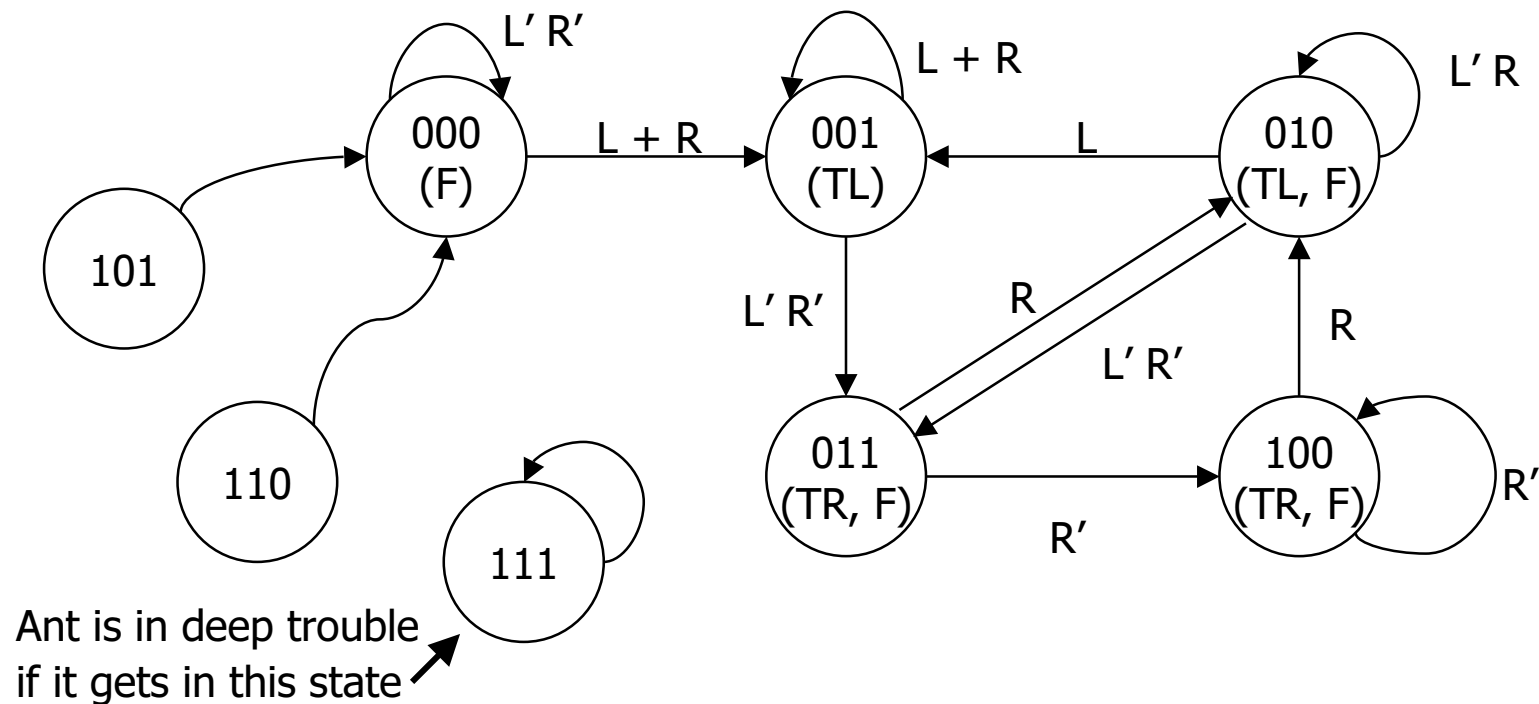- ❑ What happens to the "unused" states (101, 110, 111)?
- ❑ They were exploited as don't cares to minimize the logic
 - if the states can't happen, then we don't care what the functions do
 - if states do happen, we may be in trouble



State minimization


- ❑ Fewer states may mean fewer state variables
- ❑ High-level synthesis may generate many redundant states
- ❑ Two states are equivalent if they are impossible to distinguish from the outputs of the FSM, i. e., for any input sequence the outputs are the same
- ❑ Two conditions for two states to be equivalent:
 - 1) output must be the same in both states
 - 2) must transition to equivalent states for all input combinations

Ant brain revisited

□ Any equivalent states?


A: Following wall, touching
 B: Following wall, not touching
 C: Break in wall, not touching
 E: Wall in Front
 G: Wall to Left
 F: Lost

On track
Oriented
Getting Oriented
Lost

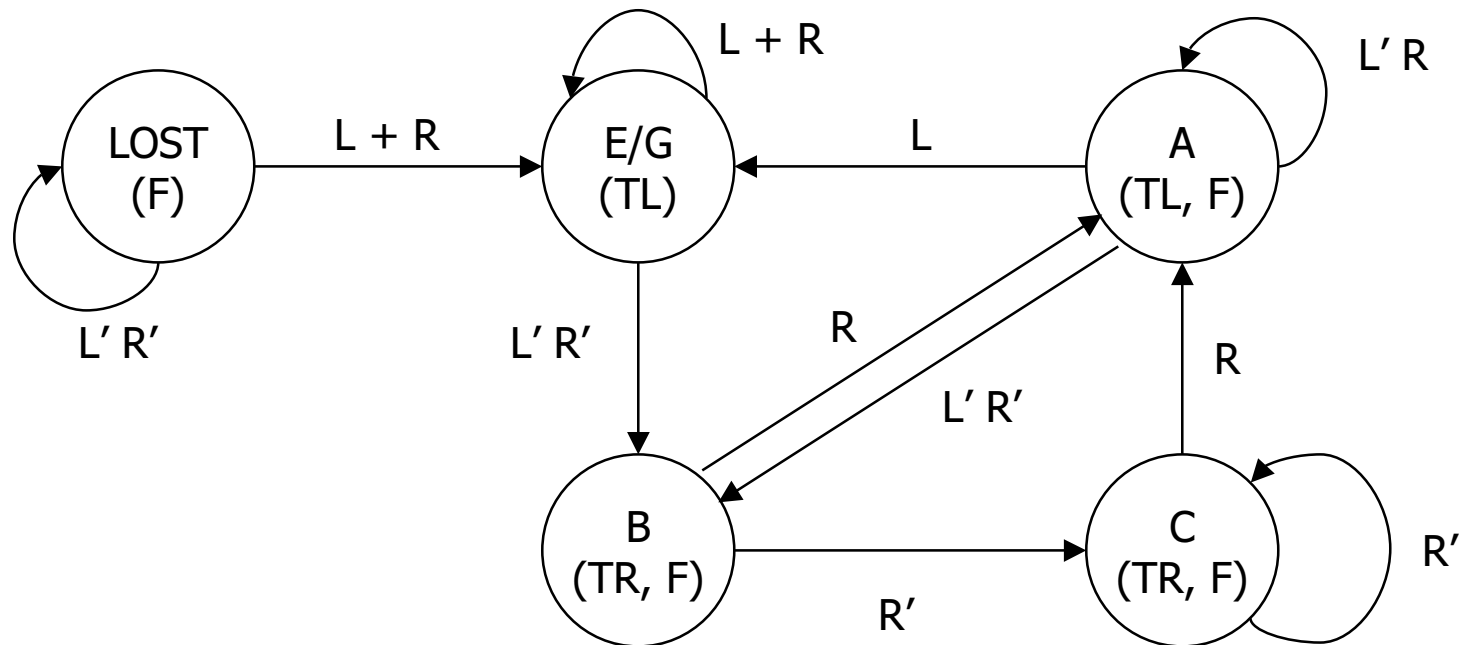

New improved brain

 - ❑ Merge equivalent B and C states
- ❑ Behavior is exactly the same as the 5-state brain
- ❑ We now need only 2 state variables rather than 3



New brain implementation

state X,Y	inputs L R	next state X',Y'	outputs F TR TL
00	0 0	00	1 0 0
00	- 1	01	1 0 0
00	1 -	01	1 0 0
01	0 0	11	0 0 1
01	- 1	10	0 0 1
01	1 -	10	0 0 1
10	0 0	11	1 0 1
10	0 1	10	1 0 1
10	1 -	01	1 0 1
11	- 0	00	1 1 0
11	- 1	10	1 1 0

$X+$

X			
0	1	0	1
0	1	1	1
0	1	1	0
0	1	0	0

L | R

Y

$Y+$

X			
0	1	0	1
1	0	0	0
1	0	0	1
1	0	0	1

L | R

Y

F

X			
1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1

L | R

Y

TR

X			
0	0	1	0
0	0	1	0
0	0	1	0
0	0	1	0

L | R

Y

TL

X			
0	1	0	1
0	1	0	1
0	1	0	1
0	1	0	1

L | R

Y

Do we really need 4 states?