


# Remaining Topics

---



- ❑ Basic State Machine Design Study Problems
  - Study Problems: 8.3, 8.5, 8.6, 8.7, 8.14, 9.2, 9.5,
- ❑ Moore v. Mealy and Timing Issues
- ❑ Communicating State Machines
- ❑ State Minimization
- ❑ State Assignment
- ❑ State Machines in Verilog
- ❑ Datapath and Control Architecture
- ❑ Counter Based Design
- ❑ Computer Organization
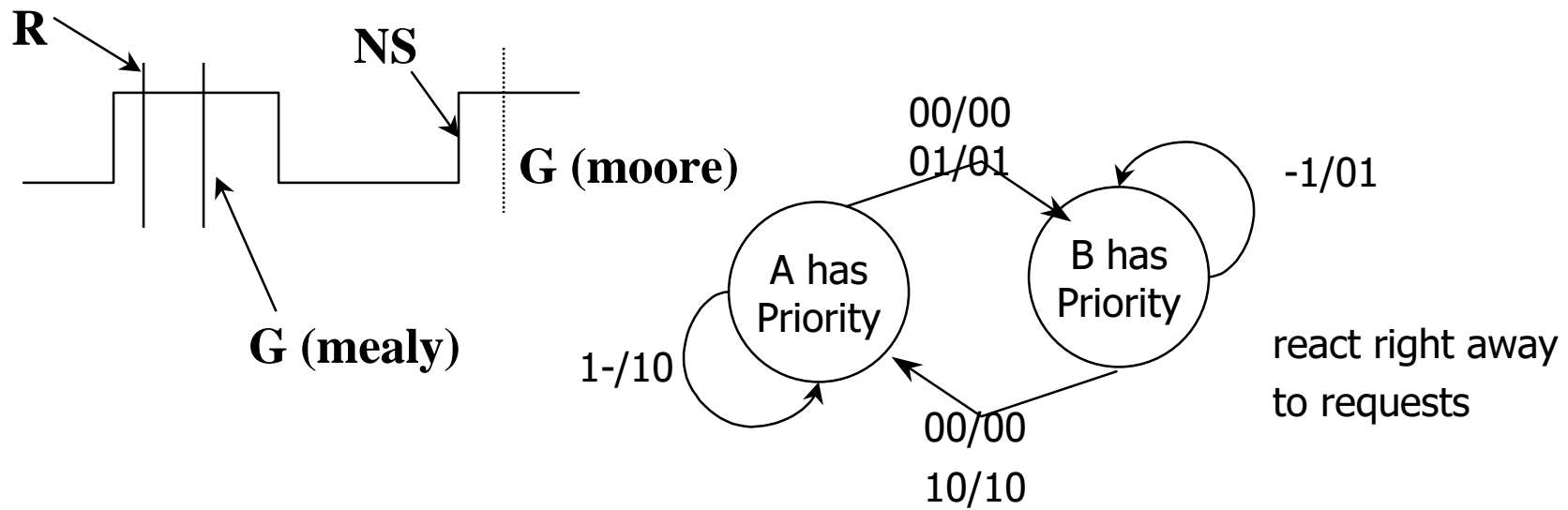
# Mealy vs. Moore machines


- ❑ Moore: outputs depend on current state only
- ❑ Mealy: outputs may depend on current state and current inputs
- ❑ Our ant brain is a Moore machine
  - output does not react immediately to input change
- ❑ We could have specified a Mealy FSM
  - outputs have immediate reaction to inputs
  - as inputs change, so does next state, doesn't commit until clocking event




# Timing Issues

 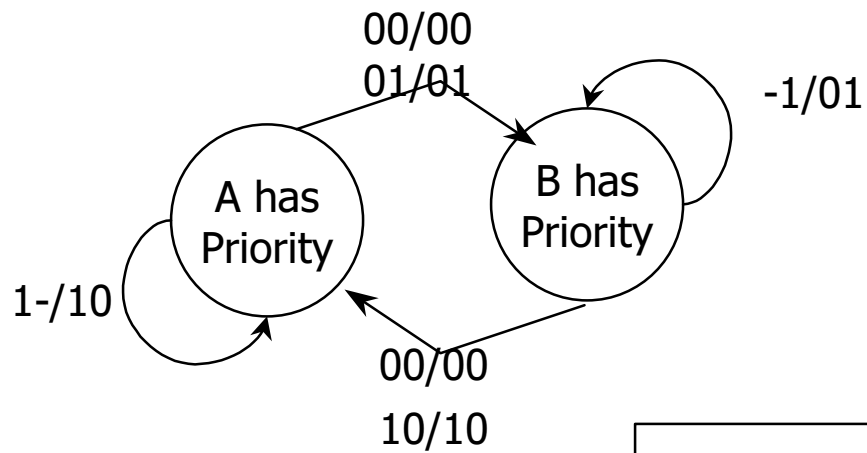

Is this safe?

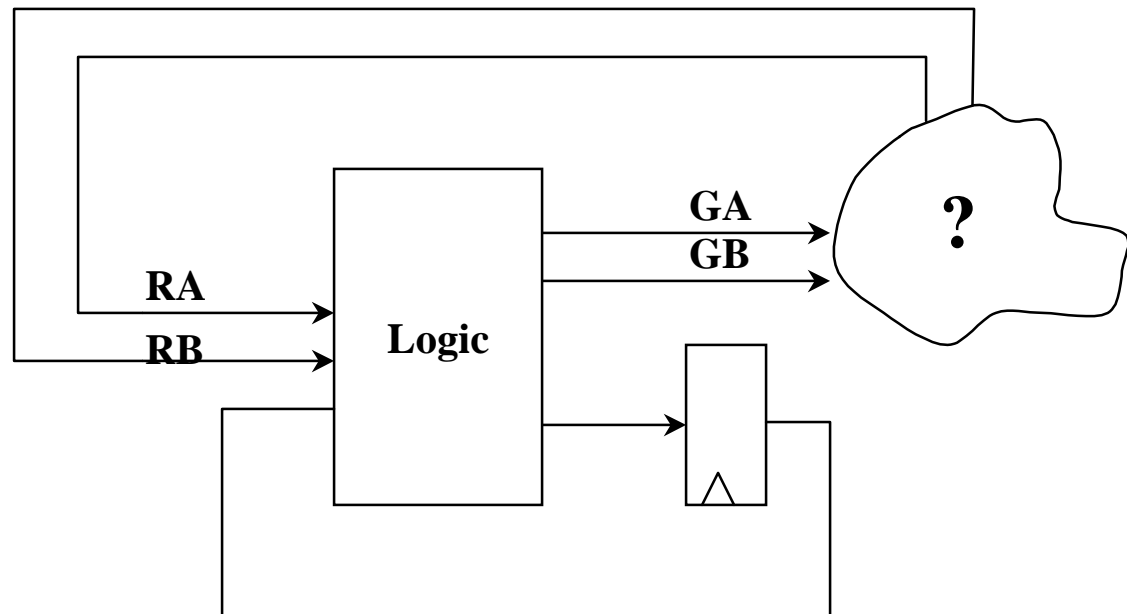

# Mealy Machine with Synchronizers

 

## ❑ Synchronous (or registered) Mealy machine



- registered state AND outputs
- avoids 'glitchy' outputs
- easy to implement in PLDs

## ❑ Moore machine with no output decoding

- outputs computed on transition to next state rather than after entering
- view outputs as expanded state vector

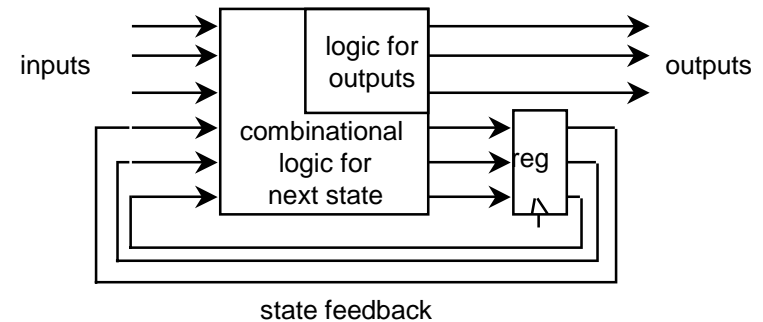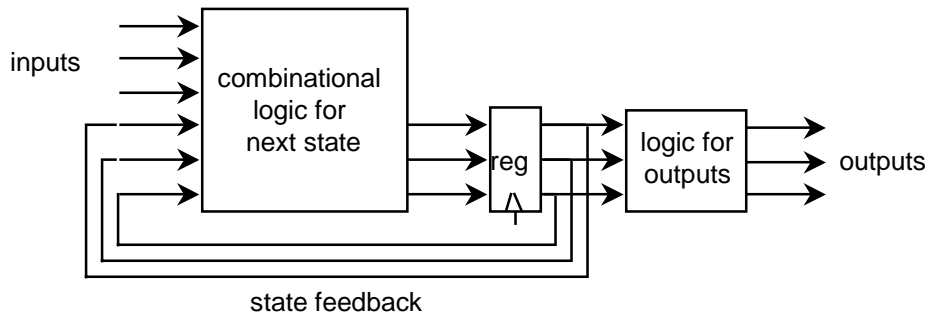
# Comparison of Mealy and Moore machines

- ❑ Mealy machines tend to have less states
  - different outputs on arcs ( $n^2$ ) rather than states ( $n$ )
- ❑ Moore machines are safer to use
  - outputs change at clock edge (always one cycle later)
  - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback
- ❑ Mealy machines react faster to inputs
  - react in same cycle – don't need to wait for clock
  - in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after


 
# Communicating State Machines (Decomposition)

- ❑ Example: A busy highway is intersected by a little used farmroad
- ❑ Detectors C sense the presence of cars waiting on the farmroad
  - with no car on farmroad, light remain green in highway direction
  - if vehicle on farmroad, highway lights go from Green to Yellow to Red, allowing the farmroad lights to become green
  - these stay green only as long as a farmroad car is detected but never longer than a set interval
  - when these are met, farm lights transition from Green to Yellow to Red, allowing highway to return to green
  - even if farmroad vehicles are waiting, highway gets at least a set interval as green



# Example: traffic light controller (cont')

❑ Tabulation of inputs and outputs

inputs    description

reset    place FSM in initial state

C        detect vehicle on the farm road


❑ outputs

description


❑ HG, HY, HR        highway lights

❑ FG, FY, FR        Farm road lights


❑ Too many states

 

# Decomposition (Parallel Processes)

 


## Decomposition

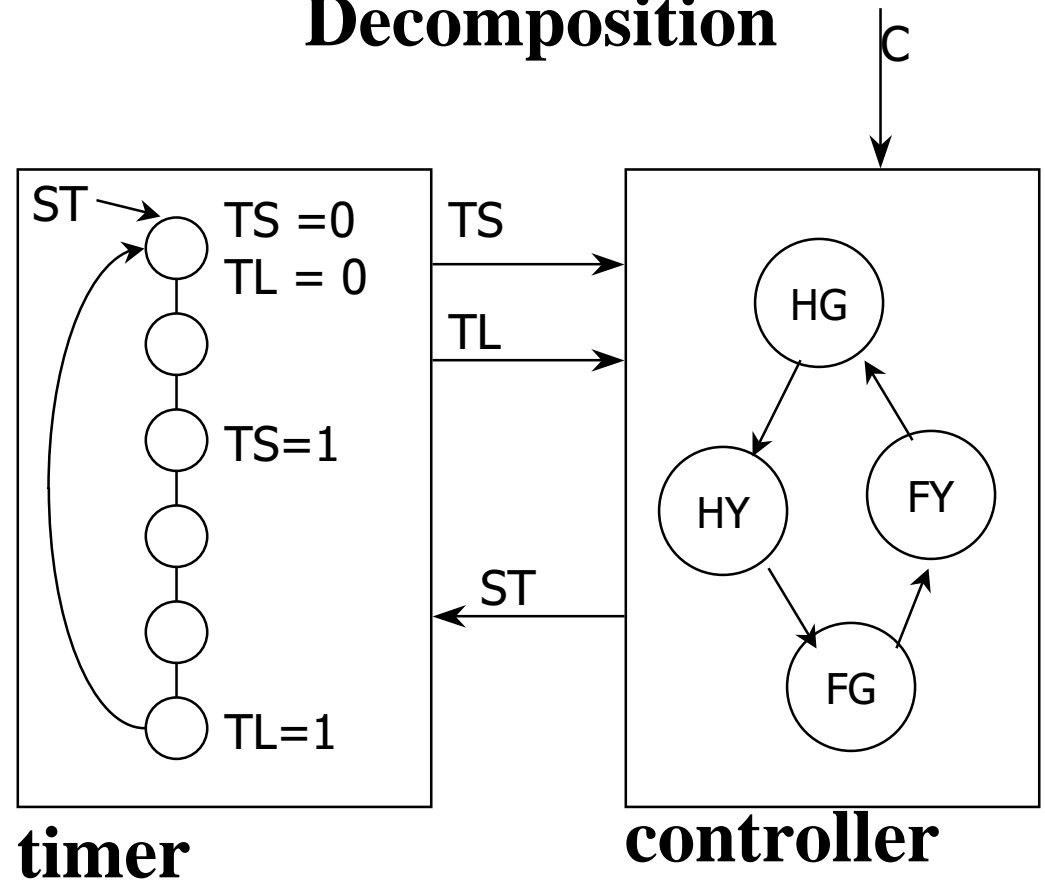




 
# Communicating finite state machines

- One machine's output is another machine's input



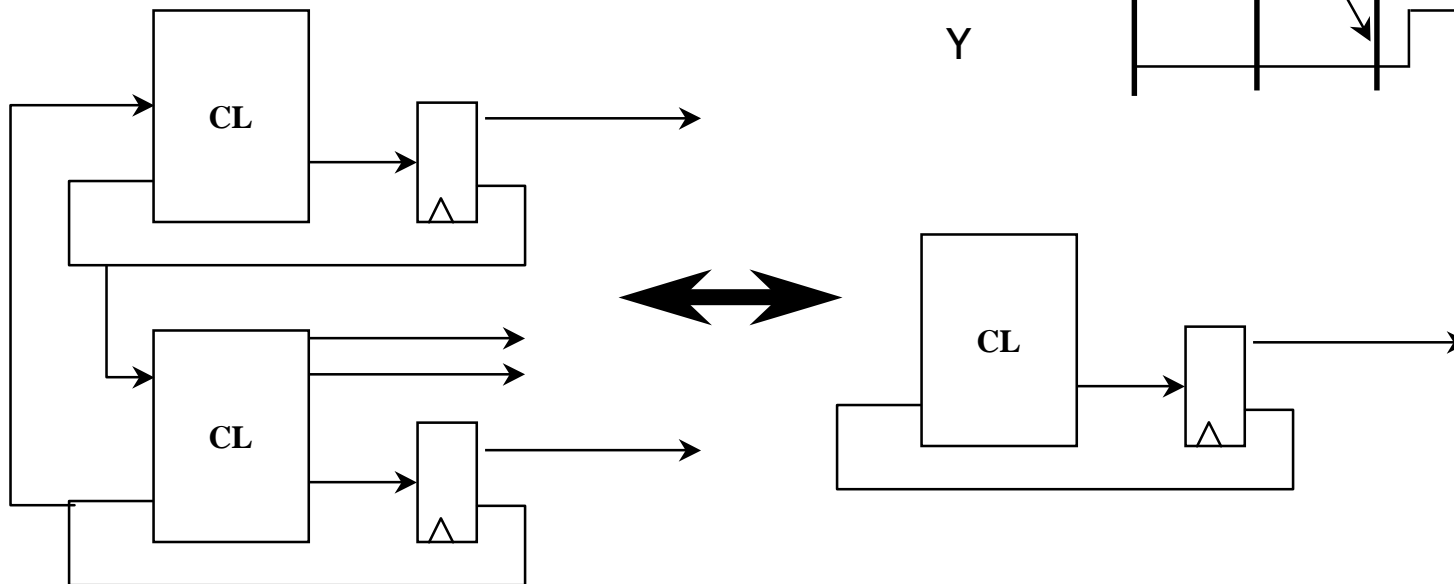 
- Its really one machine, designed as two
- HW version of parallel processes
- Be careful w/ Mealy




# Decomposition: traffic light controller

## □ Controller State diagram

States: HG, HY, FG, FY

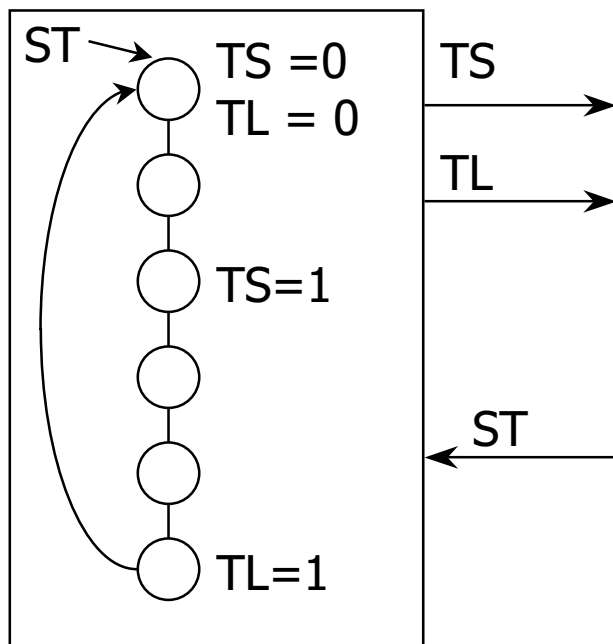

**timer**

 

# Finite state machine optimization

---

- ❑ State minimization
  - fewer states require fewer state bits
  - fewer bits require fewer logic equations
- ❑ Encodings: state, inputs, outputs
  - state encoding with fewer bits has fewer equations to implement
    - however, each may be more complex
  - state encoding with more bits (e.g., one-hot) has simpler equations
    - complexity directly related to complexity of state diagram
  - input/output encoding may or may not be under designer control

# FSM Optimization: Traffic Light Controller

- State Minimization
- State Encoding
- Output Encoding

output encoding – similar problem to state assignment  
(Green = 00, Yellow = 01, Red = 10)

Inputs			Present State	Next State	Outputs		
C	TL	TS			ST	H	F
0	–	–	HG	HG	0	Green	Red
–	0	–	HG	HG	0	Green	Red
1	1	–	HG	HY	1	Green	Red
–	–	0	HY	HY	0	Yellow	Red
–	–	1	HY	FG	1	Yellow	Red
1	0	–	FG	FG	0	Red	Green
0	–	–	FG	FY	1	Red	Green
–	1	–	FG	FY	1	Red	Green
–	–	0	FY	FY	0	Red	Yellow
–	–	1	FY	HG	1	Red	Yellow

SA1:	HG = 00	HY = 01	FG = 11	FY = 10	(gray code)
SA2:	HG = 00	HY = 10	FG = 01	FY = 11	(sequential)
SA3:	HG = 0001	HY = 0010	FG = 0100	FY = 1000	(one-hot)


# One-hot state assignment

---

- ❑ Simple
  - easy to encode
  - easy to debug
- ❑ Small logic functions
  - each state function requires only predecessor state bits as input
- ❑ Good for programmable devices
  - lots of flip-flops readily available
  - simple functions with small support (signals its dependent upon)
- ❑ Impractical for large machines
  - too many states require too many flip-flops
  - decompose FSMs into smaller pieces that can be one-hot encoded
- ❑ Many slight variations to one-hot
  - one-hot + all-0
 
# State Assignment: One Hot

SA3:      HG = 0001                  HY = 0010                  FG = 0100                  FY = 1000



SA3 (One Hot) : Read Next State logic from the state diagram!

$$NS3 = C' \cdot PS2 + TL \cdot PS2 + TS' \cdot PS3$$

$$NS2 = TS \cdot PS1 + C \cdot TL' \cdot PS2$$

$$NS1 = C \cdot TL \cdot PS0 + TS' \cdot PS1$$

$$NS0 = C' \cdot PS0 + TL' \cdot PS0 + TS \cdot PS3$$

$$ST = C \cdot TL \cdot PS0 + TS \cdot PS1 + C' \cdot PS2 + TL \cdot PS2 + TS \cdot PS3$$

$$H1 = PS3 + PS2$$

$$H0 = PS1$$

$$F1 = PS1 + PS0$$

$$F0 = PS3$$

# State Assignment: Comparison of Results

## □ SA1 (Gray Code)

$$NS1 = C \cdot TL' \cdot PS1 \cdot PS0 + TS \cdot PS1' \cdot PS0 + TS \cdot PS1 \cdot PS0' + C' \cdot PS1 \cdot PS0 + TL \cdot PS1 \cdot PS0$$

$$NS0 = C \cdot TL \cdot PS1' \cdot PS0' + C \cdot TL' \cdot PS1 \cdot PS0 + PS1' \cdot PS0$$

$$ST = C \cdot TL \cdot PS1' \cdot PS0' + TS \cdot PS1' \cdot PS0 + TS \cdot PS1 \cdot PS0' + C' \cdot PS1 \cdot PS0 + TL \cdot PS1 \cdot PS0$$

$$H1 = PS1$$

$$H0 = PS1' \cdot PS0$$

$$F1 = PS1'$$

$$F0 = PS1 \cdot PS0'$$

## □ SA2 (Sequential)

$$NS1 = C \cdot TL \cdot PS1' + TS' \cdot PS1 + C' \cdot PS1' \cdot PS0$$

$$NS0 = TS \cdot PS1 \cdot PS0' + PS1' \cdot PS0 + TS' \cdot PS1 \cdot PS0$$

$$ST = C \cdot TL \cdot PS1' + C' \cdot PS1' \cdot PS0 + TS \cdot PS1$$

$$H1 = PS0$$

$$H0 = PS1 \cdot PS0'$$

$$F1 = PS0'$$

$$F0 = PS1 \cdot PS0$$

## □ SA3 (One Hot)

$$NS3 = C' \cdot PS2 + TL \cdot PS2 + TS' \cdot PS3$$

$$NS2 = TS \cdot PS1 + C \cdot TL' \cdot PS2$$

$$NS1 = C \cdot TL \cdot PS0 + TS' \cdot PS1$$

$$NS0 = C' \cdot PS0 + TL' \cdot PS0 + TS \cdot PS3$$

$$ST = C \cdot TL \cdot PS0 + TS \cdot PS1 + C' \cdot PS2 + TL \cdot PS2 + TS \cdot PS3$$

$$H1 = PS3 + PS2$$

$$H0 = PS1$$

$$F1 = PS1 + PS0$$

$$F0 = PS3$$

**But, if we already had a counter...**

# State assignment strategies

---

- ❑ Possible strategies
  - sequential – just number states as they appear in the state table (Timer)
  - random – pick random codes
  - one-hot – use as many state bits as there are states (Small)
  - output – use outputs to help encode states (Intersection)
  - heuristic – rules of thumb that seem to work in most cases (Opcode)
- ❑ No guarantee of optimality – another intractable problem




# Heuristics for state assignment

- 1. Adjacent codes to states that share a common next state

- group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	c	j
i	b	c	k

$$c = i * a + i * b$$

 


- 2. Adjacent codes to states that share a common ancestor state

- group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	b	j
k	a	c	l

$$b = i * a$$

$$c = k * a$$

 

- 3. Adjacent codes to states that have a common output behavior


- group 1's in output map

I	Q	Q <sup>+</sup>	O
i	a	b	j
i	c	d	j

$$j = i * a + i * c$$

$$b = i * a$$

$$d = i * c$$

 

# General approach to heuristic state assignment

- ❑ All current methods are variants of this
  - 1) determine which states "attract" each other (weighted pairs)
  - 2) generate constraints on codes (which should be in same cube)
  - 3) place codes on Boolean cube so as to maximize constraints satisfied sum (distance\*weighted)
- ❑ Different weights make sense depending on whether we are optimizing for two-level or multi-level forms
- ❑ Can't consider all possible embeddings of state clusters in Boolean cube
  - heuristics for ordering embedding
  - to prune search for best embedding
  - expand cube (more state bits) to satisfy more constraints -- eventually becomes one-hot

# Example

## Common Next State

S3: S1, S4, S5

S2: S1, S2, S5


## Common Ancestor

S0: S1, S4

S5: S2, S3

S4: S2, S5

S1: S2, S3

 

b2b1b0	00	01	11	10
0	?	S4	S5	S0
1	?	S1	S2	S3

Can we satisfy all Constraints?  
How do I use empty cells?

Symbolically:  $S2 = I'(S1+S2+S4)$ . If codes for S1, S2, S4 then logic is simpler

$$S1 = I(S0)$$

$$S4 = I'(S0)$$

If codes for S1, S4 are close then logic is simpler

# Example: Output Encoding

If state machine's  
Outputs are opcodes

- s0 = [NEG] + [NOT]
- s1 = [INC] + [DEC] + [PASS] + [NEG] + [NOT]
- s2 = [DEC] + [SUB] + [CMP] + [XNOR]
- s3 = [OR]
- s4 = [ARITHMETIC]'
- s5 = [SH(L/R)]
- s6 = [AND] + [OR] + [SHR]
- s7 = [ARITHMETIC]
- s8 = [SHL]
- s9 = ([ADD] + [DEC])'

P3P2P1P0	00	01	11	10
00	OR	PASS	INC	x
01	AND	NOT	NEG	x
11	SHR	XNOR	DEC	ADD
10	SHL	XOR	CMP	SUB

# State Encoding: Output-based encoding

- Reuse outputs as state bits - use outputs to help distinguish states
  - why create new functions for state bits when output can serve as well
  - fits in nicely with synchronous Mealy implementations

Inputs			Present State	Next State	Outputs (each row is unique)		
C	TL	TS			ST	H	F
0	-	-	HG	HG	0	00	10
-	0	-	HG	HG	0	00	10
1	1	-	HG	HY	1	00	10
-	-	0	HY	HY	0	01	10
-	-	1	HY	FG	1	01	10
1	0	-	FG	FG	0	10	00
0	-	-	FG	FY	1	10	00
-	1	-	FG	FY	1	10	00
-	-	0	FY	FY	0	10	01
-	-	1	FY	HG	1	10	01

$$HG = ST' H1' H0' F1 F0' + ST H1 H0' F1' F0$$

$$HY = ST H1' H0' F1 F0' + ST' H1' H0 F1 F0'$$

$$FG = ST H1' H0 F1 F0' + ST' H1 H0' F1' F0'$$

$$FY = ST H1 H0' F1' F0' + ST' H1 H0' F1' F0$$


Output patterns are unique to states, we do not need ANY state bits – implement 5 functions (one for each output) instead of 7 (outputs plus 2 state bits)

# Current state assignment approaches

- ❑ For tight encodings using close to the minimum number of state bits
  - best of 10 random seems to be adequate (averages as well as heuristics)
  - heuristic approaches are not even close to optimality
  - used in custom chip design
- ❑ One-hot encoding
  - easy for small state machines
  - generates small equations with easy to estimate complexity
  - common in FPGAs and other programmable logic
- ❑ Output-based encoding
  - ad hoc - no tools
  - most common approach taken by human designers
  - yields very small circuits for most FSMs
- ❑ Tools for
  - Partitioning (Decomposition)
  - State and output Encoding
 
# Algorithmic approach to state minimization


- ❑ Goal – identify and combine states that have equivalent behavior
- ❑ Equivalent states:
  - same output
  - for all input combinations, states transition to same or equivalent state
- ❑ Example: Sequence Detector: 010 or 110



# State minimization example: Sequence Detector

- ❑ Goal – identify and combine states that have equivalent behavior
- ❑ Equivalent states:
  - same output
  - for all input combinations, states transition to same or equivalent state
- ❑ Sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 



# Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

( S0 S1 S2 S3 S5 ) ( S4 S6 )

( S0 S1 S2 ) ( S3 S5 ) ( S4 S6 )

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6


S3 is equivalent to S5

S1 is equivalent to S2


# Minimized FSM

- State minimized sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0 + 1	S1'	S3'	S4'	0	0
X0	S3'	S0	S0	0	0
X1	S4'	S0	S0	1	0

 


what about this case?

 

# More complex state minimization

- Multiple input example

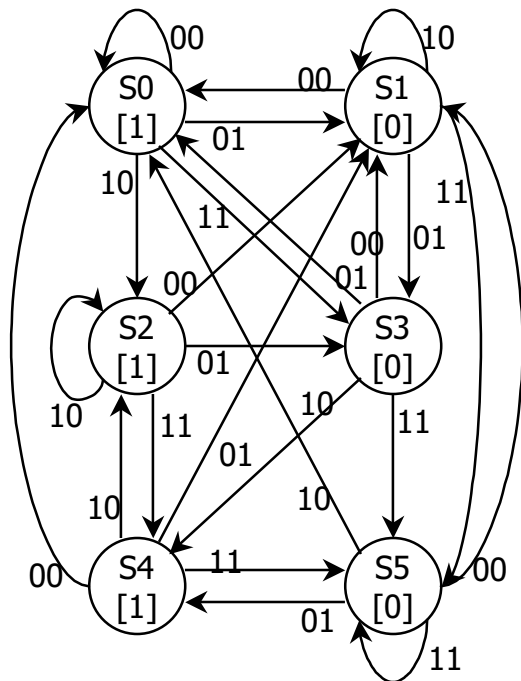

inputs here


present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table

# Minimized FSM
 
## □ Implication chart method

- cross out incompatible states based on outputs
- then cross out more cells if indexed chart entries are already crossed out



present state	next state				output
	00	01	10	11	
S0*	S0*	S1	S2	S3*	1
S1	S0*	S3*	S1	S3*	0
S2	S1	S3*	S2	S0*	1
S3*	S1	S0*	S0*	S3*	0

minimized state table  
(S0==S4) (S3==S5)

# Minimizing incompletely specified FSMs

- ❑ Equivalence of states is transitive when machine is fully specified
- ❑ But its not transitive when don't cares are present


e.g.,

state	output	
S0	– 0	S1 is compatible with both S0 and S2
S1	1 –	but S0 and S2 are incompatible
S2	– 1	

- ❑ No polynomial time algorithm exists for determining best grouping of states into equivalent sets that will yield the smallest number of final states

# Minimizing states may not yield best circuit

 - Example: edge detector - outputs 1 when input changes from 0 to 1





X	$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
-	1	1	0	0

$$Q_1^+ = X (Q_1 \text{ xor } Q_0)$$

$$Q_0^+ = X Q_1 Q_0$$
  
# Another implementation of edge detector

- ❑ "Ad hoc" solution - not minimal but cheap and fast
- ❑ State compression from 4 to 3 states not very helpful



# Sequential logic implementation summary

- ❑ Models for representing sequential circuits
  - abstraction of sequential elements
  - finite state machines and their state diagrams
  - inputs/outputs
  - Mealy, Moore, and synchronous Mealy machines
- ❑ Finite state machine design procedure
  - deriving state diagram
  - deriving state transition table
  - determining next state and output functions
  - implementing combinational logic
- ❑ Implementation of sequential logic
  - state minimization
  - state assignment
  - support in programmable logic devices



# Sequential logic examples

---

- ❑ Finite state machine concept
  - FSMs are the decision making logic of digital designs
  - partitioning designs into datapath and control elements
  - when inputs are sampled and outputs asserted
- ❑ Basic design approach: a 4-step design process
- ❑ Implementation examples and case studies
  - finite-string pattern recognizer

# General FSM design procedure

---

- ❑ (1) Determine inputs and outputs
- ❑ (2) Determine possible states of machine
  - – state minimization
- ❑ (3) Encode states and outputs into a binary code
  - – state assignment or state encoding
  - – output encoding
  - – possibly input encoding (if under our control)
- ❑ (4) Realize logic to implement functions for states and outputs
  - – Verilog model for simulation and synthesis
  - -- combinational logic implementation and optimization
  - – choices made in steps 2 and 3 can have large effect on resulting logic

# Finite string pattern recognizer (step 1)


- Finite string pattern recognizer
  - one input (X) and one output (Z)
  - output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen
  
- Step 1: understanding the problem statement
  - sample input/output behavior:

```
X: 0 0 1 0 1 0 1 0 0 1 0 ...  
Z: 0 0 0 1 0 1 0 1 0 0 0 ...
```

```
X: 1 1 0 1 1 0 1 0 0 1 0 ...  
Z: 0 0 0 0 0 0 0 1 0 0 0 ...
```
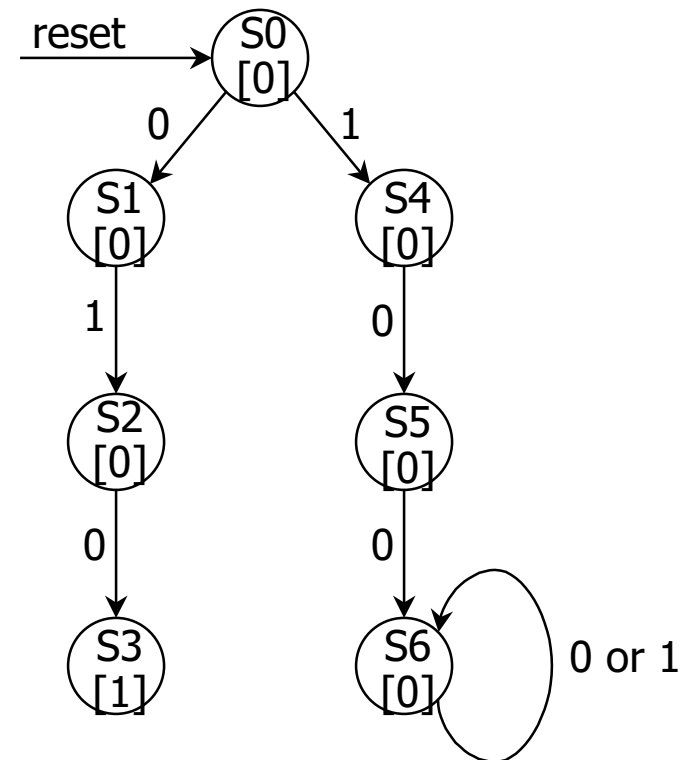
# Finite string pattern recognizer (step 2)

- Step 2: draw state diagram
  - for the strings that must be recognized, i.e., 010 and 100
  - a Moore implementation




# Finite string pattern recognizer (step 2, cont'd)

- Exit conditions from state S3: have recognized ...010
  - if next input is 0 then have ...0100 = ...100 (state S6)
  - if next input is 1 then have ...0101 = ...01 (state S2)


Exit conditions from S1:  
recognizes  
strings of form ...0 (no 1 seen)  
loop back to S1 if input is 0

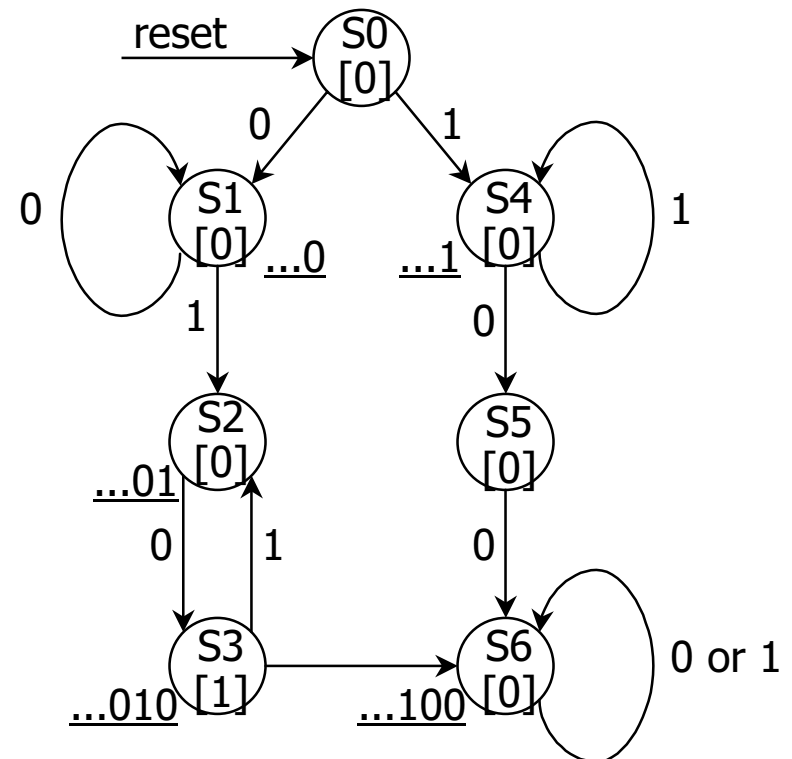Exit conditions from S4:  
recognizes  
strings of form ...1 (no 0 seen)  
loop back to S4 if input is 1


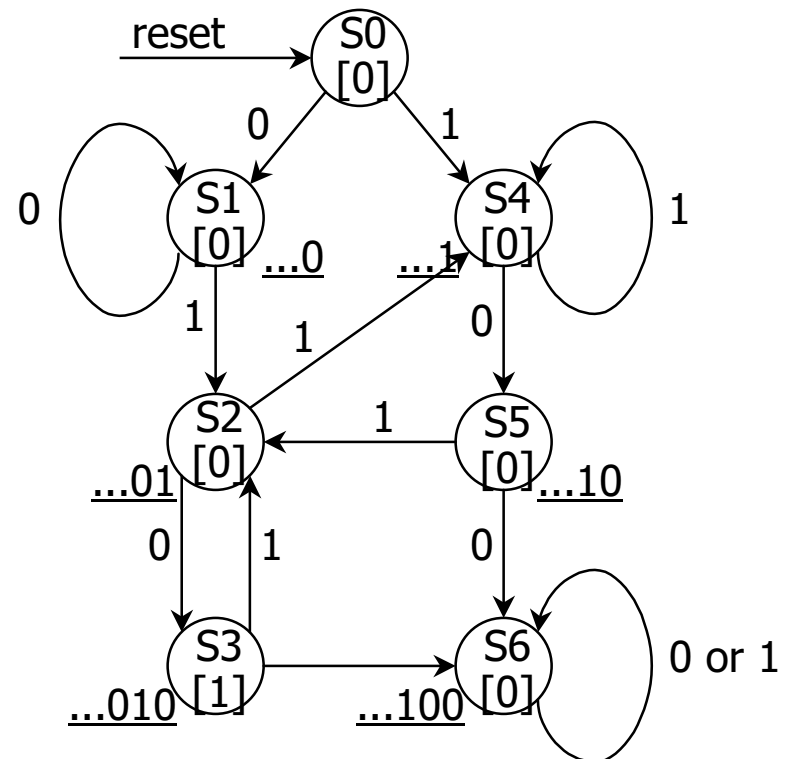
# Finite string pattern recognizer (step 2, cont'd)

- ❑ S2 and S5 still have incomplete transitions
  - S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
  - S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case
- ❑ Reuse states as much as possible
  - look for same meaning
  - state minimization leads to smaller number of bits to represent states
- ❑ Once all states have a complete set of transitions we have a final state diagram



# Finite string pattern recognizer (step 3)

- Verilog description including state assignment (or state encoding)

```
module string (clk, X, rst, Q0, Q1, Q2, Z);
input clk, X, rst;
output Q0, Q1, Q2, Z;

reg state[0:2];
`define S0 = [0,0,0]; //reset state
`define S1 = [0,0,1]; //strings ending in ...0
`define S2 = [0,1,0]; //strings ending in ...01
`define S3 = [0,1,1]; //strings ending in ...010
`define S4 = [1,0,0]; //strings ending in ...1
`define S5 = [1,0,1]; //strings ending in ...10
`define S6 = [1,1,0]; //strings ending in ...100

assign Q0 = state[0];
assign Q1 = state[1];
assign Q2 = state[2];
assign Z = (state == `S3);

always @(posedge clk) begin
  if rst state = `S0;
  else
    case (state)
      `S0: if (X) state = `S4 else state = `S1;
      `S1: if (X) state = `S2 else state = `S1;
      `S2: if (X) state = `S4 else state = `S3;
      `S3: if (X) state = `S2 else state = `S6;
      `S4: if (X) state = `S4 else state = `S5;
      `S5: if (X) state = `S2 else state = `S6;
      `S6: state = `S6;
    default: begin
      $display ("invalid state reached");
      state = 3'bxxx;
    endcase
  end
endmodule
```

# Finite string pattern recognizer

---

- Review of process
  - understanding problem
    - write down sample inputs and outputs to understand specification
  - derive a state diagram
    - write down sequences of states and transitions for sequences to be recognized
  - minimize number of states
    - add missing transitions; reuse states as much as possible
  - state assignment or encoding
    - encode states with unique patterns
  - simulate realization
    - verify I/O behavior of your state diagram to ensure it matches specification