

Hardware description languages

- Describe hardware at varying levels of abstraction
- Structural description
 - ┆ textual replacement for schematic
 - ┆ hierarchical composition of modules from primitives
- Behavioral/functional description
 - ┆ describe what module does, not how
 - ┆ synthesis generates circuit for module
- Simulation semantics

HDLs

- Abel (circa 1983) - developed by Data-I/O
 - ┆ targeted to programmable logic devices
 - ┆ not good for much more than state machines
- ISP (circa 1977) - research project at CMU
 - ┆ simulation, but no synthesis
- Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
 - ┆ similar to Pascal and C
 - ┆ delays is only interaction with simulator
 - ┆ fairly efficient and easy to write
 - ┆ IEEE standard
- VHDL (circa 1987) - DoD sponsored standard
 - ┆ similar to Ada (emphasis on re-use and maintainability)
 - ┆ simulation semantics visible
 - ┆ very general but verbose
 - ┆ IEEE standard

Verilog

- Supports structural and behavioral descriptions
- Structural
 - ┆ explicit structure of the circuit
 - ┆ e.g., each logic gate instantiated and connected to others
- Behavioral
 - ┆ program describes input/output behavior of circuit
 - ┆ many structural implementations could have same behavior
 - ┆ e.g., different implementation of one Boolean function
- We'll only be using behavioral Verilog in DesignWorks
 - ┆ rely on schematic when we want structural descriptions

Structural model

```
module xor_gate (out, a, b);
  input    a, b;
  output   out;
  wire     abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);

endmodule
```

Simple behavioral model

■ Continuous assignment

```
module xor_gate (out, a, b);  
  input      a, b;  
  output    out;  
  reg       out;  
  
  assign #6 out = a ^ b;  
  
endmodule
```

simulation register -
keeps track of
value of signal

delay from input change
to output change

Simple behavioral model

■ always block

```
module xor_gate (out, a, b);  
  input      a, b;  
  output    out;  
  reg       out;  
  
  always @(a or b) begin  
    #6 out = a ^ b;  
  end  
  
endmodule
```

specifies when block is executed
ie. triggered by which signals

Driving a simulation

```
module stimulus (x, y);  
  output      x, y;  
  reg [1:0]   cnt;  
  
  initial begin  
    cnt = 0;  
    repeat (4) begin  
      #10 cnt = cnt + 1;  
      $display ("@ time=%d, x=%b, y=%b, cnt=%b",  
        $time, x, y, cnt); end  
    #10 $finish;  
  end  
  
  assign x = cnt[1];  
  assign y = cnt[0];  
endmodule
```

2-bit vector

initial block executed only once at start of simulation


print to a console

directive to stop simulation

CSE 370 - Spring 1999 - Hardware Description Languages - 7

Complete Simulation

- Instantiate stimulus component and device to test in a schematic

 

CSE 370 - Spring 1999 - Hardware Description Languages - 8

Comparator Example

```
module Compare1 (A, B, Equal, Alarger, Blarger);
  input      A, B;
  output     Equal, Alarger, Blarger;

  assign #5 Equal = (A & B) | (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

More Complex Behavioral Model

```
module life (n0, n1, n2, n3, n4, n5, n6, n7, self, out);
  input      n0, n1, n2, n3, n4, n5, n6, n7, self;
  output     out;
  reg        out;
  reg [7:0] neighbors;
  reg [3:0] count;
  reg [3:0] i;

  assign neighbors = {n7, n6, n5, n4, n3, n2, n1, n0};

  always @(neighbors or self) begin
    count = 0;
    for (i = 0; i < 8; i = i+1) count = count + neighbors[i];
    out = (count == 3);
    out = out | ((self == 1) & (count == 2));
  end
endmodule
```

Hardware Description Languages vs. Programming Languages

- Program structure
 - instantiation of multiple components of the same type
 - specify interconnections between modules via schematic
 - hierarchy of modules (only leaves can be HDL in DesignWorks)
- Assignment
 - continuous assignment (logic always computes)
 - propagation delay (computation takes time)
 - timing of signals is important (when does computation have its effect)
- Data structures
 - size explicitly spelled out - no dynamic structures
 - no pointers
- Parallelism
 - hardware is naturally parallel (must support multiple threads)
 - assignments can occur in parallel (not just sequentially)

CSE 370 - Spring 1999 - Hardware Description Languages - 11

Hardware Description Languages and Combinational Logic

- Modules - specification of inputs, outputs, bidirectional, and internal signals
- Continuous assignment - a gate's output is a function of its inputs at all times (doesn't need to wait to be "called")
- Propagation delay- concept of time and delay in input affecting gate output
- Composition - connecting modules together with wires
- Hierarchy - modules encapsulate functional blocks
- Specification of don't care conditions (accomplished by setting output to "x")

CSE 370 - Spring 1999 - Hardware Description Languages - 12

Hardware Description Languages and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers)
- Data-paths = ALUs + registers
 - use of arithmetic/logical operators
 - control of storage elements
- Parallelism
 - multiple state machines running in parallel
- Sequential don't cares

CSE 370 - Spring 1999 - Hardware Description Languages - 13

Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock edge

```
module dff (clk, d, q);  
  
    input  clk, d;  
    output q;  
    reg   q;  
  
    always @(posedge clk)  
        q = d;  
  
endmodule
```

CSE 370 - Spring 1999 - Hardware Description Languages - 14

More Flip-flops

- Synchronous/asynchronous reset/set
 - single thread that waits for the clock
 - three parallel threads – only one of which waits for the clock

```
module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge clk)
        if (reset) q = 1'b0;
        else if (set) q = 1'b1;
        else q = d;
endmodule

module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge reset)
        q = 1'b0;
    always @(posedge set)
        q = 1'b1;
    always @(posedge clk)
        q = d;
endmodule
```

Structural View of an FSM

- Traffic light controller: two always blocks - flip-flops separate from logic

```
module FSM (HL, FL, ST, clk, C, TS, TL);
    output [2:0] HL, FL;    reg [2:0] HL, FL;
    output ST;            reg ST;
    input clk;
    input C, TS, TL;
    reg [1:0] present_state;
    reg [1:0] next_state;

    initial begin HL = 3'b001; FL = 3'b100; present_state = 2'b00; end

    always @(posedge clk) // registers
        present_state = next_state;

    always @(present_state or C or TS or TL)
        // compute next-state and output logic whenever state or inputs change
        // put equations here for next_state[1:0], HL[2:0], FL[2:0], and ST
        // as functions of C, TS, TL, and present_state[1:0]
endmodule
```


Behavioral View of an FSM

■ Specification of inputs, outputs, and state elements

```
module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
  output HR;
  output HY;
  output HG;
  output FR;
  output FY;
  output FG;
  output ST;
  input TS;
  input TL;
  input C;
  input reset;
  input Clk;

  reg [6:1] state;
  reg ST;

  `define highwaygreen 6'b001100
  `define highwayyellow 6'b010100
  `define farmroadgreen 6'b100001
  `define farmroadyellow 6'b100010

  assign HR = state[6];
  assign HY = state[5];
  assign HG = state[4];
  assign FR = state[3];
  assign FY = state[2];
  assign FG = state[1];
endmodule
```

specify state bits and codes
for each state as well as
connections to outputs

CSE 370 - Spring 1999 - Hardware Description Languages - 17

Behavioral View of an FSM (cont'd)

```
initial begin state = `highwaygreen; ST = 0; end

always @(posedge Clk)
begin
  if (reset)
    begin state = `highwaygreen; ST = 1; end
  else
    begin
      ST = 0;
      case (state)
        `highwaygreen:
          if (TL & C) begin state = `highwayyellow; ST = 1; end
        `highwayyellow:
          if (TS) begin state = `farmroadgreen; ST = 1; end
        `farmroadgreen:
          if (TL | !C) begin state = `farmroadyellow; ST = 1; end
        `farmroadyellow:
          if (TS) begin state = `highwaygreen; ST = 1; end
      endcase
    end
  end
endmodule
```

case statement
triggered by
clock edge

CSE 370 - Spring 1999 - Hardware Description Languages - 18

Timer for Traffic Light Controller

■ Another FSM

```
module Timer(TS, TL, ST, Clk);
    output TS;
    output TL;
    input  ST;
    input  Clk;
    integer value;

    assign TS = (value >= 4); // 5 cycles after reset
    assign TL = (value >= 14); // 15 cycles after reset

    always @(posedge ST) value = 0; // async reset

    always @(posedge Clk) value = value + 1;

endmodule
```

Complete Traffic Light Controller

■ Tying it all together (FSM + timer)

```
module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);
    output HR, HY, HG, FR, FY, FG;
    input  reset, C, Clk;

    Timer part1(TS, TL, ST, Clk);
    FSM  part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
endmodule
```

Verilog FSM - Reduce 1s example

Moore machine


```

`define zero 0
`define one1 1 ← state assignment
`define twols 2

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg [2:1] state; // state variables
  reg [2:1] next_state;

  always @(posedge clk)
    if (reset) state = `zero;
    else state = next_state;

```

 

Moore Verilog FSM (cont'd)

```

always @(in or state) ←
  case (state)
  `zero:
  // last input was a zero
  begin
    if (in) next_state = `one1;
    else next_state = `zero;
  end
  `one1:
  // we've seen one 1
  begin
    if (in) next_state = `twols;
    else next_state = `zero;
  end
  `twols:
  // we've seen at least 2 ones
  begin
    if (in) next_state = `twols;
    else next_state = `zero;
  end
  endcase

```

crucial to include
all signals that are
input to state and
output equations

note that output only
depends on state

```

always @(state)
  case (state)
  `zero: out = 0;
  `one1: out = 0;
  `twols: out = 1;
  endcase

```


endmodule

Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  `register state;      // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = `zero;
    else      state = next_state;

  always @(in or state)
    case (state)
      `zero:      // last input was a zero
        begin
          out = 0;
          if (in) next_state = `one;
          else   next_state = `zero;
        end
      `one:      // we've seen one 1
        if (in) begin
          next_state = `one; out = 1;
        end else begin
          next_state = `zero; out = 0;
        end
    endcase
endmodule
```

 

CSE 370 - Spring 1999 - Hardware Description Languages - 23

Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = `zero;
    else
      case (state)
        `zero:      // last input was a zero
          begin
            out = 0;
            if (in) state = `one;
            else   state = `zero;
          end
        `one:      // we've seen one 1
          if (in) begin
            state = `one; out = 1;
          end else begin
            state = `zero; out = 0;
          end
      endcase
endmodule
```

CSE 370 - Spring 1999 - Hardware Description Languages - 24