

## Drawbacks of single cycle implementation

- All instructions take the same time although
  - some instructions are longer than others;
    - e.g. load is longer than add since it has to access data memory in addition to all the other steps that add does
  - thus the “cycle” has to be for the “longest path”
- Some combinational units must be replicated since used in the same cycle
  - e.g., ALU for computing branch address and ALU for computing branch outcome
    - but this is no big deal (these duplicate resources will be needed when we will pipeline instructions)

10/27/2004

CSE378 Multicycle impl.,

1

## Alternative to single cycle

- Have a shorter cycle and instructions execute in multiple (shorter) cycles
- The (shorter) cycle time determined by the longest delay in individual functional units (e.g., memory or ALU etc.)
- Possibility to streamline some resources since they will be used at different cycles
- Since there is need to keep information “between cycles”, we’ll need to add some stable storage (registers) not visible at the ISA level
- Not all instructions will require the same number of cycles

10/27/2004

CSE378 Multicycle impl.,

2

## Multiple cycle implementation

- Follows the decomposition of the steps for the execution of instructions
  - Cycle 1. Instruction fetch and increment PC
  - Cycle 2. Instruction decode and read source registers and branch address computation
  - Cycle 3. ALU execution or memory address calculation or set PC if branch successful
  - Cycle 4. Memory access (load/store) or write register (arith/log)
  - Cycle 5 Write register (load)
- Note that branch takes 3 cycles, load takes 5 cycles, all others take 4 cycles

10/27/2004

CSE378 Multicycle impl.,

3

## Instruction fetch

- Because fields in the instruction are needed at different cycles, the instruction has to be kept in stable storage, namely an *Instruction Register (IR)*
- The register transfer level actions during this step
  - $IR \leftarrow Memory[PC]$
  - $PC \leftarrow PC + 4$
- Resources required
  - Memory (but no need to distinguish between instruction and data memories; later on we will because the need will reappear when we pipeline instructions)
  - Adder to increment PC
  - IR

10/27/2004

CSE378 Multicycle impl.,

4

## Instruction decode and read source registers

- Instruction decode: send opcode to control unit and...(see later)
- Perform “optimistic” computations that are not harmful
  - Read *rs* and *rt* and store them in *non-ISA visible registers A* and *B* that will be used as input to ALU
  - $A \leftarrow REG[IR[25:21]]$  (read *rs*)
  - $B \leftarrow REG[IR[20:16]]$  (read *rt*)
  - Compute the branch address just in case we had a branch!
  - $ALUout \leftarrow PC + (sign-ext(IR[15:0]) * 4)$  (ALUout is also a *non-ISA visible register*)
- New resources
  - A, B, ALUout

10/27/2004

CSE378 Multicycle impl.,

5

## ALU execution

- If instruction is R-type
  - $ALUout \leftarrow A \text{ op. } B$
- If instruction is Immediate
  - $ALUout \leftarrow A \text{ op. } sign\text{-extend}(IR[15:0])$
- If instruction is Load/Store
  - $ALUout \leftarrow A + sign\text{-extend}(IR[15:0])$
- If instruction is branch
  - If (A=B) then  $PC \leftarrow ALUout$  (note this is the ALUout computed in the previous cycle)
- No new resources

10/27/2004

CSE378 Multicycle impl.,

6

## Memory access or ALU completion

- If Load  
 $MDR \leftarrow Memory[ALUout]$  (MDR is the *Memory Data Register* non-ISA visible register)
- If Store  
 $Memory[ALUout] \leftarrow B$
- If arith  
 $Reg[IR[15:11]] \leftarrow ALUout$
- New resources
  - MDR

10/27/2004

CSE378 Multicycle impl.,

7

## Load completion

- Write result register  
 $Reg[IR[20:16]] \leftarrow MDR$

10/27/2004

CSE378 Multicycle impl.,

8

## Streamlining of resources


- No distinction between instruction and data memory
- Only one ALU
- But a few more muxes and registers (IR, MDR etc.)

10/27/2004

CSE378 Multicycle impl.,

9

## FloorPlan for Multicycle MIPS

 

10/27/2004

CSE378 Multicycle impl.,

10

## Control Unit for Multiple Cycle Implementation

- Control is more complex than in single cycle since:
  - Need to define control signals for each step
  - Need to know which step we are on
- Two methods for designing the control unit
  - Finite state machine and hardwired control (extension of the single cycle implementation)
  - Microprogramming (read the book about it)

10/27/2004

CSE378 Multicycle impl.,

11



## What are the control signals needed?

- Let's look at control signals needed at each of 5 steps
- Signals needed for
  - reading/writing memory
  - reading/writing registers
  - control the various muxes
  - control the ALU (recall how it was done for single cycle implementation)

10/27/2004

CSE378 Multicycle impl.,

12

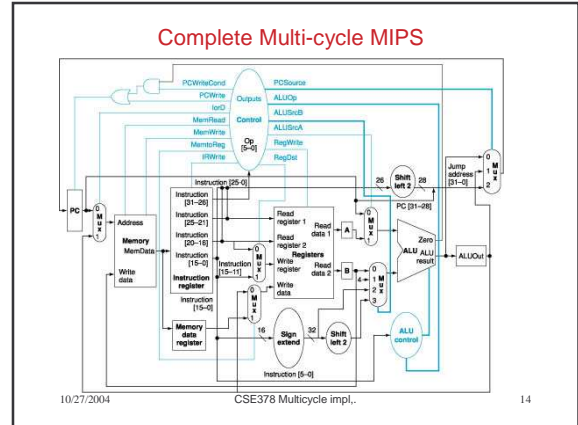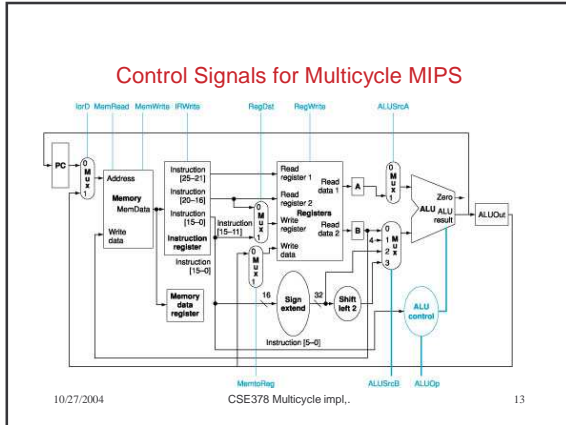

- ### Instruction fetch
- Need to read memory
    - Choose input address (mux with signal  $lorD = 0$ )
    - Set  $MemRead$  signal
    - Set  $IRWrite$  signal (note that there is no write signal for MDR; Why?)
  - Set sources for ALU
    - Source 1: mux set to “come from PC” (signal  $ALUSrcA = 0$ )
    - Source 2: mux set to “constant 4” (signal  $ALUSrcB = 01$ )
  - Set ALU control to “+” (e.g.,  $ALUOp = 00$  and don’t care for the function bits)
- 10/27/2004 CSE378 Multicycle impl., 15

- ### Instruction fetch (PC increment)
- Set the mux to store in PC as coming from ALU (signal  $PCsource = 01$ )
  - Set  $PCwrite$ 
    - Note: this could be wrong if we had a branch but it will be overwritten in that case; see step 3 of branch instructions
- 10/27/2004 CSE378 Multicycle impl., 16

- ### Instruction decode and read source registers
- Read registers in A and B
    - No need for control signals. This will happen at every cycle. No problem since neither IR (giving names of the registers) nor the registers themselves are modified. When we need A and B as sources for the ALU, e.g., in step 3, the muxes will be set accordingly
  - Branch target computations. Select inputs for ALU
    - Source 1: mux set to “come from PC” (signal  $ALUSrcA = 0$ )
    - Source 2: mux set to “come from IR, sign-extended, shifted left 2” (signal  $ALUSrcB = 11$ )
  - Set ALU control to “+” ( $ALUOp = 00$ )
- 10/27/2004 CSE378 Multicycle impl., 17

- ### Concept of “state”
- During steps 1 and 2, all instructions do the same thing
  - At step 3, opcode is directing
    - What control lines to assert (it will be different for a load, an add, a branch etc.)
    - What will be done at subsequent steps (e.g., access memory, writing a register, fetching the next instruction)
  - At each cycle, the control unit is put in a specific state that depends only on the previous state and the opcode
    - (current state, opcode) → (next state) *Finite state machine* (cf. CSE370, CSE 322)
- 10/27/2004 CSE378 Multicycle impl., 18

## The first two states


- Since the data flow and the control signals are the same for all instructions in step 1 (instr. fetch) there is only one state associated with step 1, say *state 0*
- And since all operations in the next step are also always the same, we will have the transition
  - (state 0, all) → (state 1)

10/27/2004

CSE378 Multicycle impl.,

19

## Customary notation

 

10/27/2004

CSE378 Multicycle impl.,

20

## Transitions from State 1


- After the decode, the data flow depends on the type of instructions:
  - Register-Register: Needs to compute a result and store it
  - Load/Store: Needs to compute the address, access memory, and in the case of a load write the result register
  - Branch: test the result of the condition and, if need be, change the PC
  - Jump: need to change the PC
  - Immediate: Not shown in the figures. Do it as an exercise

10/27/2004

CSE378 Multicycle impl.,

21

## State transitions from State 1

 

10/27/2004

CSE378 Multicycle impl.,

22

## State 2: Memory Address Computation


- Set sources for ALU
  - Source 1: mux set to "come from A" (signal  $ALUSrcA = 1$ )
  - Source 2: mux set to "imm. extended" (signal  $ALUSrcB = 10$ )
- Set ALU control to "+" ( $ALUop = 00$ )
- Transition from State 2
  - If we have a "load" transition to State 3
  - If we have a "store" transition to State 5

10/27/2004

CSE378 Multicycle impl.,

23

## State 2: Memory address computation

 

10/27/2004

CSE378 Multicycle impl.,

24

