

Levels in Processor Design


- Circuit design
 - Keywords: transistors, wires etc. Results in gates, flip-flops etc.
- Logical design
 - Putting gates (AND, NAND, ...) and flip-flops together to build basic blocks such as registers, ALU's etc (cf. CSE 370)
- *Register transfer*
 - Describes execution of instructions by showing data flow between the basic blocks
- **Processor description** (the ISA)
- **System description**
 - Includes memory hierarchy, I/O, multiprocessing etc

Register transfer level

- Two types of components (cf. CSE 370)
 - *Combinational* : the output is a function of the input (e.g., adder)
 - *Sequential*: state is remembered (e.g., register)


Synchronous design

 - Use of a **periodic clock**
 - *edge-triggered* clocking determines when signals can be read and when the output of circuits is stable
 - Values in storage elements can be updated only at clock edges
 - Clock tells when events can occur, e.g., when signals sent by control unit are obeyed in the ALU



Note: the same storage element can be read/written in the same cycle

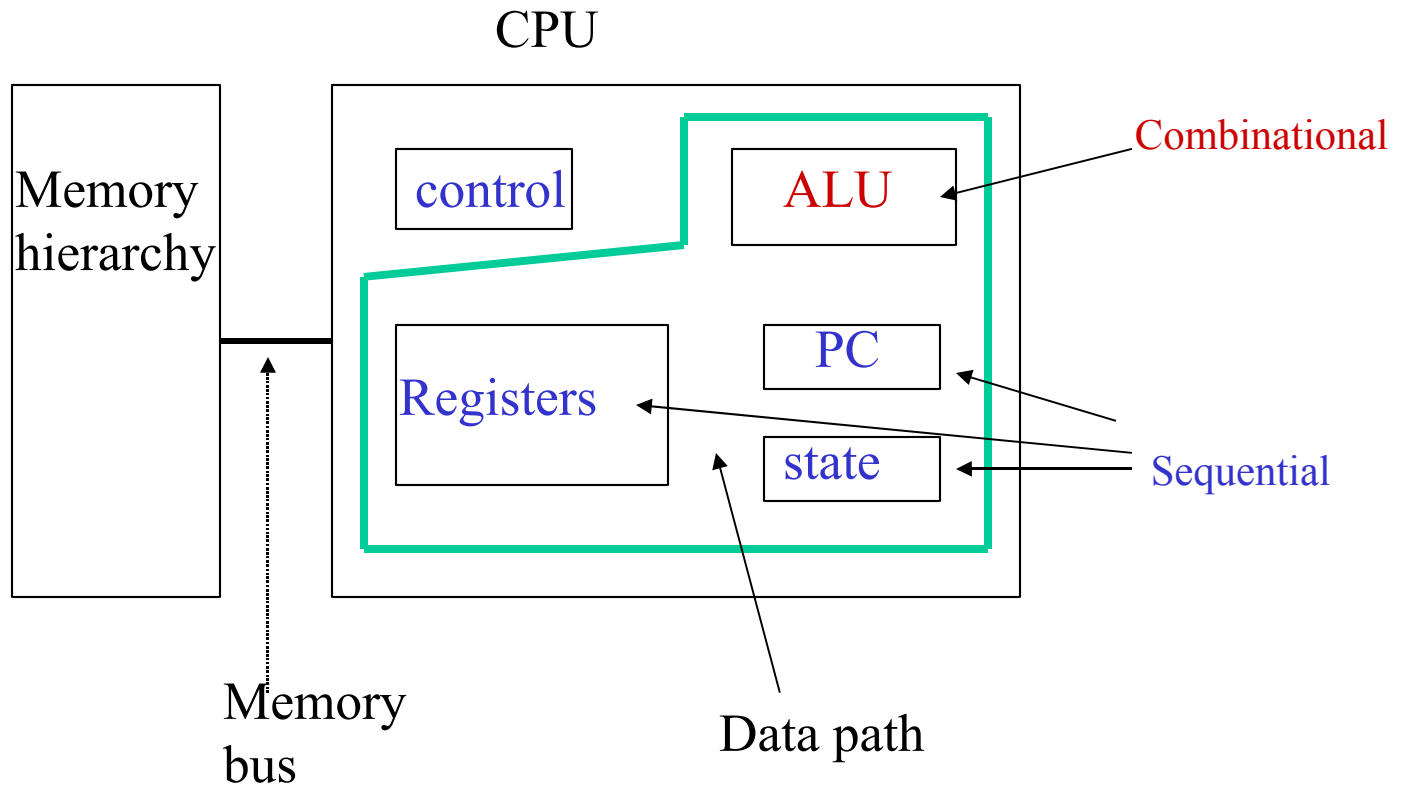Processor design: data path and control unit




Processor design

- Data path
 - How does data flow between various basic blocks
 - What operations can be performed when data flows
 - What can be done in one clock cycle
- Control unit
 - Sends signals to data path elements
 - Tells what data to move, where to move it, what operations are to be performed
- Memory hierarchy
 - Holds program and data

Data path basic building blocks.


Storage elements

 - Basic building block (at the RT level) is a register
- In our mini-MIPS implementation registers will be 32-bits
- A register can be read or written




Register file

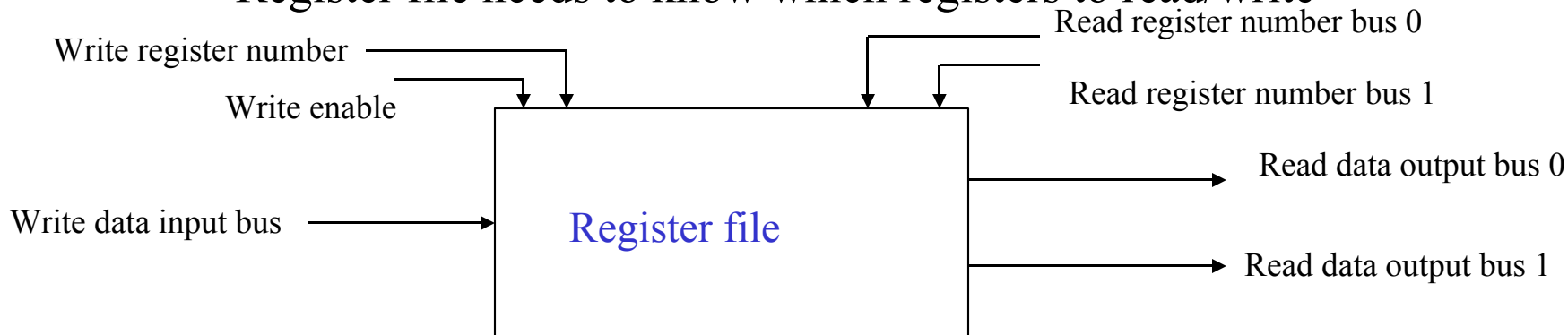- Array of registers (32 for the integer registers in MIPS)
- ISA tells us that we should be able to:
 - read 2 registers, write one register in a given instruction (at this point we want one instruction per cycle)
 - Register file needs to know which registers to read/write




Memory

 - Conceptually, like register file but much larger
- Can only **read one location or write to one location per cycle**




Combinational elements

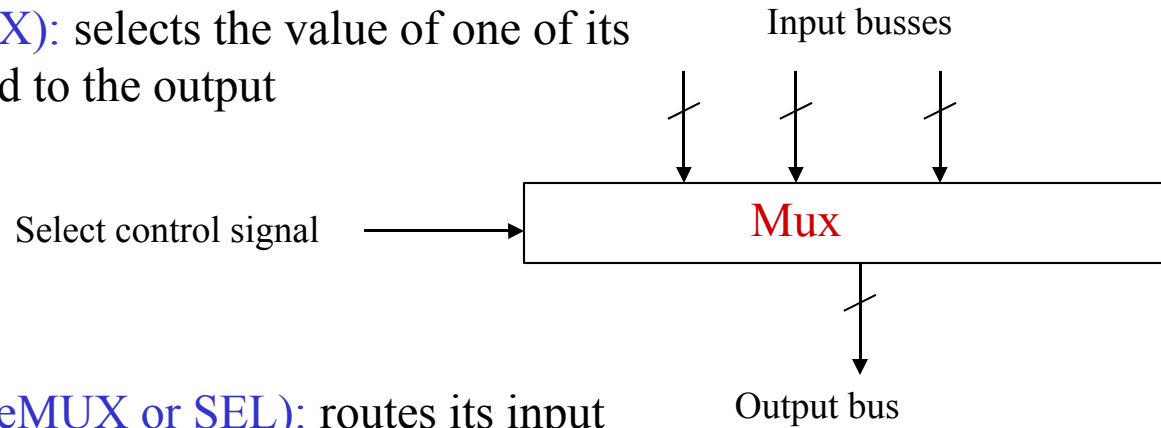Multiplexor (MUX): selects the value of one of its inputs to be routed to the output




 Demultiplexor (deMUX or SEL): routes its input to one of its outputs




Arithmetic and Logic Unit (ALU - combinational)

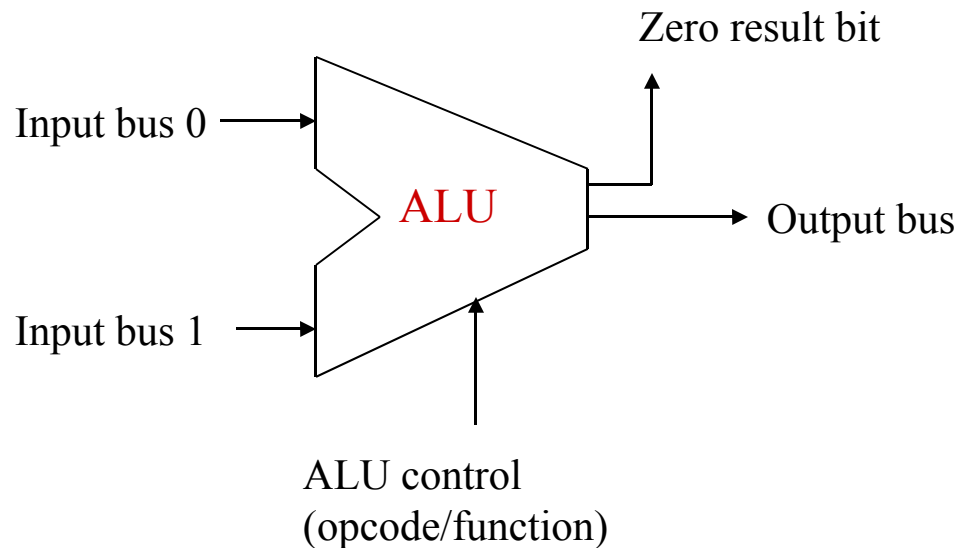
- Computes (arithmetic or logical operation) output from its two inputs



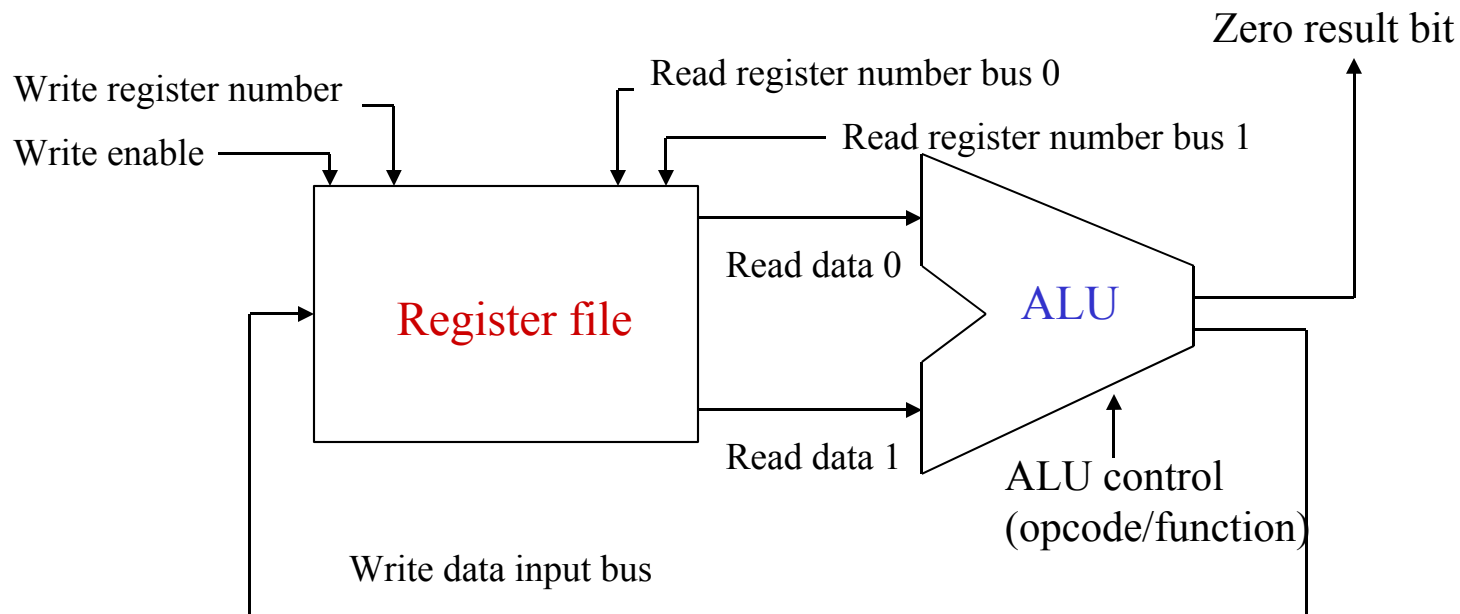
Putting basic blocks together (skeleton of data path for arith/logical operations)




Introducing instruction fetch

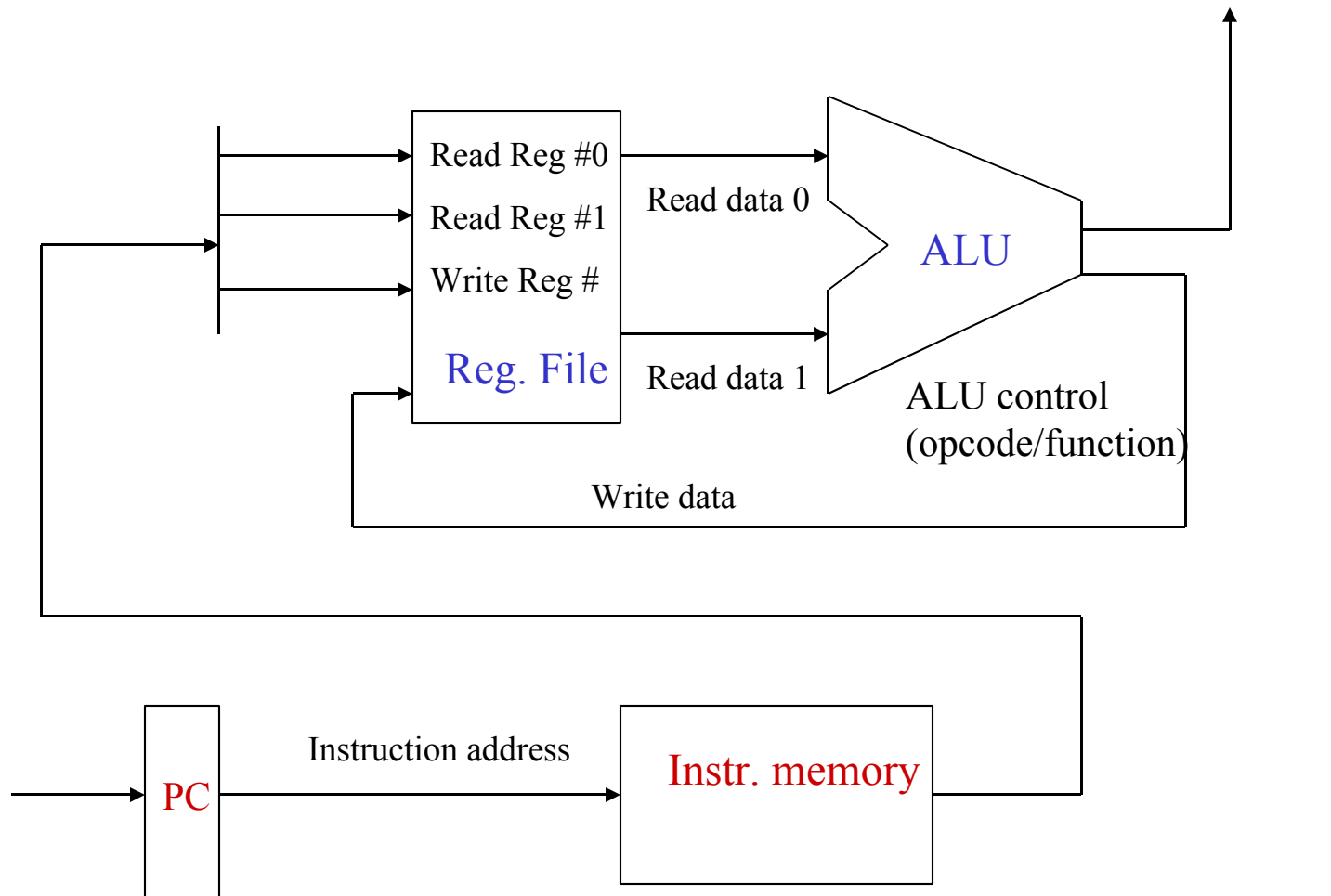

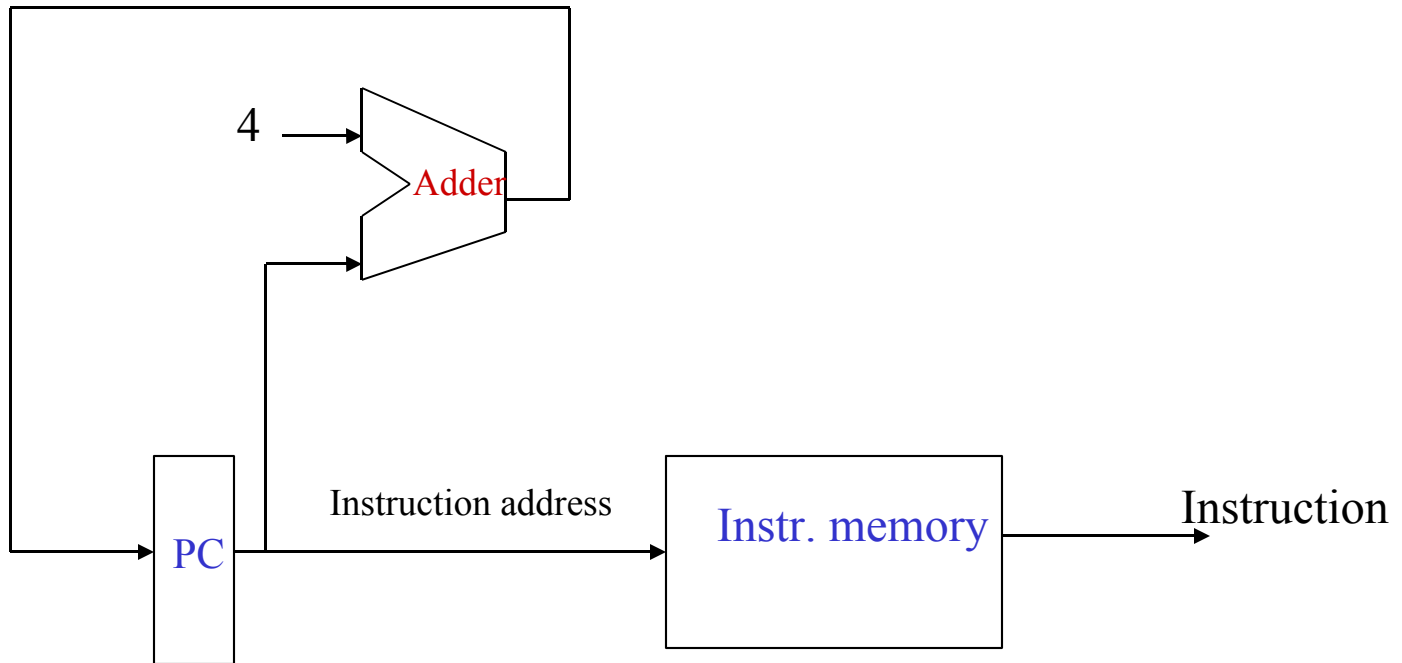
PC has to be incremented (assume no branch)




Load-Store instructions

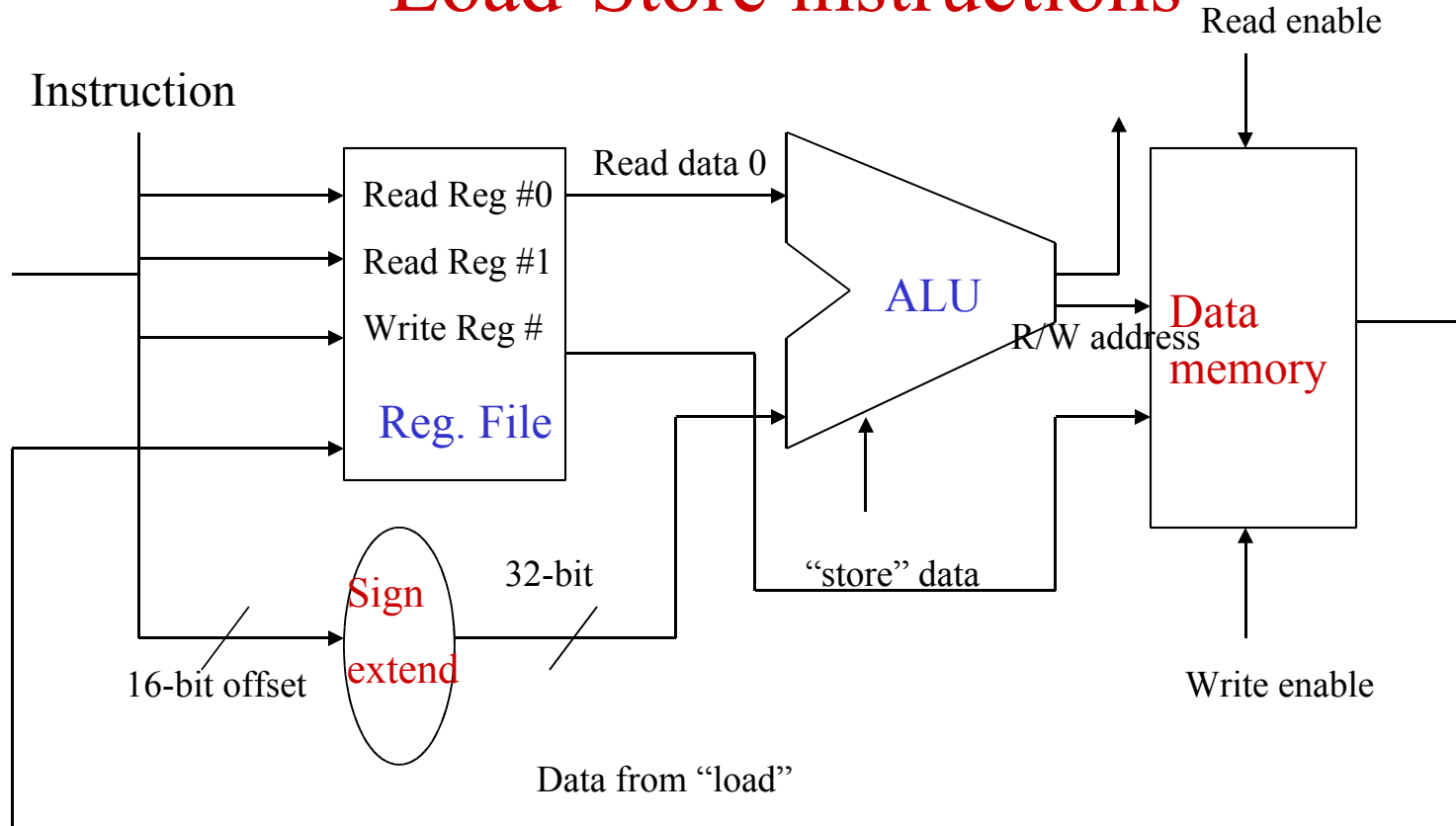

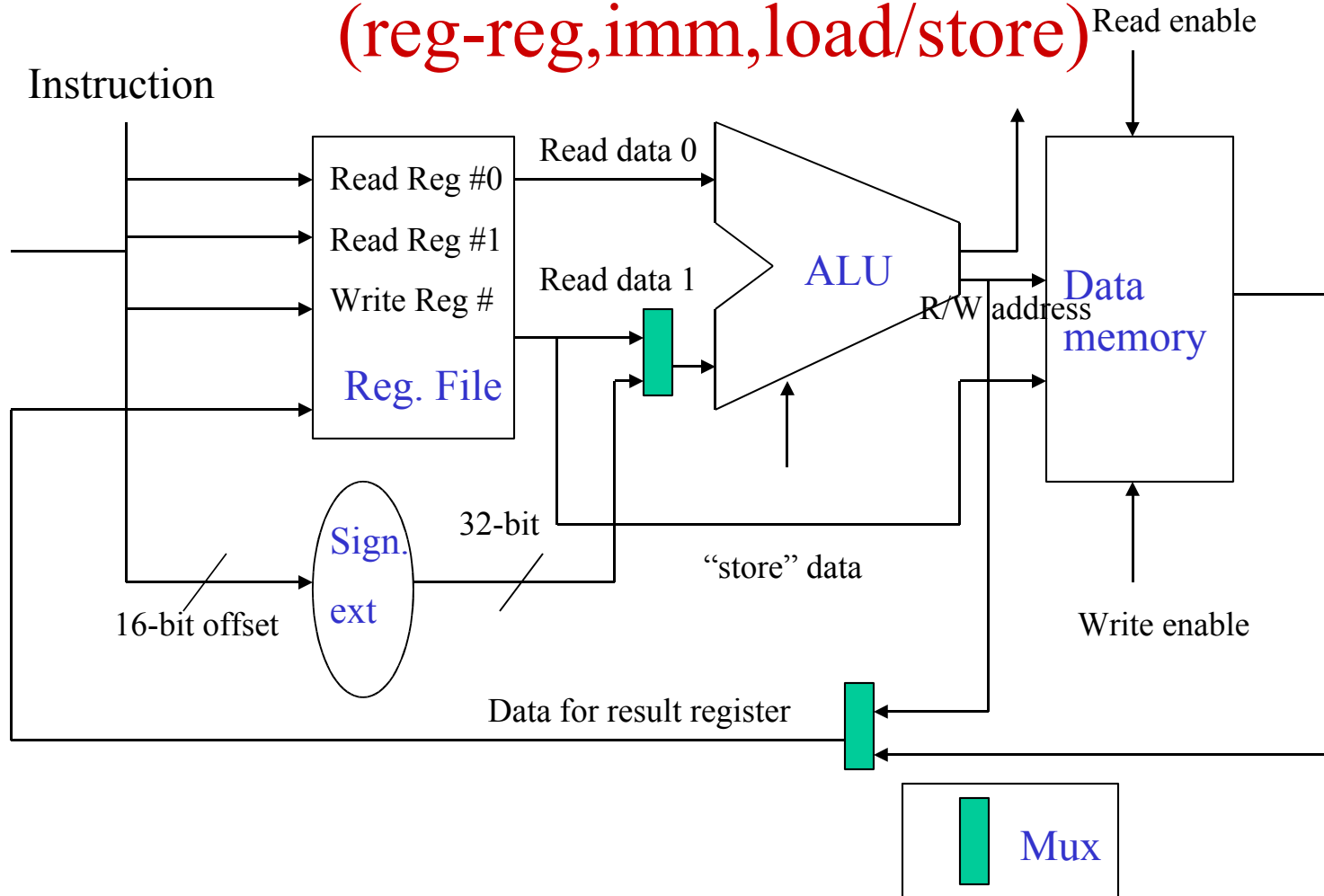Data path for straight code (reg-reg,imm,load/store)



Branch data path

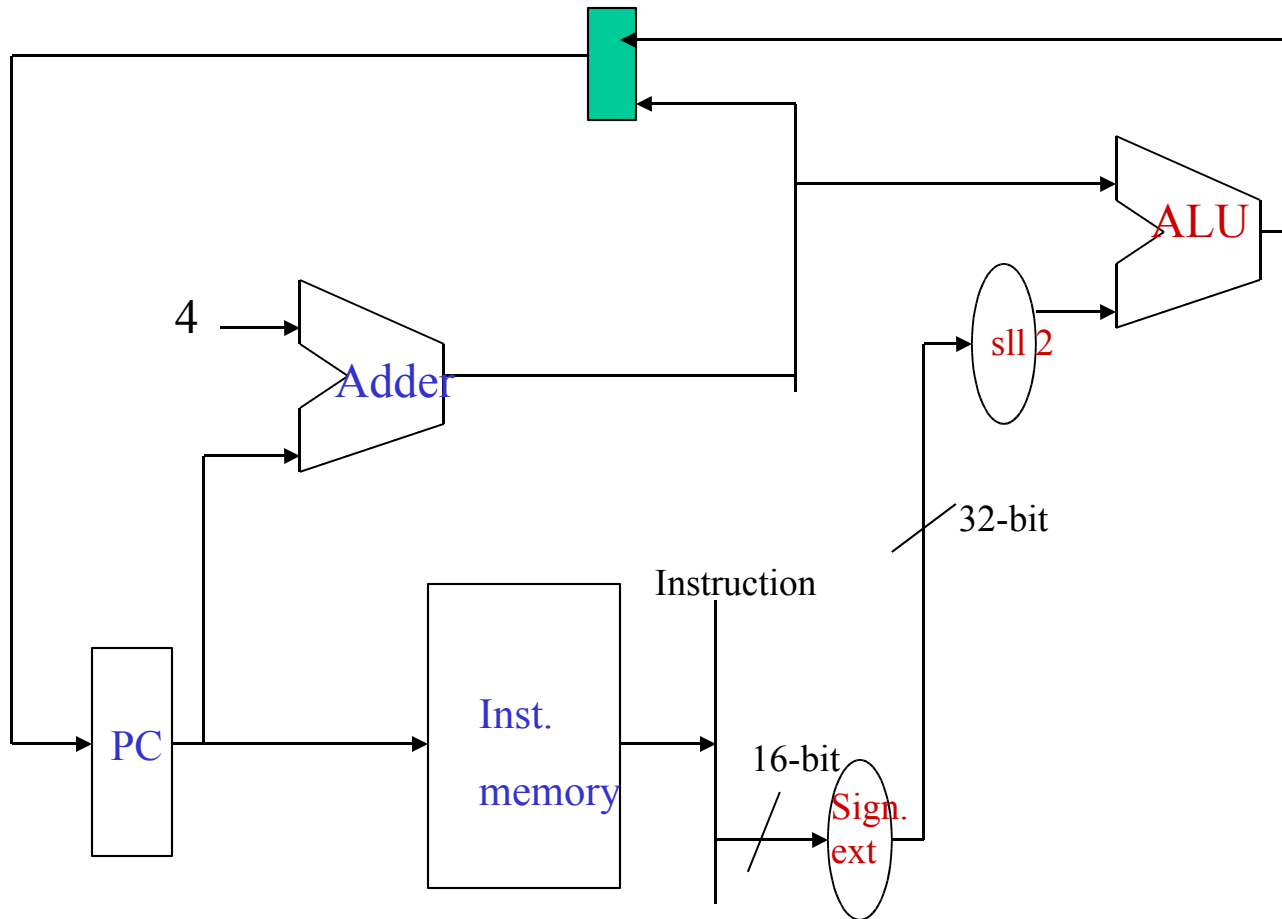

CSE378 Single cycle implementation.

Control Unit

- Control unit sends control signals to data path and memory depending
 - on the opcode (and function field)
 - results in the ALU (for example for Zero test)
- These signals control
 - muxes; read/write enable for registers and memory etc.
- Some “control” comes directly from instruction
 - register names
- Some actions are performed at every instruction so no need for control (in this single cycle implementation)
 - incrementing PC by 4; reading instr. memory for fetching next inst.

Building the control unit

- Decompose the problem into
 - Data path control (register transfers)
 - ALU control
- Setting of control lines by control unit totally specified in the ISA
 - for ALU by opcode + function bits if R-R format
 - for register names by instruction (including opcode)
 - for reading/writing memory and writing register by opcode
 - muxes by opcode
 - PC by opcode + result of ALU

Example

- Limit ourselves to:
 - R-R instructions: add, sub, and, or, slt –
 - Opcode = 0 but different function bits
 - Load-store: lw, sw
 - Branch: beq
- ALU control
 - Need to *add* for: add, lw, sw
 - Need to *sub* for: sub, beq
 - Need to *and* for :and
 - Need to *or* for :or
 - Need to *set less than* for : slt

ALU Control

- ALU control: combination of opcode and function bits
- Decoding of opcodes yields 3 possibilities hence 2 bits
 - AluOp1 and ALUOp2
- ALU control:
 - Input 2 ALUop bits and 6 function bits
 - Output one of 5 possible ALU functions
 - Of course lots of don't care for this *very* limited implementation

Implementation of Overall Control Unit

- Input: opcode (and function bits for R-R instructions)
- Output: setting of control lines
- Can be done by logic equations
- If not too many, like in RISC machines
 - Use of PAL's (cf. CSE 370).
 - In RISC machines the control is “hardwired”
- If too large (too many states etc.)
 - Use of microprogramming (a microprogram is a hardwired program that interprets the ISA)
- Or use a combination of both techniques (Pentium)

Where are control signals needed (cf. Figure 5.15)

- Register file
 - **RegWrite** (Register write signal for R-type, Load)
 - **RegDst** (Register destination signal: rd for R-type, rt for Load)
- ALU
 - **ALUSrc** (What kind of second operand: register or immediate)
 - **ALUOp** (What kind of function: ALU control for R-type)
- Data memory
 - **MemRead** (Load) or **MemWrite** (Store)
 - **MemtoReg** (Result register written from ALU or memory)
- Branch control
 - **PCSrc** (PC modification if branch is taken)

How are the control signals asserted

- Decoding of the opcode by control unit yields
 - Control of the 3 muxes (RegDst, ALUSrc, MemtoReg): 3 control lines
 - Signals for RegWrite, Memread, Memwrite: 3 control lines
 - Signals to activate ALU control (e.g., restrict ourselves to 2)
 - Signal for branch (1 control line)
 - decoding of opcode ANDed with ALU zero result
- Input Opcode: 6 bits
- Output 9 control lines (see Figure 5.17)