

# Avoiding pain in 378

Autumn '09


CSE378

Jacob Nelson

# Agenda

- Pep talk
- Lab overview
- Verilog
  - Mapping Verilog to hardware
  - Verilog tips and traps

# My desktop circa 1998

 

RAL 1989 Annual Report

Your processor



>>

Sun 3/50

# What can we do?



<http://www.xkl.com>

  

<http://pulse-sequencer.sourceforge.net>

# Free as in { freedom | beer }

*simulation:* Icarus Verilog; GTKWave

*schematics/board design:* gEDA


*chips/implementation:* Xilinx, Altera, etc.

*boards:* cheap PCB houses; toaster oven

*programming/debugging:* OpenOCD

Not doing it for you?

# PARALLEL CRISIS!!!

 

The Landscape of Parallel Computing Research: A View From Berkeley



# Funky parallelism

- Hardware is inherently parallel
- FPGA =  
Fine-grained massively parallel computer
- Verilog =  
Funky parallel programming language

# Lab Process and Goals

# Four main lab tasks


- *One*: build single-cycle datapath; create jump/branch logic
- *Two*: build control logic for single-cycle CPU
- *Three*: add pipeline registers
- *Four*: finish pipeline with forwarding and hazard detection

# First task

- Mostly connecting things together in BDE; write Verilog for jumps and branches
- We provide testbenches, but they're incomplete (add tests?)
- Final step: write small program to flash lights

 PROPERTY OF UNIVERSITY OF WASHINGTON  
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING  
DONATION BY ALTERA CORPORATION

003  
 
# Our hardware

- Altera Cyclone II EP2C20
  - 18,752 4-input lookup tables
  - 18,752 one-bit registers
  - 240 kilobytes of memory on the chip
- (everything else on the board)

# A few tools

- Aldec Active-HDL simulates Verilog and BDE
  - Assembler turns code into bits for memory
- Altera Quartus does three things:
  - translates Verilog to hardware primitives
  - arranges hardware primitives on the chip
  - downloads design to chip

# Hardware primitives



# Logic

```
module foo (a,b,f,g);  
  input wire a, b;  
  output wire f;  
  output reg g;  
  
  assign f = a && b;  
  always @(*)  
    g = a && b;  
endmodule
```


# Registers

```
input wire nextFoo;  
reg foo;
```


```
always @(posedge clk)  
    foo <= nextFoo;
```

# Our Computational Substrate

(from Altera Cyclone II datasheet)

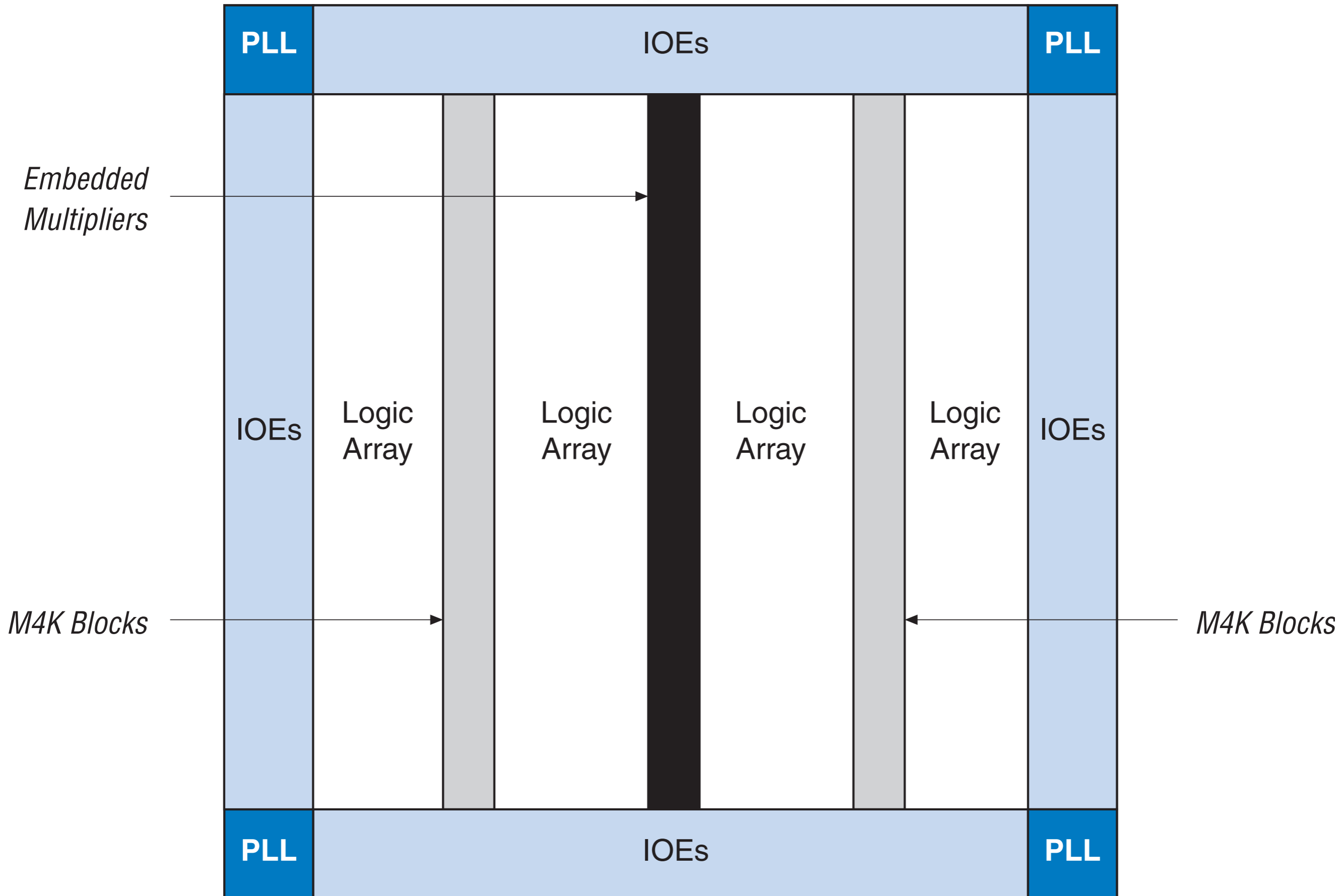

**Figure 2-2. Cyclone II LE**

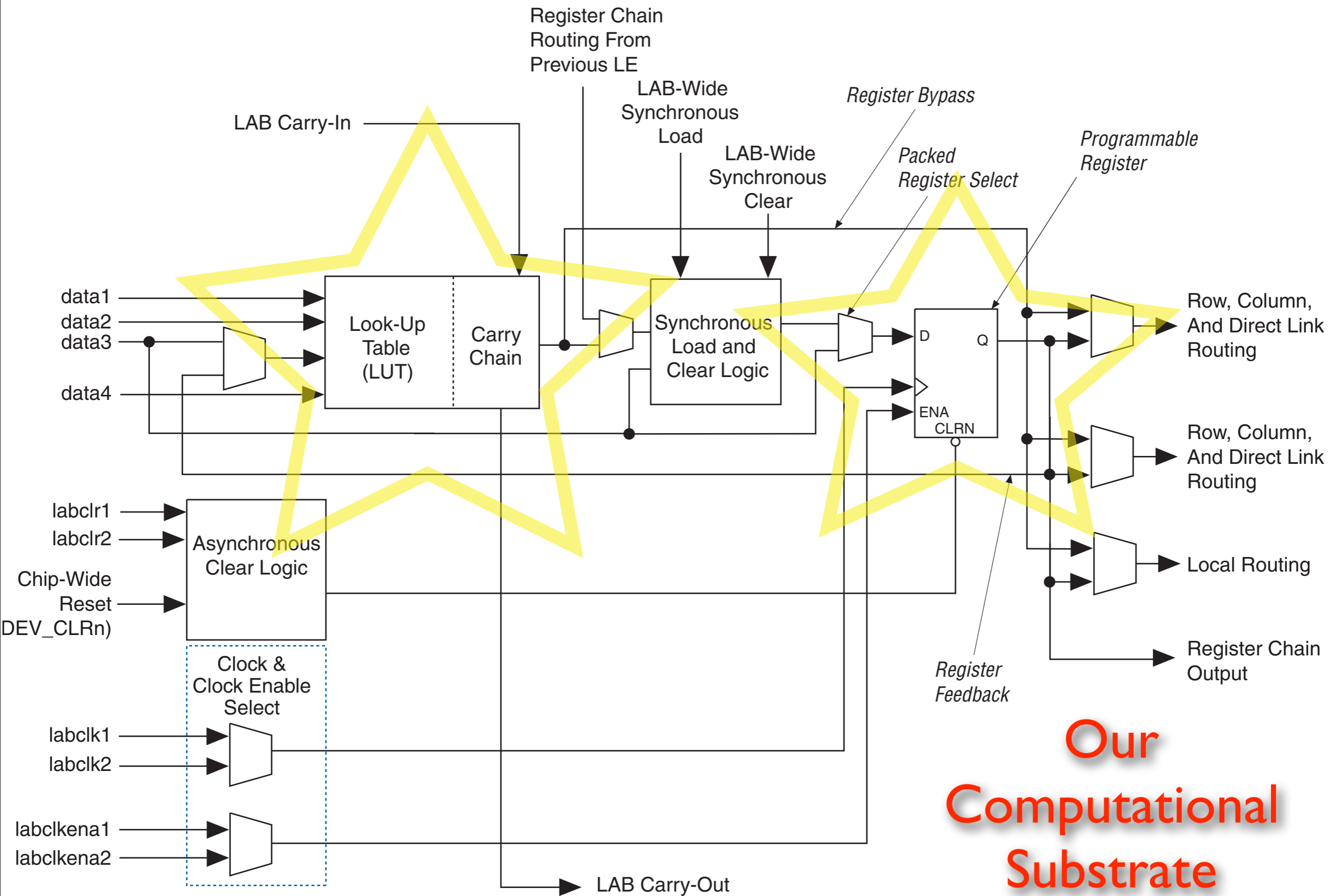

**Our  
Computational  
Substrate**

(from Altera Cyclone II datasheet)

# Muxes

- assign f =  
s[1] ?

```
(s[0] ? a : b) :  
(s[0] ? c : d);
```

```
always @(*)  
case (s)  
2'b00 : g = a;  
2'b01 : g = b;  
2'b10 : g = c;  
default: g = d; // 2'b11  
endcase
```

```
always @(*)  
if (s == 2'b00)  
    h = a;  
else if (s == 2'b01)  
    h = b;  
else if (s == 2'b10)  
    h = c;  
else // s == 2'b11  
    h = d;
```


# Adders/subtractors

- `assign f = a + b;`  
`assign g = a - b;`
- `wire [8:0] s;`  
`wire [7:0] a, b;`  
`assign s = {0,a} + {0,b}; // pick up carry out`
- How big are they? How fast?

# Comparators

- `assign isZero = (a == 0);`
- `assign isGreater = (a > b); // unsigned!!!`  
`assign isLTZ = (a < 0); // is this ever true?`
- can do signed compares if ALL signals involved are declared “signed”.  
`wire signed [7:0] a, b;`
- How big? How fast?

# Check with RTL view

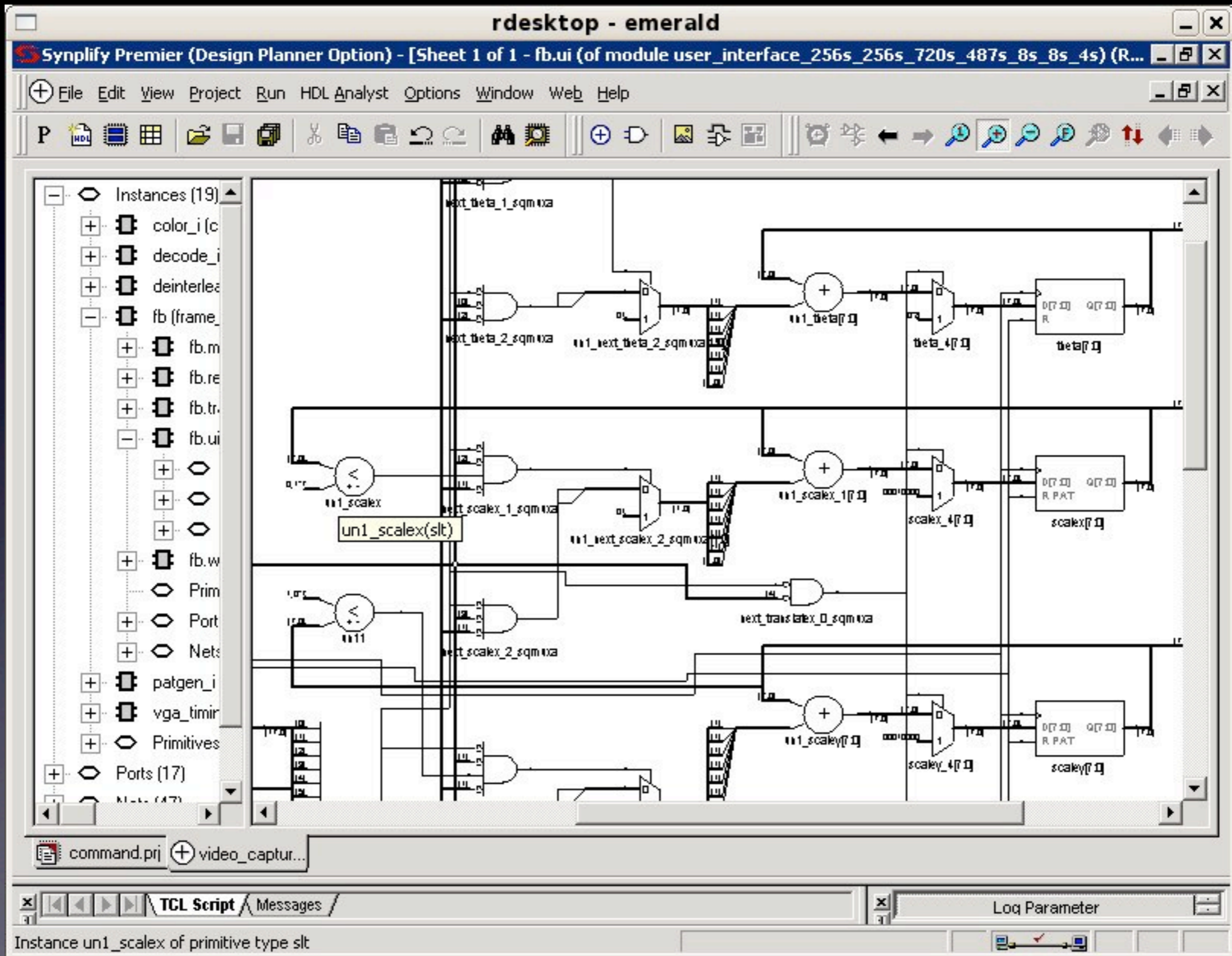



# Verilog tips and traps

# HW Tools: pain in digital form?

- We should teach ideas, not tools!  
But tools help express ideas
- HW tools often kind of suck, but  
don't blame tools for bad craftsmanship,  
do good craftsmanship with bad tools.
- Patience and care will win

= vs. <=

- Simple rule:
  - If you want sequential logic, use always @(posedge clk) with <=.
  - If you want combinational logic, use always @(\*) with =.

# Constants: 32 bits, decimal

- `wire [7:0] foo = 127; // synthesis warning!`
- `wire [7:0] foo = 8'd127;`
- `wire [7:0] foo = 8'b11111111;`
- `wire [7:0] foo = 8'hff;`
- `wire [7:0] foo = 8'hFF;`
- watch out: `1010` looks like `4'b1010!`

# Truncation

```
wire [7:0] a = 8'hAB;  
wire b;           // oops! forgot width  
wire [7:0] c;  
  
assign b = a;    // synthesis warning if lucky.  
  
assign c = a;
```

# reg vs. wire

- wire f;    reg g, h;

```
assign f = a & b;
```

```
always @(posedge clk)  
  g <= a & b;
```

```
always @(*)  
  h = a & b;
```

# Assign in one block

```
input wire a, b;  
output reg f;
```

```
always @(posedge clk)  
    if (a) f <= 1'b0; // race!
```

```
always @(posedge clk)  
    if (b) f <= 1'b1; // race!
```

= vs. <=

- Simple rule:
  - If you want sequential logic, use always @(posedge clk) with <=.
  - If you want combinational logic, use always @(\*) with =.



= vs. <=

- always @(posedge clk)

```
begin
```

```
  f <= a + b;
```

```
  g <= f + c;
```

```
end
```

- always @(posedge clk)

```
begin
```

```
  f = a + b;
```

```
  g = f + c; // a + b + c
```

```
end
```

- always@(posedge clk)

```
begin
```

```
  f2 <= f1;
```

```
  f3 <= f2;
```

```
  f4 = f3;
```

```
  f5 = f4; // f5 = f3 !!
```

```
  f7 = f6;
```

```
  f6 = f5;
```

```
end
```

# More specifically,

```
initial
```

```
    state = 0;
```

```
always @(posedge clk)
```

```
    begin
```

```
        if (state == 0) state = 1;
```

```
        if (state == 1) state = 2;
```

```
        if (state == 2) state = 0;
```

```
    end
```

# Aargh.

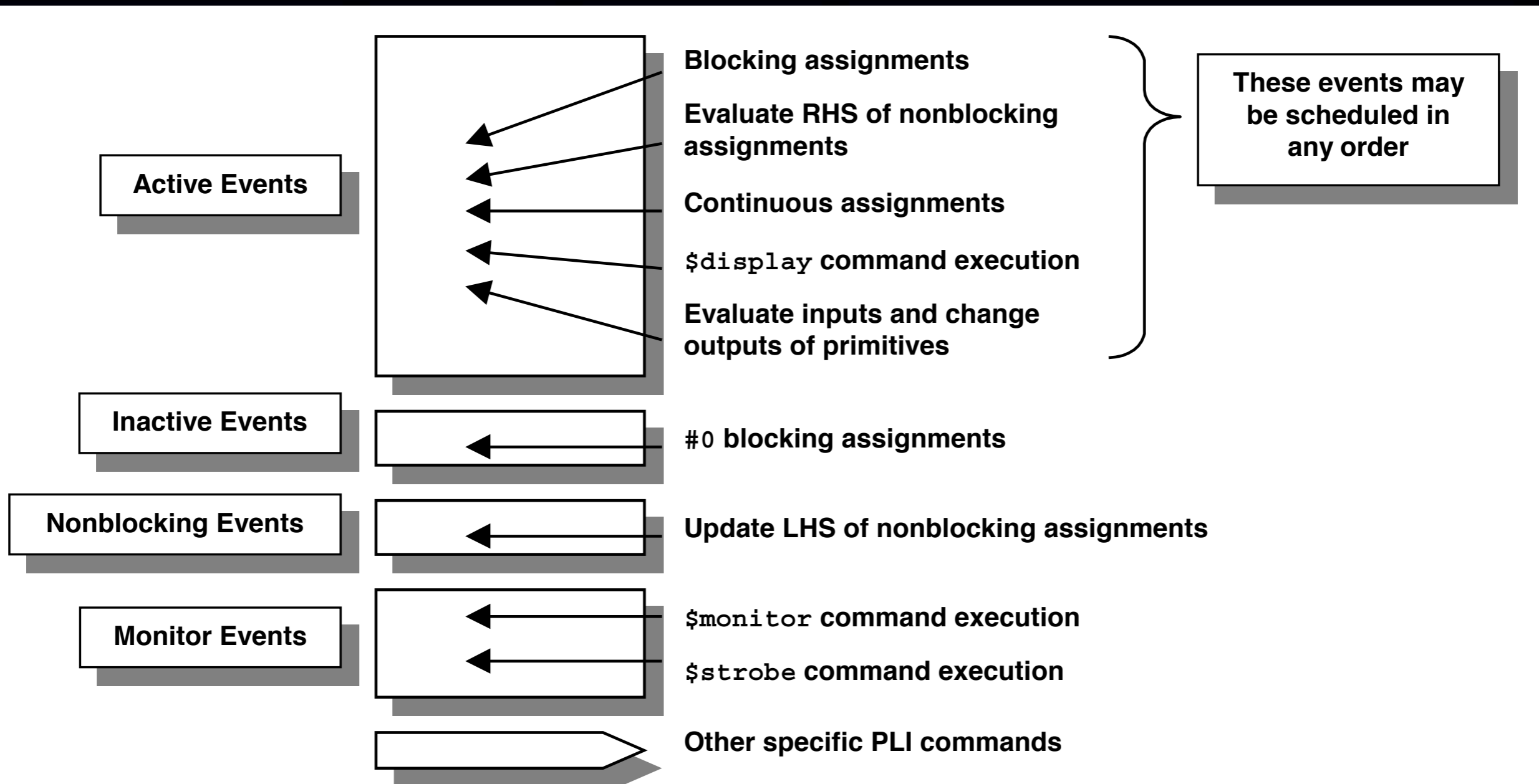


Figure 1 - Verilog "stratified event queue"

from Cliff Cummings' "Nonblocking Assignments in Verilog Synthesis, Coding Styles That Kill!"

# Incomplete sensitivity lists

- always @(a or b) // it's or, not ||  
f = a & b;
- always @(a)  
f = a & b;
- always  
f = a & b;
- Just use always@(\*) for combinational logic

# Enables and Latches

- always @(posedge clk)

```
if (a == 1)
    f <= 1;
else if (a == 2)
    f <= 2;
else if (a == 3)
    f <= 3;
```

- implicitly:  
else  
f <= f;

- always @(\*)

```
if (a == 1)
    f = 1;
else if (a == 2)
    f = 2;
else if (a == 3)
    f = 3;
```

- implicitly:  
else  
f = f;  
this is memory!

= vs. <=

- Simple rule:
  - If you want sequential logic, use always @(posedge clk) with <=.
  - If you want combinational logic, use always @(\*) with =.

# Combinational and Sequential

```
input wire a, b, s;  
output reg f, g, h;
```

```
always @(posedge clk)  
begin
```

```
    f <= (a & ~s) | (b & s);
```

```
    g <= s ? a : b;
```

```
    if (s)
```

```
        h <= a;
```

```
    else
```

```
        h <= b;
```

```
end
```

# Displaying things

- works for most stuff:  
`$display("the answer is %h.", ans);`
- for nonblocking assignments, you may sometimes want:  
`$strobe("the answer is %h.", ans);`  
(see Aargh. for reason)



# X's

- X's are for undefined values:  
wire a;  
\$display(a); // prints an X
- Pins that aren't hooked up will be X's:  
Often, 32'hxxxxxf4 indicates an Active-HDL bus with default width.
- 1'b1 & 1'bX yields 1'bX  
1'b1 + 1'bX yields 1'bX

# Z's

- Z's are for bus sharing. You won't need this.
- $a \leq 1'bZ$ ;  $b \leq 1'bZ$ ;  
 $a \leq 2'b0$ ;  $b \leq 1'b1$ ;  
// a will be 0 and b will be 1
- Z's turn into X's sometimes:  
 $1'b1 \& 1'bZ$  yields  $1'bX$ .  
 $1'b1 + 1'bZ$  yields  $1'bX$ .

# Initial values

- Synthesis sometimes ignores (!?!), so better include a reset line.

- Maybe:  
reg foo = 1'b1;

- Maybe:  
initial begin  
foo = 1'b1;  
end

- module fooReg;  
input wire newFoo;  
output reg foo;

```
initial #0 foo = 1'b0;
```

```
always @(posedge clk)  
if (reset == 1'b1)
```

```
foo <= 1'b0;
```

```
else
```

```
foo <= newFoo;
```

```
endmodule
```

Whew.

Questions?