
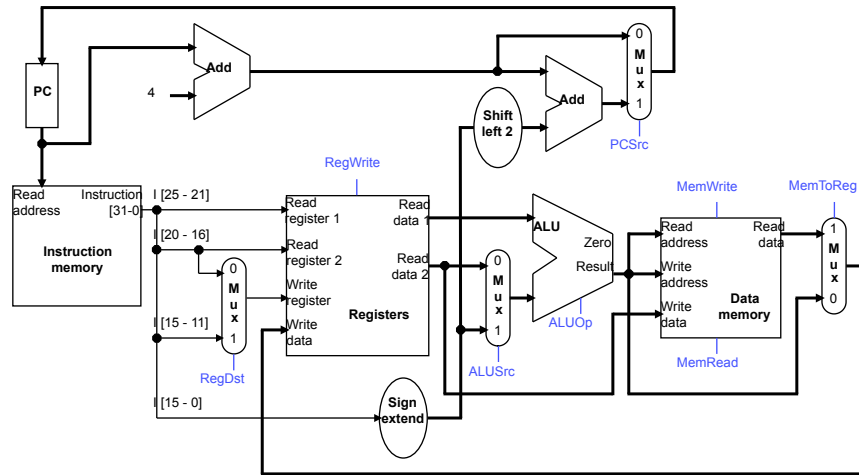


Review: What is it? What does it do?

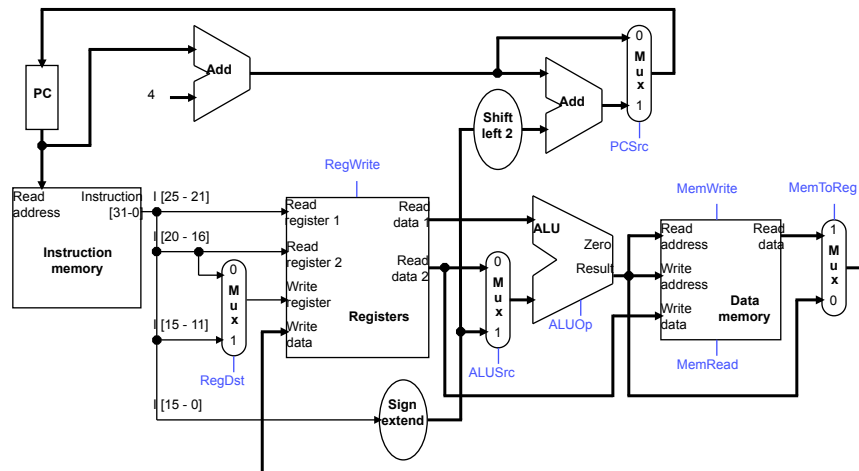

1

slti \$4, \$5, 6



2

Control

The **control unit** is responsible for setting all the control signals so that each instruction is executed properly

- ❖ The control unit's input is the 32-bit instruction word
- ❖ The outputs are values for the blue control signals in the datapath

Most of the signals can be generated from the instruction opcode alone, and not the entire 32-bit word


To illustrate the relevant control signals, we will show the route that is taken through the datapath by R-type, lw, sw and beq instructions

3

R-type instruction path

R-type instructions include **add**, **sub**, **and**, **or**, and **slt**

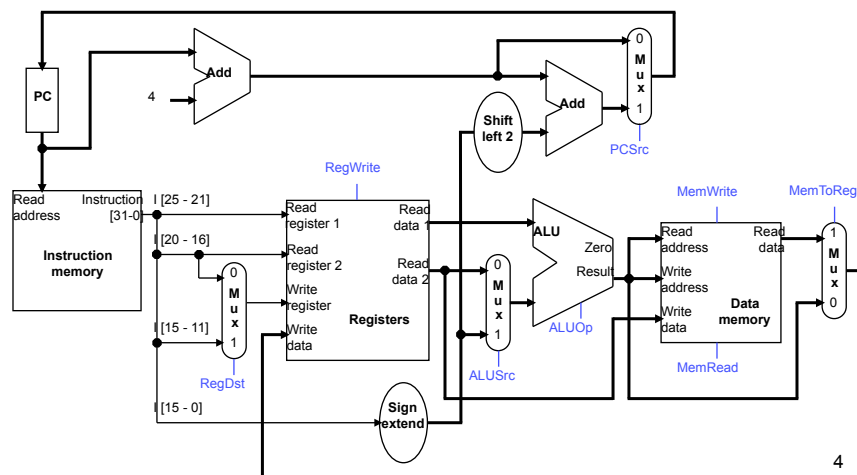
ALUOp is determined by the instruction's "func" field



lw instruction path

An example load instruction is `lw $t0, -4($sp)`

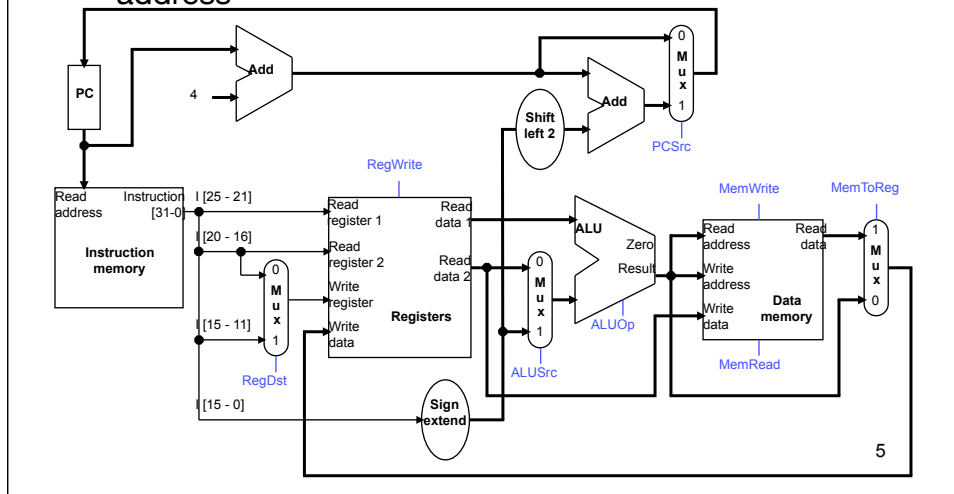
ALUOp must be 010 (add) to compute the effective address



sw instruction path

An example store instruction is `sw $a0, 16($sp)`

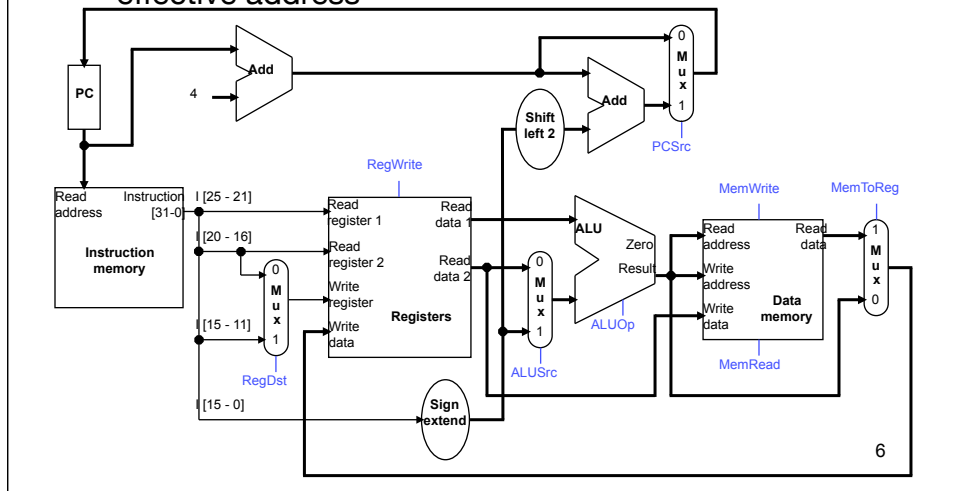
ALUOp must be 010 (add) again to compute the effective address



beq instruction path

A sample branch instruction is `beq $at, $0, offset`.

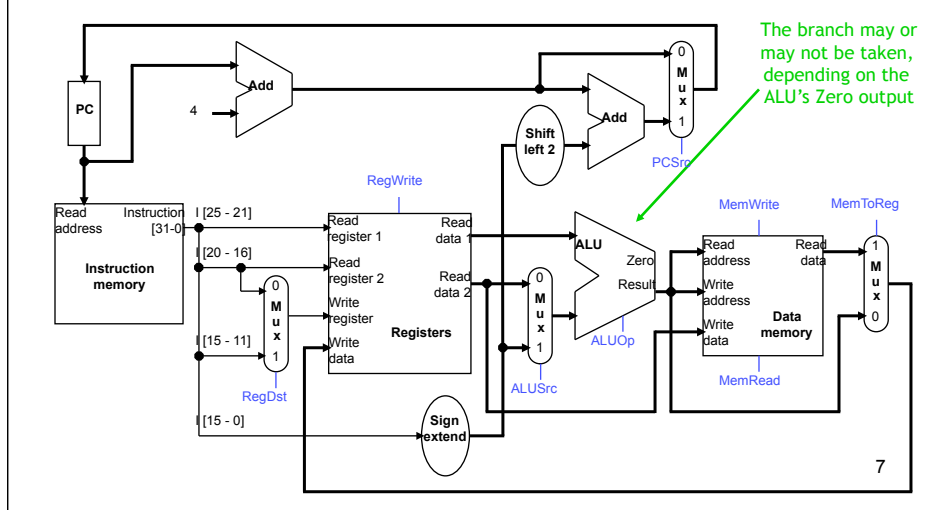The **ALUOp** is 110 (subtract) to test for equality



Control signal table

| Operation | RegDst | RegWrite | ALUSrc | ALUOp | MemWrite | MemRead | MemToReg |
|-----------|--------|----------|--------|-------|----------|---------|----------|
| add | 1 | 1 | 0 | 010 | 0 | 0 | 0 |
| sub | 1 | 1 | 0 | 110 | 0 | 0 | 0 |
| and | 1 | 1 | 0 | 000 | 0 | 0 | 0 |
| or | 1 | 1 | 0 | 001 | 0 | 0 | 0 |
| slt | 1 | 1 | 0 | 111 | 0 | 0 | 0 |
| lw | 0 | 1 | 1 | 010 | 0 | 1 | 1 |
| sw | X | 0 | 1 | 010 | 1 | 0 | X |
| beq | X | 0 | 0 | 110 | 0 | 0 | X |

sw and beq are the only instructions that don't write any registers

lw and sw are the only instructions that use the constant field.

They also depend on the ALU to compute the effective memory address

ALUOp for R-type instructions depends on the instructions' func field

The PCSrc control signal (not listed) should be set if the instruction is beq and the ALU's Zero output is true

Generating control signals


The control unit needs 13 bits of inputs

- ❖ Six bits make up the instruction's opcode
- ❖ Six bits come from the instruction's func field
- ❖ It also needs the Zero output of the ALU

The control unit generates 10 bits of output, corresponding to the signals mentioned earlier

You can build the actual circuit by using big K-maps, big Boolean algebra, or big circuit design programs

 The textbook presents a slightly different control unit



9


Logic Array

| Input or output | Signal name | R-format | Iw | sw | beq |
|-----------------|-------------|----------|----|----|-----|
| Inputs | Op5 | 0 | 1 | 1 | 0 |
| | Op4 | 0 | 0 | 0 | 0 |
| | Op3 | 0 | 0 | 1 | 0 |
| | Op2 | 0 | 0 | 0 | 1 |
| | Op1 | 0 | 1 | 1 | 0 |
| | Op0 | 0 | 1 | 1 | 0 |
| Outputs | RegDst | 1 | 0 | X | X |
| | ALUSrc | 0 | 1 | 1 | 0 |
| | MemtoReg | 0 | 1 | X | X |
| | RegWrite | 1 | 1 | 0 | 0 |
| | MemRead | 0 | 1 | 0 | 0 |
| | MemWrite | 0 | 0 | 1 | 0 |
| | Branch | 0 | 0 | 0 | 1 |
| | ALUOp1 | 1 | 0 | 0 | 0 |
| ALUOp0 | 0 | 0 | 0 | 1 | |

10

A Closer Look At the Operation

 
Consider the instruction `add $t1, $t1, $t2`



- Assume \$t1 and \$t2 initially contain 1 and 2 respectively.
- Executing this instruction involves several steps.
 1. The instruction word is read from the instruction memory, and the program counter is incremented by 4
 2. The sources \$t1 and \$t2 are read from the register file
 3. The values 1 and 2 are added by the ALU
 4. The result (3) is stored back into \$t1 in the register file

11


The `add` moving through the datapath

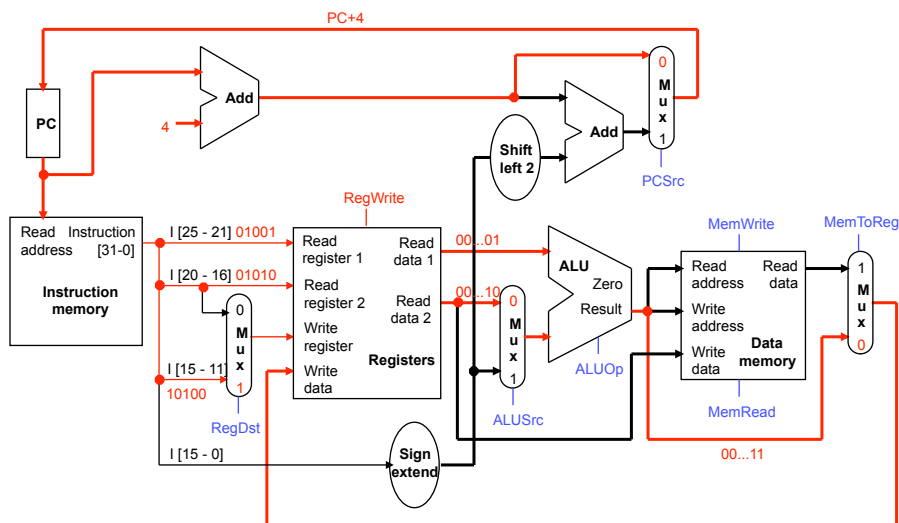

12

State Elements

 - In an instruction like `add $t1, $t1, $t2`, how do we know `$t1` is not updated until *after* its original value is read?



13

The datapath and the clock


- STEP 1:** A new instruction is loaded from memory. The control unit sets the datapath signals appropriately so that
 - ❖ registers are read,
 - ❖ ALU output is generated,
 - ❖ data memory is read and
 - ❖ branch target addresses are computed
- STEP 2:**
 - ❖ The register file is updated for arithmetic or lw instructions
 - ❖ Data memory is written for a sw instruction
 - ❖ The PC is updated to point to the next instruction
- In a **single-cycle datapath** everything in Step 1 must complete within one clock cycle.

14

The lw moves through the datapath

Consider `lw $t0, -4($sp)` execution


100011 | 11101 | 01000 | 1111 1111 1111 1100

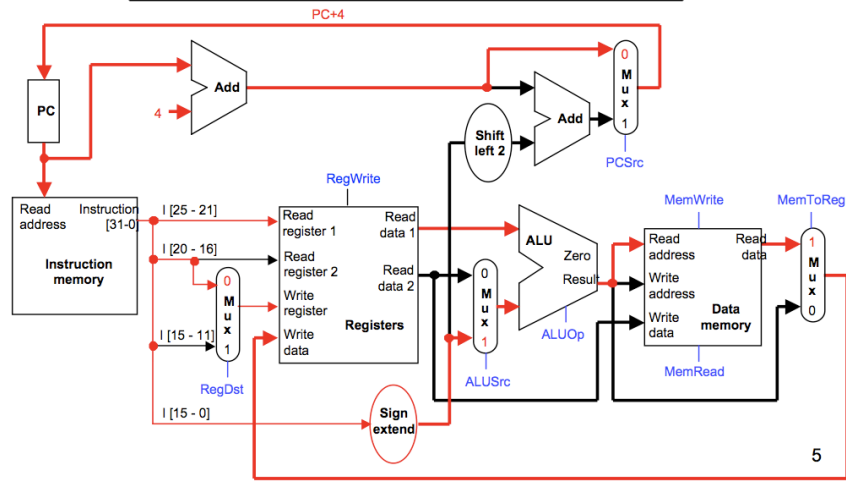

The beq moves through the datapath

Recall `beq $at, $0, offset` compute branch addr: $PC + 4 + (\text{offset} \times 4)$

000100 | 00001 | 00000 | 0000 0000 0000 0011

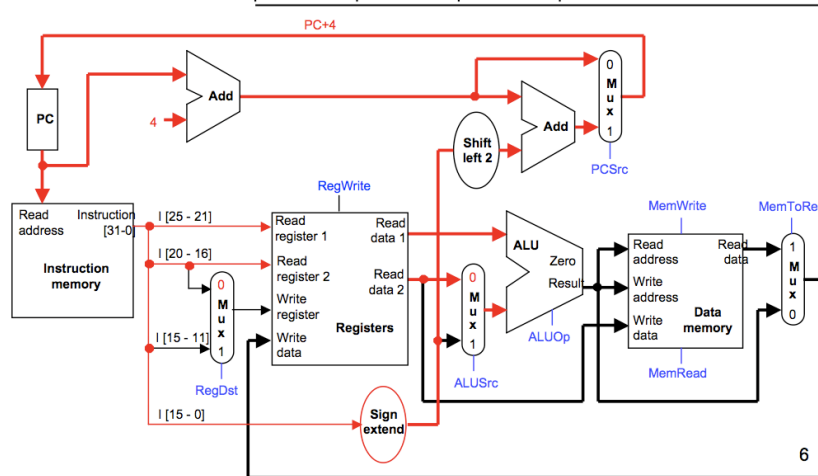

Next Steps


- Designing a computer is only the first step
 - ❖ Next, we must consider how fast it runs,
 - ❖ And how to make it run faster
- We have a “single cycle” design that assumes all operations complete within one clock cycle

17

The slowest instruction...

- If all instructions must complete within 1 clock cycle, then the cycle time \geq *slowest* instruction
- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here

| | | | |
|---------------------------------|-----|---|-----|
| reading the instruction memory | 2ns | } | 8ns |
| reading the base register \$sp | 1ns | | |
| computing memory address \$sp-4 | 2ns | | |
| reading the data memory | 2ns | | |
| storing data back to \$t0 | 1ns | | |

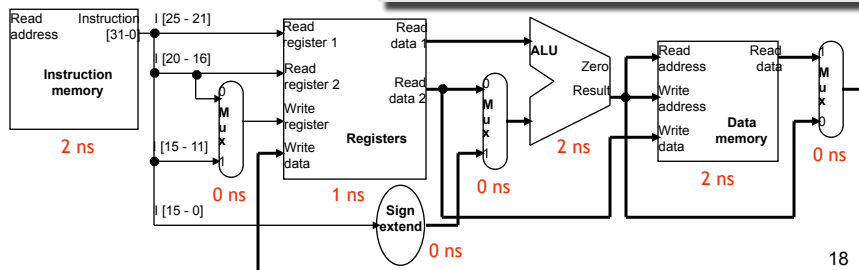

18

