

## Lecture 8

- Announcement:
  - HW1 due today. Hope you had fun!
    - Remember, 2 late days only so we can post solution and talk about it
  - HW2 out. Functions, stack smashing ☹️.
- Today:
  - Assembly and machine language wrap-up
  - Single-cycle implementation
    - Yay, we'll starting seeing how your instructions actually gets carried by electrons working hard.



1

## Assembly Language Wrap-Up

We've introduced MIPS assembly language  
Remember these ten facts about it

- MIPS is representative of all assembly languages - you should be able to learn any other easily
- Assembly language is machine language expressed in symbolic form, using decimal and naming
- R-type instruction  $op\ \$r1, \$r2, \$r3$  is  $\$r1 = \$r2\ op\ \$r3$
- I-type instruction  $op\ \$r1, \$r2, imm$  is  $\$r1 = \$r2\ op\ imm$
- I-type is used for arithmetic, branches, load & store, so the roles of the fields change
- Moving data to/from memory uses  $imm(\$rs)$  for the effective address,  $ea = imm + \$rs$ , to reference  $M[ea]$

2

## Ten Facts Continued

- Branch and Jump destinations *in instructions* refer to words (instructions) not bytes
- Branch offsets are relative to PC+4
- By convention registers are used in a disciplined way; following it is wise!
- "Short form" explanation is on the green card, "Long form" is in appendix B



3

## Instruction Format Review

Register-to-register arithmetic instructions are R-type

op	rs	rt	rd	shamt	func
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Load, store, branch, & immediate instructions are I-type

op	rs	rt	address
6 bits	5 bits	5 bits	16 bits

The jump instruction uses the J-type instruction format

op	address
6 bits	26 bits

4


## Review

- If three instructions have opcodes 1, 7 and 15 are they all of the same type?
- If we were to add an instruction to MIPS of the form  $MOD\ \$t1, \$t2, \$t3$ , which performs  $\$t1 = \$t2\ MOD\ \$t3$ , what would be its opcode?
- How can you tell if the immediate field is positive or negative?
- Could the distance J jumps be increased by using an opcode of fewer bits?

5
 
## A single-cycle MIPS processor

- An instruction set architecture is an *interface* that defines the hardware operations which are available to software.
- Any instruction set can be implemented in many different ways. Over the next few weeks we'll see several possibilities.
  - In a basic *single-cycle implementation* all operations take the same amount of time—a single cycle.
  - A *multicycle implementation* allows faster operations to take less time than slower ones, so overall performance can be increased.
  - Finally, *pipelining* lets a processor overlap the execution of several instructions, potentially leading to big performance gains.



6

### Single-cycle implementation

- We will describe the implementation a simple MIPS-based instruction set supporting just the following operations.
  - Arithmetic: add sub and or slt
  - Data Transfer: lw sw
  - Control: beq
- Today we'll start building a single-cycle implementation of this instruction set.
  - All instructions will execute in the same amount of time; this will determine the clock cycle time for our performance equations.
  - We'll explain the datapath first, and then make the control unit.

7

### Computers are state machines

- A computer is just a big fancy state machine.
  - Registers, memory, hard disks and other storage form the state.
  - The processor keeps reading and updating the state, according to the instructions in some program.

8

### John von Neumann

- In the old days, "programming" involved actually changing a machine's physical configuration by flipping switches or connecting wires.
  - A computer could run just one program at a time.
  - Memory only stored data that was being operated on.
- Then around 1944, John von Neumann and others got the idea to encode instructions in a format that could be stored in memory just like data.
  - The processor interprets and executes instructions from memory.
  - One machine could perform many different tasks, just by loading different programs into memory.
  - The "stored program" design is often called a Von Neumann machine.

9

### Memories

- It's easier to use a Harvard architecture at first, with programs and data stored in separate memories.
  - To fetch instructions and read & write words, we need these memories to be 32-bits wide (buses are represented by dark lines here). We still want byte addressability, so these are  $2^{30} \times 32$  memories.
- Blue lines represent control signals. MemRead and MemWrite should be set to 1 if the data memory is to be read or written respectively, and 0 otherwise.
  - When a control signal does something when it is set to 1, we call it active high (vs. active low) because 1 is usually a higher voltage than 0.
- For now, we will assume you cannot write to the instruction memory.
  - Pretend it's already loaded with a program, which doesn't change while it's running.

10

### Instruction fetching

- The CPU is always in an infinite loop, fetching instructions from memory and executing them.
- The program counter or PC register holds the address of the current instruction.
- MIPS instructions are each four bytes long, so the PC should be incremented by four to read the next instruction in sequence.

11

### Encoding R-type instructions

- Last lecture, we saw encodings of MIPS instructions as 32-bit values.
- Register-to-register arithmetic instructions use the R-type format.
  - op is the instruction opcode, and func specifies a particular arithmetic operation (see textbook).
  - rs, rt and rd are source and destination registers.

op	rs	rt	rd	shamt	func
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

- An example instruction and its encoding:
 

```

add $s4, $t1, $t2
      
```

000000	01001	01010	10100	00000	1000000
	rs	rt	rd		

12

## Registers and ALUs


- R-type instructions must access registers and an ALU.
- Our **register file** stores thirty-two 32-bit values.
  - Each register specifier is 5 bits long.
  - You can read from two registers at a time.
  - RegWrite** is 1 if a register should be written.
- Here's a simple ALU with five operations, selected by a 3-bit control signal **ALUOp**.

ALUOp	Function
000	and
001	or
010	add
110	subtract
111	sll

13
 
## Executing an R-type instruction


- Read an instruction from the instruction memory.
- The **source registers**, specified by instruction fields **rs** and **rt**, should be read from the register file.
- The ALU performs the desired operation.
- Its result is stored in the destination register, which is specified by field **rd** of the instruction word.




14
 
## Encoding I-type instructions

- The **lw**, **sw** and **beq** instructions all use the **I-type** encoding.
  - rt** is the **destination** for **lw**, but a **source** for **beq** and **sw**.
  - address** is a 16-bit signed constant.




- Two example instructions:

 

15
 
## Accessing data memory


- For an instruction like **lw \$t0, -4(\$sp)**, the base register **\$sp** is added to the **sign-extended** constant to get a data memory address.
- This means the ALU must accept **either** a register operand for arithmetic instructions, **or** a sign-extended immediate operand for **lw** and **sw**.
- We'll add a multiplexer, controlled by **ALUSrc**, to select either a register operand (0) or a constant operand (1).



16
 
## MemToReg


- The register file's "Write data" input has a similar problem. It must be able to store **either** the ALU output of R-type instructions, **or** the data memory output for **lw**.
- We add a mux, controlled by **MemToReg**, to select between saving the ALU result (0) or the data memory output (1) to the registers.




17
 
## RegDst

- A final annoyance is the destination register of **lw** is in **rt** instead of **rd**.



 - We'll add one more mux, controlled by **RegDst**, to select the destination register from either instruction field **rt** (0) or field **rd** (1).



18


## Branches

- For branch instructions, the constant is not an address but an *instruction offset* from the current program counter to the desired address.

```

beq $at, $0, L
add $v1, $v0, $0 1
add $v1, $v1, $v1 2
j   Somewhere 3 2
L:  add $v1, $v0, $v0
  
```

 - The target address L is three *instructions* past the *beq*, so the encoding of the branch instruction has 0000 0000 0000 0011 for the address field.



- Instructions are four bytes long, so the actual memory offset is 12 bytes.

19


## The steps in executing a beq

- Fetch the instruction, like `beq $at, $0, offset`, from memory.
- Read the source registers, `$at` and `$0`, from the register file.
- Compare the values by subtracting them in the ALU.
- If the subtraction result is 0, the source operands were equal and the PC should be loaded with the target address,  $PC + 4 + (offset \times 4)$ .
- Otherwise the branch should not be taken, and the PC should just be incremented to  $PC + 4$  to fetch the next instruction sequentially.




20

## Branching hardware

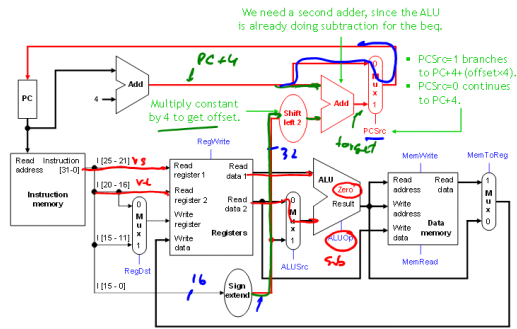

21

## The final datapath

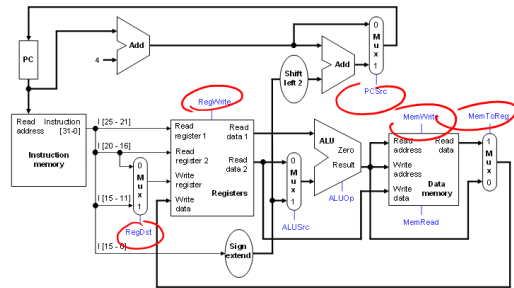

22


## Control

- The **control unit** is responsible for setting all the control signals so that each instruction is executed properly.
  - The control unit's input is the 32-bit instruction word.
  - The outputs are values for the blue control signals in the datapath.
- Most of the signals can be generated from the instruction opcode alone, and not the entire 32-bit word.
- To illustrate the relevant control signals, we will show the route that is taken through the datapath by R-type, lw, sw and beq instructions.

23
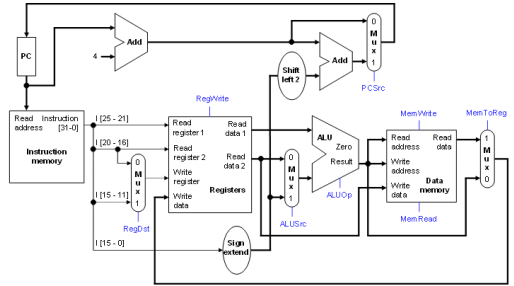
## R-type instruction path


- The R-type instructions include `add`, `sub`, `and`, `or`, and `slt`.
- The ALUOp is determined by the instruction's "func" field.



24
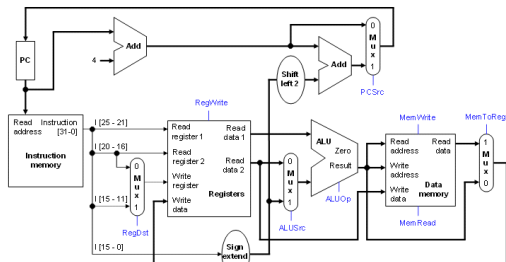
### lw instruction path


- An example load instruction is `lw $t0, -4($sp)`.
- The ALUOp must be 010 (add), to compute the effective address.



25
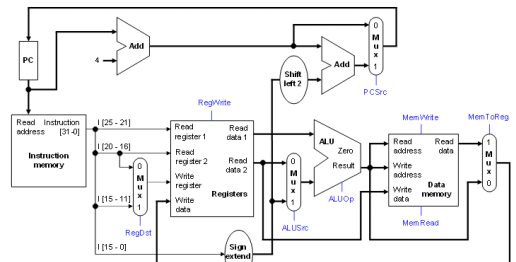
### sw instruction path


- An example store instruction is `sw $a0, 16($sp)`.
- The ALUOp must be 010 (add), again to compute the effective address.



26
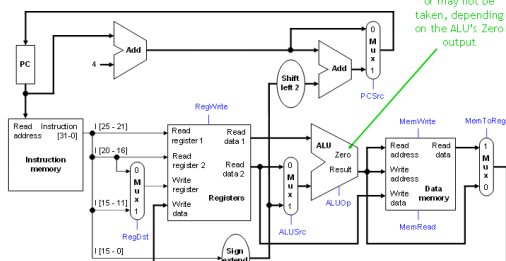
### beq instruction path

- One sample branch instruction is `beq $at, $0, offset`.
- The ALUOp is 110 (subtract), to test for equality.



27

### Control signal table


Operation	RegDst	RegWrite	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg
add	1	1	0	010	0	0	0
sub	1	1	0	110	0	0	0
and	1	1	0	000	0	0	0
or	1	1	0	001	0	0	0
slt	1	1	0	111	0	0	0
lw	0	1	1	010	0	1	1
sw	X	0	1	010	1	0	X
beq	X	0	0	110	0	0	X

- `sw` and `beq` are the only instructions that do not write any registers.
- `lw` and `sw` are the only instructions that use the constant field. They also depend on the ALU to compute the effective memory address.
- ALUOp for R-type instructions depends on the instructions' func field.
- The PCSrc control signal (not listed) should be set if the instruction is `beq` and the ALU's Zero output is true.

28
 
### Generating control signals

- The control unit needs 13 bits of inputs.
  - Six bits make up the instruction's opcode.
  - Six bits come from the instruction's func field.
  - It also needs the Zero output of the ALU.
- The control unit generates 10 bits of output, corresponding to the signals mentioned on the previous page.
- You can build the actual circuit by using big K-maps, big Boolean algebra, or big circuit design programs.
- The textbook presents a slightly different control unit.



29

### Summary

- A **datapath** contains all the functional units and connections necessary to implement an instruction set architecture.
  - For our **single-cycle implementation**, we use two separate memories, an ALU, some extra adders, and lots of multiplexers.
  - MIPS is a 32-bit machine, so most of the buses are 32-bit wide.
- The **control unit** tells the datapath what to do, based on the instruction that's currently being executed.
  - Our processor has **ten control signals** that regulate the datapath.
  - The control signals can be generated by a combinational circuit with the instruction's 32-bit binary encoding as input.
- Next, we'll see the performance limitations of this single-cycle machine and try to improve upon it.



30