

378 Survival Guide

Lab tips, Verilog tricks, and other useful info

Aaron Miller

Winter 2010

Some content graciously borrowed from Jacob Nelson



Agenda

- ❖ Lab/Section Info
- ❖ Lab Overview
- ❖ Why care?
- ❖ Verilog Tips and Pitfalls
- ❖ Verilog \leftrightarrow Hardware Examples




Lab / Section

- ❖ When announced, we'll have section for the 1st hour of your scheduled lab section.
- ❖ Otherwise, lab section == office hours
 - ❖ TA(s) & SLAs will be available in 003
 - ❖ Attendance != required
 - ❖ Use time wisely to get help w/ difficult issues
- ❖ So, make sure you're on the class e-mail list and check that account!



Lab

- ❖ Goal: Build pipelined MIPS processor capable of running complied C code
 - ❖ Four Tasks
 1. Build single-cycle datapath + create jump & branch logic
 2. Build control logic for single-cycle CPU
 3. Add pipeline registers
 4. Complete pipeline with forwarding & hazard detection
 - ❖ 2 weeks to complete each part
 - ❖ Highly suggest you work in pairs
- 

First Task

- ❖ Mostly following instructions and connecting components in block diagram
- ❖ Writing some Verilog for jump & branch logic
- ❖ Test benches are provided, but they're not 100% robust
- ❖ Demonstration: write short assembly program to blink lights on board



The Hardware




The Hardware – Details

- ❖ FPGA: Altera Cyclone II EP2C20F484C7N
 - ❖ 18,752 4-input lookup tables
 - ❖ 18,752 1-bit registers (aka flip-flops)
 - ❖ 240 KB of memory (enough to store several frames of an ASCII-encoded rickroll)




Useful Tools

 - ❖ Aldec's Active-HDL lets us simulate Verilog and block diagrams (BDEs)
 - ❖ Its assembler turns your code into bits and provides useful console output and waveforms for debugging
- ❖ Altera's Quartus software does 3 things:
 - i. Translates Verilog to hardware primitives
 - ii. Arranges hardware primitives on the chip
 - iii. Programs design to chip



Why Lab Matters

- ❖ In 370 you designed a bunch of special-purpose circuits to fulfill one specific role.
 - ❖ In 378 you'll design the best-known and one of the most-useful general-purpose circuits: the processor!
 - ❖ Important to understand hardware that your high-level code runs on and abstractions between them
 - ❖ Companies think so too!
 - ❖ If nothing else, you're required to take this class to get a degree in CS/CE
- 

Short Verilog Quiz

- ❖ What are the two types of logic?
 - ❖ Combinational & sequential
- ❖ Inside an always block, which assignment operator should you use for combinational logic (= or <=)? Sequential?
 - ❖ Combinational: = Sequential: <=
- ❖ What's the syntax for declaring an 8-bit-wide bus named fooBar?
 - ❖ `wire [7:0] fooBar;`



Hardware Primitives – Logic

```
module foo(a, b, f, g);  
    input wire a, b;  
    output wire f;  
    output reg g;  
  
    assign f = a & b;  
    always @ (*) begin  
        g = a & b;  
    end  
endmodule
```

Questions:

Are f and g the same?

What does "always @ (*)" mean?



Hardware Primitives – Register

```
module foo(clk, a, bar);  
    input wire a, clk;  
    wire nextBar;  
    output reg bar;  
  
    always @ (posedge clk) begin  
        bar <= nextBar ^ a;  
    end  
endmodule
```

Questions:

What does this represent in hardware?

Why did we use "always @ (posedge clk)"?



Hardware Primitives – Muxes

```
assign f = s[1] ? (s[0] ? a : b) : (s[0] ? c : d);
```

```
always @ (*) begin
    case (s)
        2'b00: f = d;
        2'b01: f = c;
        2'b10: f = b;
        2'b'11: f = a;
    endcase
end
```

```
always @ (*) begin
    if (s == 2'b00)
        f = d;
    else if (s == 2'b01)
        f = c;
    else if (s == 2'b10)
        f = b;
    else //s == 2'b11
        f = a;
end
```



HW Primitives – Adders / Subtractors

```
assign f = a + b;  
assign g = a - b;
```

```
wire [8:0] sum;  
wire [7:0] a, b;  
assign sum = {0, a} + {0, b};    // picks-up carry-out
```

```
wire [7:0] foo, bar  
wire [7:0] a;  
wire [3:0] b;  
assign foo = a + {4'b0, b};    // what's different between  
assign bar = a + {b, 4'b0};    // foo and bar?
```



HW Primitives – Comparators

```
assign isZero = (a == 0);
```

```
assign isGreater = (a > b);           // is this signed?  
assign isLTZ = (a < 0);              // is this ever true?
```

To do signed comparison ALL signals used in the comparison must be additionally declared as "signed"

Ex: input wire signed [7:0] foo;

What other way do we know of for checking sign?



Verilog Tips – Constants

- ❖ `wire [7:0] foo = 127; // synthesis warning! Why?`
 - ❖ Missing number type (decimal, binary, hex)
 - ❖ Active will assume its decimal if not specified!
- ❖ What other ways can we specify this?
 - ❖ `wire [7:0] foo = 8'd127;`
 - ❖ `wire [7:0] foo = 8'b1111_1111;`
 - ❖ `wire [7:0] foo = 8'hff;`
 - ❖ `wire [7:0] foo = 8'hFF;`



Verilog Tips – Truncation

```
wire [7:0] a = 8'hAB;  
wire b;  
wire [7:0] c;
```

```
assign b = a;
```

```
assign c = a;
```

Questions:

What's wrong?

Will you get a synthesis warning?



Verilog Tips – reg vs. wire

```
wire f;  
reg g, h;
```

```
assign f = a & b;
```

```
always @ (posedge clk)  
    g <= a & b;
```

```
always @ (*)  
    h = a & b;
```

Questions:

When do you declare something as a reg?

Are f and g the same? What about f and h?



Verilog Traps – Multiple always blocks

```
input wire a, b;  
output reg f;
```

```
always @ (posedge clk)  
    if (a) f <= 1'b0;
```

```
always @ (posedge clk)  
    if (b) f <= 1'b1;
```

Questions:

What happens when $a = 1$ and $b = 1$?

How can we fix this?




= vs. <=

- ❖ One simple rule:
 - ❖ If you want sequential logic, use always @ (posedge clk) with <=
 - ❖ If you want combinational logic, use always @ (*) with =



Incomplete Sensitivity Lists

- ❖ What is a sensitivity list?
 - ❖ Examples of problematic lists:
 - ❖ always @ (a || b)
 - ❖ always @ (a)
 $f = a \& b$
 - ❖ always
 $f = a \& b;$
 - ❖ Tip: Use always @ (*) for combinational logic!
- 

Latches!

```
always @ (posedge clk) begin
  if (a == 1)
    f <= 1;
  else if (a == 2)
    f <= 2;
  else if (a == 3)
    f <= 3;
end
```

Implicitly this adds:

```
else
  f <= f;
```

But we're okay...

```
always @ (*) begin
  if (a == 1)
    f = 1;
  else if (a == 2)
    f = 2;
  else if (a == 3)
    f = 3;
end
```

Implicitly this adds:

```
else
  f = f;
```

This is memory, but in
a non-sequential
circuit!



Displaying Stuff

- ❖ `$display()` is equivalent to C's `printf()`
 - ❖ Same format strings
 - ❖ `%d` for a decimal
 - ❖ `%h` for hex
 - ❖ Ex: `$display("%d in hex is: %h", foo, foo);`
- ❖ For something which is assigned to with the non-blocking assignment operator (`<=`) you may want to use `$strobe()`




X's

- ❖ X's are for undefined values
- ❖ Pins that are not connected will be X's. Often, `32'hxxxxxxf4` indicates that you forgot to specify the bus's full width (Active-HDL defaults to 8-bit-wide buse)
- ❖ $1'b1 \ \& \ 1'bX \implies 1'bX$
- ❖ $1'b1 \ + \ 1'bX \implies 1'bX$



Z's

- ❖ More than the things you won't be catching as much of at night, Z's are primarily for bus sharing.
 - ❖ You don't need them in 378
 - ❖ $a \leq 1'bZ$; $b \leq 1'bZ$
 - ❖ $a \leq 2'b0$; $b \leq 1'b1$;
 - ❖ a will be 00 and b will be 1 in this case
 - ❖ Sometimes Z's turn into X's !
 - ❖ $1'b1 \& 1'bZ \implies 1'bX$
 - ❖ $1'b1 + 1'bZ \implies 1'bX$
- 

Initial Values

- ❖ Synthesis doesn't always properly initialize wires/buses
- ❖ You can use an initial block but it's better design to have a reset input and reset logic to properly initialize things
- ❖ Initial block example:

```
Initial begin  
    foo = 1'b1;  
end
```



Other

- ❖ We use Verilog 2001, your green sheet is in System Verilog. There are some syntactic differences:
 - ❖ Sign extension: `foo = {16{bar[15]}, bar}; // S Verilog`
`foo = {{16{bar[15]}}, bar}; // our Verilog`
- ❖ Active-HDL uses a default bus width of 8 bits! Most of the buses in the lab need to be 32 bits wide!
 - ❖ Specify in the bus's declaration. Ex: `wire [31:0] short;`
- ❖ Give all of your buses names! This will alleviate many problems & makes debugging easier!

Verilog <--> HW



Thanks for your attention!

For today: Make sure you can get into 003 and log-in.

Questions?

