

Levels in Processor Design


- Circuit design
 - Keywords: transistors, wires etc. Results in gates, flip-flops etc.
- Logical design
 - Putting gates (AND, NAND, ...) and flip-flops together to build basic blocks such as registers, ALU's etc (cf. CSE 370)
- **Register transfer**
 - Describes execution of instructions by showing data flow between the basic blocks
- **Processor description** (the ISA)
- *System description*
 - Includes memory hierarchy, I/O, multiprocessing etc


Register transfer level

- Two types of components (cf. CSE 370)
 - *Combinational* : the output is a function of the input (e.g., adder)
 - *Sequential*: state is remembered (e.g., register)

Synchronous design

 
- Use of a **periodic clock**
 - *edge-triggered* clocking determines when signals can be read and when the output of circuits is stable
 - Values in storage elements can be updated only at clock edges
 - Clock tells when events can occur, e.g., when signals sent by control unit are obeyed in the ALU



 

Logic may need several cycles to propagate values

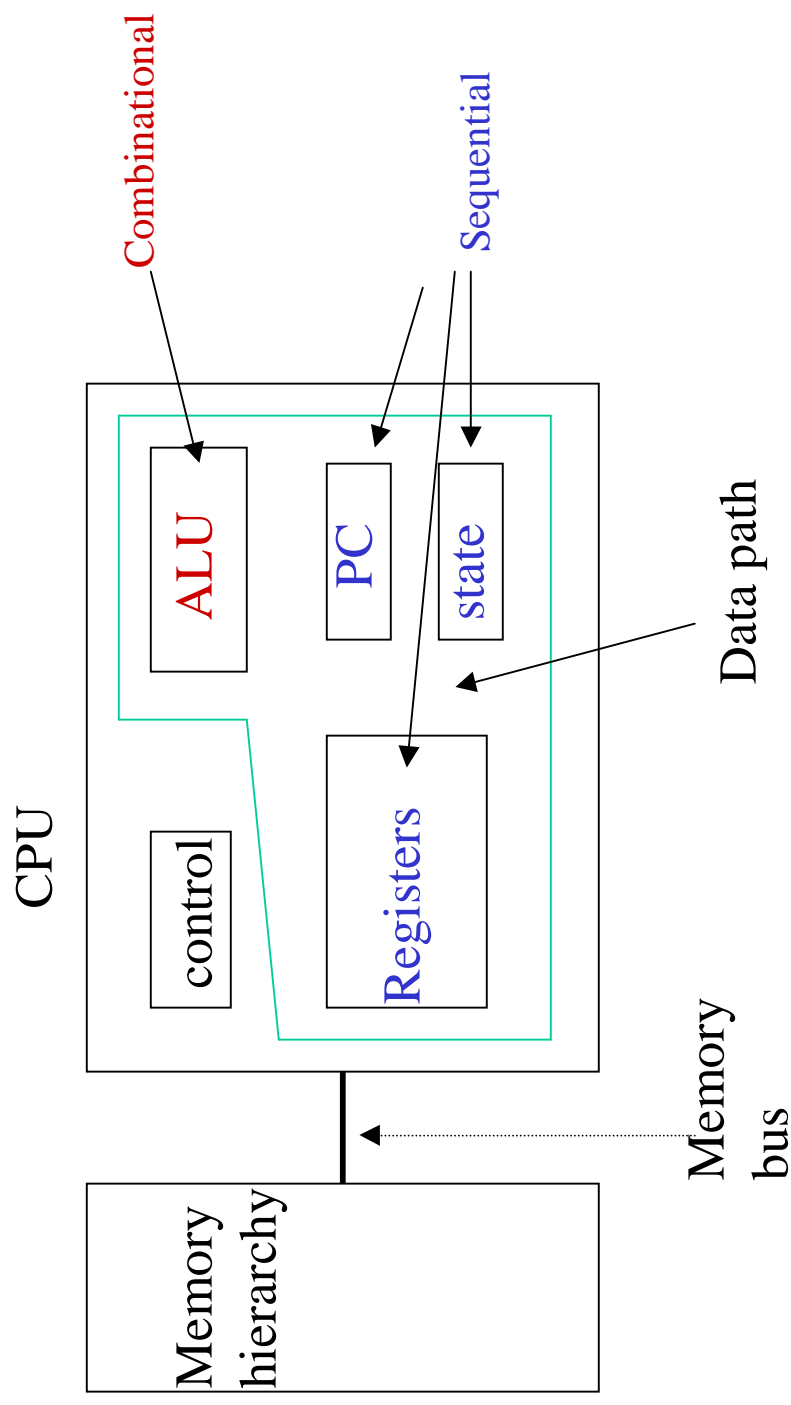Processor design: data path and control unit




Processor design

- Data path
 - How does data flows between various basic blocks
 - What operations can be performed when data flows
 - What can be done in one clock cycle
- Control unit
 - Sends signals to data path elements
 - Tells what data to move, where to move it, what operations are to be performed
- Memory hierarchy
 - Holds program and data


Data path basic building blocks. Storage elements

 - Basic building block (at the RT level) is a register
- In our mini-MIPS implementation registers will be 32-bits
- A register can be read or written




Register file

 - Array of registers (32 for the integer registers in MIPS)
- ISA tells us that we should be able to:
 - read 2 registers, write one register in a given instruction (at this point we want one instruction per cycle)
 - Register file needs to know which registers to read/write




Memory

 - Conceptually, like register file but much larger
- Can only read one location or write to one location per cycle




Combinational elements

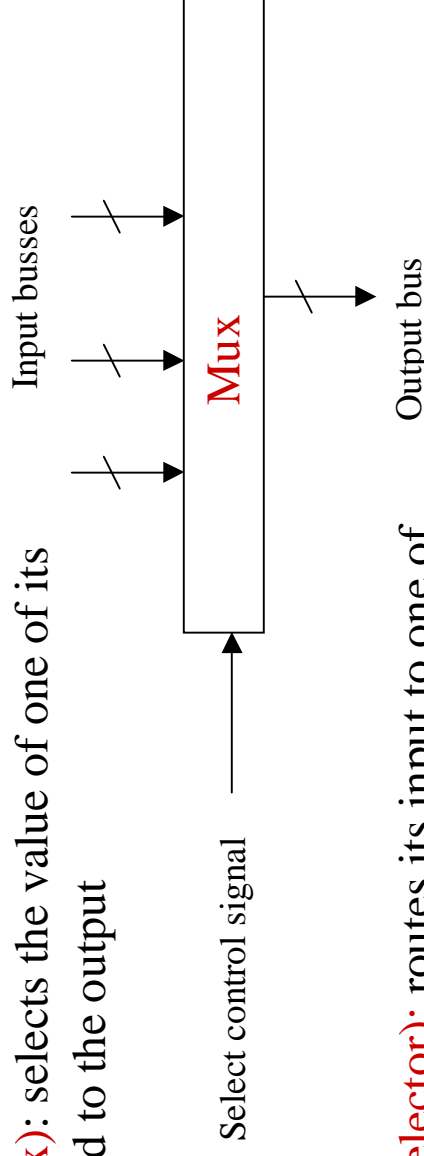Multiplexor (Mux): selects the value of one of its inputs to be routed to the output




 Demultiplexor (selector): routes its input to one of its outputs




Arithmetic and Logic Unit (ALU - combinational)

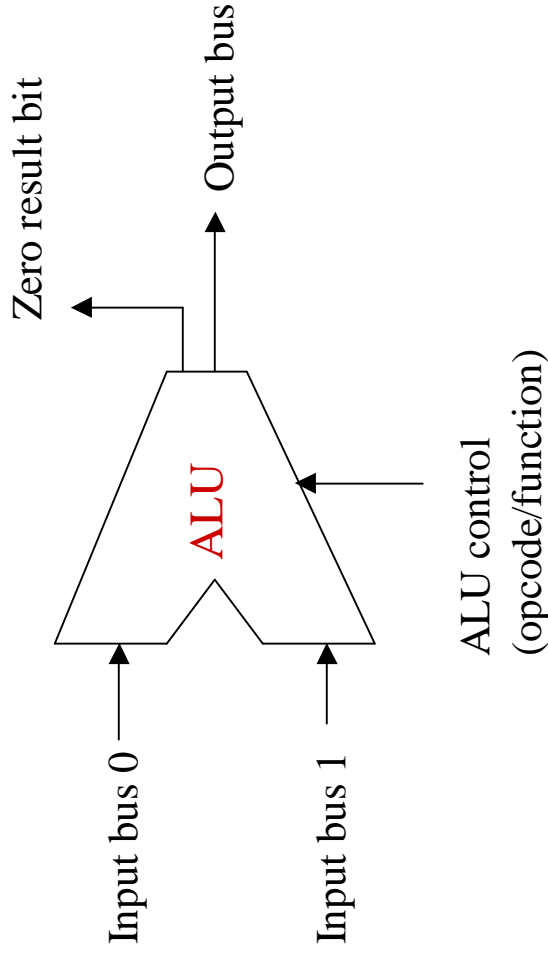
- Computes (arithmetic or logical operation) output from its two inputs



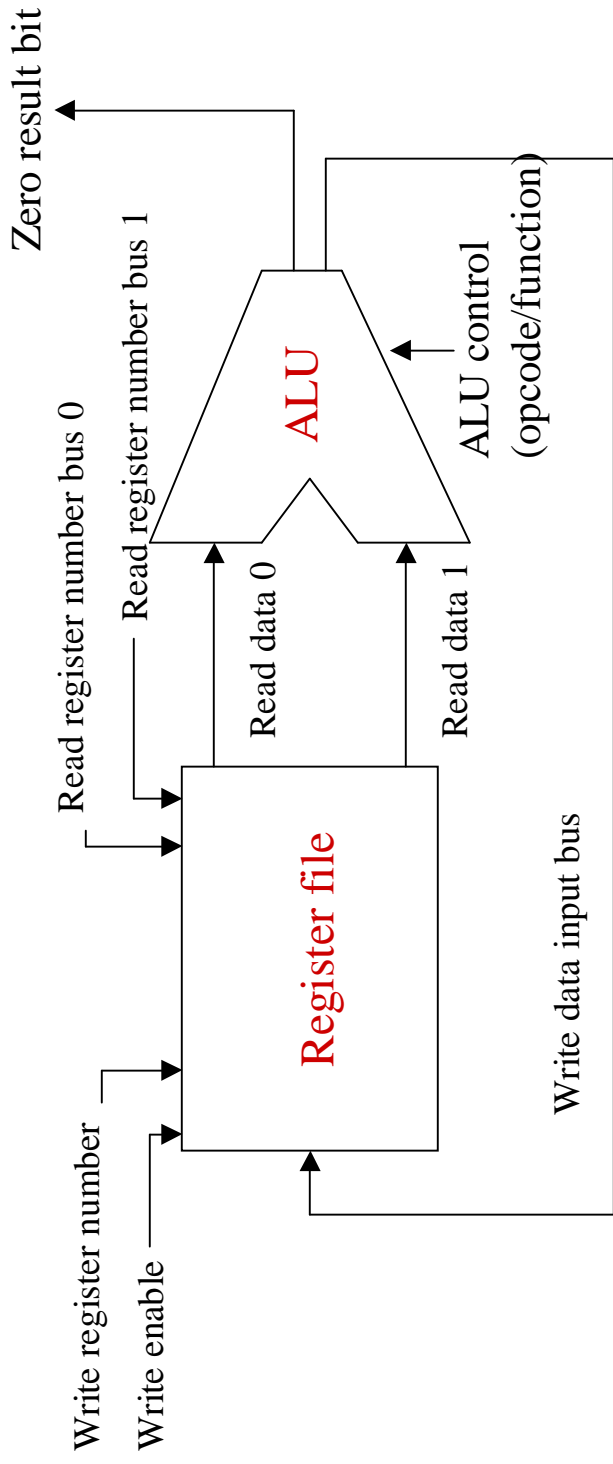
Putting basic blocks together (skeleton of data path for arith/logical operations)




Introducing instruction fetch

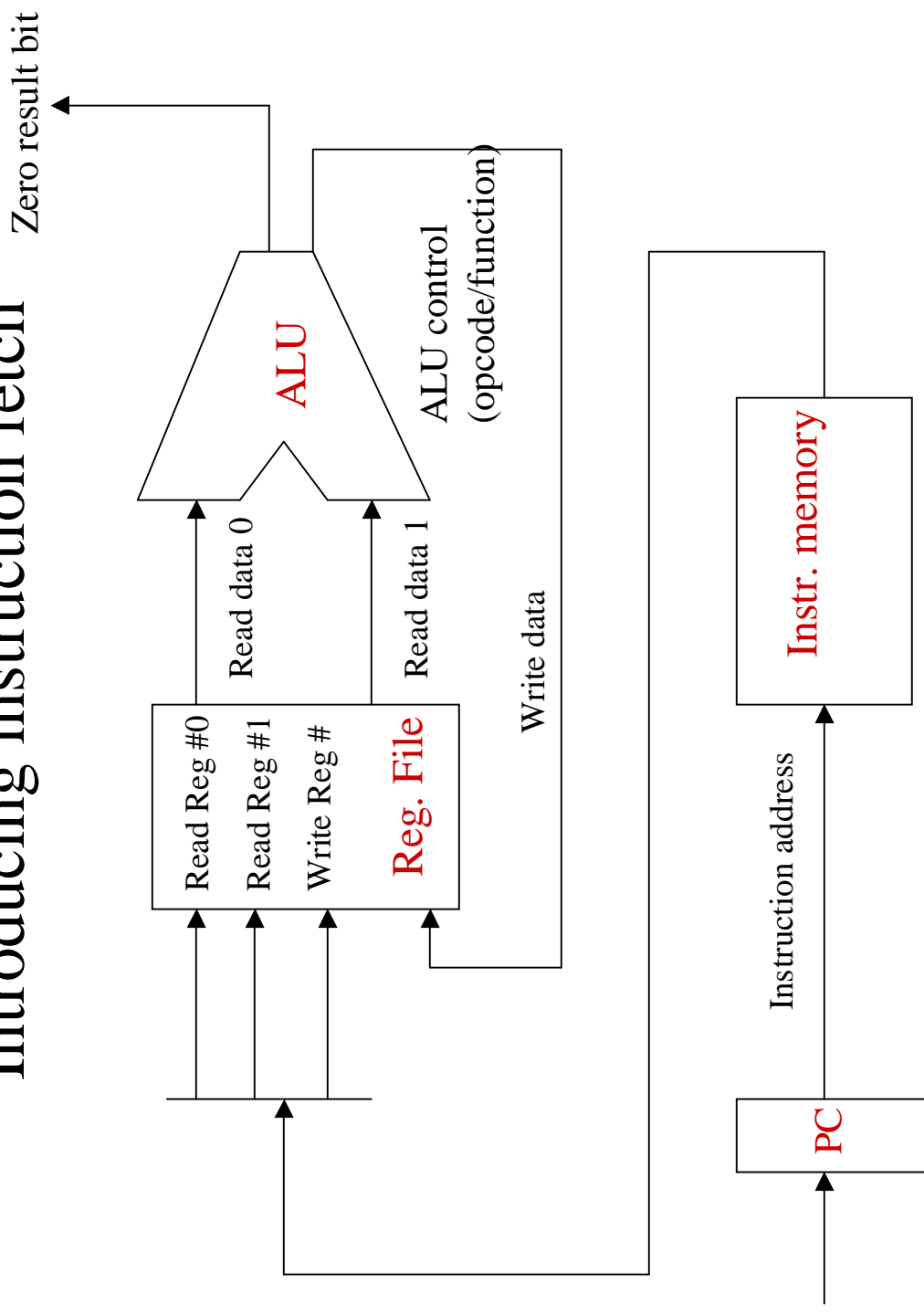

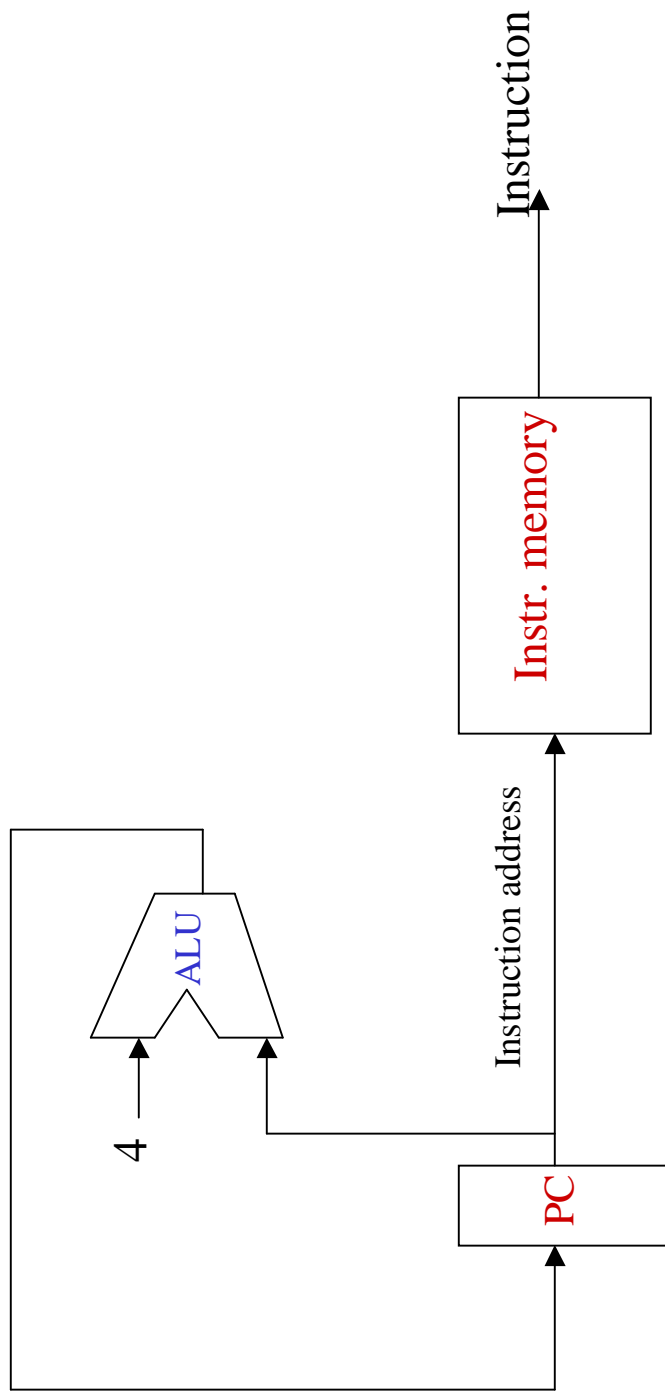PC has to be incremented (assume no branch)



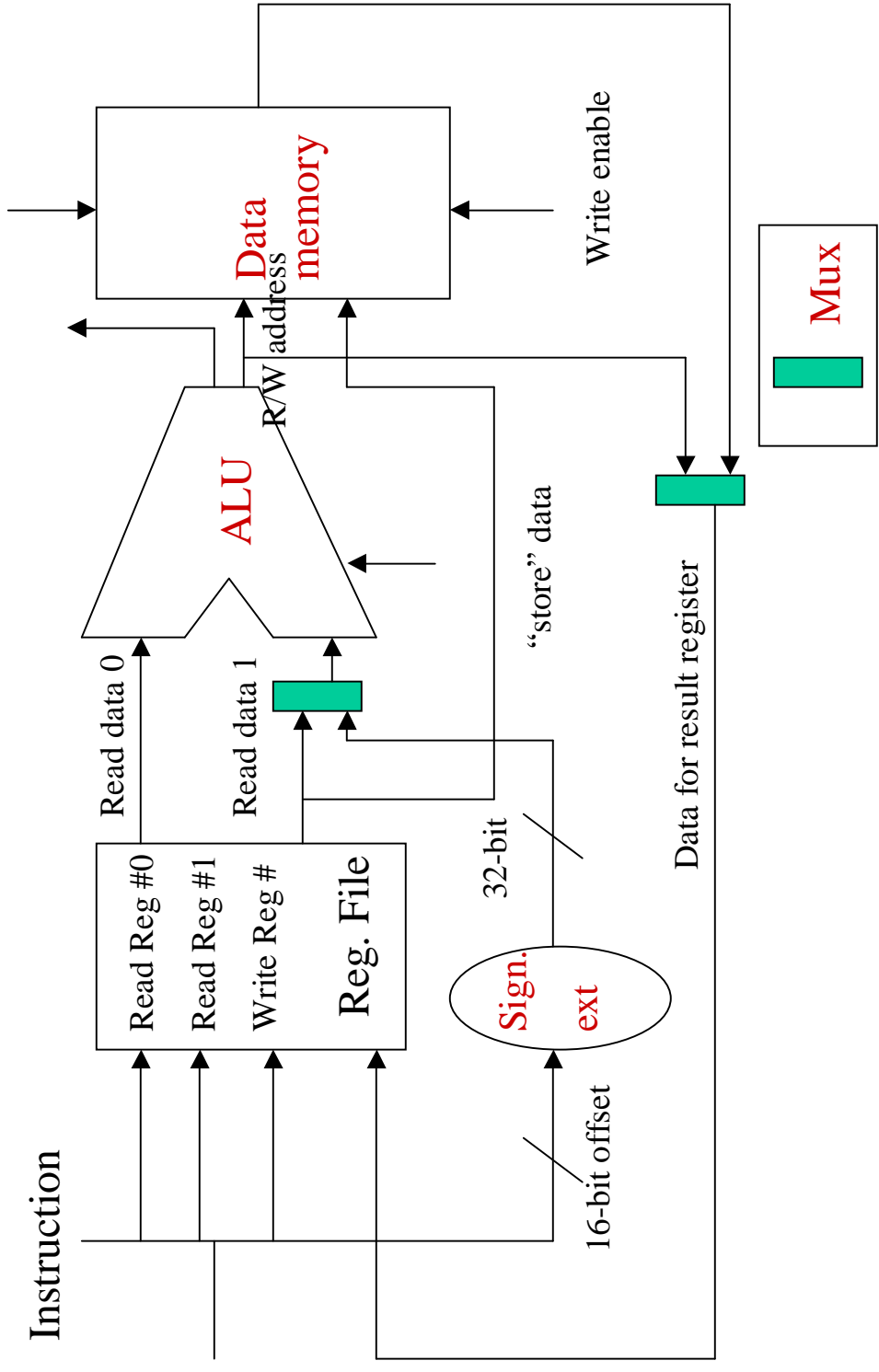Data path for straight code(reg-reg,imm,load/store)



Branch data path

