

Charge

Two hydrogen atoms meet. One says
"I've lost my electron."


The other says "Are you sure?"

The first replies "Yes, I'm positive."

1

Basic Concepts of Electricity

- Voltage
- Current
- Resistance

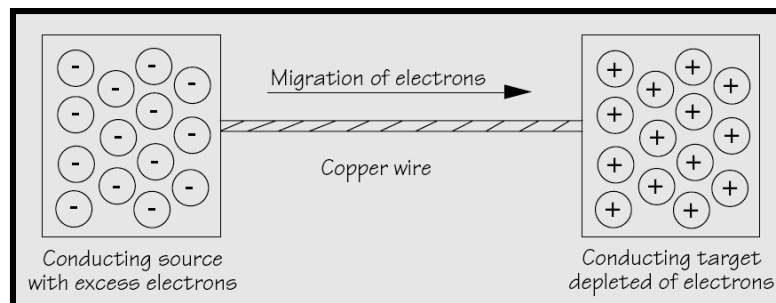

2



Electric Fields

- An electric field applies a force to a charge
 - Force on positive charge is in direction of electric field, negative is opposite
- Charges move if they are mobile
- An electric field is produced by charges (positive and negative charges)
- Electric fields can be produced by time varying magnetic fields (generator, antenna radiation)



3



Voltage Difference

- Voltage difference is the difference in potential energy in an electric field
- $E = V/d$
- As you move closer to a positive charge the voltage increases

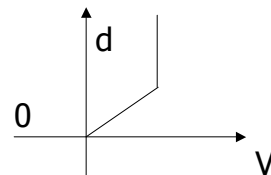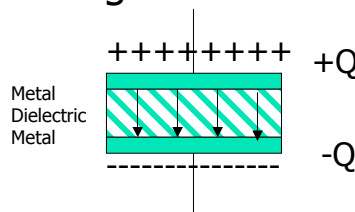Capacitor
(electric field
constant between
parallel plates)



4



Current

- An electric current is produced by the flow of electric charges
- Current = rate of charge movement
= amount of charge crossing a surface per unit time
- In conductors, current flow is due to electrons
- Conventional current is defined by the direction positive charges will flow
- Direction of electron flow is opposite to direction of conventional current

5




Resistance

- In materials electrons accelerate in an electric field
- Electrons lose energy when they hit atoms - lost energy appears as heat and light
- The result is that electrons drift with constant velocity (superimposed on random thermal motion)
- Resistance is the ratio Voltage/current
$$R = V/I$$

6

Voltage, Current, and Resistance

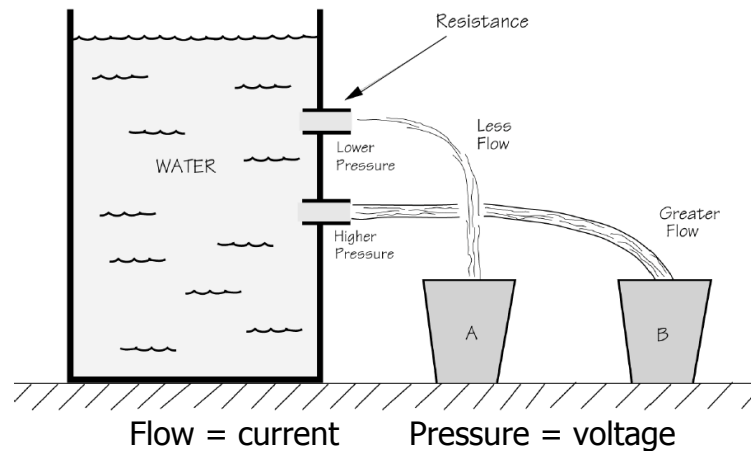

7

Material Conductivity


- Conductors - negligible resistance
- Insulators - extremely large resistance
- Semiconductors - some resistance
- Resistors - are devices designed to have constant resistance across a range of voltages

8




Resistor Combination

Series resistance

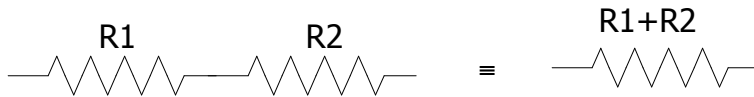

Parallel resistance

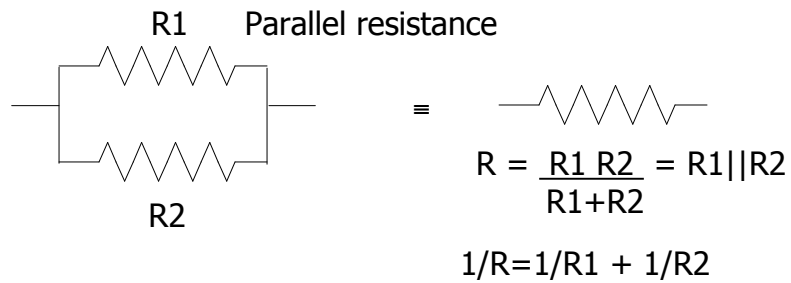

9




Kirchoff's Voltage Law

- Kirchoff's voltage law (KVL)
 - The sum of voltage differences around any loop in a circuit equals 0
 - Equivalently, the voltage between two points is the same no matter what path is traversed

10

Voltage Divider

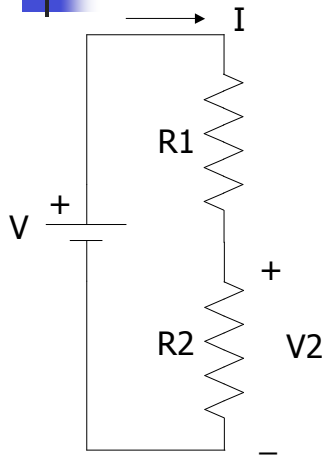

$$V_2 = \frac{V R_2}{R_1 + R_2}$$


Solution:

Goal: Find V_2 given V

- Find V_2 in terms of I
- Current through R_2 in terms of I
- Voltage across R_1
- Find voltage across R_1 and R_2 using two different methods

11

Potentiometer (Variable Resistor)

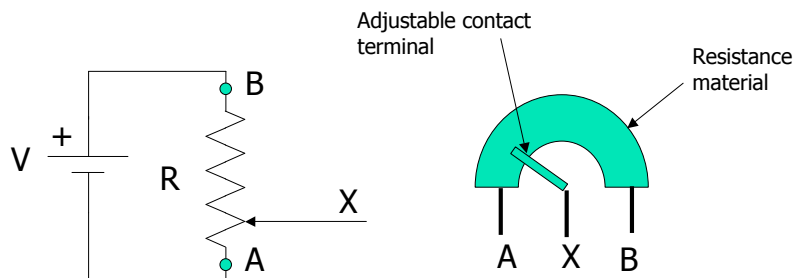

$$V_X = V * \text{Distance AX} / \text{Distance AB}$$

(linear potentiometer)

A trimpot is a small variable resistor mounted on a printed circuit board that can be adjusted by a small screwdriver to make semi-permanent adjustments to a circuit

12



Input Transducers

- These are devices that produce electric signals in accordance with changes in some physical effect e.g. convert temperature, light level to a voltage level or resistance
- e.g. microphones, strain gauge, photo-detectors, ion-selective membranes, thermistors
- Sometimes the definition of transducer is that of a device that converts non-electrical energy to electrical energy

13



Output Transducers

- Devices which convert an electrical quantity into some other physical quantity or effect e.g. relay, loudspeaker, solenoid

14



Light Dependent Resistors (LDRs)

- Devices whose resistance changes (usually decreases) with light striking it
- (also called photocells, photoconductors)
- Light striking a semiconducting material can provide sufficient energy to cause electrons to break away from atoms.
- Free electrons and holes can be created which causes resistance to be reduced

15




LDRs


- Typical materials used are Cadmium Sulphide (CdS), Cadmium Selenide (CdSe), Lead Sulphide
- With no illumination, resistance can be greater than 1 M Ω (dark resistance).
- Resistance varies inversely proportional to light intensity.
- Reduces down to 10-100s ohms
- 100ms/10ms response time

16

LDRs

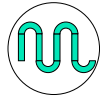

CdS LDR
Top view

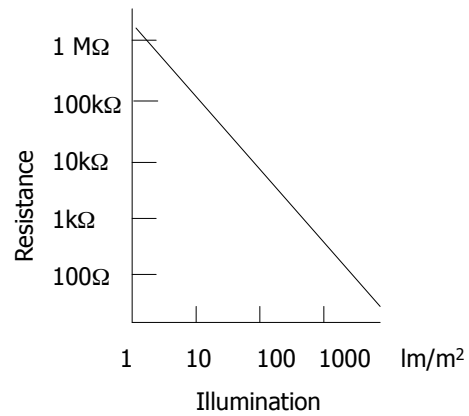

17

LDRs

- LDRs have a low energy gap
- Operate over a wide wavelengths (some, into infrared)
- Indium antimonide is good for IR. When cooled is very sensitive, used for thermal scanning of earth's surface


18

Capacitors

- A component constructed from two conductors separated by an insulating material (dielectric) that stores electric charge (+Q, -Q)
- As a consequence there is a voltage difference across the capacitor, V
- Capacitance = $C = Q/V$
- The dielectric material operates to reduce the electric field between the conductors and so allow more charge to be stored for a given voltage

19


Capacitors

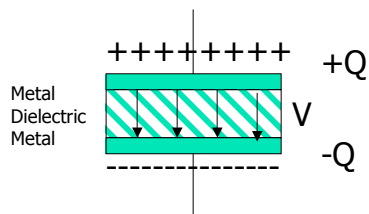

$$C = Q/V$$

$$(Q = CV)$$


Bucket analogy

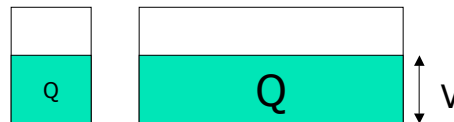

A small bucket (capacitor, C) holds less charge (Q) for given level (voltage V) than a large bucket

20

Charging a Capacitor

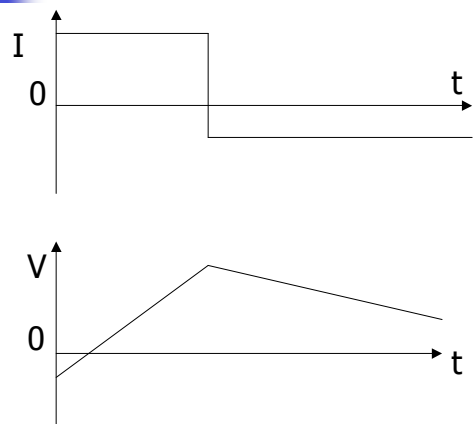


The bucket analogy can be used to describe capacitor charging

When current flows in at a constant rate the voltage increases linearly and vice versa for current flowing out

Semiconductors

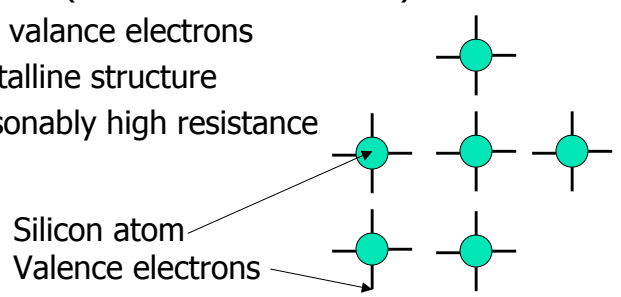- Silicon is used as an example (other semiconductors include Germanium, Gallium Arsenide, Gallium phosphide, indium arsenide, indium phosphide)
- Pure silicon (intrinsic semiconductor)
 - Four valance electrons
 - Crystalline structure
 - Reasonably high resistance





Electrons and holes


- Due to thermal energy some electrons in the valance shell become free
- Create:
 - One free electron +
 - One hole in the valance band that can be filled by electrons from the valance band in an adjacent silicon atom
- Current in silicon can flow due to both movement of electrons and holes

23



n-type silicon

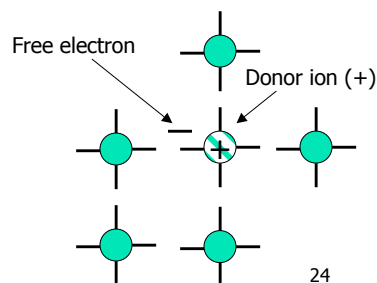
- Add donor impurities (e.g. Phosphorus, arsenic, indium) with 5 electrons in the valance band
- As only four electrons can bond with neighbouring silicon atoms one free electron is left
- Increases concentration of free electrons
- Reduces concentration of holes (due to increased chance of recombination)
- Resistance reduced



24

p-type silicon

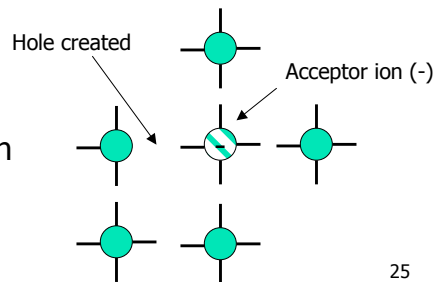- p-type silicon is created by adding acceptor impurities which have three valence electrons (e.g. boron)
- This leaves an unbound valence electron in an adjacent silicon atom creating a hole
- Increases concentration of holes
- Reduces concentration of free electrons
- P-type silicon has lower resistance than pure silicon



25

Diodes

- If a piece of n-type silicon and p-type silicon are joined directly together a diode (di - electrode) device is created



26



Macro-behaviour


- A diode is a device that allows current flow easily in one direction easily and allows hardly any current flow in the opposite direction

27



Forward bias

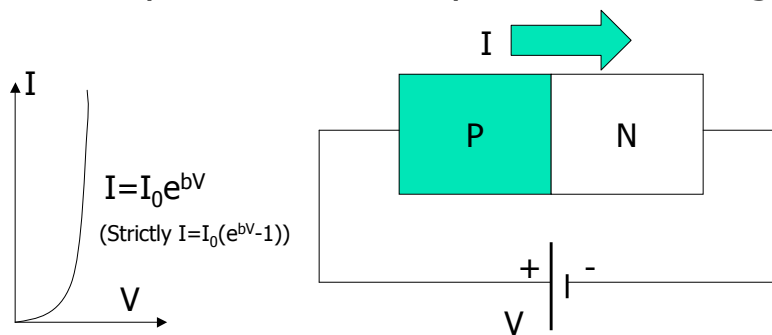- Current flows easily if the P region is positive with respect to the N region




28



Reverse bias

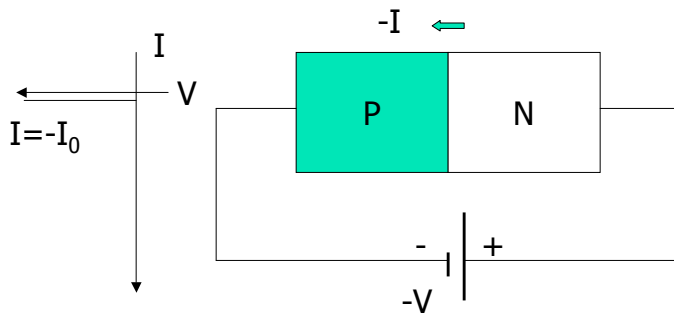
- Current hardly flows if the P region is negative with respect to the N region



29



Diode and resistor circuit

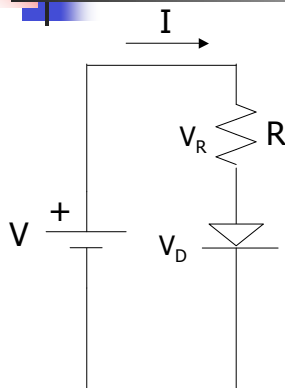

Currents and voltages determined by:
(work backwards to find V_D)

- V_D related to I by diode equation
- Current in resistor and diode equal
- $V_R = IR$
- voltage across diode and voltage resistor add up to voltage source V

Short cut rule of thumb, V_D is approx 0.6-0.7 volts and $V_R \approx V - 0.6$


For LEDs V_D is about 1.8 - 4.0 V, depending on color

Forward biased diode

30



Diode and resistor circuit

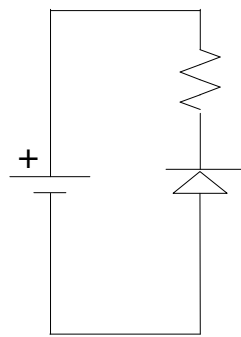

Reverse biased diode

Assume no reverse-bias current flows (ideal case)

Therefore no voltage occurs across the resistor

Therefore the full supply voltage appears across the diode

31



LEDs

- Light emitting diode
- When an electron moves down from the conduction band to the valence band it loses energy
- In silicon and germanium the energy-momentum relationships mean that this energy is lost heat
- In gallium arsenide it produces a photon

32



LEDs

- The light intensity is proportional to current
- Pure gallium arsenide produces infrared light
- GaAsP produces red or yellow light
- GaP produces red or green

33




Circuit design using LEDs

- LEDs behave just like normal diodes except that the forward bias voltages are greater (typically 1.8 - 4.0 V)
- A typical forward bias current of 10-20 mA is used.

34

Example

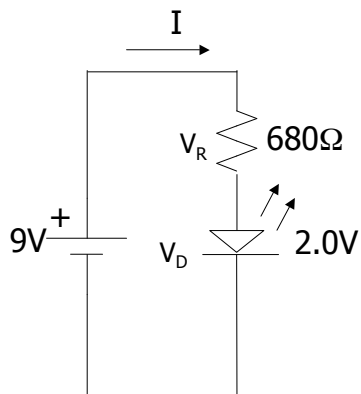

$$I = \frac{9 - 2.0}{680} \\ = 10.29 \text{ mA}$$

35

Introduction to AVR

Atmel AVR Microcontroller


36

AVR Key Features

- High Performance 8-Bit MCU
- RISC Architecture
 - 32 Registers
 - 2-Address Instructions
 - Single Cycle Execution
- Low Power
- Large linear address spaces
- Efficient C Language Code Density
- On-chip in-system programmable memories

RISC Performance with CISC Code Density

37

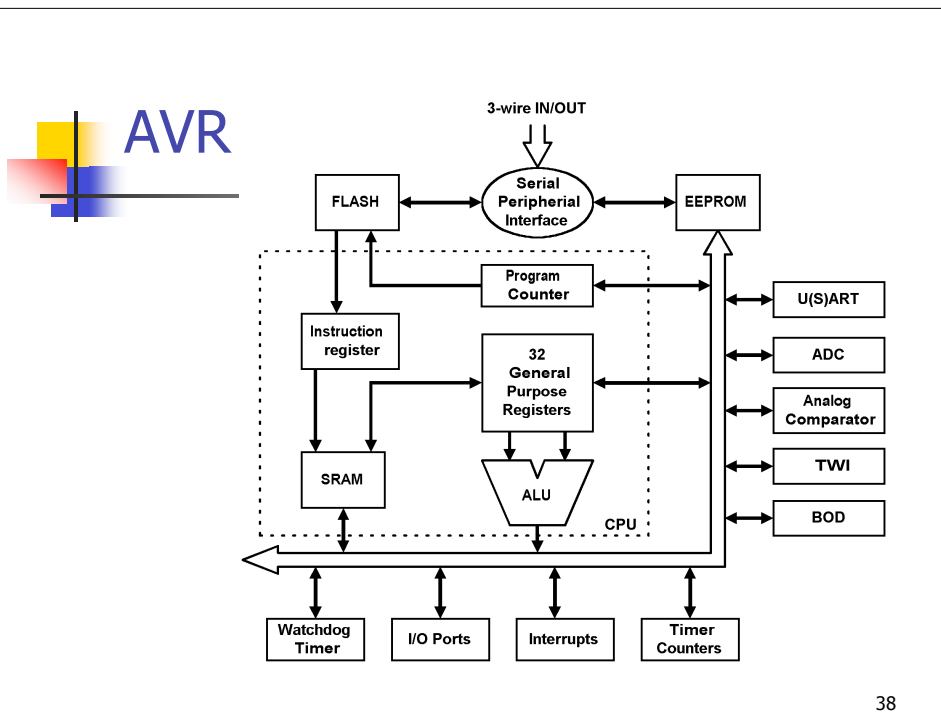

38



ATmega16(L)

- 40/44 pin packages
- 16 KBytes ISP Flash, Self Programmable
- 512 Bytes ISP EEPROM
- 1 KBytes SRAM
- Full Duplex UART
- SPI – Serial Interface
- TWI – Serial Interface
- 8- and 16-bits Timer/Counters with PWM
- 2 External Interrupts
- 10-bit ADC with 8 Multiplexed Inputs
- RTC with Separate 32 kHz Oscillator
- Analog Comparator
- JTAG Interface with On-Chip Debugger

39



Typical Applications, ATmega16(L)

- Smart Battery
- Advanced Battery Charger
- Power Meter
- Temperature Logger
- Voltage Logger
- Tension Control
- Touch Screen Sensor
- Metering Applications
- UPS
- 3 Phase Motor Controller
- Industrial Control
- Power Management

40



I/O Ports General Features

- Push-Pull Drivers
- High Current Drive (sinks up to 40 mA)
- Pin-wise Controlled Pull-Up Resistors
- Pin-wise Controlled Data Direction
- Fully Synchronized Inputs
- Three Control/Status Bits per Bit/Pin
- Real Read-Modify-Write



41




3 Control/Status Bits per Pin

- DDx Data Direction Control Bit
- PORTx Output Data or Pull-Up Control Bit
- PINx Pin Level Bit

42

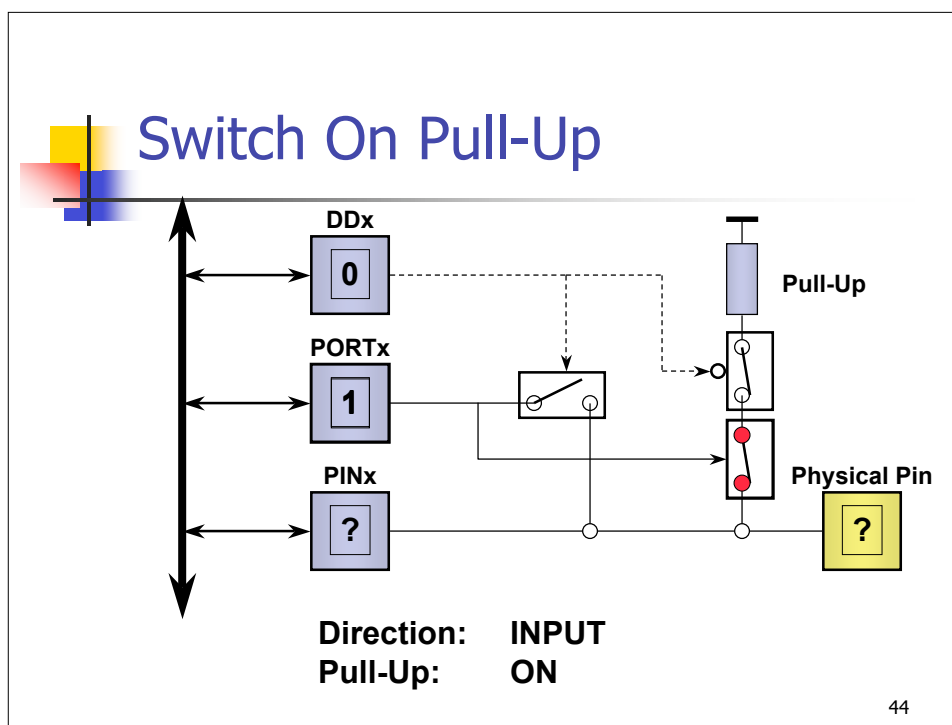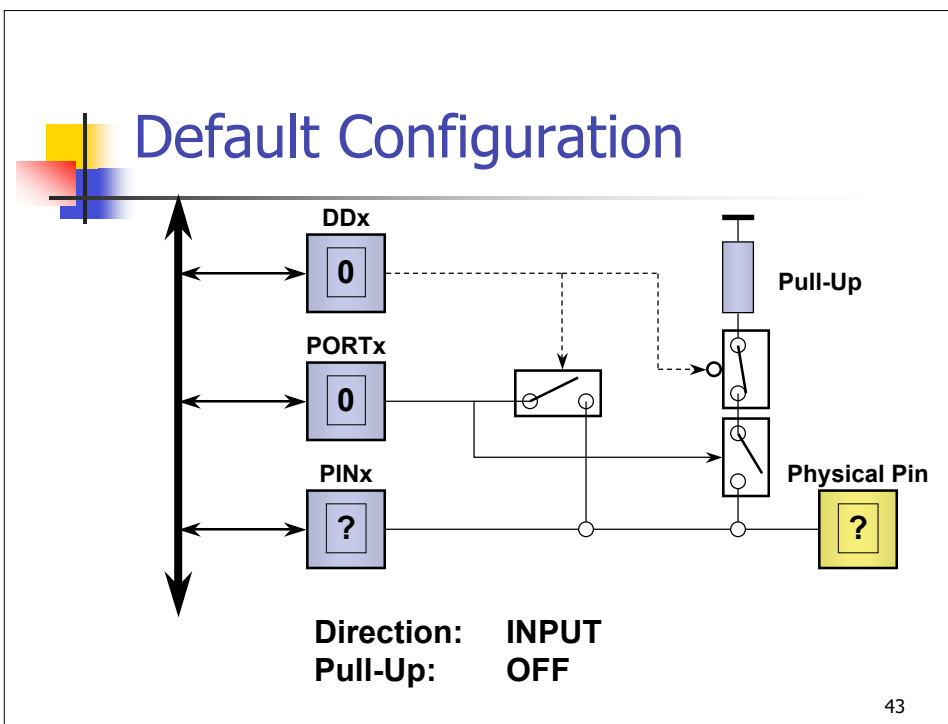

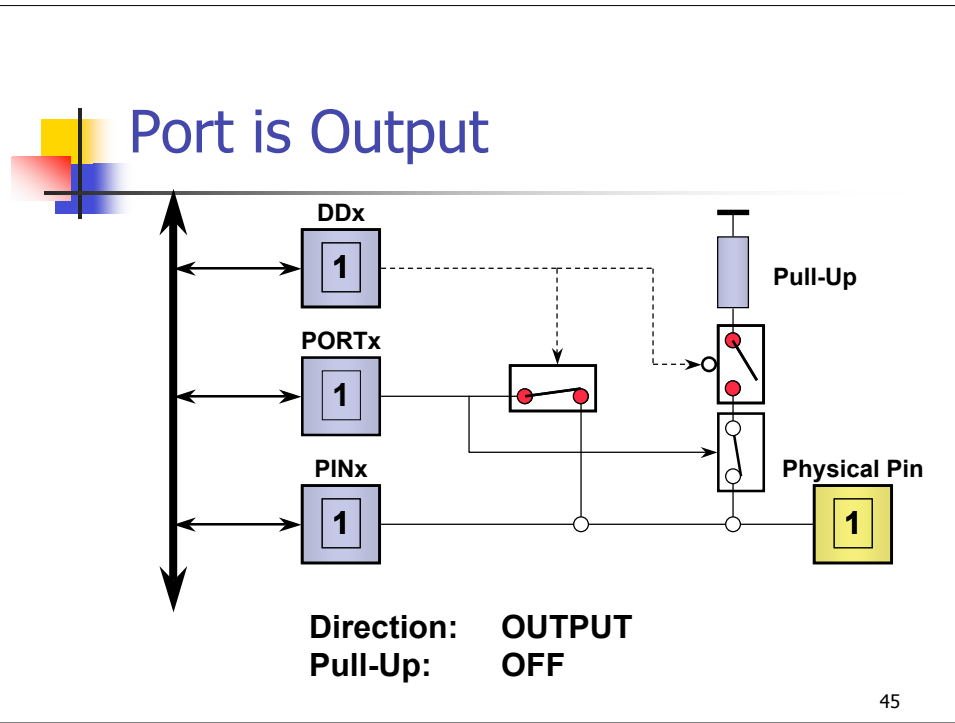


- ## General Timer/Counter Features
- Various Clock Prescaling Options
 - Can Run at Undivided XTAL Frequency (High Resolution)
 - Can be Set to Any Value at Any Time
 - Can be Clocked Externally by Signals with Transition Periods down to XTAL/2
 - Can be Clocked Externally on both Rising and Falling Edge
 - The features vary from device to device, see datasheets for details
- 46

16 Bit Timer/Counter

- Prescaler
- Overflow Interrupt
- Output Compare Function with Interrupt
- Input Capture with Interrupt and Noise Cancler
- PWM

47

16 Bit T/C Block Diagram

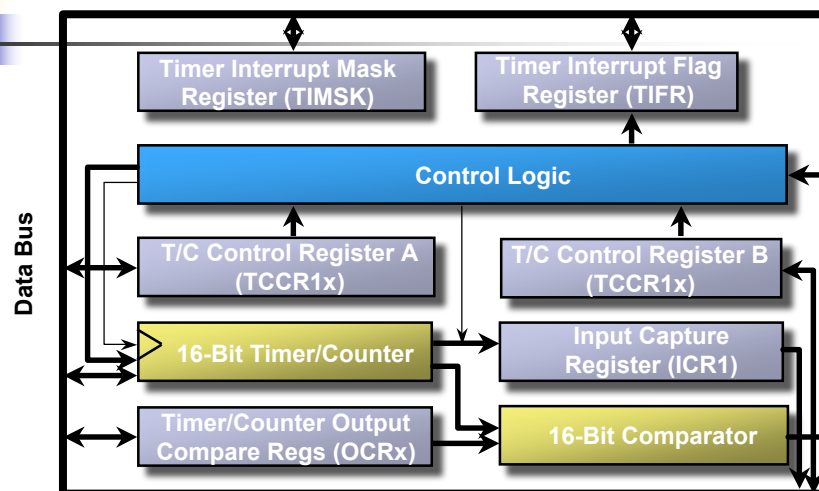

48



Output Compare Features

- Compare match can control an external pin (Rise, Fall or Toggle) even if the Interrupt is disabled.
- As an option, the timer can be automatically cleared when a compare match occurs.

49




PWM (Pulse Width Modulator) Features

- Selectable 8, 9 or 10-Bit Resolution.
- Frequency @ 10 MHz (8-bit): 19 KHz
- Centered Pulses
- Glitch-Free Pulse Width Change
- Selectable Polarity

50


PWM Operation

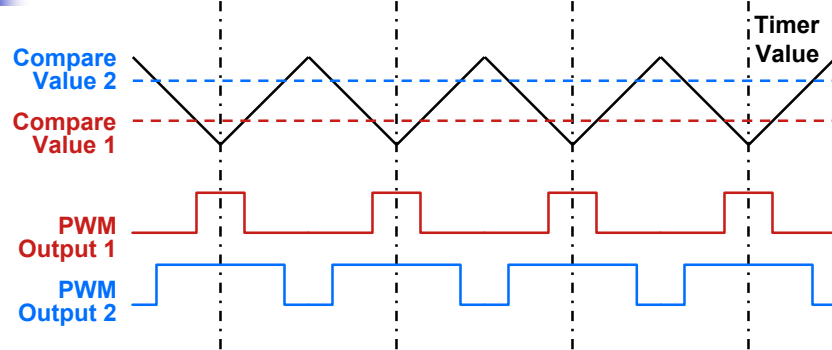

51

Self Programming

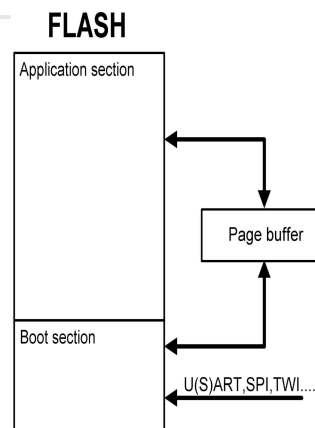- Dual memory areas
 - Application section
 - Boot section (optional)
- Read data from
 - Any communication interface
 - Application section
 - Boot section
- Write it to a page buffer
- Transfer the buffer to the Flash page in Application or Boot section



52



AVR websites and mail

- ATMEL website www.atmel.com
 - Datasheets
 - Application Notes
 - FAQ
- Unofficial AVR websites
 - www.avrfreaks.net
 - www.avr-forum.com