

CSE 369: Introduction to Digital Design

- ❖ Professor Georg Seelig, CSE 228
(gseelig@uw.edu)
 - ❖ Office Hours: email w/schedule for a slot
- ❖ Book: Brown & Vranesic *Fundamentals of Digital Logic with Verilog Design* (3rd Edition)
- ❖ TAs:
 - ❖ Ta-Tung Yen (ttyen@uw.edu)
 - ❖ Sixto Josue Rios (jrios777@uw.edu)
- ❖ Lab Hours: TBA (check website)

Grading

- ❖ 70% - Labs
- ❖ 10% - Quizzes
- ❖ 20% - Final Exam
- ❖ Late penalties for uploading lab materials:
 - ❖ <24 hours: -10%
 - ❖ <48 hours: -30%
 - ❖ <72 hours: -60%
 - ❖ >72 hours: not accepted

Joint Work Policy

- ❖ Labs will be done alone
- ❖ Students may not collaborate on labs/projects, nor between groups on the specifics of homeworks.
- ❖ OK:
 - ❖ Studying together for exams
 - ❖ Discussing lectures or readings
 - ❖ Talking about general approaches
 - ❖ Help in debugging, tools peculiarities, etc.
- ❖ Not OK:
 - ❖ Developing a lab together
- ❖ Violation of these rules is grounds for failing the class

Class & Lab Meetings

- ❖ Labs:
 - ❖ Each student assigned a lab kit, can work where-ever.
 - ❖ In addition to the official sections, TAs will have some blocks of office hours to help with labs, etc.
 - ❖ Signups for lab demos will be posted shortly.
- ❖ Quiz: Tue, Oct 27 and Tue, Nov 24 in class
- ❖ Final: Mon, June 8, 8:30-10:20


Motivation

- ❖ Readings: 1-1.4, 2-2.4
- ❖ Electronics an increasing part of our lives
 - ❖ Computers & the Internet
 - ❖ Car electronics
 - ❖ Robots
 - ❖ Electrical Appliances
 - ❖ Cellphones
 - ❖ Portable Electronics
- ❖ Class covers digital logic design & implementation

Example: Car Electronics


- ❖ Door Ajar (DriverDoorOpen, PassDoorOpen):

$$DA = DDO \text{ OR } PDO$$

 

- ❖ High-beam indicator (lights, high beam selected):

$$HBI = LIGHTS \text{ AND } HBS$$

 

Example: Car Electronics (cont.)


- ❖ Seat Belt Light (driver belt in):

$$SBL = \text{NOT}(DBI)$$




- ❖ Seat Belt Light (driver belt in, passenger belt in, passenger present):
 
$$SBL = \text{NOT}(DBI) \text{ OR } (PP \text{ AND } \text{NOT}(PBI))$$




Basic Logic Gates

 
- ❖ AND: If A and B are True, then Out is True




 
- ❖ OR: If A or B is True, or both, then Out is True



 
- ❖ Inverter (NOT): If A is False, then Out is True



TTL Logic

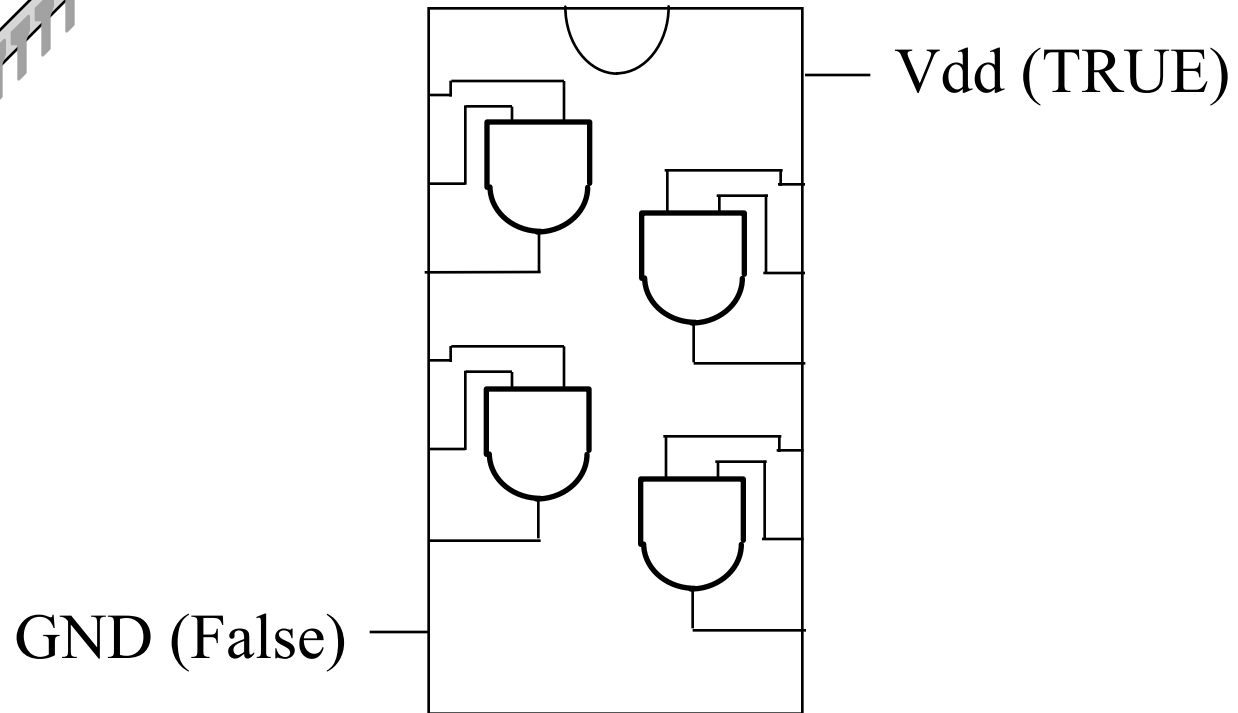 


Digital vs. Analog

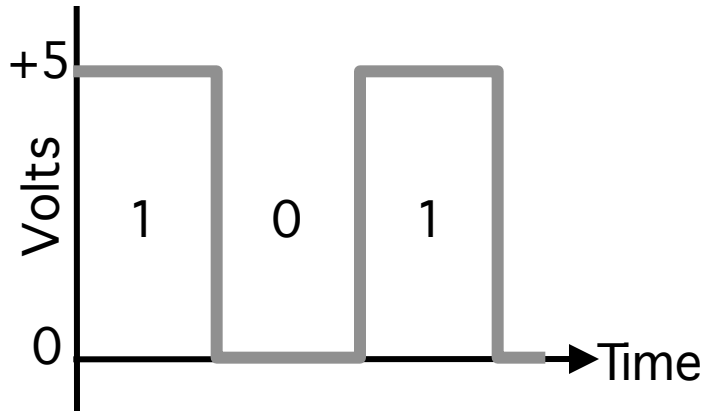

Digital:
only assumes discrete values

 Binary/Boolean (2 values)
yes, on, 5 volts, high, TRUE, "1"
no, off, 0 volts, low, FALSE, "0"



Analog:
values vary over a broad range
continuously


Advantages of Digital Circuits

- ❖ Analog systems: slight error in input yields large error in output
- ❖ Digital systems more accurate and reliable
 - ❖ Readily available as self-contained, easy to cascade building blocks
- ❖ Computers use digital circuits internally
- ❖ Interface circuits (i.e., sensors & actuators) often analog

This course is about logic design, not system design (processor architecture), not circuit design (transistor level)


Combinational vs. Sequential Logic

Sequential logic

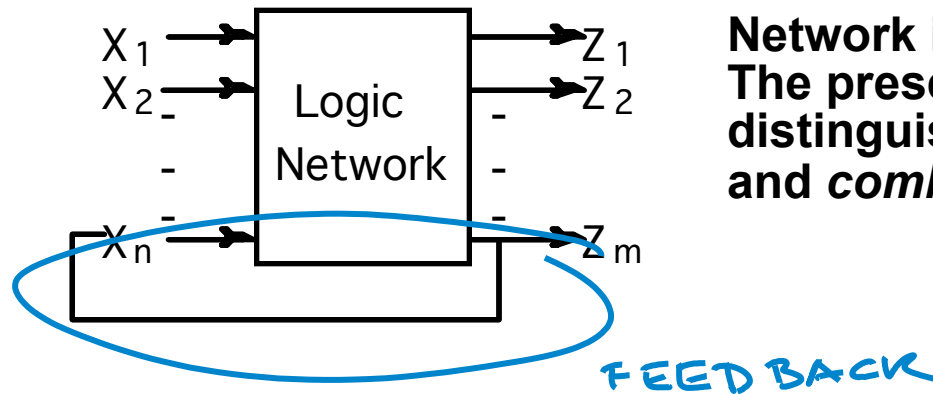

Network implemented from logic gates. The presence of feedback distinguishes between *sequential* and *combinational* networks.

Combinational logic

 

No feedback among inputs and outputs. Outputs are a function of the inputs only.

Boolean Elements and truth tables

Algebra: variables, values, operations

In Boolean algebra, the values are the symbols 0 and 1

If a logic statement is false, it has value 0

If a logic statement is true, it has value 1

Operations: AND, OR, NOT



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

X	NOT X
0	1
1	0

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1



NAND and NOR Gates

■ NAND Gate: NOT(AND(A, B))

  

X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0


■ NOR Gate: NOT(OR(A, B))

  

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

XOR and XNOR Gates

 
- XOR Gate: $Z=1$ if X is different from Y



$$X \oplus Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR Gate: $Z=1$ if X is the same as Y

 

$$\overline{X \oplus Y}$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

Boolean Equations

Boolean Algebra

values: 0, 1

variables: A, B, C, . . . , X, Y, Z

operations: NOT, AND, OR, . . .

NOT X is written as \bar{X}

X AND Y is written as $X * Y$, or sometimes $X Y$ or $X \& Y$

X OR Y is written as $X + Y$

Deriving Boolean equations from truth tables:

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Carry = AB

OR'd together *product* terms
for each truth table
row where the function is 1

if input variable is 0, it appears in
complemented form;
if 1, it appears uncomplemented

$$\text{Sum} = \bar{A}B + A\bar{B} = A \oplus B$$

Boolean Algebra/Logic Minimization

$$\bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \text{ vs. } AB + AC_{in} + BC_{in}$$

Logic Minimization: reduce complexity of the gate level implementation

- **reduce number of literals (gate inputs)**
- **reduce number of gates**
- **reduce number of levels of gates**

fewer inputs implies faster gates in some technologies

fan-ins (number of gate inputs) are limited in some technologies

fewer levels of gates implies reduced signal propagation delays

number of gates (or gate packages) influences manufacturing costs

Basic Boolean Identities:

$$X + 0 = X$$

$$X * 1 = X$$

$$X + 1 = 1$$

$$X * 0 = 0$$

$$X + X = X$$

$$X * X = X$$

$$X + \bar{X} = 1$$

$$X * \bar{X} = 0$$

$$\overline{\bar{X}} = X$$

Basic Laws

Commutative Law:

$$X + Y = Y + X$$

$$XY = YX$$

Associative Law:

$$X+(Y+Z) = (X+Y)+Z$$

$$X(YZ)=(XY)Z$$

Distributive Law:

$$X(Y+Z) = XY + XZ$$

$$X+YZ = (X+Y)(X+Z)$$

Advanced Laws (Absorbtion)

$$\blacksquare X + XY = X(1 + Y) = X$$

$$\blacksquare XY + X\bar{Y} = X(Y + \bar{Y}) = X$$

$$\blacksquare X + \bar{X}Y = X + Y$$

$$\blacksquare X(X + Y) = XX + XY = X(1 + Y) = X$$

$$\blacksquare (X + Y)(X + \bar{Y}) = X + X(Y + \bar{Y}) = X$$

$$\blacksquare X(\bar{X} + Y) = X\bar{X} + XY = XY$$

Boolean Manipulations (cont.)

■ Boolean Function: $F = \overline{X}YZ + XZ$

Truth Table:


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Reduce Function:

$$= (\overline{x}y + x)z$$

$$= (x + y)z$$

$$= \underline{xz} + \underline{yz}$$

 

DeMorgan's Law

$$\overline{(X + Y)} = \bar{X} * \bar{Y}$$

X	Y	\bar{X}	\bar{Y}	$\overline{X+Y}$	$\bar{X} * \bar{Y}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$\overline{(X * Y)} = \bar{X} + \bar{Y}$$

X	Y	\bar{X}	\bar{Y}	$\overline{X*Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

DeMorgan's Law can be used to convert AND/OR expressions to OR/AND expressions

Example:

$$Z = (\bar{A} \bar{B} C) + (\bar{A} B \bar{C}) + (A \bar{B} C) + (A B \bar{C})$$

$$\bar{Z} = (A + B + \bar{C}) * (A + \bar{B} + \bar{C}) * (\bar{A} + B + \bar{C}) * (\bar{A} + \bar{B} + C)$$



DeMorgan's Law example

- If $F = (XY+Z)(\bar{Y}+\bar{X}Z)(X\bar{Y}+\bar{Z})$,

$$\begin{aligned}\bar{F} &= \overline{(XY+Z)} + \overline{(\bar{Y}+\bar{X}Z)} + \overline{(X\bar{Y}+\bar{Z})} \\ &= \overline{(XY)}\bar{Z} + Y\overline{(\bar{X}Z)} + \overline{(X\bar{Y})}Z \\ &= (\bar{x}+\bar{y})\bar{z} + y(x+\bar{z}) + (\bar{x}+y)z \\ &= \bar{x}\bar{z} + \bar{y}\bar{z} + xy + y\bar{z} + \bar{x}z + yz \\ &= \bar{x} + xy + \bar{z} + yz \\ &= \bar{x} + y + \bar{z} \quad (? \text{ CHECK!})\end{aligned}$$

Mapping truth tables to logic gates

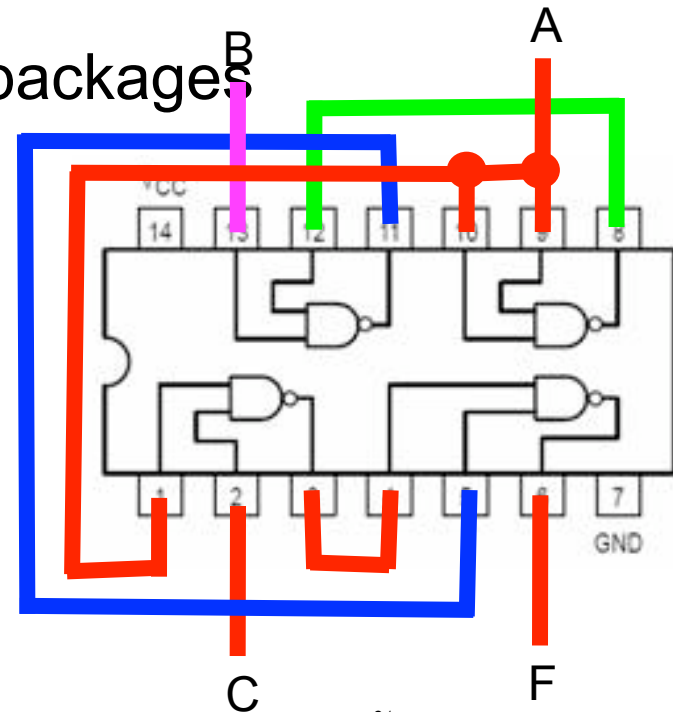 - Given a truth table:
 - Write the Boolean expression
 - Minimize the Boolean expression
 - Draw as gates
 - Map to available gates
 - Determine number of packages and their connections



7 nets (wires)
in this design

Breadboarding circuits

