 


# Review Problem: AND/OR to NAND

- Convert the following circuit to **NAND**/NOR form



$$\overline{A+B} = \overline{A} \cdot \overline{B}$$
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

# Review problem: circuit design

- ❖ Rock (00), Paper (01), Scissors (10) for two players.
- ❖ Output: Winner = Winner's ID (0/1)  
Tie = 1 if Tie, 0 if not

		P1		P0		WIN	TIE
		A	B	C	D		
0	0	0	0	-	-	0	0
	1	0	0	-	-	0	0
1	0	0	1	-	-	1	0
	1	1	0	-	-	0	1

Handwritten annotations in purple:

- Two 'X' marks in the top-left quadrant (00, 00) and (00, 01) with arrows pointing to them and the text "INPUT DON'T CARE".
- Two 'X' marks in the top-right quadrant (00, 10) and (00, 11) with arrows pointing to them and the text "OUTPUT DON'T CARE".
- The word "K-MAPS" written and underlined on the right side.


# Review Problem: Basic Verilog

---

- Write the Verilog for a 2-input gate that is TRUE when an odd number of inputs are true.

# Combinational vs. Sequential Logic

## ❖ Readings: 5-5.4.4

 


Network implemented from logic gates. The presence of feedback distinguishes between **sequential** and **combinational** networks.
 
### **Combinational logic**



no feedback among inputs and outputs  
outputs are a pure function of the inputs  
e.g., seat belt light:

(Dbelt, Pbelt, Passenger) mapped into (Light)


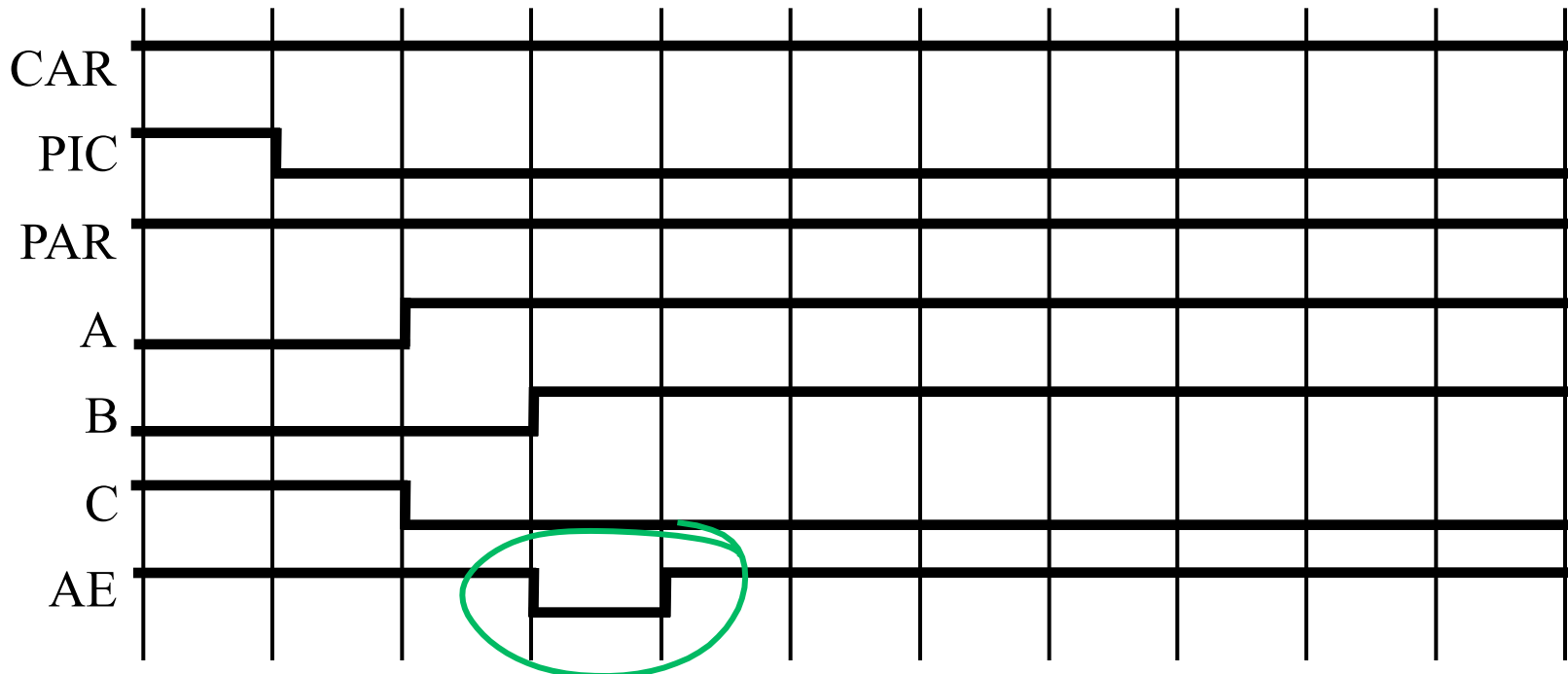 
# Hazards/Glitches


- Circuit can temporarily go to incorrect states



❖ Must filter out temporary states
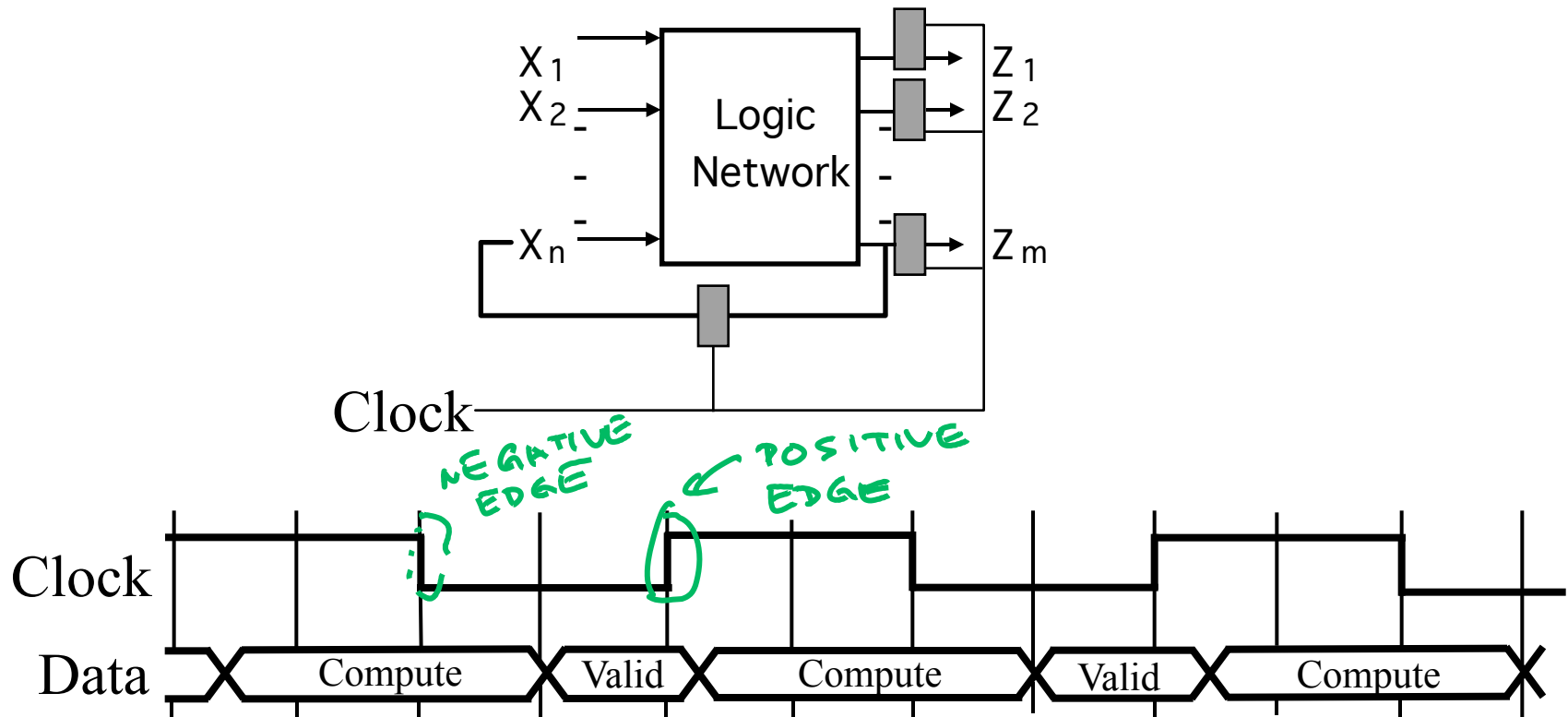
# Safe Sequential Circuits

- Clocked elements on feedback, perhaps outputs
  - Clock signal synchronizes operation
  - Clocked elements hide glitches/hazards



STATE HOLDING ELEMENT  
CHANGES VALUE AT CLOCK EDGE

# Basic D Flip Flop

```
// Basic D flip-flop
```

```
module basic_D_FF (q, d, clk);
```

```
    output q;
```



```
    input d, clk;
```

```
    reg q; // Indicate that q is stateholding
```

```
    always @(posedge clk)
```


```
        q <= d; // ALWAYS use <= to assign to clocked elements
```

```
endmodule
```

  

← POSITIVE EDGE TRIGGERED

 ← IF YOU ARE WRITING AFTER always@(..) , USE ←



# Blocking and Non-Blocking Assignments

- Blocking assignments ( $X=A$ )
  - completes the assignment before continuing on to next statement
- Non-blocking assignments ( $X<=A$ )
  - completes in zero time and doesn't change the value of the target until a blocking point (delay/wait) is encountered
- Example: swap

```
always @(posedge CLK)
begin
    temp = B;
    B = A;
    A = temp;
end
```

```
always @(posedge CLK)
begin
    A <= B;
    B <= A;
end
```


~~begin  
A = B;  
B = A;  
end~~


 
# D Flip Flop w/Synchronous Reset

```
// D flip-flop w/synchronous reset WITH CLOCK EDGE
```

```
module D_FF (q, d, reset, clk);  
    output q;  
    input d, reset, clk;  
    reg q; // Indicate that q is stateholding  
  
    always @(posedge clk)  
        if (reset)  
            q <= 0; // On reset, set to 0  
        else  
            q <= d; // Otherwise out = d  
  
endmodule
```



# Verilog Testbench

```

module stimulus;
  reg clk, reset, d;
  wire q;

  parameter ClockDelay = 100;

  D_FF dut (.q, .d, .reset, .clk); // Instantiate the D FF

  initial clk <= 0; // Set up the clock
  always #(ClockDelay/2) clk <= ~clk; // Toggle clock every 50 time units

  initial // Set up the reset signal
  begin
    d <= 0; reset <= 1; @(posedge clk);
    reset <= 0; @(posedge clk);
    d <= 1;          @(posedge clk);
    d <= 0;          @(posedge clk);
    d <= 1;          @(posedge clk);
    $stop(); // end the simulation
  end


endmodule

```

TIME	D	R	C	Q
0	0	1	0	X
50	0	0	1	0
100	0	0	0	0
150	1	0	1	0
200	1	0	0	0
250	0	0	1	1
300	0	0	0	0
350	1	0	0	0
400	0	0	0	0



# Testbench Waveforms

---

 


# Flipflop Realities 1: Gating the Clock

---

  


- **NEVER put a logic gate between the clock and DFF's CLK input.**
 
## Flipflop Realities 2: Clock Period, Applying Stimulus





- Clock Period?
- Apply Inputs when?

 
 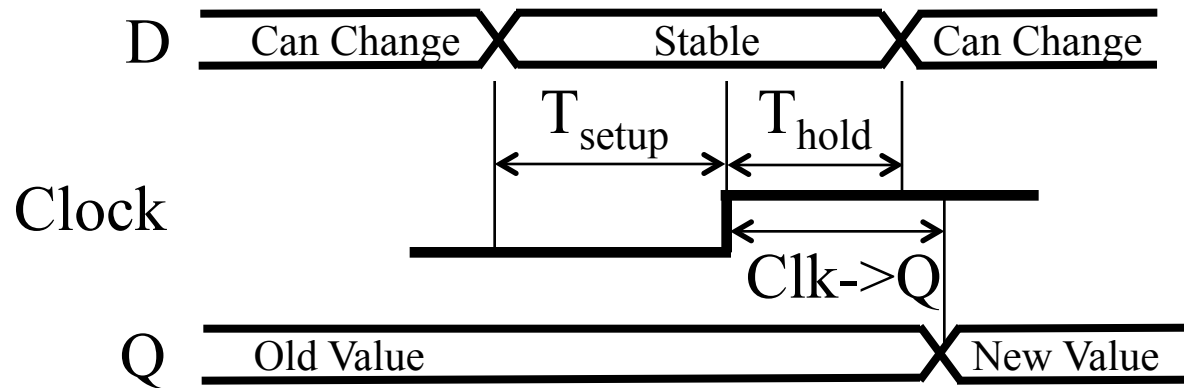
# $T_{\text{setup}}$ , $T_{\text{hold}}$ , Clk->Q

- Flipflops require their inputs be stable for time period around clock edge



# Timing Definitions


---

- $T_{\text{setup}}$ : Time D must be stable BEFORE clock edge
  - Adds to critical path delay
- Clk->Q: Time from clock edge to Q changing
  - Adds to critical path delay
- $T_{\text{hold}}$ : Time D must be stable AFTER clock edge
  - Sets minimum path from Q of one DFF to D of another
 
# Flipflop Realities 3: External Inputs

---

- External inputs aren't synchronized to the clock







# Dealing with Metastability

---

## ■ Single DFF

 

## ■ 2 DFFs in series

 

## ■ 2 DFFs in parallel

