 


# Review Problem


- If gate delays are 1.0ns each,  $T_{\text{setup}}$  is 0.5, and  $T_{\text{hold}}$  is 1.5, what is the best clock period for this computation?



CLOCK PERIOD  $\geq 3.5ns = \text{CRITICAL PATH TIME} + T_{\text{SETUP}}$

SHORTEST PATH  $\geq T_{\text{HOLD}}$


BETTER DESIGN:

 
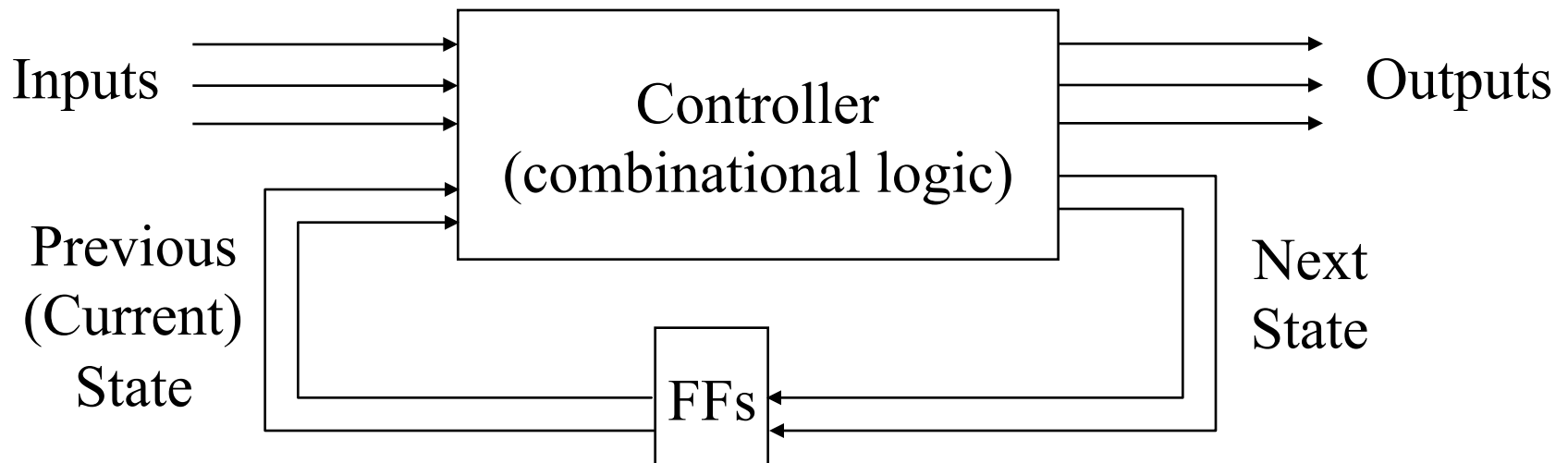
# Finite State Machines

---


- **Readings: 6-6.4.7**
- Need to implement circuits that remember history
  - Traffic Light controller, Sequence Lock, ...
- History will be held in flip flops
- Sequential Logic needs more complex design steps
  - State Diagram to describe behavior
  - State Table to specify functions (like Truth Table)
  - Implementation of combinational logic as controller



# Finite State Machine Example

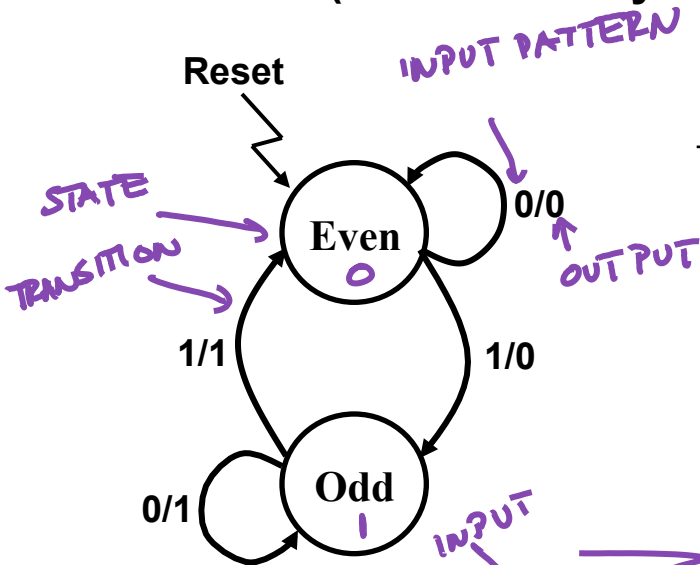
## Example: Odd Parity Checker

Assert output whenever have previously seen an odd # of 1's  
(I.e. how many have you seen NOT INCLUDING the current one)



Present State	Input	Output	Next State
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

State Diagram


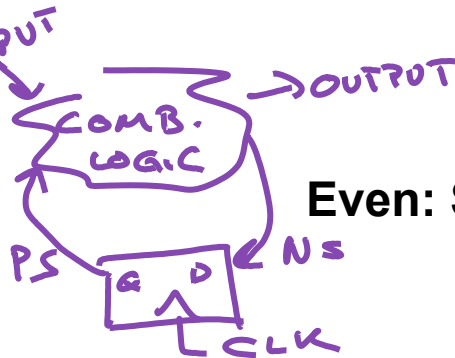


$OUTPUT = PS$   
 $NS = PS \oplus I$

Even: State = 0, Odd: State = 1
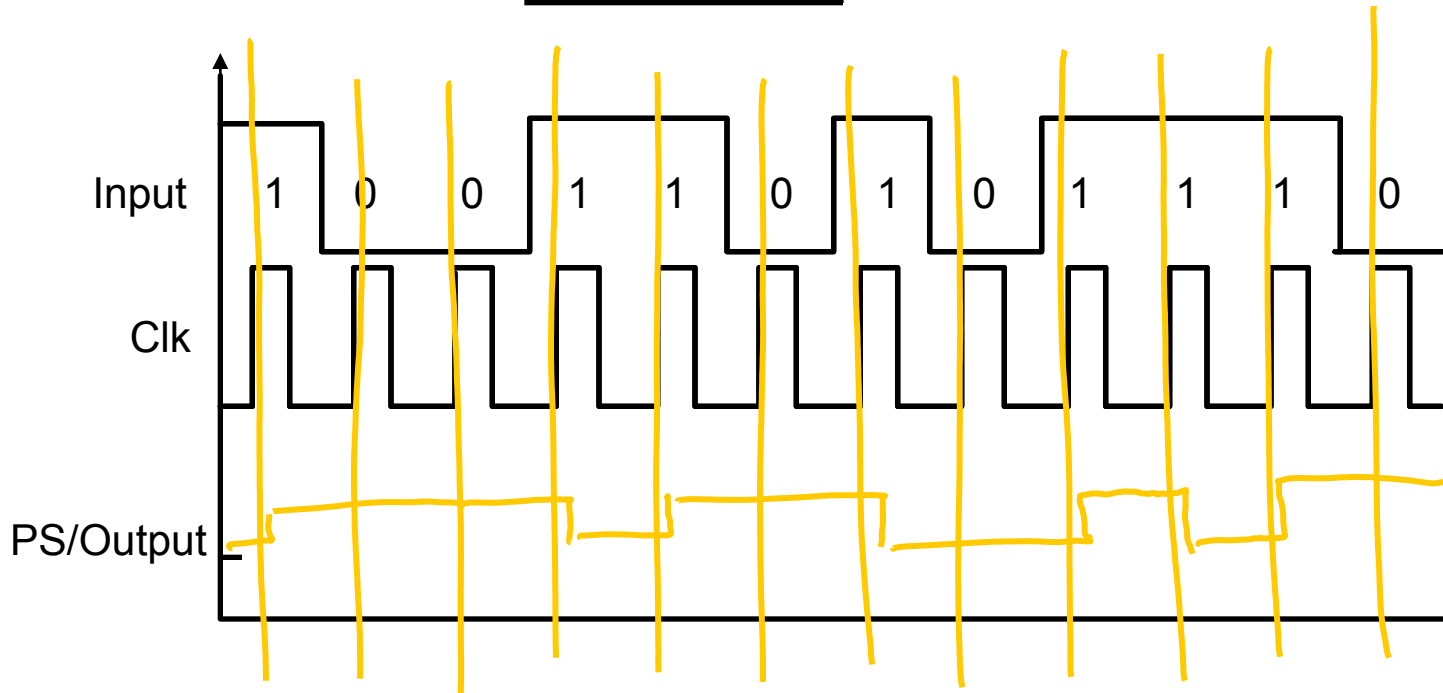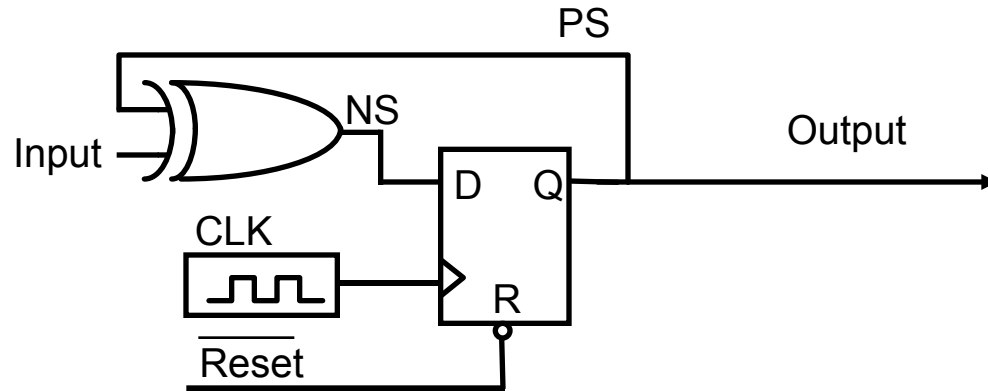
# Finite State Machine Example (cont.)


$$\text{NS} = \text{PS} \text{ xor Input}; \quad \text{OUT} = \text{PS}$$


 
# State Diagrams

---

- Graphical diagram of FSM behavior
- States represented by circles
- Transitions (actions) represented by arrows connecting states
- Labels on Transitions give  $\langle \text{triggering input pattern} \rangle / \langle \text{outputs} \rangle$ 
  - Note: We cover Mealy machines here; Moore machines put outputs on states, not transitions
- Finite State Machine: State Diagram with finite number of states



# FSM Design Process

---



- 1. Understand the problem
- 2. Draw the state diagram
- 3. Use state diagram to produce state table
- 4. Implement the combinational control logic

# Vending Machine Example

## ■ Vending Machine:

- Deliver package of gum after  $\geq 10$  cents deposited
- Single coin slot for dimes, nickels
- No change returned

## ■ State Diagram:

 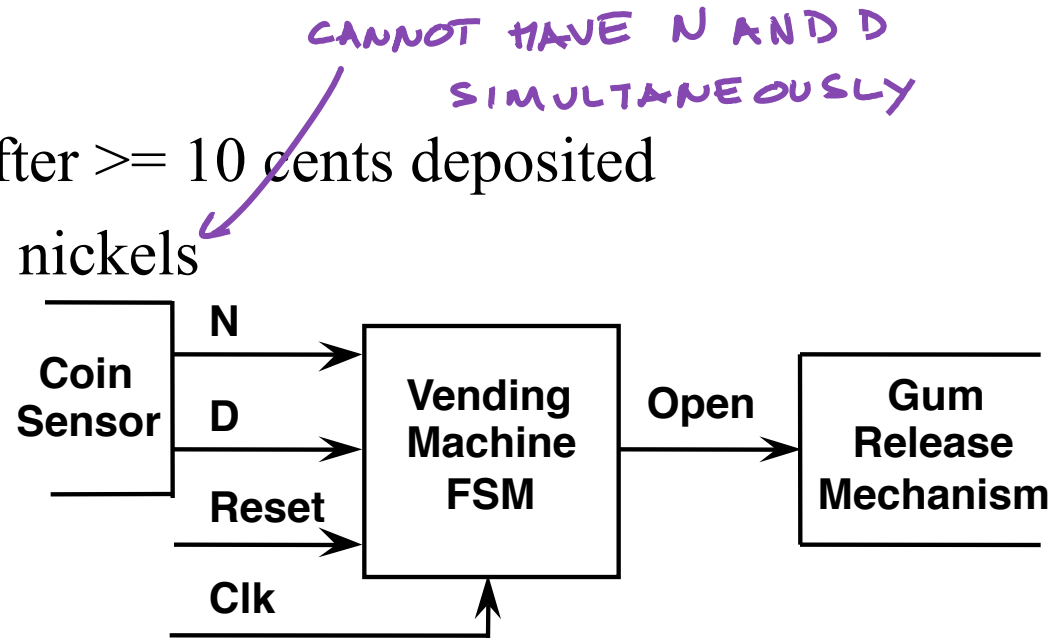


# Vending Machine Example (cont.)

## State Table:

PS	N	D	OPEN	NS
0	0	0	0	0
	0	1	1	0
	1	0	0	1
	1	1	0	1
1	0	0	0	1
	0	1	1	0
	1	0	1	0
	1	1	X	X

$$\Rightarrow \Rightarrow \text{OPEN} = D + PS \cdot N$$
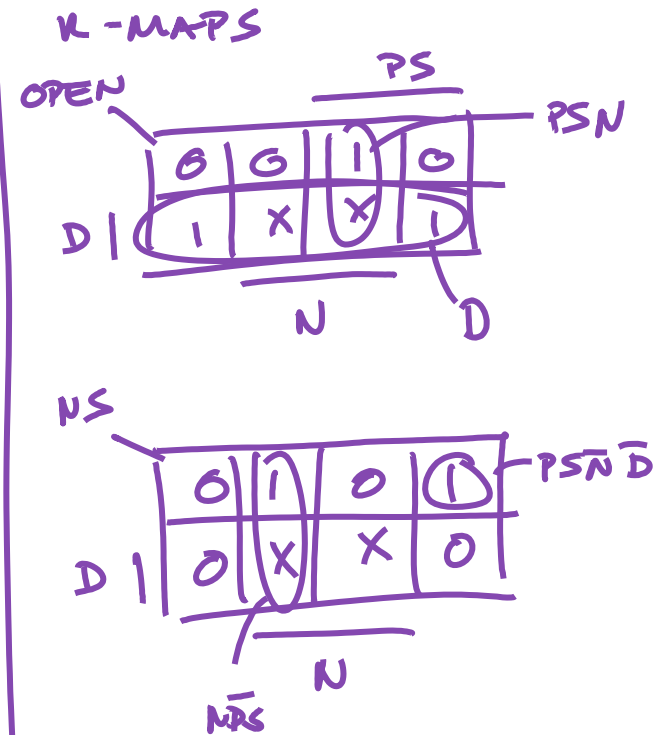
$$\text{NS} = \overline{N}PS + PS\overline{N}\overline{D}$$




FYI, NOT COVERED  
IN THIS CLASS



# Vending Machine Example (cont.)

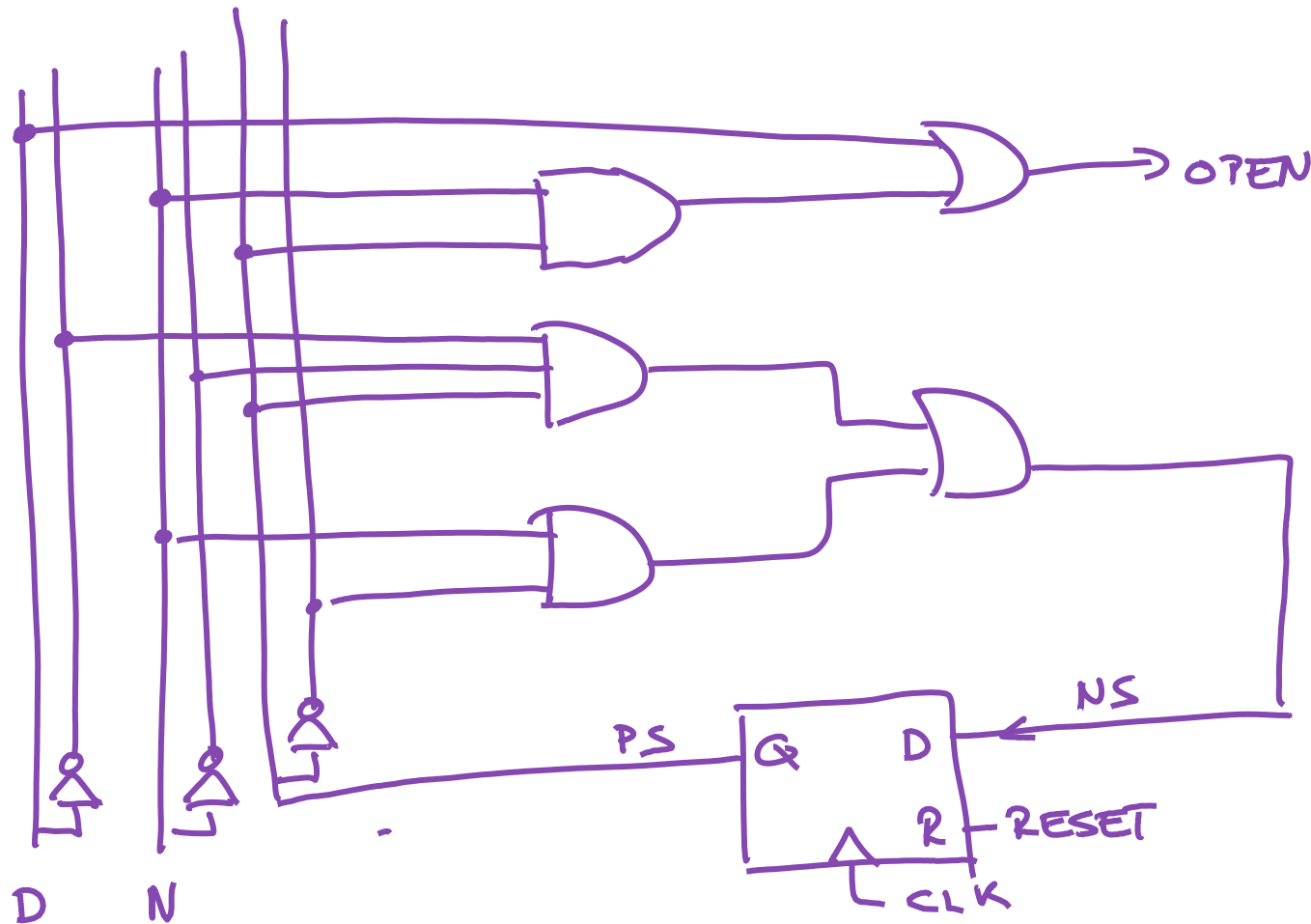
## Implementation:

$$OPEN = D + PSN \quad NS = N\bar{P}S + P S \bar{N} \bar{D}$$


 
# FSMs in Verilog - Declarations

```
module simple (clk, reset, w, out);  
  input      clk, reset, w;  
  output     out;  
  
  reg [1:0] ps; // Present State  
  reg [1:0] ns; // Next State
```



# FSMs in Verilog – Combinational Logic

```
parameter [1:0] A = 2'b00, B = 2'b01, C = 2'b10;
```

STATE ENCODING

```
// Next State Logic
```

```
always @(*) begin
```

```
  case (ps)
```

```
    A: if (w)  ns = B;
```

```
        else  ns = A;
```

```
    B: if (w)  ns = C;
```

```
        else  ns = A;
```

```
    C: if (w)  ns = C;
```

```
        else  ns = A;
```

```
    default:  ns = 2'bxx;
```

NEEDS!

```
  endcase
```

```
end
```


```
// Output Logic - could also be "always",
```

```
// or part of next-state logic.
```

```
assign out = (ps == C);
```

# State Diagram of FSM



---

 

# FSMs in Verilog – DFFs

```
// Sequential Logic (DFFs)
always @(posedge clk)
  if (reset)
    ps <= A;
  else
    ps <= ns;

endmodule
```

  

# FSM Testbench

---

```
module simple_testbench();  
    reg        clk, reset, w;  
    wire      out;
```

```
→ simple dut (.clk, .reset, .w, .out);
```

```
// Set up the clock.  
parameter CLOCK_PERIOD=100;
```

```
initial clk=1;
```



```
always begin  
    #(CLOCK_PERIOD/2);  
    clk = ~clk;  
end
```

# FSM Testbench (cont.)

---

```
// Design inputs. Each line is a clock cycle.
// ONLY USE THIS FORM for testbenches!!!
initial begin
    @ (posedge clk);
    reset <= 1; @ (posedge clk);
    reset <= 0; w <= 0; @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    w <= 1; @ (posedge clk);
    w <= 0; @ (posedge clk);
    w <= 1; @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    w <= 0; @ (posedge clk);
    @ (posedge clk);
    $stop; // End the simulation.
end
endmodule
```

# Testbench Waveforms

  



# String Recognizer Example

---

- Recognize the string: 101

- Input: 1 0 0 1 0 1 0 1 1 0 0 1 0

- Output:

- State Machine:

# String Recognizer Example (cont.)

---

- State Table:

= vs. <=

---

- = (“Blocking”) assign immediately
- <= (“Non-Blocking”) first eval all righthand sides, then do all assignments simultaneously.

```
module swap1();
  ...
  reg [3:0] val0, val1;

  always @(posedge clk) begin
    if (swap) begin
      val0=val1;
      val1=val0;
    end
    out=val1;
  end
endmodule
```

```
module swap2();
  ...
  reg [3:0] val0, val1;

  always @(posedge clk) begin
    if (swap) begin
      val0<=val1;
      val1<=val0;
    end
    out<=val1;
  end
endmodule
```

# = vs. <= in practice

---

- = in combinational logic: always @\*
- <= in sequential, ps<=ns: always @(posedge clk)
- NEVER mix in one always block!
- Each variable written in only one always block

```
// Output logic
always @(*) begin
    out = (ps == A);

// Next State Logic
always @(*) begin
    case (ps)
        A: if (w)    ns = B;
           else    ns = A;
        B: if (w)    ns = C;
           else    ns = A;
        C: if (w)    ns = C;
           else    ns = A;
        default: ns = 2'bxx;
    endcase
end
```


```
// Sequential Logic
always @(posedge clk) begin
    if (reset)
        ps <= A;
    else
        ps <= ns;
end
```

# Subdividing FSMs

---

- Some problems best solved with multiple pieces
- Psychic Tester:
  - Machine generates pattern of 4 values (on or off)
  - If user guesses 8 patterns in a row, they're psychic

## ■ States?

 

# Subdividing FSMs (cont.)

## ■ Pieces?

