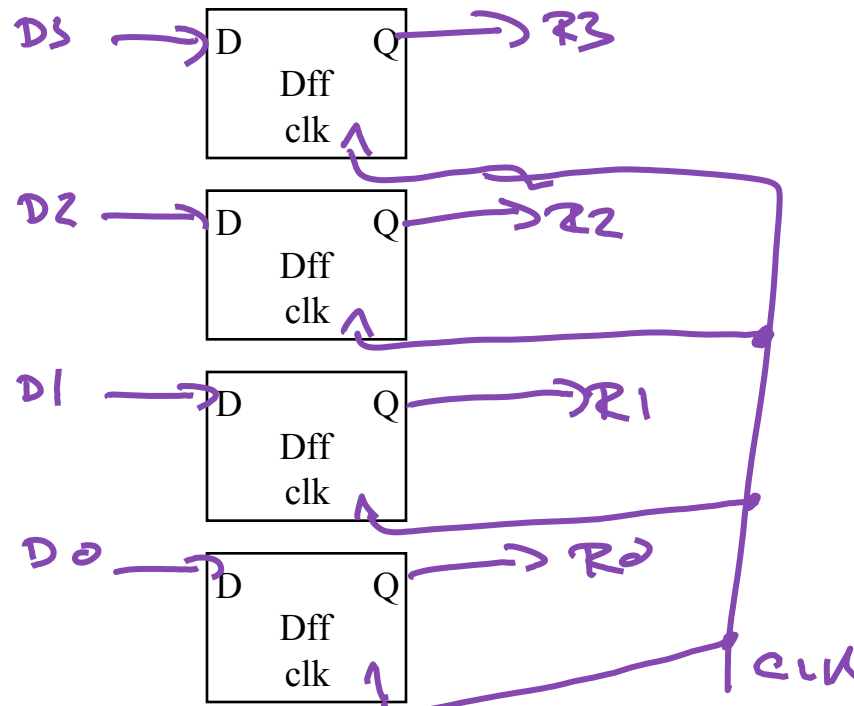


Registers



- Readings: 5.8-5.9.3
- Storage unit. Can hold an n-bit value
- Composed of a group of n flip-flops
 - Each flip-flop stores 1 bit of information

D₃ D₂ D₁ D₀




Shift Register

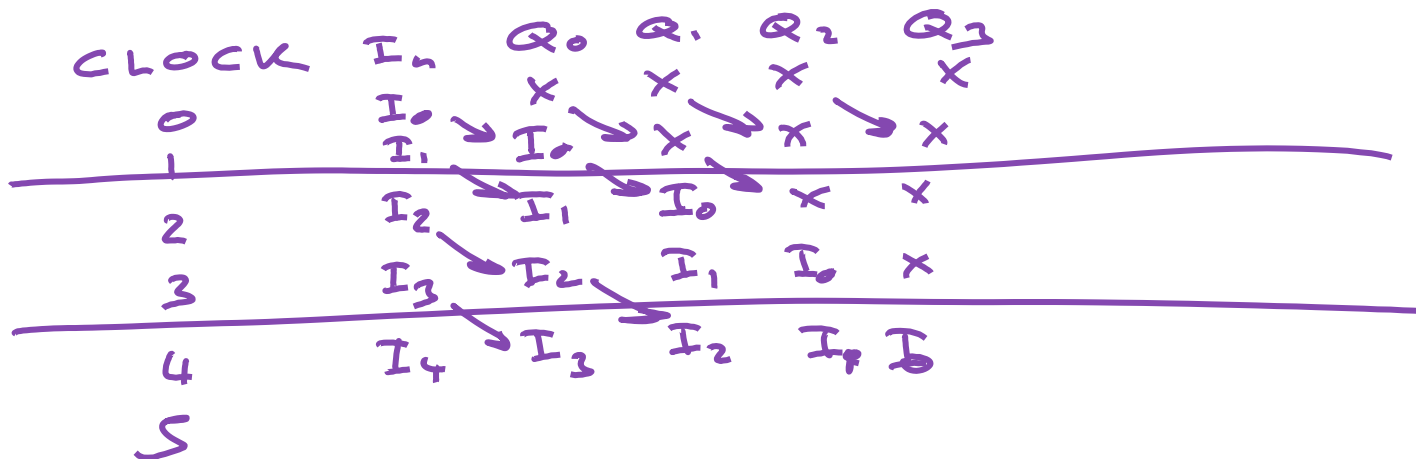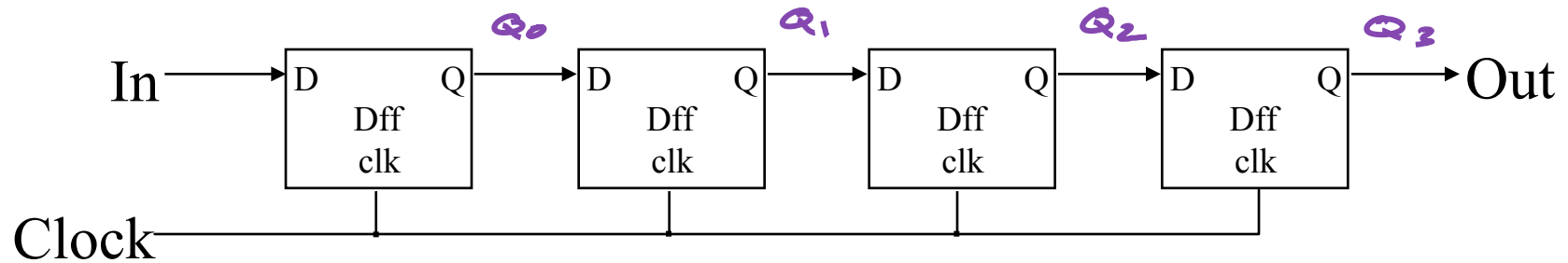- Register that shifts the binary values in one or both directions




Transfer of Data

 - 2 modes of communication: Parallel vs. Serial
 - Parallel: all bits transferred at the same time
 - Serial: one bit transferred at a time
- Shift register can be used for serial transfer




Shift Register w/Parallel Load

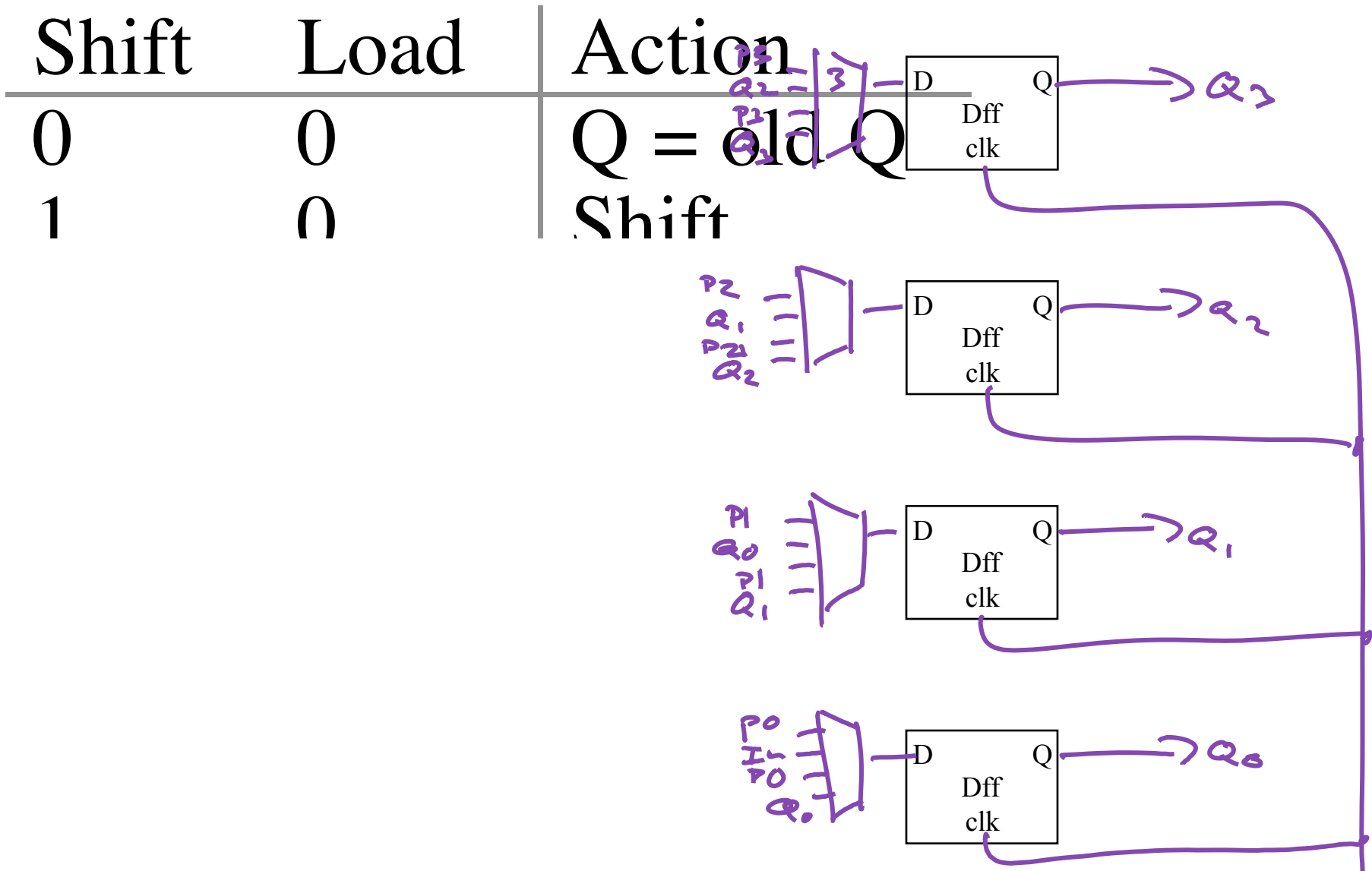


Conversion between Parallel & Serial

COMPUTER

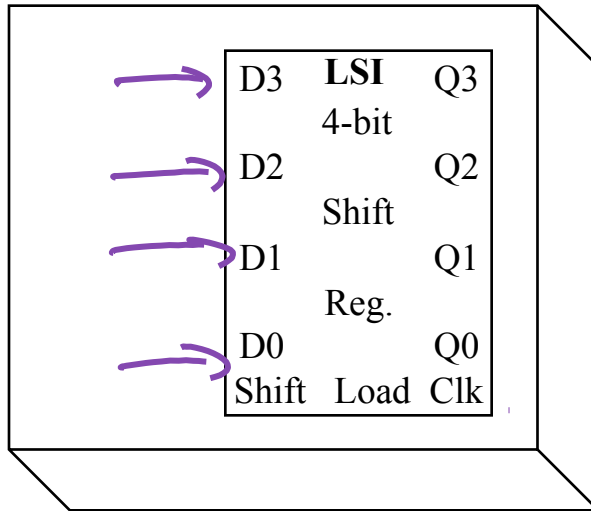

PRINTER


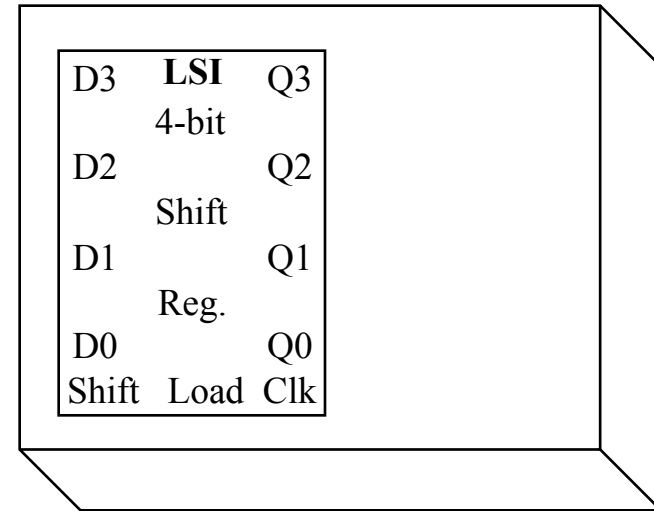


CLOCK	MODE	Q_0	Q_1	Q_2	Q_3
0	LOAD	X	X	X	X
1	SHIFT	D_0	D_1	D_2	D_3
2	SHIFT	X	D_0	D_1	D_2
3	SHIFT	X	X	D_0	D_1
4	LOAD	X	X	X	D_0
5	SHIFT	D_0	D_1	D_2	D_3
6	SHIFT				

MODE	Q_0	Q_1	Q_2	Q_3
	X	X	X	X
SHIFT	X	X	X	X
SHIFT	D_2	X	X	X
SHIFT	D_2	D_2	X	X
SHIFT	D_1	D_2	D_3	X
SHIFT	D_0	D_1	D_2	D_3

Counters

  - A reg. that goes through a specific state sequence
- *n-bit Binary Counter*: counts from 0 to 2^N-1 in binary
- *Up Counter*: Binary value increases by 1
- *Down Counter*: Binary value decreases by 1
- 3-bit binary up counter state diagram:



$$NS_0 = \overline{PS_0}$$

$$NS_1 = PS_1 \oplus PS_0$$


$$NS_2 = PS_2 \oplus PS_1 \oplus PS_0$$

$$NS_i = PS_i \oplus (PS_{i-1} \cdot \dots \cdot PS_0)$$

Binary Up-Counter Imp.

Complex Binary Counter

Load	Count	Action
0	0	$Q = \text{old } Q$
0	1	Up Count

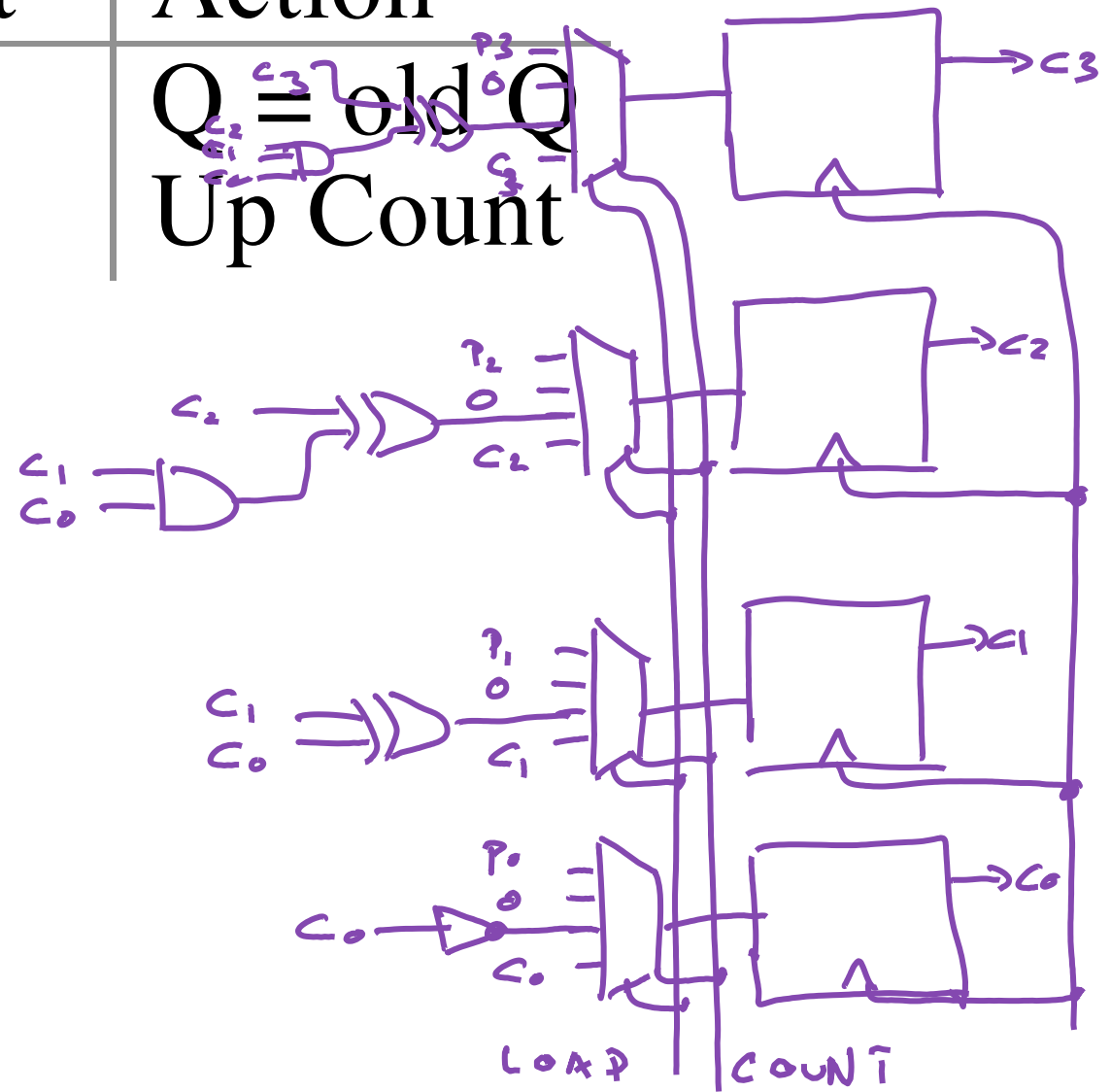

Arbitrary Sequence Counters

- Design a 3-bit count that goes through the sequence
000->010->100->101->111->110->001->011->000->...

⇒ STATE DIAGRAM ⇒ STATE TABLE

⇒ SOLVE

Counters in Verilog

```
module upcounter #(parameter WIDTH=8)
  (out, incr, reset, clk);

  output reg [WIDTH-1:0] out;
  input                incr, reset, clk;
```


```
  always @(posedg clk) begin
    if (reset)
      out <= 0;
    else if (incr)
      out <= out + 1;
    else
      out <= out;
  end
```

```
endmodule
```

Memory

- Need method for storing large amounts of data
 - Computer programs, data, pictures, etc.


Address	Data
000000	00111110
000001	01101011
000010	01011101
000011	01100011
000100	00111110
000101	00000000
000110	11111111

 

- RAM: Random Access Memory, Read/Write
- ROM: Read-only Memory

WRITE = 1, STORING
WRITE = 0, READING

8x4 RAM



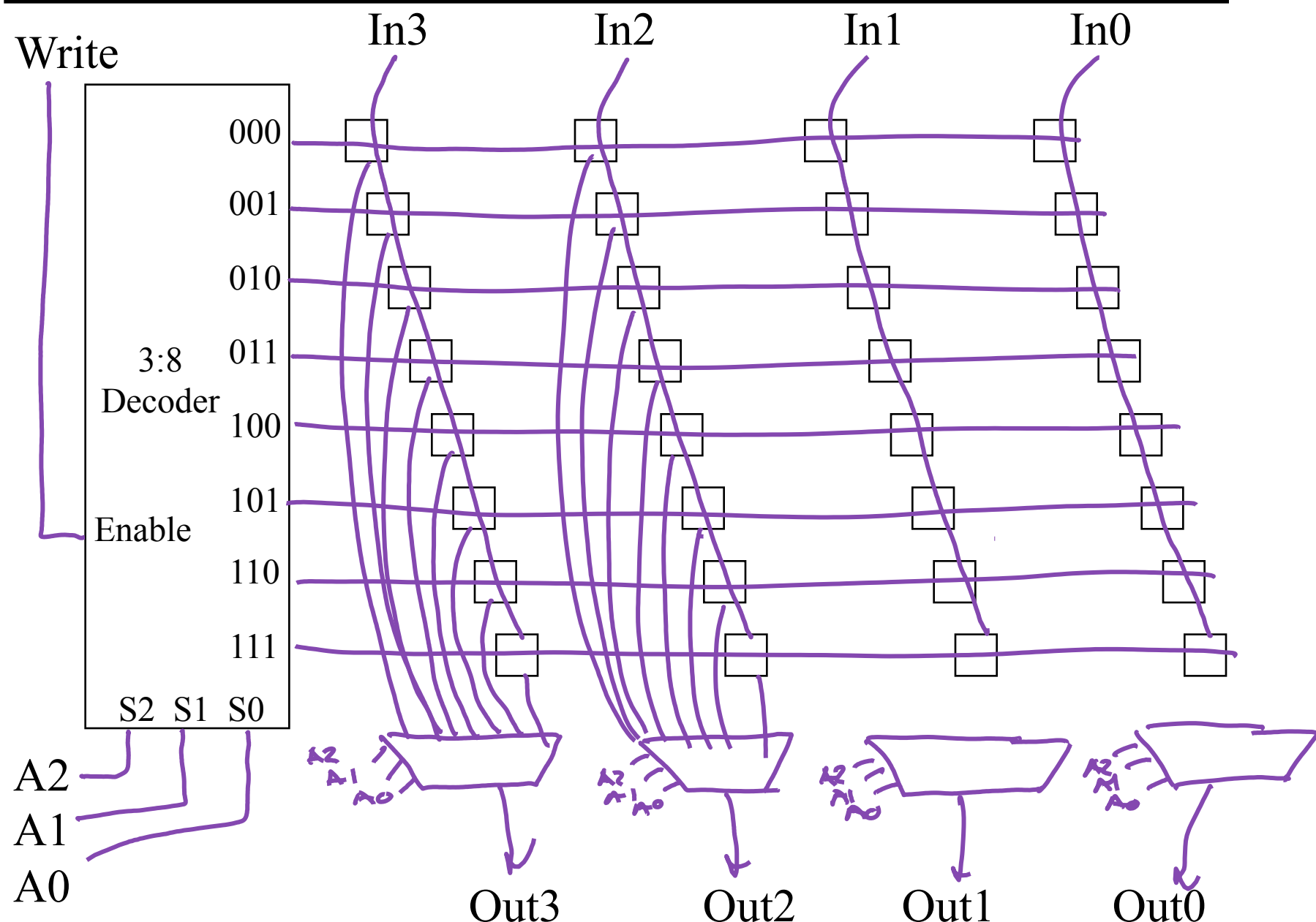


RAM Cell

■ Requirements:

- Store one bit of data
- Change data based on input when row is selected


SR	Q
00	HOLD
01	0
10	1
11	FORBIDDEN

   

W	ROW	R	S	Q
0	0	0	0	HOLD
0	1	0	1	0
1	0	0	0	HOLD
1	1	1	0	1

RAM example

 - Use a memory to do a programmable 32-picture animation on a 7-segment display



Verilog Memories

```
module memory16x6 (data_out, data_in, addr, we, clk);
    output reg [5:0] data_out;
    input [5:0] data_in;
    input [3:0] addr;
    input we, clk;

    reg [5:0] mem [15:0];

    always @(*)
        data_out = mem[addr];

    always @(posedge clk)
        if (we)
            mem[addr] <= data_in;

endmodule
```