

# CSE 369 Autumn 2015 – Quiz 1 (3 November)


Name:

---

<b>Problem</b>	<b>Max Score</b>	<b>Score</b>
1	10	
2	10	
3	10	
<b>TOTAL</b>	<b>30</b>	
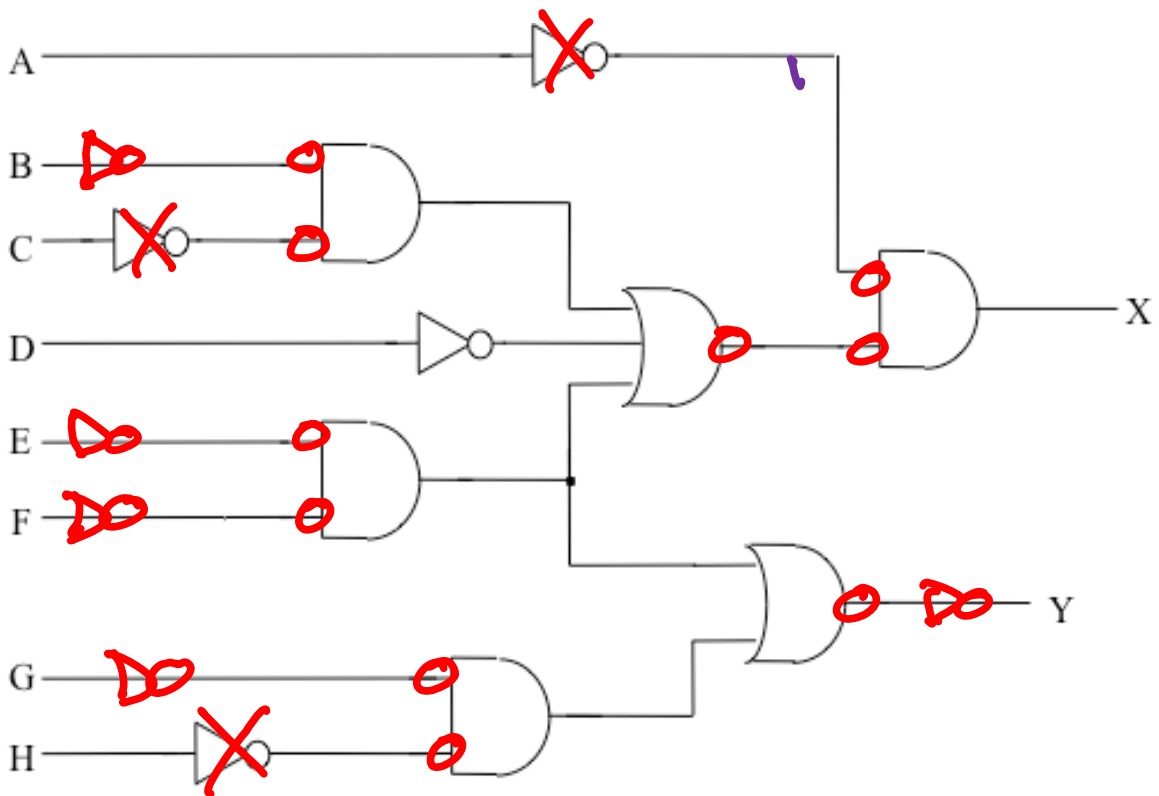
### 1. Logic gates (10 points)

Modify the following circuit diagram such that the final circuit uses only NOR and NOT gates. Use the minimal necessary number of additional gates.



## 2. Verilog (10 points)

Briefly explain what this module does. Describe the overall function in one sentence and add 1-2 brief comments into the code to explain salient features.


```
module Unknown (C, D, E, A, B);  
  input  A, B;  
  output C, D, E;  
  
  assign #5 C = (A & B) | (~A & ~B);  
  assign #3 D = (A & ~B);  
  assign #3 E = (~A & B);  
endmodule
```

TRUE IF  $A = B$   
 $A > B$   
 $A < B$

"COMPARATOR" CIRCUIT
 
### 3. Storage element (10 points)

Create the truth table for the storage element shown below. What is the value of Q for every combination of the inputs R and S? Briefly explain your reasoning.



IF ONE INPUT TO  
A NAND GATE IS "0"  
THE OUTPUT IS ALWAYS  
IF BOTH INPUTS ARE "1"  
ASSUME  $Q=0$  (OR  $Q=1$ ),  
THEN CHECK FOR  
CONSISTENCY.

R	S	Q	$\bar{Q}$
0	0	1	1
0	1	0	1
1	0	1	0
1	1	Q	$\bar{Q}$

(SR-LATCH)