

# Intro to Digital Design

## FSM Design, MUXes, Adders

**Instructor:** Justin Hsia

**Teaching Assistants:**

Emilio Alcantara

Eujean Lee

Naoto Uemura

Pedro Amarante

Wen Li

# Relevant Course Information

- ❖ Lab 6 – Connecting multiple FSMs in Tug of War game
  - *Bigger* step up in difficulty from Lab 5
  - Putting together complex system – interconnections!
  - Bonus points for smaller resource usage

# Clock Divider (not for simulation)

❖ Why/how does this work?

CLOCK\_50: 50 MHz clock on your FPGA

→ use `divided_clocks [#]` everywhere else in your system

```
// divided_clocks[0]=25MHz, [1]=12.5Mhz, ...
module clock_divider (clock, divided_clocks);
  input logic clock;
  output logic [31:0] divided_clocks;


  initial
    divided_clocks = 0;

  always_ff @(posedge clock)
    divided_clocks <= divided_clocks + 1;

endmodule // clock_divider
```

↑ 32 slower "clocks"

 changes every fourth trigger  
changes every other trigger  
changes every clock trigger




divided\_clocks = 32'b 0...000  
32'b 0...001  
0...010  
0...011  
0...100


# Outline

- ❖ **FSM Design**
- ❖ Multiplexors
- ❖ Adders

# FSM Design Process

- 1) Understand the problem 
- 2) Draw the state diagram  
*311 knowledge*
- 3) Use state diagram to produce state table  
*read off transitions*
- 4) Implement the combinational control logic

*CL + SL*  
*gates + registers*

 


# Practice: String Recognizer FSM

- ① Draw the FSM
- ② Truth Table
- ③ Simplify Logic
- ④ Circuit Diagram

❖ Recognize the string 101 with the following behavior

- Input: 1 0 0 1 0 1 0 1 1 0 0 1 0
- Output: 0 0 0 0 0 1 0 1 0 0 0 0 0

❖ State diagram to implementation:

 

③

		PS	00	01	11	10
In	0	0	1	X	0	
	1	0	0	X	0	

$NS_1 = \bar{In} \cdot PS_0$

		PS	00	01	11	10
In	0	0	0	X	0	
	1	1	1	X	1	


$NS_0 = In$

		PS	00	01	11	10
In	0	0	0	X	0	
	1	0	0	X	1	

$Out = In \cdot PS_1$

②

PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	10	0
01	1	00	1
10	0	10	0
10	1	00	1
11	0	X	X
11	1	X	X

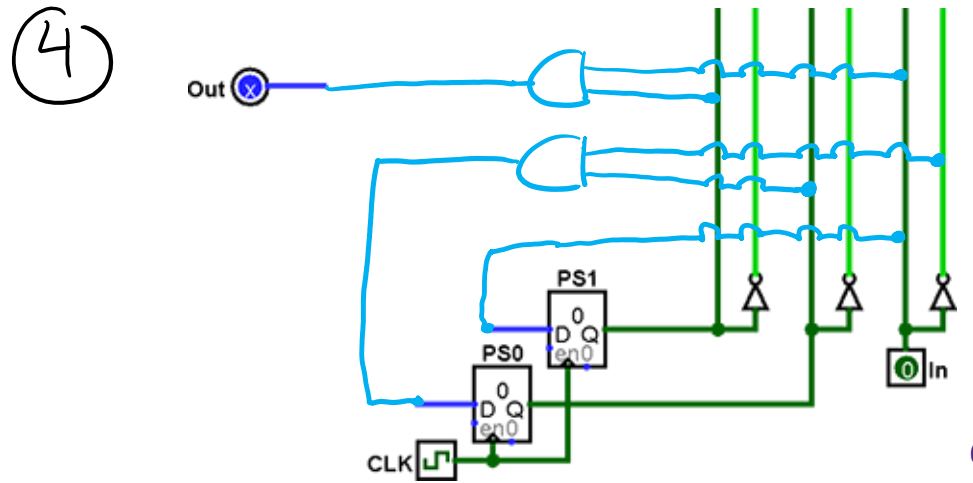

# HDL Organization

- ❖ Most problems are best solved with multiple pieces – how to best organize your system and code?
- ❖ Everything is computed in parallel
  - We use routing elements (next lecture) to select between (or ignore) multiple outcomes/parts
  - This is why we use block diagrams and waveforms
- ❖ A module is not a *function*, it is closest to a *class*
  - Something that you *instantiate*, not something that you *call* – hardware cannot appear and disappear spontaneously
  - Should treat modules as *resource managers* rather than temporary helpers
    - This can include having internal modules

# Block Diagrams

- ❖ Block diagrams are the basic design tool for digital logic.
  - The diagram itself is a module → **inputs and outputs shown and connected**
  - Major components are represented by blocks (“black boxes”) with their internals abstracted away → **each block becomes its own module**
  - All ports for each block should be shown and labeled and connected to the appropriate part(s) of the rest of the system → **sets your port connections**
  - Wires and other basic building blocks can be added/shown as needed
- ❖ From [Wikipedia](#): The goal is to “[end] in block diagrams detailed enough that each individual block can be easily implemented.”
  - For designs that involve multiple modules, should always create your block diagram *before* coding anything!



# Subdividing FSMs Example


## ❖ “Psychic Tester”

- Machine generates a 4-bit pattern
- User tries to guess 8 patterns in a row to be deemed psychic

$2^4 = 16$  patterns

0-7 correct guesses so far (8 total)

## ❖ States?

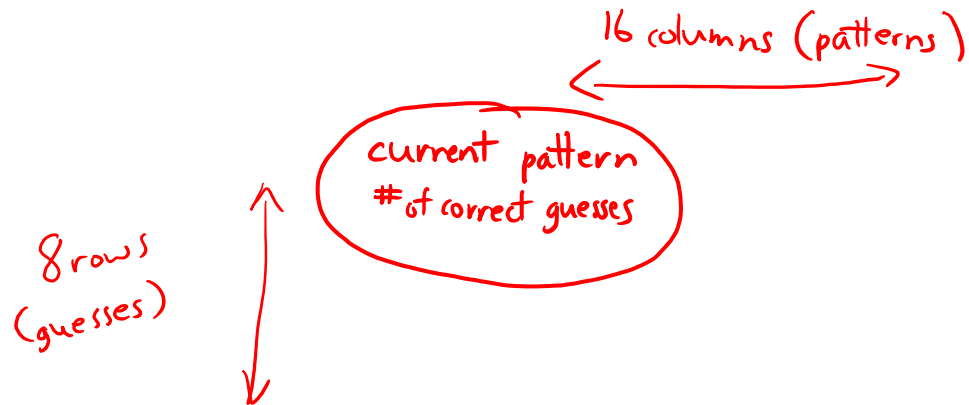


$\approx 128$  states total

# Example: Plan First with Block Diagram
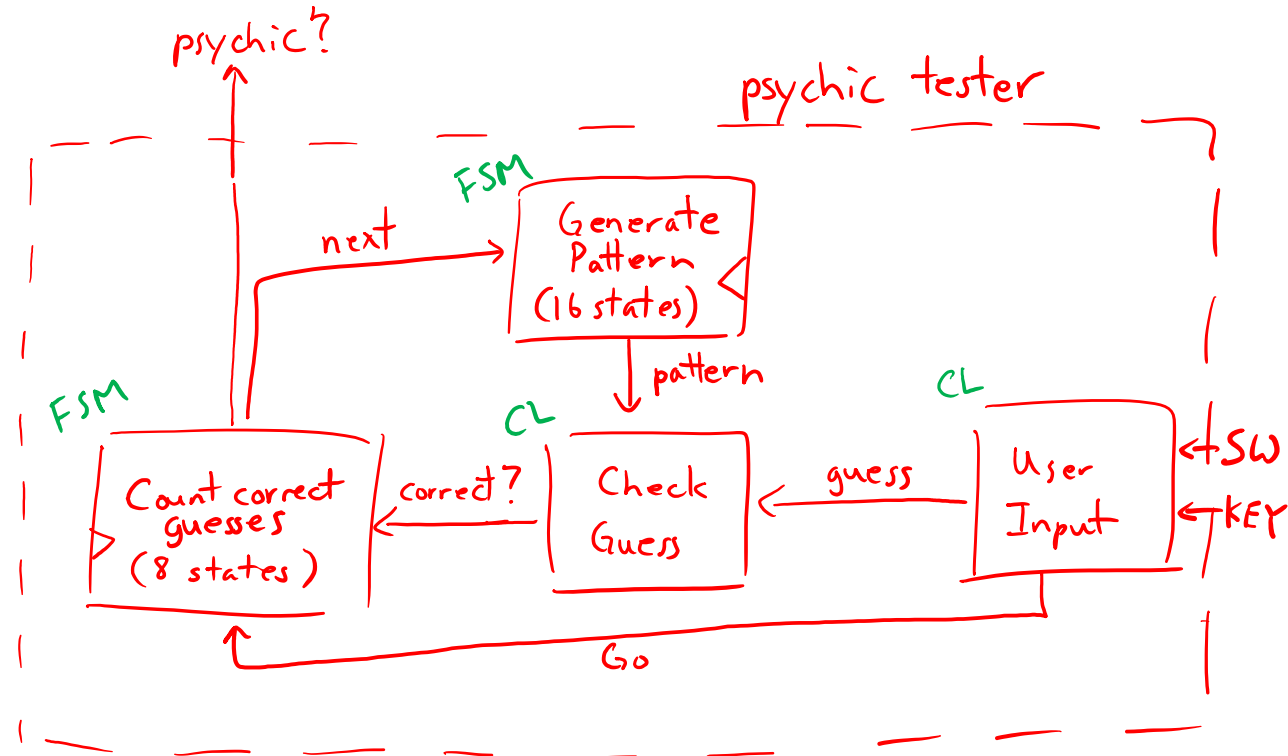
## ❖ Pieces?

- Generate/pick pattern
- User input (guess)
- Check guess
- Count correct guesses



# Example: Blocks → Modules

## ❖ Pieces?

- Generate/pick pattern
  - `module genPatt (pattern, next, clock);`
- User input (guess)
  - `module userIn (guess, enable, KEY);`
- Check guess
  - `module checkGuess (correct, guess, pattern);`
- Count correct guesses
  - `module countRight (psychic, next, correct, enable, clock);`

# Example: Implementation & Testing

- 1) Create individual submodules
- 2) Create submodules test benches – test as usual
  - CL – run through all input combinations
  - SL – take every transition that you care about
- 3) Create top-level module
  - Create instance of each submodule
  - Create wires/nets to connect signals between submodules, inputs, and outputs
- 4) Create top-level test bench
  - Goal is to check the interconnections between submodules – does input/state change in one submodule trigger the expected change in other submodules?

# Outline

- ❖ FSM Design
- ❖ **Multiplexors**
- ❖ Adders

# Data Multiplexor


- ❖ Multiplexor (“MUX”) is a *selector*
  - Direct one of many ( $N = 2^s$ )  $n$ -bit wide inputs onto output
  - Called a  $n$ -bit,  $N$ -to-1 MUX

$s = \lceil \log_2 N \rceil$

bus widths  $\uparrow$  possible selections

- ❖ Example:  $n$ -bit 2-to-1 MUX

 
- Input  $S$  ( $s$  bits wide) selects between two inputs of  $n$  bits each



This input is passed to output if selector bits match shown value

# Review: Implementing a 1-bit 2-to-1 MUX

❖ Schematic:

 


❖ Boolean Algebra:

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

❖ Truth Table:


s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

❖ Circuit Diagram:

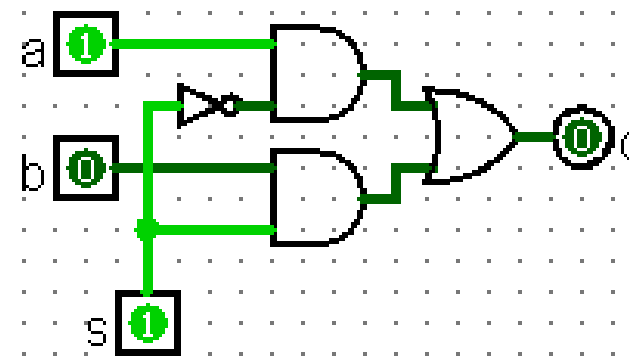

# 1-bit 4-to-1 MUX

## ❖ Schematic:

 

## ❖ Truth Table: How many rows? *6 inputs → 2<sup>6</sup> rows*


## ❖ Boolean Expression:

$$e = \bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$$



 
# 1-bit 4-to-1 MUX

- ❖ Can we leverage what we've previously built?
  - Alternative hierarchical approach:


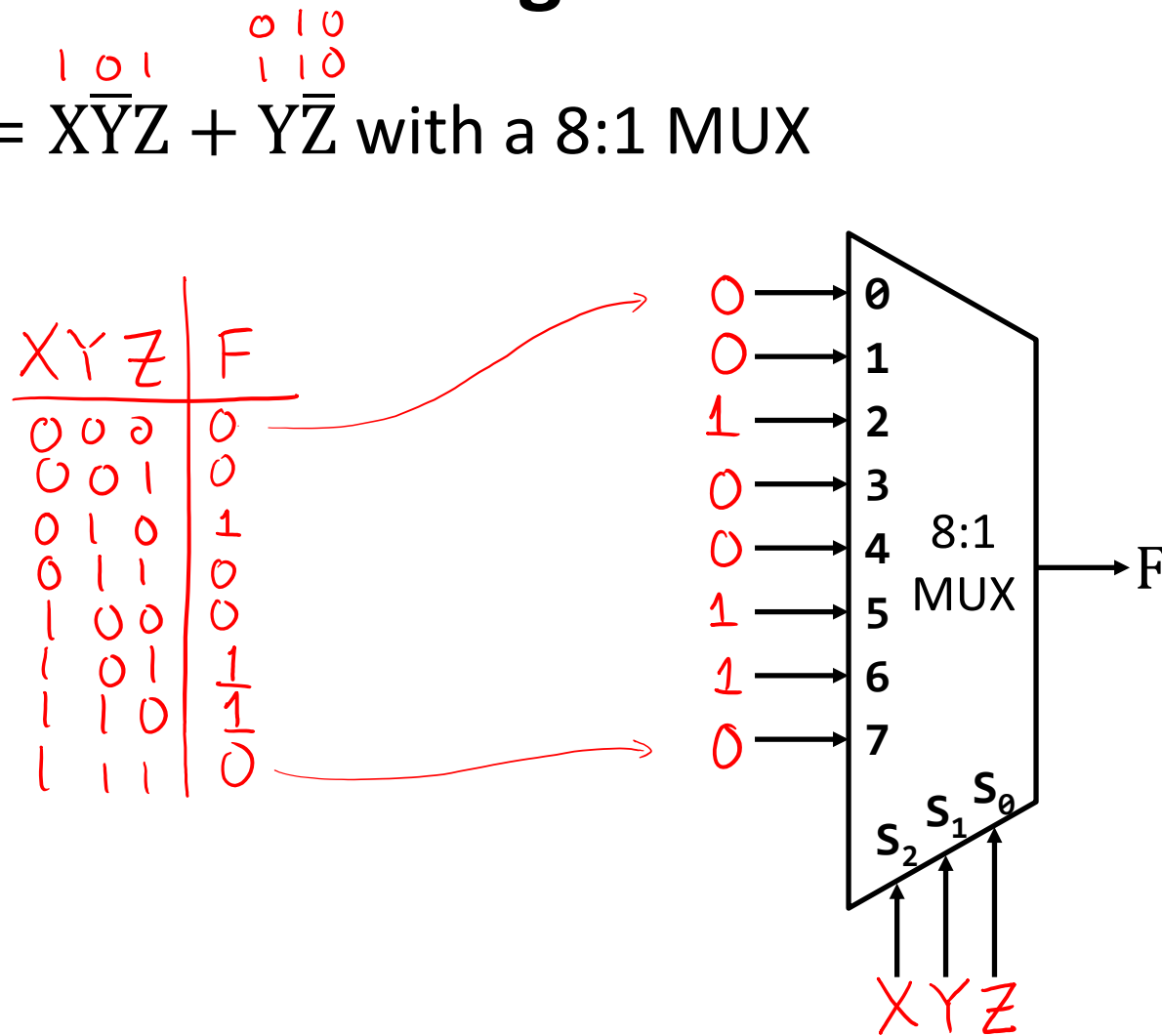
# Multiplexers in General Logic

- ❖ Implement  $F = X\bar{Y}Z + Y\bar{Z}$  with a 8:1 MUX



# Technology Break

# Outline


- ❖ FSM Design
- ❖ Multiplexors
- ❖ **Adders**

# Review: Unsigned Integers

- ❖ Unsigned values follow the standard base 2 system
  - $b_7b_6b_5b_4b_3b_2b_1b_0 = b_72^7 + b_62^6 + \dots + b_12^1 + b_02^0$
- ❖ In  $n$  bits, represent integers 0 to  $2^n-1$
- ❖ Add and subtract using the normal “carry” and “borrow” rules, just in binary

	<i>Carry</i>		
	<i>1 1 1</i>		
63	00111111	64	01000000
+ 8	+00001000	- 8	-00001000
71	01000111	56	00111000

# Review: Two's Complement (Signed)

 


## ❖ Properties:

- In  $n$  bits, represent integers  $-2^{n-1}$  to  $2^{n-1} - 1$
- Positive number encodings match unsigned numbers
- Single zero (encoding = all zeros)

## ❖ Negation procedure:

- Take the bitwise complement and then add one

$$(\sim x + 1 == -x)$$

 

# Addition and Subtraction in Hardware

❖ The same bit manipulations work for both unsigned and two's complement numbers!

■ Perform subtraction via adding the negated 2<sup>nd</sup> operand:


$$A - B = A + (-B) = A + (\sim B) + 1$$

❖ 4-bit examples:

	Two's	Un
0 0 1 0	+2	2
+ 1 1 0 0	-4	12
<u>1 1 1 0</u>	-2	14
0 1 1 0	+6	6
<del>- 0 0 1 0</del>	<del>+2</del>	<del>2</del>
<u>+ 1 1 0 1</u>		
<u>0 1 0 0</u>	+4	4

	Two's	Un
1 0 0 0	-8	8
+ 0 1 0 0	+4	4
<u>1 1 0 0</u>	-4	12
1 1 1 1	-1	15
<del>- 1 1 1 0</del>	<del>-2</del>	<del>14</del>
<u>+ 0 0 0 1</u>		
<u>0 0 0 1</u>	+1	1


# Half Adder (1 bit)

 

Carry =  $a_0 b_0$   
 Sum =  $a_0 \oplus b_0$


Carry-out bit

$a_0$	$b_0$	$c_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 



# Full Adder (1 bit)

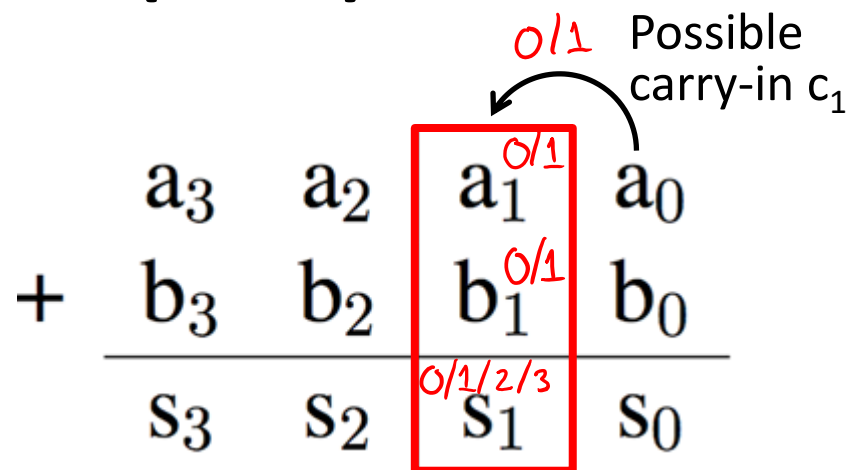


$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i)$$

$$= a_i b_i + a_i c_i + b_i c_i$$


Carry-in  $c_i$       Carry-out  $c_{i+1}$

$c_i$	$a_i$	$b_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 
 
# Multi-Bit Adder (N bits)

- ❖ Chain 1-bit adders by connecting  $\text{CarryOut}_i$  to  $\text{CarryIn}_{i+1}$ :




# Subtraction?

❖ Can we use our multi-bit adder to do subtraction?


■ Flip the bits and add 1?

- $X \oplus 1 = \bar{X}$
- CarryIn<sub>0</sub> (using full adder in all positions)

$x \& 0 = 0$   
 $x \& 1 = x$   
 $x | 0 = x$   
 $x | 1 = 1$   
 $x \wedge 0 = x$   
 $x \wedge 1 = \bar{x}$

 

# Multi-bit Adder/Subtractor

 

# Detecting Arithmetic Overflow

- ❖ **Overflow:** When a calculation produces a result that can't be represented in the current encoding scheme
  - Integer range limited by fixed width
  - Can occur in both the positive and negative directions
- ❖ **Unsigned Overflow**
  - Result of add/sub is  $> U_{Max}$  or  $< U_{min}$   
 $0b11\dots 1$        $0b00\dots 0$
- ❖ **Signed Overflow**
  - Result of add/sub is  $> T_{Max}$  or  $< T_{Min}$   
 $0b01\dots 1$        $0b10\dots 0$
  - $(+) + (+) = (-)$  or  $(-) + (-) = (+)$

# Signed Overflow Examples

0 1 0 1	+5	
+ 0 0 1 1	+3	
1 0 0 0	-8	overflow

$\underbrace{\quad\quad\quad}_X \quad \underbrace{\quad\quad\quad}_\sim$

1 0 0 1	-7	
+ 1 1 1 0	-2	
0 1 1 1	+7	overflow

$\underbrace{\quad\quad\quad}_\sim \quad \underbrace{\quad\quad\quad}_X$

sign bit

0 1 0 1	+5	
+ 0 0 1 0	+2	
0 1 1 1	7	


$\underbrace{\quad\quad\quad}_X \quad \underbrace{\quad\quad\quad}_X$

1 1 0 0	-4	
+ 0 1 0 0	4	
0 0 0 0	0	

$\underbrace{\quad\quad\quad}_\sim \quad \underbrace{\quad\quad\quad}_\sim$

$$\text{overflow} = C_n \wedge C_{n-1}$$

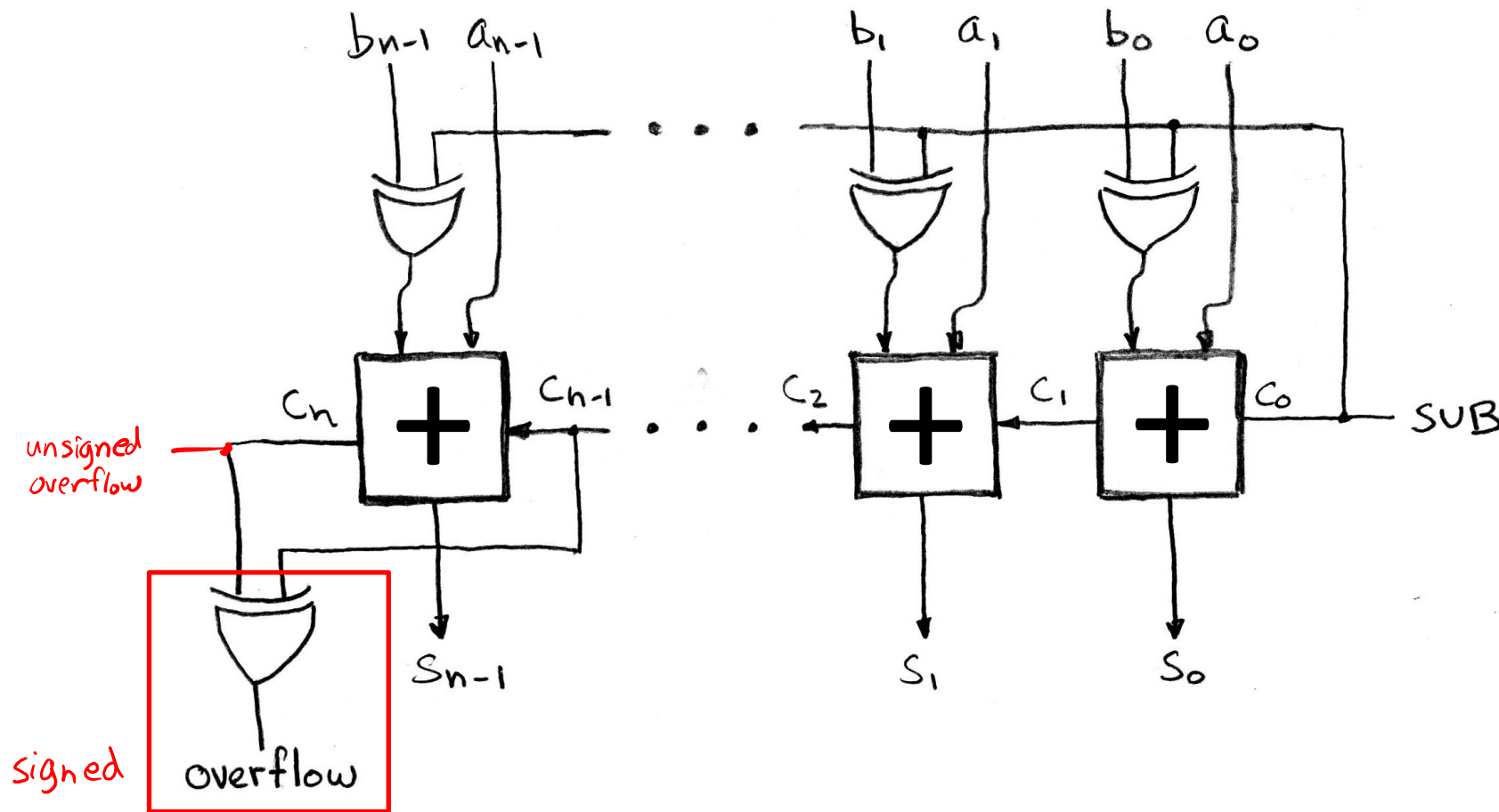
# Multi-bit Adder/Subtractor with Overflow



# Arithmetic and Logic Unit (ALU)

- ❖ Processors contain a special logic block called the “Arithmetic and Logic Unit” (ALU)
  - Here’s an easy one that does ADD, SUB, bitwise AND, and bitwise OR (for 32-bit numbers)

- ❖ **Schematic:**

 


when  $S=00$ ,  $R = A+B$   
when  $S=01$ ,  $R = A-B$   
when  $S=10$ ,  $R = A \& B$   
when  $S=11$ ,  $R = A | B$

*"arbitrary" choice,  
but affects  
implementation*



# Simple ALU Schematic

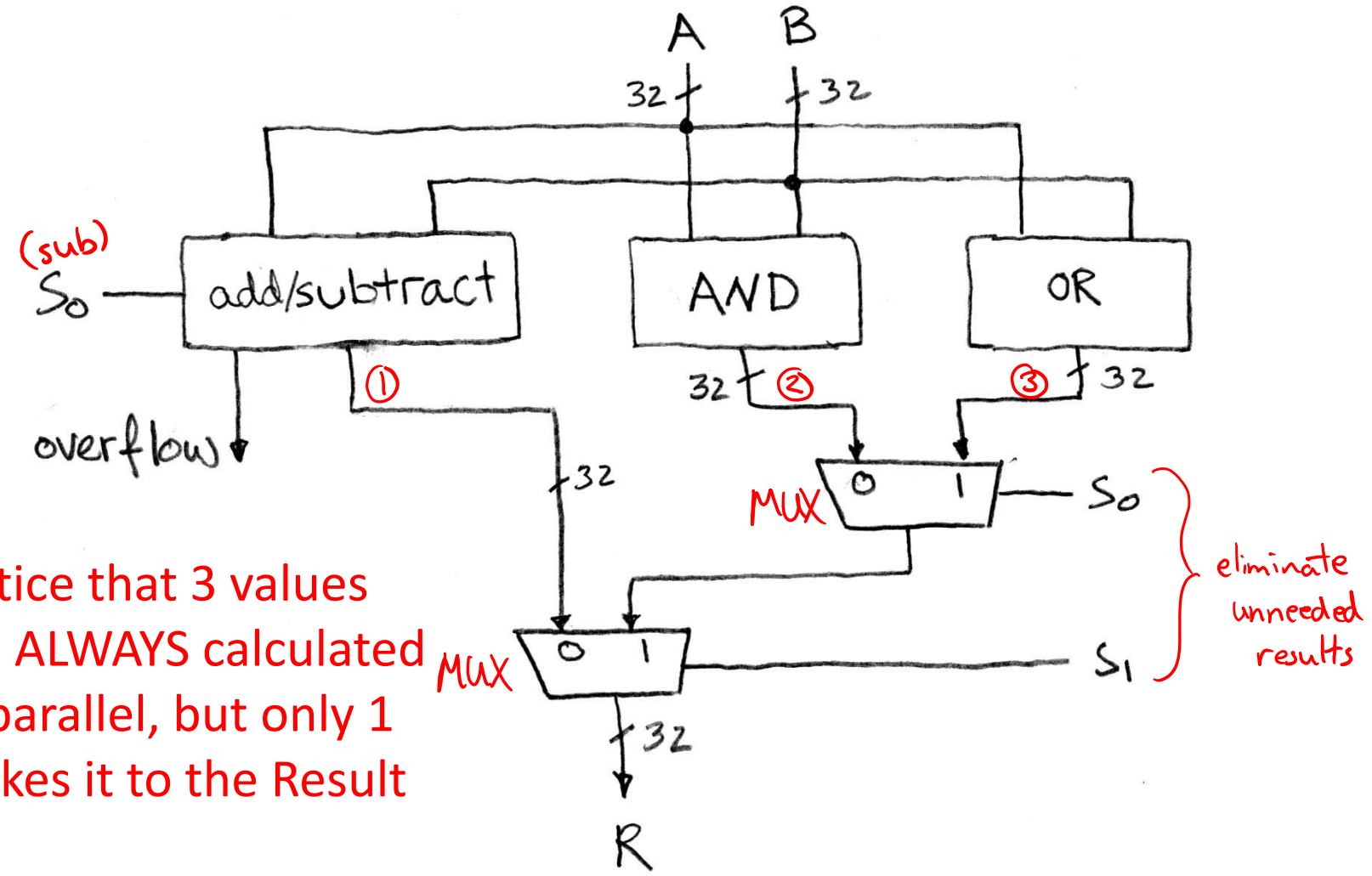

Notice that 3 values are ALWAYS calculated in parallel, but only 1 makes it to the Result

eliminate unneeded results

# 1-bit Adders in Verilog

## ❖ What's wrong with this?

- Truncation!

```
module halfadd1 (s, a, b);  
    output logic s;  
    input logic a, b;  
    always_comb begin  
        s = a + b;  
    end  
endmodule
```

*single bit* (handwritten red text with arrows pointing to 's' and 'a')

## ❖ Fixed:

- Use of {sig, ..., sig} for *concatenation*

```
module halfadd2 (c, s, a, b);  
    output logic c, s;  
    input logic a, b;  
  
    always_comb begin  
        {c, s} = a + b;  
    end  
endmodule
```

*could have been:*  
 $s = a \wedge b;$   
 $c = a \& b;$


*order matters!* (handwritten red text with arrow pointing to '{c, s}' in the code)

# Ripple-Carry Adder in Verilog

```
module fulladd (cout, s, cin, a, b);  
    output logic cout, s;  
    input  logic cin, a, b;  
  
    always_comb begin  
        {cout, s} = cin + a + b;  
    end  
endmodule
```
 
## ❖ Chain full adders?

```
module add2 (cout, s, cin, a, b);  
    output logic cout; output logic [1:0] s;  
    input  logic cin;  input  logic [1:0] a, b;  
    logic  c1;  
  
    fulladd b1 (cout, s[1], c1, a[1], b[1]);  
    fulladd b0 (c1, s[0], cin, a[0], b[0]);  
endmodule
```



# Add/Sub in Verilog (parameterized)

- ❖ Variable-width add/sub (with overflow, carry)

```

module addN #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic      OF, CF;      // overflow and carry "flags"
  output logic [N-1:0] S;
  input  logic      sub;
  input  logic [N-1:0] A, B;
  logic  [N-1:0] D;      // possibly flipped B
  logic          C2;     // second-to-last carry-out

  always_comb begin
    D = B ^ {N{sub}}; // replication operator
    {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
    {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
    OF = CF ^ C2;
  end
endmodule // addN

```

*default value* (pointing to N=32)  
*parameter changes bus widths* (pointing to sub and [N-1:0])  
*flip all bits of B if sub==1* (pointing to B ^ {N{sub}})

- Here using OF = overflow flag, CF = carry flag (from condition flags in x86-64 CPUs)

# Add/Sub in Verilog (parameterized)

```
module addN_tb ();
  parameter N = 4;
  logic      sub;
  logic [N-1:0] A, B;
  logic      OF, CF;
  logic [N-1:0] S;

  addN #(N(N)) dut (.OF, .CF, .S, .sub, .A, .B);

  initial begin
    #100; sub = 0; A = 4'b0101; B = 4'b0010; // 5 + 2
    #100; sub = 0; A = 4'b1101; B = 4'b1011; // -3 + -5
    #100; sub = 0; A = 4'b0101; B = 4'b0011; // 5 + 3
    #100; sub = 0; A = 4'b1001; B = 4'b1110; // -7 + -2
    #100; sub = 1; A = 4'b0101; B = 4'b1110; // 5 - (-2)
    #100; sub = 1; A = 4'b1101; B = 4'b0101; // -3 - 5
    #100; sub = 1; A = 4'b0101; B = 4'b1101; // 5 - (-3)
    #100; sub = 1; A = 4'b1001; B = 4'b0010; // -7 - 2
    #100;
  end
endmodule // addN_tb
```

*test different scenarios*