

# Intro to Digital Design

## Sequential Logic

**Instructor:** Justin Hsia

**Teaching Assistants:**

Caitlyn Rawlings

Donovan Clay

Emilio Alcantara

Joy Jung


Naoto Uemura

# Relevant Course Information

- ❖ Lab 3 Demos due during your assigned demo slots
  - Don't forget to submit your lab materials *before* Wednesday at 2:30 pm, regardless of your demo time
  
- ❖ Lab 4 – 7-seg displays
  
- ❖ Quiz 1 is next week in lecture
  - Last 20 minutes, worth 10% of your course grade
  - On Lectures 1-3: CL, K-maps, Waveforms, and Verilog
  - Past Quiz 1 (+ solutions) on website: Course Info → Quizzes

# Synchronous Digital Systems (SDS)


## ❖ Combinational Logic (CL)

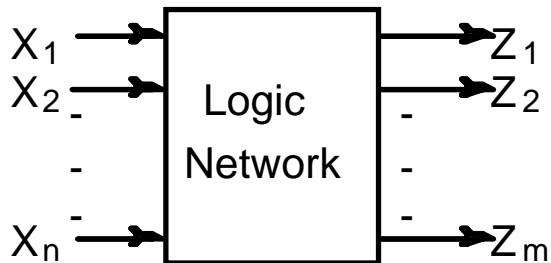

Network of logic gates without feedback.

Outputs are functions only of inputs.

## ❖ Sequential Logic (SL)

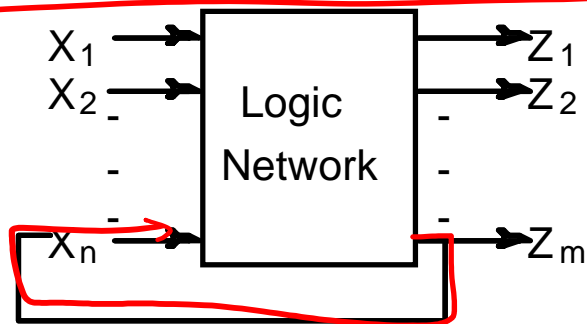

The presence of feedback introduces the notion of “state.”



Circuits can “remember” or store information.

# Uses for Sequential Logic

- ❖ Place to store values for some amount of time:
  - Registers
  - Memory
- ❖ *Help control flow of information between combinational logic blocks* timing!
  - Hold up the movement of information to allow for orderly passage through CL

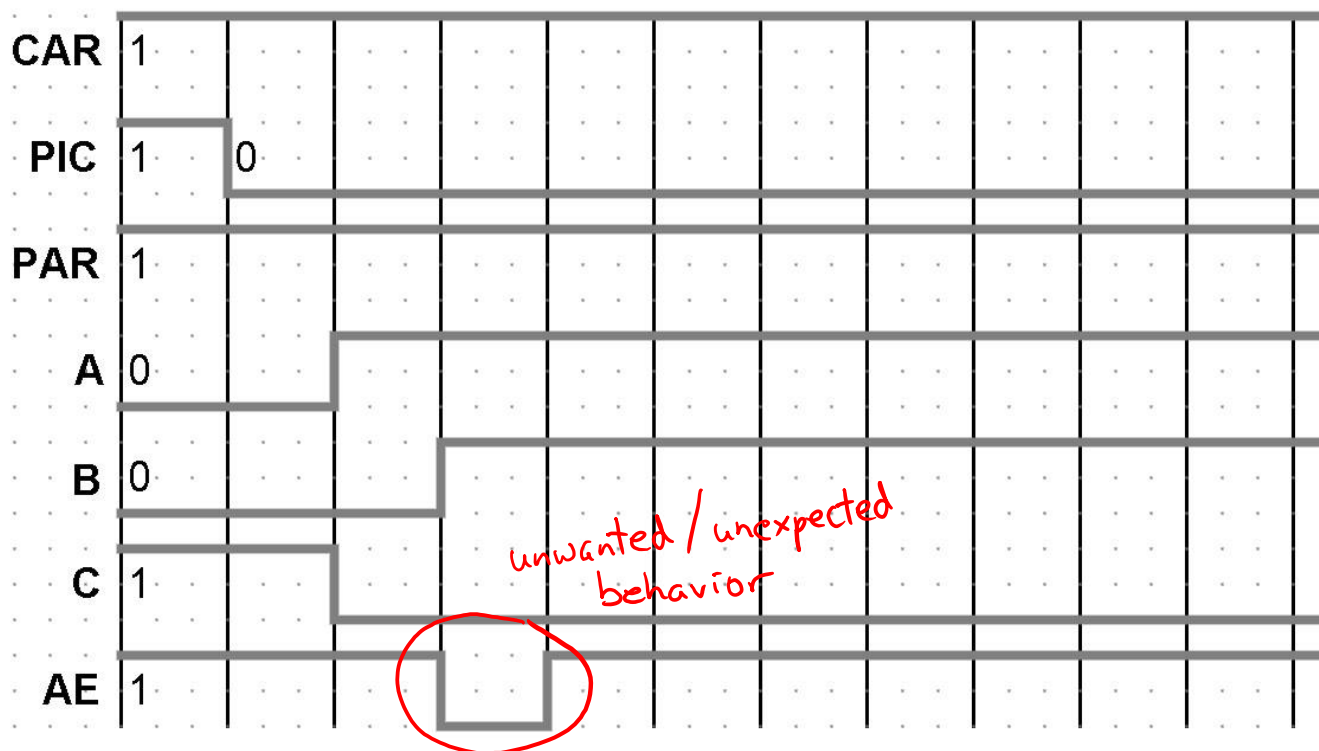 
# Control Flow of Information?

❖ Circuits can temporarily go to incorrect states!


 
# Accumulator Example

- ❖ An example of why we would need to control the flow of information.



- ❖ Want:
 

```

S = 0; initialize?
for (i=0; i<n; i++)
  S = S + X_i;
      
```


*stop condition?*

*sequence of inputs*
- ❖ Assume:
  - Each  $X$  value is applied in succession, one per cycle
  - The sum since cycle 0 is present on  $S$

# Accumulator: First Try

Does this work?


- No

 


- 1) How to control the next iteration of the 'for' loop?
- 2) How do we say: 'S=0'?

# State Element: Flip-Flop
 
## ❖ Positive edge-triggered D-type flip flop




 - “On the rising edge of the clock (  $0 \rightarrow 1$  ), input  $d$  is sampled and transferred to the output  $q$ . At other times, the input  $d$  is ignored and the previously sampled value is retained.”






# State Element: Register

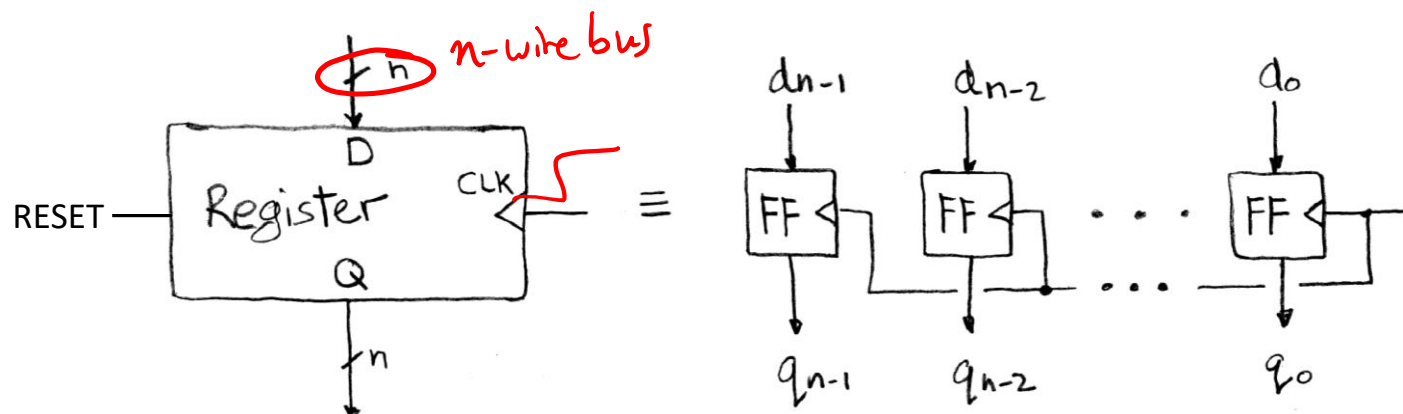


- ❖  $n$  instances of flip-flops together
  - One for every bit in input/output bus width
- ❖ Output  $Q$  resets to zero when RESET signal is high *during* clock trigger
  - Some extra circuitry required for this

# Accumulator: Second Try

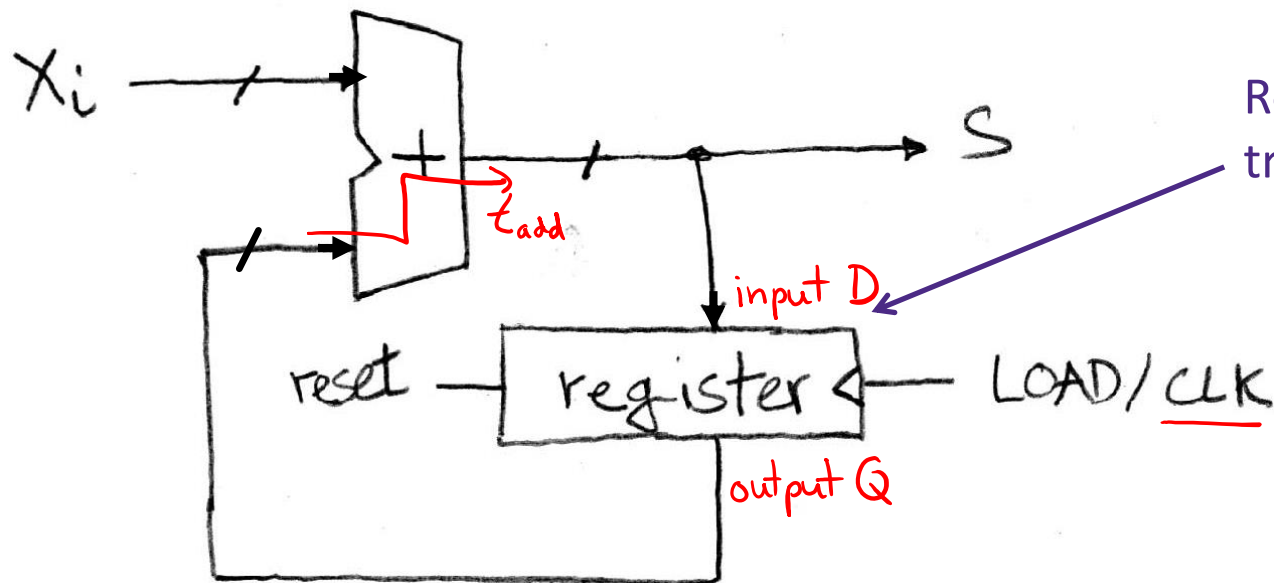


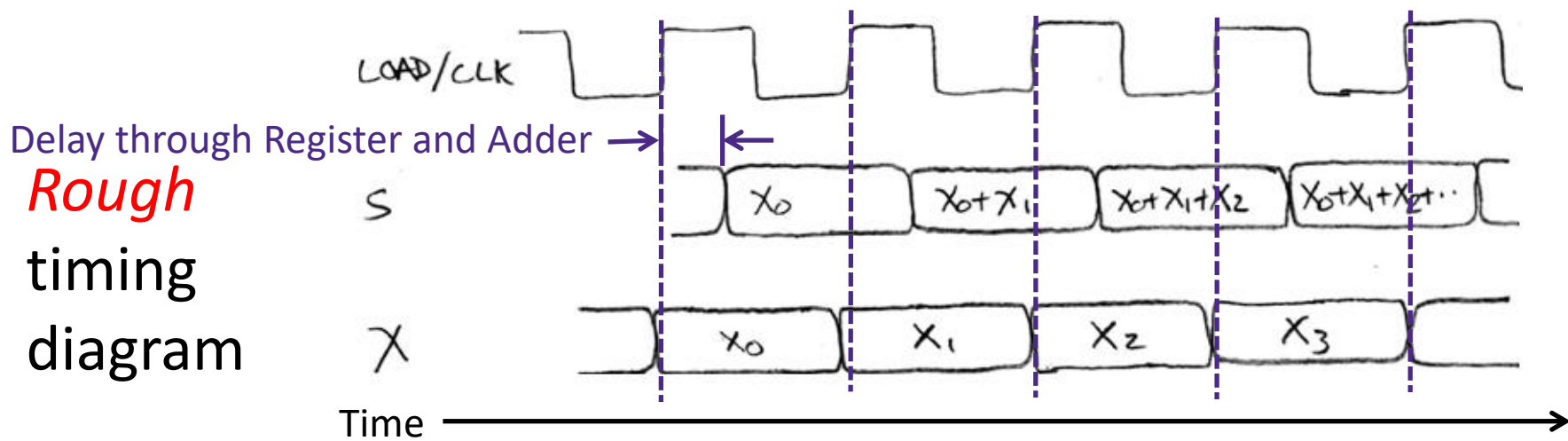Register holds up the transfer of data to adder


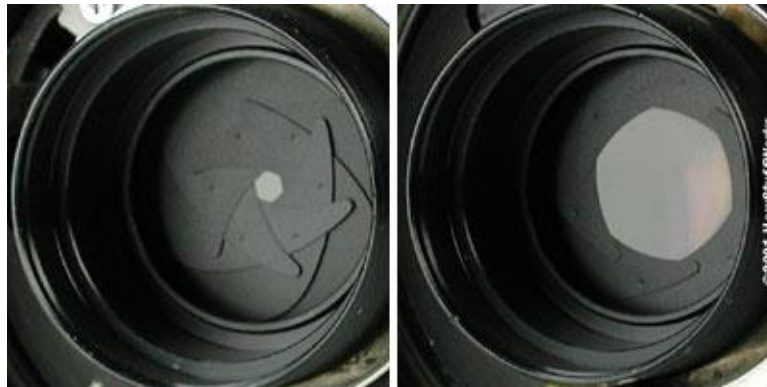
# Flip-Flop Timing Terminology (1/2)


- ❖ Camera Analogy: non-blurry digital photo
  - *Don't move* while camera shutter is opening
  - *Don't move* while camera shutter is closing
  - *Check for blurriness* once image appears on the display



# Flip-Flop Timing Terminology (2/2)




- ❖ Now applied to sequential logic elements:
  - **Setup Time:** how long the input must be stable *before* the CLK trigger for proper input read
  - **Hold Time:** how long the input must be stable *after* the CLK trigger for proper input read
  - **“CLK-to-Q” Delay:** how long it takes the output to change, measured from the CLK trigger

# Flip-Flop Timing Behavior

 
  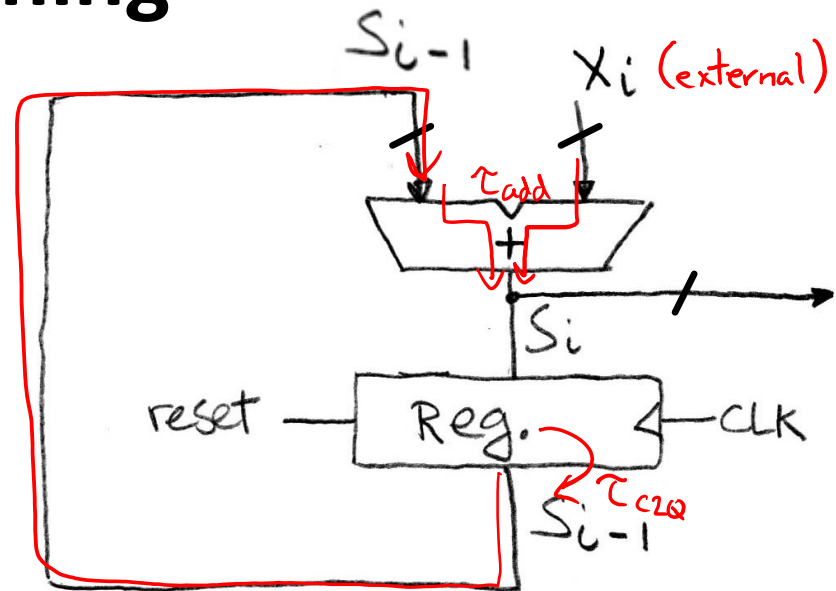
# Accumulator: Proper Timing


- reset signal shown
- Also, in practice  $X_i$  might not arrive at the adder at the same time as  $S_{i-1}$
- $S_i$  temporarily is wrong, but register always captures correct value
- In good circuits, instability never happens around rising edge of CLK



# Review Question

- ❖ Which of the following statements is TRUE?
- (A) The input to a flip-flop must remain stable throughout the ~~CLK to-Q delay~~.  
*setup & hold times*
- (B) A flip-flop ~~switches between 0 and 1 on each trigger~~.  
*input D → output Q*
- (C) In a SDS, we only need to know setup time, hold time, and clk-to-q delay constants to ensure correct behavior. *also need CL delays, clock period, external input timing, etc.*
- (D) None of the above.**

# Model for Synchronous Digital Systems

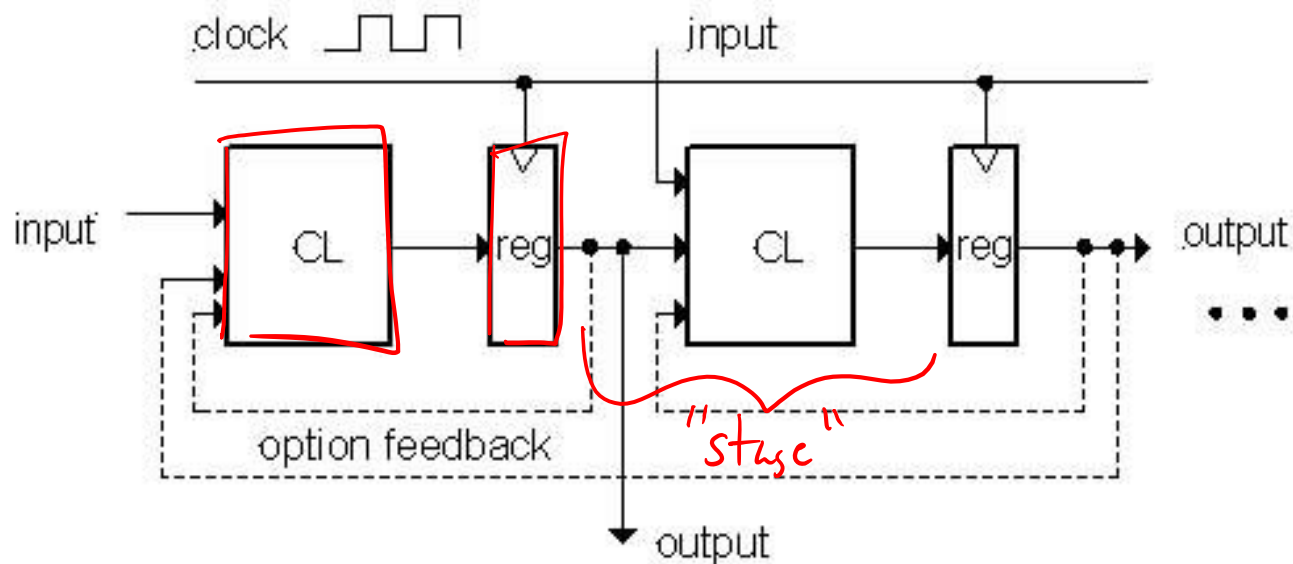

- ❖ Combinational logic blocks separated by registers
  - Clock signal connects only to sequential logic elements
  - Feedback is optional depending on application
- ❖ How do we ensure proper behavior?
  - How fast can we run our clock?




# When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time ( $t_{hold}$ ) or setup time ( $t_{setup}$ ) constraints within a clock period ( $t_{period}$ )
- ❖ Let  $t_{input,i}$  be the time it takes for the input of a register to change for the  $i$ -th time in a single clock cycle, measured from the CLK trigger:
  - Then we need  $t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$  for all  $i$
  - Two separate constraints!


$$\textcircled{1} \quad t_{input,1} \geq t_{hold}$$
 
$$\textcircled{2} \quad t_{input,n} \leq t_{period} - t_{setup}$$


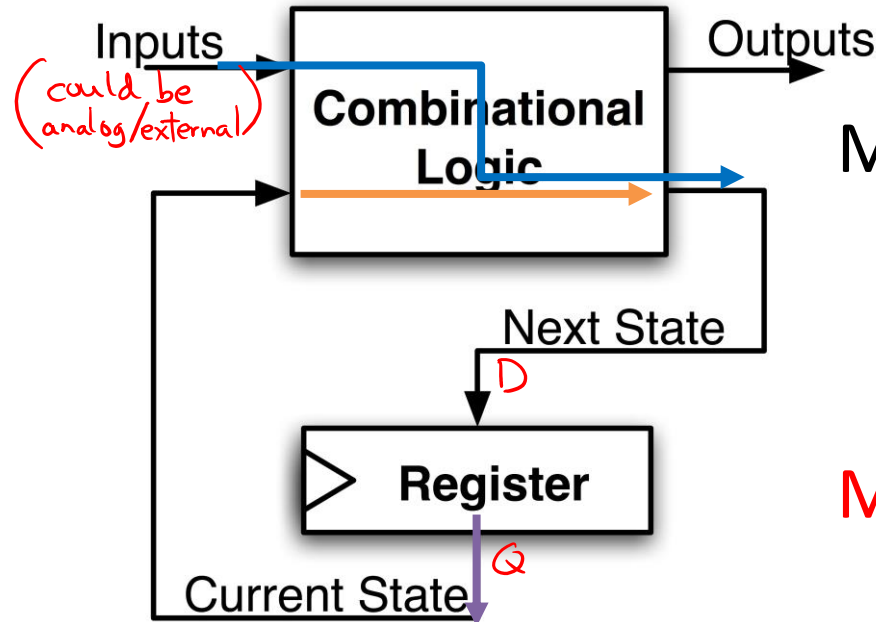
# Minimum Delay

- ❖ If shortest path to register input is too short, might violate hold time constraint
  - Input could change before state is “locked in”
  - Particularly problematic with *asynchronous* signals




$$\text{Min Delay} = \min(\text{CLK-to-Q Delay} + \text{Min CL Delay}, \text{Min CL Delay})$$

$$\text{Min Delay} \geq \text{Hold Time}$$
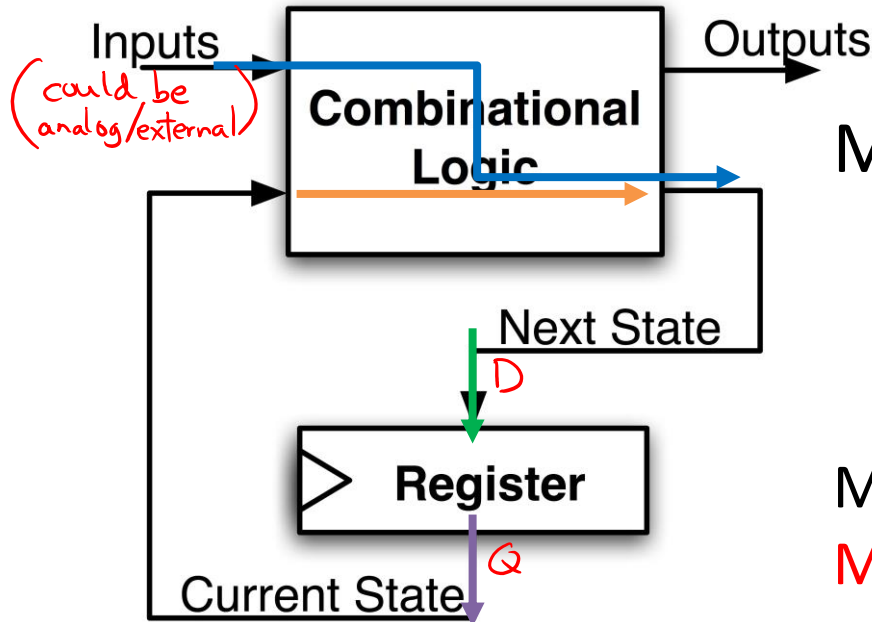
# Maximum Clock Frequency

- ❖ What is the max frequency of this circuit?
  - Limited by how much time needed to get correct Next State to Register ( $t_{setup}$  constraint)




$$\text{Max Delay} = \max(\text{CLK-to-Q Delay} + \text{Max CL Delay}, + \text{Max CL Delay})$$

$$\text{Min Period} = \text{Max Delay} + \text{Setup Time}$$

$$\text{Max Freq} = 1/\text{Min Period}$$
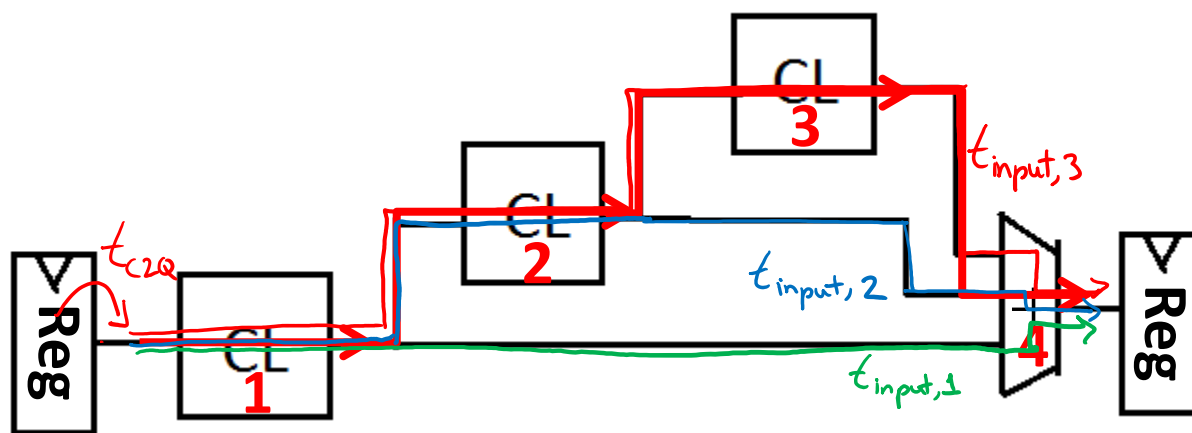
# The Critical Path

- ❖ The *critical path* is the longest delay between any two registers in a circuit
- ❖ The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register



**Critical Path =**

CLK-to-Q Delay  
 + CL Delay 1  
 + CL Delay 2  
 + CL Delay 3  
 + Adder Delay  
 + Setup Time

# Practice Question

milli  $10^{-3}$   
 micro  $10^{-6}$   
 nano  $10^{-9}$   
 pico  $10^{-12}$


$freq = 10^9 s^{-1} \rightarrow period = 10^{-9} s = 1 ns = \frac{t_{period}}{1000} = 1000 ps$

❖ We want to run on 1 GHz processor.  $t_{add} = 100 ps$ .

$t_{mult} = 200 ps$ .  $t_{setup} = t_{hold} = 50 ps$ . What is the

maximum  $t_{clk-to-q}$  we can use?

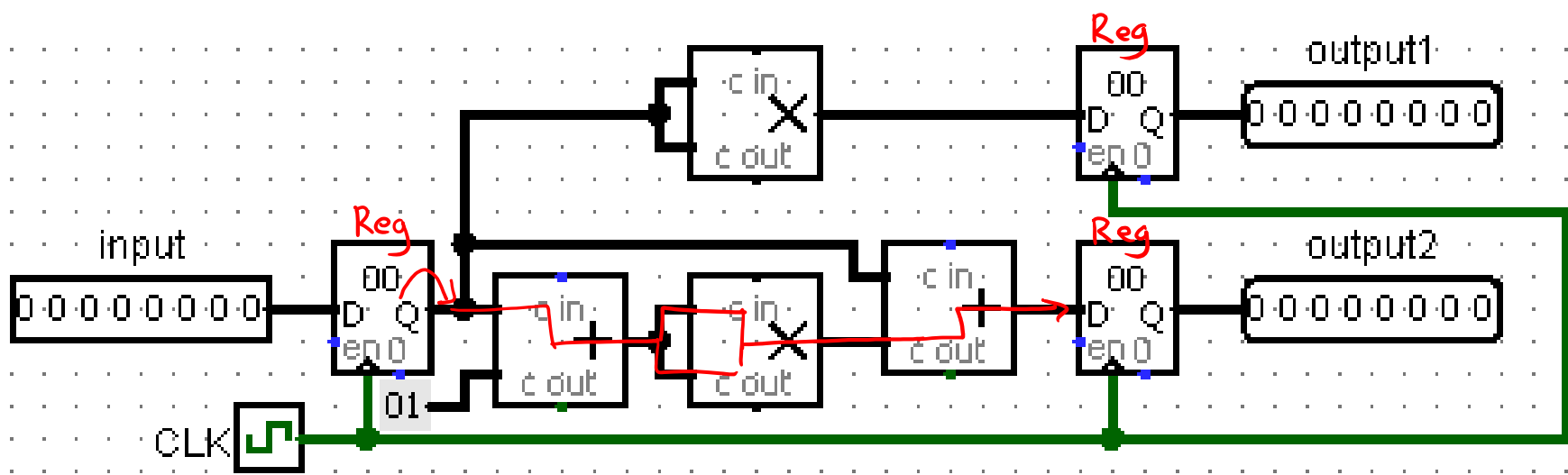$t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$




$t_{input,n} = t_{cq} + t_{add} + t_{mult} + t_{add} \leq t_{period} - t_{setup} \Rightarrow t_{cq} \leq 550 ps$   
 $\quad \quad \quad 100 \quad 200 \quad 100 \quad \quad \quad 1000 \quad 50$

- (A) 550 ps (B) 750 ps (C) 500 ps (D) 700 ps

# Technology Break

# Where Do Timing Terms Come From?



Edge-triggered  
D flip-flop:

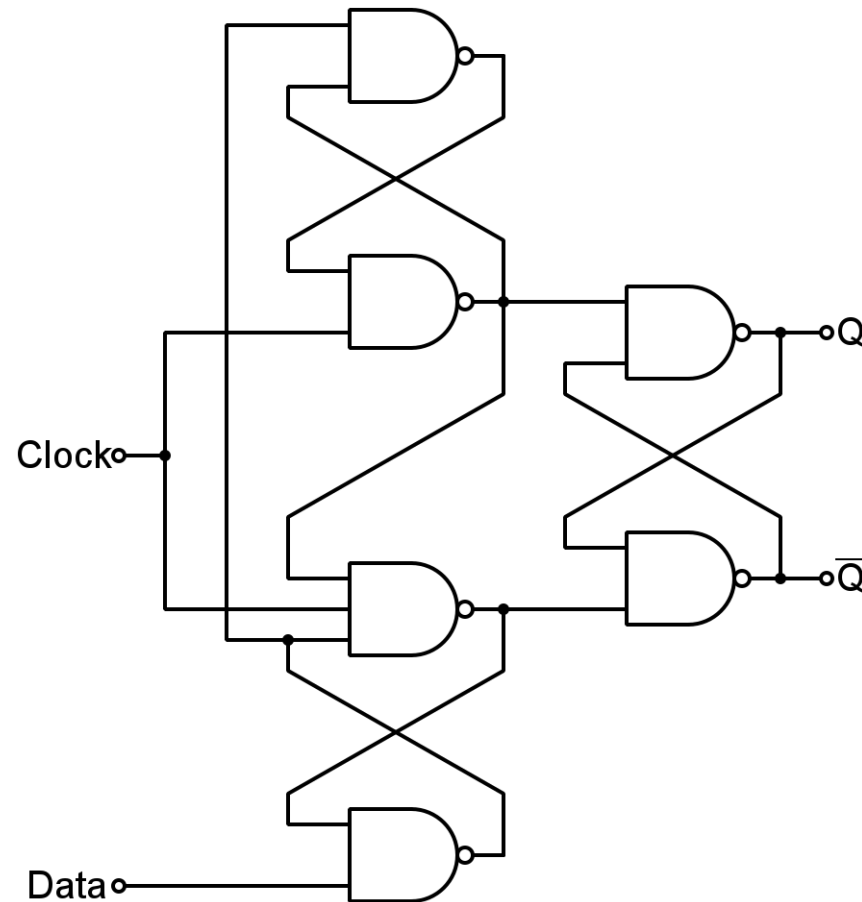

By Nolanjshettle at English Wikipedia, CC BY-SA 3.0,  
<https://commons.wikimedia.org/w/index.php?curid=40852354>
  
# Safe Sequential Circuits



- ❖ Clocked elements on feedback, perhaps outputs
  - Clock signal synchronizes operation
  - Clocked elements hide glitches/hazards




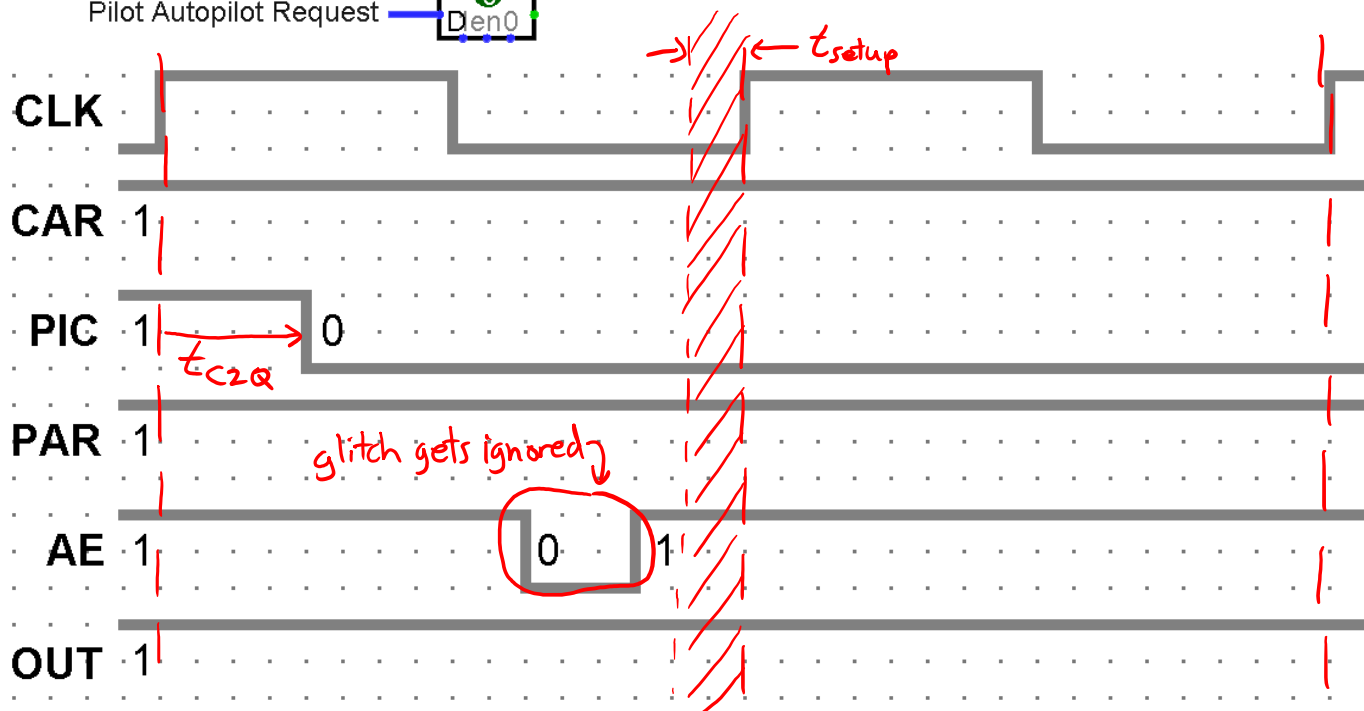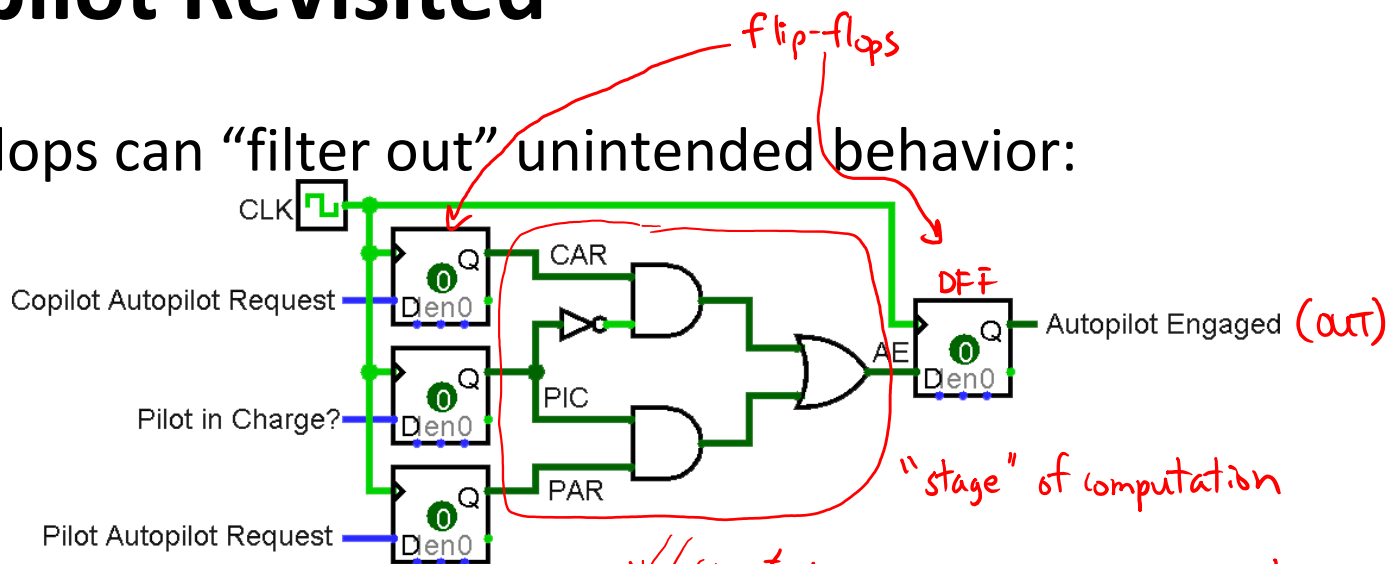
# Autopilot Revisited

- ❖ Flip-flops can “filter out” unintended behavior:





# Waveform Diagrams Revisited

- ❖ Easiest to start with CLK on top
  - Solve signal by signal, from inputs to outputs
  - Can only draw the waveform for a signal if *all* of its input waveforms are drawn
- ❖ When does a signal update?
  - A state element<sup>(SL)</sup> updates based on CLK triggers
  - A combinational element<sup>(CL)</sup> updates ANY time ANY of its inputs changes
  
# Example: SDS Waveform Diagram

- Assume:  $t_{C2Q} = 3$  ticks,  $t_{XOR} = 2$  ticks,  $t_{NOT} = \underline{1}$  tick;  $t_s = t_h = 0$ 
  - Note: clocking the gate is a *terrible* idea



		Xor
0	0	0
0	1	1
1	0	1
1	1	0

1 tick

# Verilog: Basic D Flip-Flop, Register


```

module basic_D_FF (q, d, clk);
  output logic q; // q is state-holding
  input logic d, clk;

  always_ff @ (posedge clk)
    q <= d; // use <= for clocked elements
endmodule

```

react to rising edges of clk signal

 


```

module basic_reg (q, d, clk);
  output logic [7:0] q;
  input logic [7:0] d;
  input logic clk;

  always_ff @ (posedge clk)
    q <= d;
endmodule

```

bus widths of 8


 


# Procedural Blocks

- ❖ `always`: loop to execute over and over again
  - Block gets triggered by a *sensitivity list*
  - Any object that is assigned a value in an `always` statement must be declared as a variable (`logic` or `reg`).
  - Example:
    - `always @ (posedge clk)`
- ❖ `always_ff`: special SystemVerilog for SL
  - *Only for use with sequential logic – signal intent that you want flip-flops*
  - Example:
    - `always_ff @ (posedge clk)`
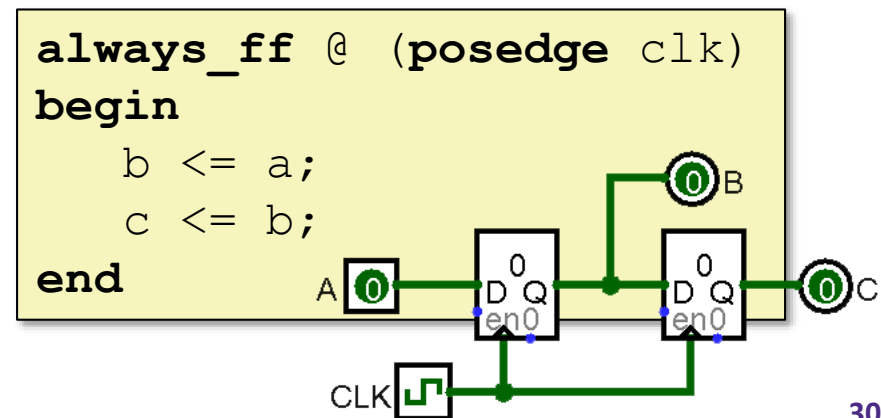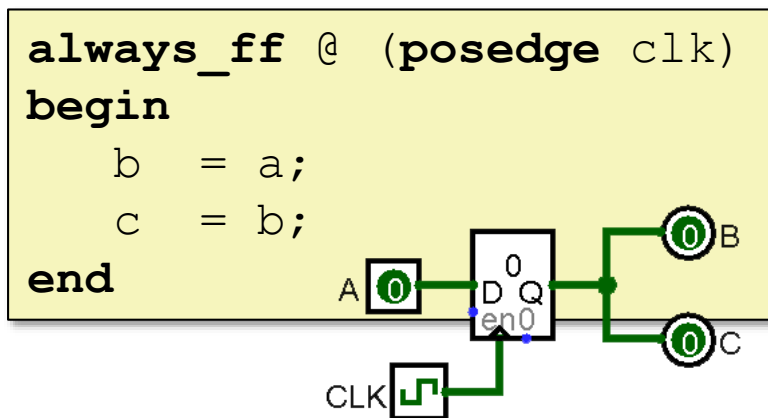
# Blocking vs. Nonblocking


- ❖ **Blocking** statement (=): statements executed sequentially
  - Resembles programming languages
- ❖ **Nonblocking** statement (<=): statements executed “in parallel”
  - Resembles hardware
- ❖ Example:



# SystemVerilog Coding Guidelines

- 1) When modeling sequential logic, use *nonblocking* assignments
- 2) When modeling combinational logic with an `always_comb` block, use *blocking* assignments
- 3) When modeling both sequential and combinational logic within the same `always_ff` block, use *nonblocking* assignments
- 4) Do not mix *blocking* and *nonblocking* assignments in the same `always_*` block
- 5) Do not make assignments to the same variable from more than one `always_*` block

# Verilog: Reset Functionality

 


## ❖ Option 1: synchronous reset

```
module D_FF1 (q, d, reset, clk);  
  output logic q; // q is state-holding  
  input  logic d, reset, clk;  
  
  always_ff @(posedge clk)  
    if (reset) ← reset can only occur on clock trigger  
      q <= 0; // on reset, set to 0  
    else  
      q <= d; // otherwise pass d to q  
  
endmodule
```



# Verilog: Reset Functionality

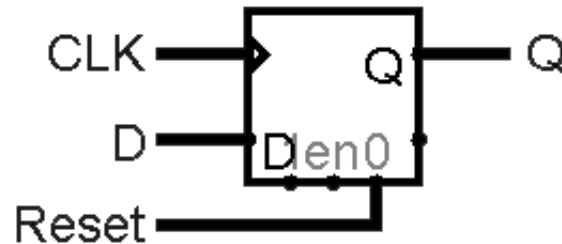

## ❖ Option 2: asynchronous reset

```
module D_FF1 (q, d, reset, clk);  
  output logic q; // q is state-holding  
  input  logic d, reset, clk;  
  
  always_ff @(posedge clk or posedge reset)  
    if (reset)  
      q <= 0; // on reset, set to 0  
    else  
      q <= d; // otherwise pass d to q  
  
endmodule
```

any reset posedge, no matter where in the clock cycle

# Verilog: Simulated Clock

- ❖ For simulation, you need to generate a clock signal:
  - For entirety of simulation/program, so use `always` block

Explicit  
Edges:

```
initial
  clk = 0;
always begin
  #50  clk <= 1;
  #50  clk <= 0;
end
```

Toggle:

```
initial
  clk = 0;
always
  #50  clk <= ~clk;
```

*half-period*

- ❖ Define clock period:

- Define **parameter**

*like #define macro substitution  
in C*

```
parameter period = 100;
initial
  clk = 0;
always
  #(period/2)  clk <= ~clk;
```

# Verilog Testbench with Clock

```

module D_FF_testbench;
  logic CLK, reset, d; ← simulated inputs
  logic q; ← DUT output

  parameter PERIOD = 100;

  D_FF dut (.q, .d, .reset, .CLK); // Instantiate the D_FF

  initial CLK <= 0; // Set up clock
  always #(PERIOD/2) CLK<= ~CLK;

  initial begin // Set up signals
    d <= 0; reset <= 1;
    @ (posedge CLK); reset <= 0;
    @ (posedge CLK); d <= 1;
    @ (posedge CLK); d <= 0;
    @ (posedge CLK); #(PERIOD/4) d <= 1;
    @ (posedge CLK);
    $stop(); // end the simulation
  end
endmodule

```

toggle form of clock

these occur just after clock triggers

$t=0$  →

$t=100$  →

$t=200$  →

$t=300$  →

$t=400$  →


$t=500$  →

no statement here by choice

# Timing Controls

- ❖ Delay: `#<time>`
  - Delays by a specific amount of simulation time
  - Can do calculations in `<time>`
  - Examples: `# (PERIOD/4)`, `#50`
- ❖ Edge-sensitive: `@ (<pos/negedge> signal)`
  - Delays next statement until specified transition on signal
  - Example: `@ (posedge CLK)`
- ❖ Level-sensitive Event: `wait (<expression>)`
  - Delays next statement until `<expression>` evaluates to TRUE
  - Example: `wait (enable == 1)`

# ModelSim Waveforms

 

```

initial begin
    d <= 0; reset <= 1;
    @ (posedge CLK) ;          reset <= 0;
    @ (posedge CLK) ; d <= 1;
    @ (posedge CLK) ; d <= 0;
    @ (posedge CLK) ; # (PERIOD/4) d <= 1;
    @ (posedge CLK) ;
    $stop();
end
    
```

*happens just after posedge*

*wait after posedge*

*no statement occurs exactly at posedge*

# Summary (1/2)

- ❖ State elements controlled by clock
  - Store information
  - Control the flow of information between other state elements and combinational logic
- ❖ Registers implemented from flip-flops
  - Triggered by CLK, pass input to output, can reset
- ❖ Critical path constrains clock rate
  - Timing constants: setup time, hold time, clk-to-q delay, propagation delays

# Summary (2/2)

- ❖ Generating a clock
  - Manually create using `always` block
  - Need to decide on period
- ❖ Blocking vs. Non-blocking
  - Blocking: Statements executed “in series”
  - Non-blocking: Statements executed “in parallel”
  - Always use non-blocking for clocked elements
- ❖ Synchronous vs. Asynchronous
  - Whether signals are controlled by clock or not