

# Intro to Digital Design

## Circuit Building Blocks I

**Instructor:** Justin Hsia

**Teaching Assistants:**

Caitlyn Rawlings

Donovan Clay

Emilio Alcantara

Joy Jung

Naoto Uemura

# Relevant Course Information

- ❖ Lab 6 – Connecting multiple FSMs in Tug of War game
  - *Bigger* step up in difficulty from Lab 5
  - Putting together complex system – interconnections!
  - Bonus points for smaller resource usage

# Clock Divider (not for simulation)

## ❖ Why/how does this work?

```
// divided_clocks[0]=25MHz, [1]=12.5Mhz, ...  
module clock_divider (clock, divided_clocks);  
  input  logic          clock;  
  output logic [31:0] divided_clocks;  
  
  initial  
    divided_clocks = 0;  
  
  always_ff @(posedge clock)  
    divided_clocks <= divided_clocks + 1;  
  
endmodule
```

# Outline

- ❖ **FSM Design**
- ❖ Multiplexors
- ❖ Adders

# FSM Design Process

- 1) Understand the problem
- 2) Draw the state diagram
- 3) Use state diagram to produce state table
- 4) Implement the combinational control logic



# Practice: String Recognizer FSM

❖ Recognize the string 101 with the following behavior

■ Input: 1 0 0 1 0 1 0 1 1 0 0 1 0

■ Output: 0 0 0 0 0 1 0 1 0 0 0 0 0

❖ State diagram to implementation:

  

# HDL Organization

- ❖ Most problems are best solved with multiple pieces – how to best organize your system and code?
- ❖ Everything is computed in parallel
  - We use routing elements (next lecture) to select between (or ignore) multiple outcomes/parts
  - This is why we use block diagrams and waveforms
- ❖ A module is not a *function*, it is closest to a *class*
  - Something that you *instantiate*, not something that you *call* – hardware cannot appear and disappear spontaneously
  - Should treat modules as *resource managers* rather than temporary helpers
    - This can include having internal modules

# Subdividing FSMs Example

- ❖ “Psychic Tester”
  - Machine generates a 4-bit pattern
  - User tries to guess 8 patterns in a row to be deemed psychic
  
- ❖ States?



# Example: Plan First with Block Diagram

- ❖ Pieces?
  - Generate/pick pattern
  - User input (guess)
  - Check guess
  - Count correct guesses

# Example: Implementation & Testing


- 1) Create individual submodules
- 2) Create submodules test benches – test as usual
  - CL – run through all input combinations
  - SL – take every transition that you care about
- 3) Create top-level module
  - Create instance of each submodule
  - Create wires/nets to connect signals between submodules, inputs, and outputs
- 4) Create top-level test bench
  - Goal is to check the interconnections between submodules – does input/state change in one submodule trigger the expected change in other submodules?

# Outline

- ❖ FSM Design
- ❖ **Multiplexors**
- ❖ Adders

 
# Data Multiplexor

- ❖ Multiplexor (“MUX”) is a *selector*
  - Direct one of many ( $N = 2^s$ )  $n$ -bit wide inputs onto output
  - Called a  $n$ -bit,  $N$ -to-1 MUX
- ❖ Example:  $n$ -bit 2-to-1 MUX
  - Input  $S$  ( $s$  bits wide) selects between two inputs of  $n$  bits each



# Review: Implementing a 1-bit 2-to-1 MUX

## ❖ Schematic:

 


## ❖ Truth Table:

s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

## ❖ Boolean Algebra:


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

## ❖ Circuit Diagram:

 

# 1-bit 4-to-1 MUX

## ❖ Schematic:

 


## ❖ Truth Table: How many rows? $2^6$

## ❖ Boolean Expression:

$$e = \bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$$

 
# 1-bit 4-to-1 MUX

- ❖ Can we leverage what we've previously built?
  - Alternative hierarchical approach:


 
# Multiplexers in General Logic

- ❖ Implement  $F = X\bar{Y}Z + Y\bar{Z}$  with a 8:1 MUX





# Technology Break

# Outline

- ❖ FSM Design
- ❖ Multiplexors
- ❖ **Adders**

# Review: Unsigned Integers

- ❖ Unsigned values follow the standard base 2 system
  - $b_7b_6b_5b_4b_3b_2b_1b_0 = b_72^7 + b_62^6 + \dots + b_12^1 + b_02^0$
- ❖ In  $n$  bits, represent integers 0 to  $2^n-1$
- ❖ Add and subtract using the normal “carry” and “borrow” rules, just in binary

$$\begin{array}{r}
 63 \quad 00111111 \\
 + \underline{8} \quad + \underline{00001000} \\
 71 \quad 01000111
 \end{array}$$

$$\begin{array}{r}
 64 \quad 01000000 \\
 - \underline{8} \quad - \underline{00001000} \\
 56 \quad 00111000
 \end{array}$$

# Review: Two's Complement (Signed)

$b_{w-1}$  has weight  $-2^{w-1}$ , other bits have usual weights  $+2^i$




## ❖ Properties:

- In  $n$  bits, represent integers  $-2^{n-1}$  to  $2^{n-1} - 1$
- Positive number encodings match unsigned numbers
- Single zero (encoding = all zeros)

## ❖ Negation procedure:

- Take the bitwise complement and then add one

$$(\sim x + 1 == -x)$$

 

# Addition and Subtraction in Hardware

- ❖ The same bit manipulations work for both unsigned and two's complement numbers!

- Perform subtraction via adding the negated 2<sup>nd</sup> operand:

$$A - B = A + (-B) = A + (\sim B) + 1$$

- ❖ 4-bit examples:

	Two's	Un
0 0 1 0	+2	2
<u>+ 1 1 0 0</u>	-4	12

0 1 1 0	+6	6
<u>- 0 0 1 0</u>	+2	2

	Two's	Un
1 0 0 0	-8	8
<u>+ 0 1 0 0</u>	+4	4

1 1 1 1	-1	15
<u>- 1 1 1 0</u>	-2	14

# Half Adder (1 bit)


	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

Carry =  $a_0 b_0$


Sum =  $a_0 \oplus b_0$

Carry-out bit

$a_0$	$b_0$	$c_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

# Full Adder (1 bit)

 


$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i)$$


$$= a_i b_i + a_i c_i + b_i c_i$$

Carry-in	$c_i$	$a_i$	$b_i$	Carry-out	$c_{i+1}$	$s_i$
	0	0	0		0	0
	0	0	1		0	1
	0	1	0		0	1
	0	1	1		1	0
	1	0	0		0	1
	1	0	1		1	0
	1	1	0		1	0
	1	1	1		1	1

 
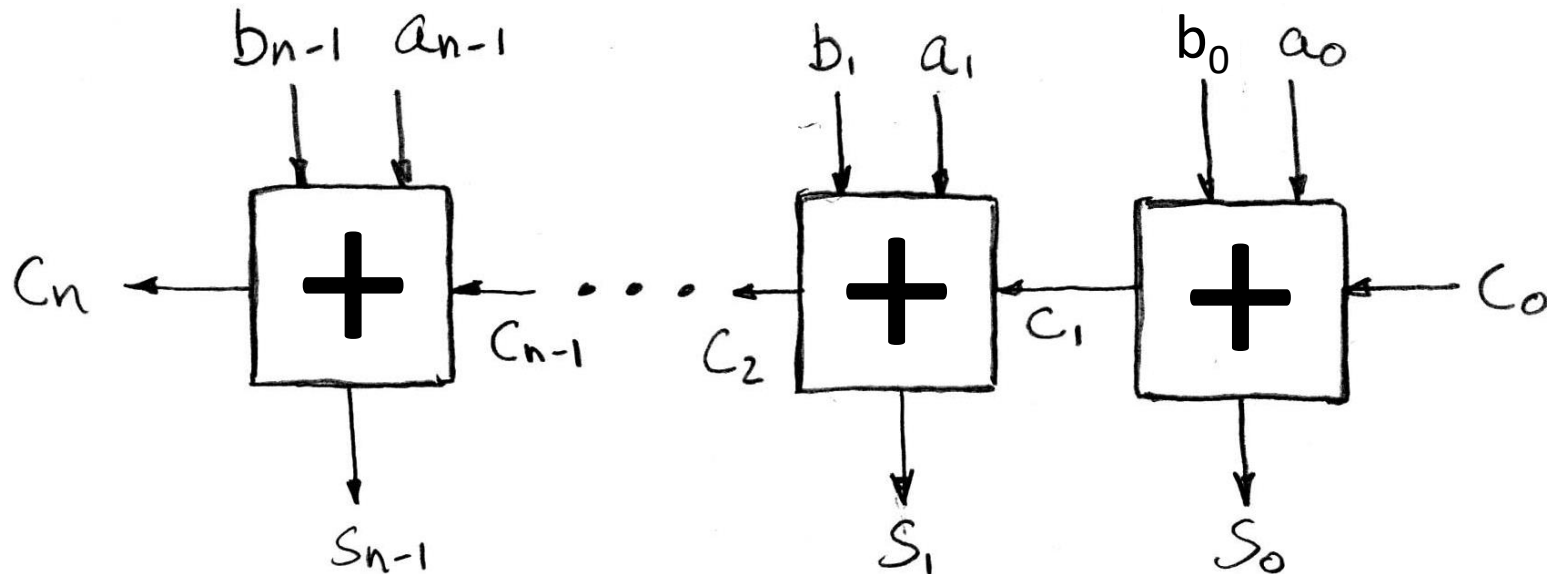
# Multi-Bit Adder (N bits)


- ❖ Chain 1-bit adders by connecting  $\text{CarryOut}_i$  to  $\text{CarryIn}_{i+1}$ :





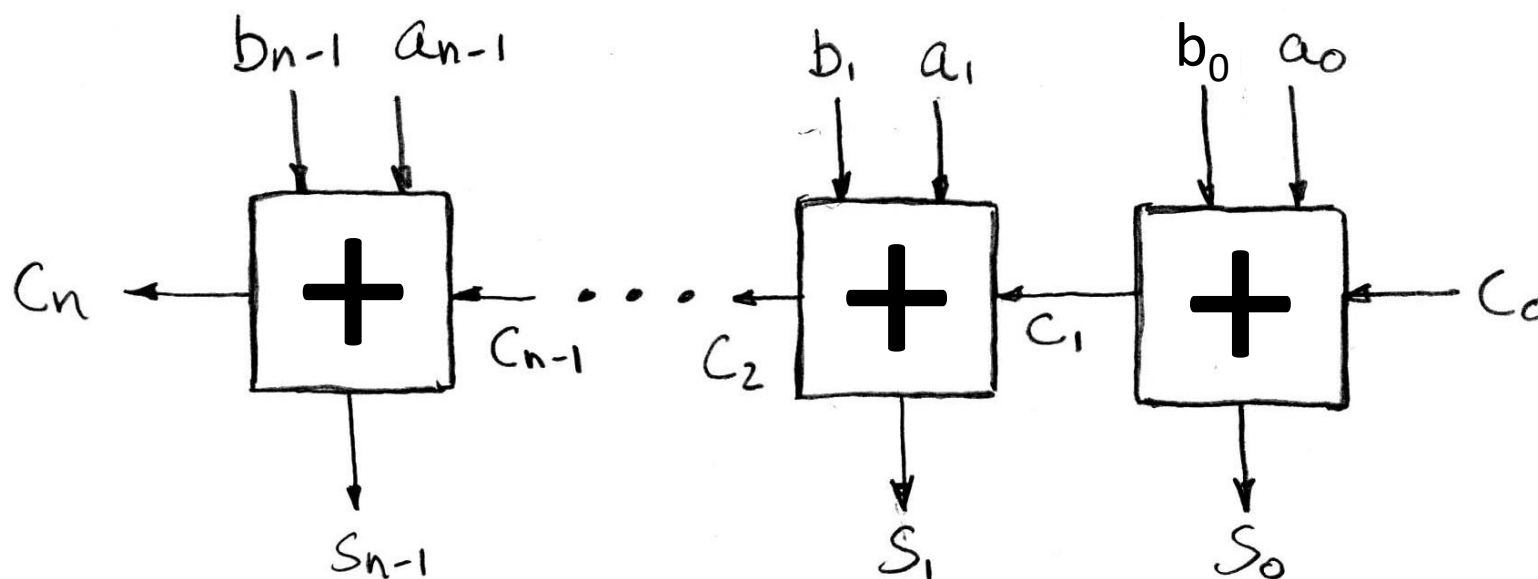
# Subtraction?

- ❖ Can we use our multi-bit adder to do subtraction?
  - Flip the bits and add 1?
    - $X \oplus 1 = \bar{X}$
    - CarryIn<sub>0</sub> (using full adder in all positions)



# Multi-bit Adder/Subtractor

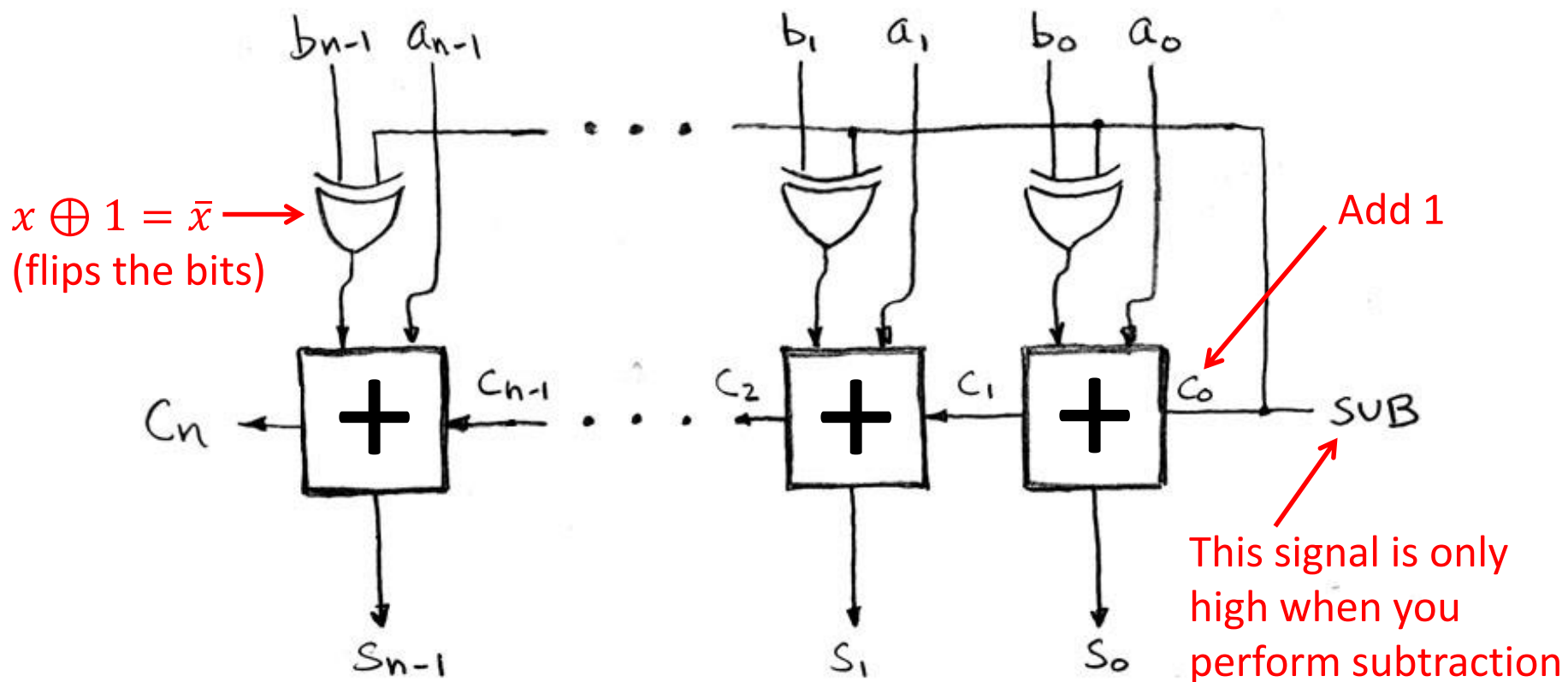

# Detecting Arithmetic Overflow

- ❖ **Overflow:** When a calculation produces a result that can't be represented in the current encoding scheme
  - Integer range limited by fixed width
  - Can occur in both the positive and negative directions
- ❖ **Unsigned Overflow**
  - Result of add/sub is  $> U_{Max}$  or  $< U_{min}$
- ❖ **Signed Overflow**
  - Result of add/sub is  $> T_{Max}$  or  $< T_{Min}$
  - $(+) + (+) = (-)$  or  $(-) + (-) = (+)$

# Signed Overflow Examples


$$\begin{array}{r}
 \phantom{+} 0\ 1\ 0\ 1 \\
 + 0\ 0\ 1\ 1 \\
 \hline
 \end{array}
 \begin{array}{l}
 \text{Two's} \\
 +5 \\
 +3
 \end{array}$$

$$\begin{array}{r}
 \phantom{+} 1\ 0\ 0\ 1 \\
 + 1\ 1\ 1\ 0 \\
 \hline
 \end{array}
 \begin{array}{l}
 \text{Two's} \\
 -7 \\
 -2
 \end{array}$$

$$\begin{array}{r}
 \phantom{+} 0\ 1\ 0\ 1 \\
 + 0\ 0\ 1\ 0 \\
 \hline
 \end{array}
 \begin{array}{l}
 \text{Two's} \\
 +5 \\
 +2
 \end{array}$$


$$\begin{array}{r}
 \phantom{+} 1\ 1\ 0\ 0 \\
 + 0\ 1\ 0\ 0 \\
 \hline
 \end{array}
 \begin{array}{l}
 \text{Two's} \\
 -4 \\
 4
 \end{array}$$
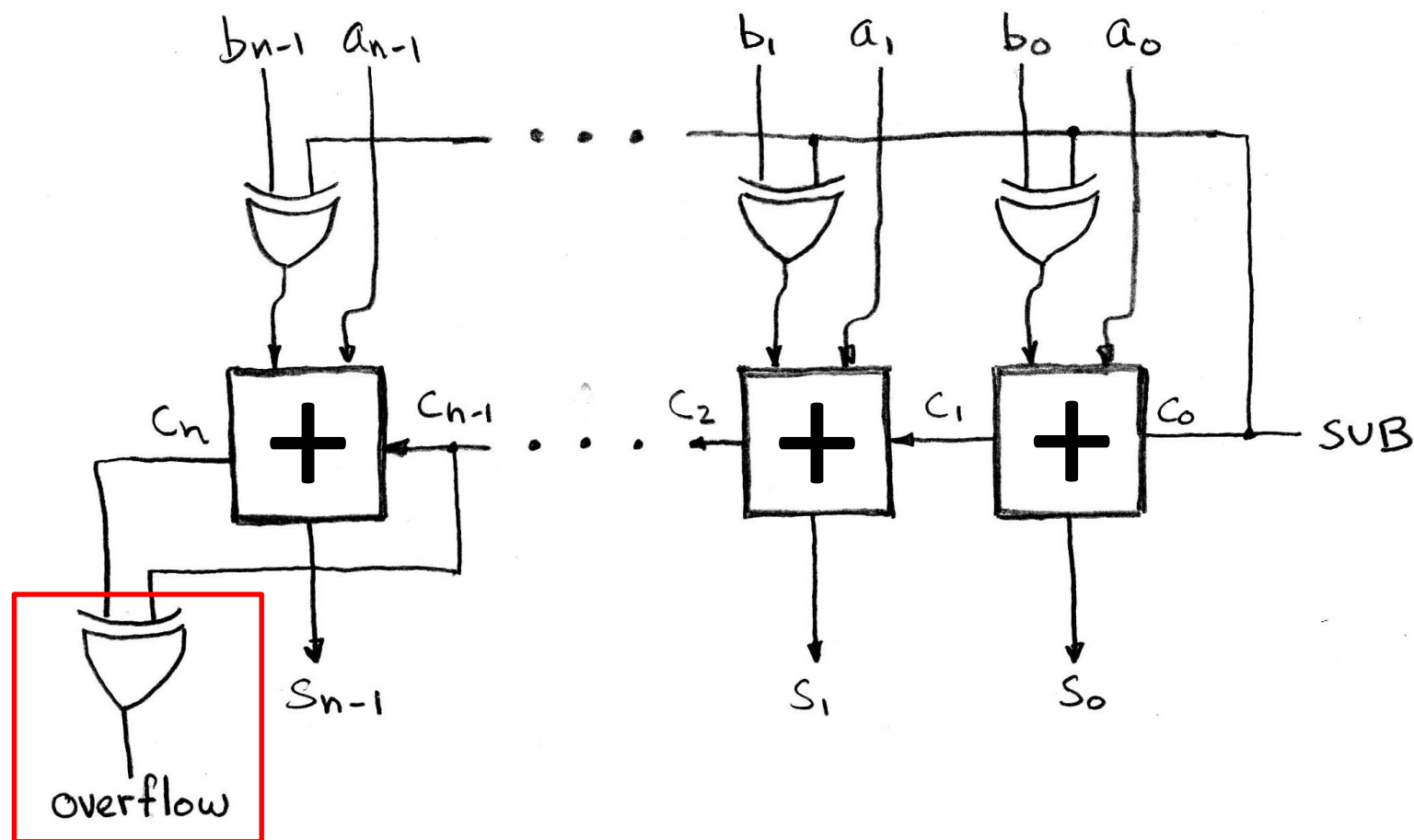
# Multi-bit Adder/Subtractor with Overflow



 
# Arithmetic and Logic Unit (ALU)

- ❖ Processors contain a special logic block called the “Arithmetic and Logic Unit” (ALU)
  - Here’s an easy one that does ADD, SUB, bitwise AND, and bitwise OR (for 32-bit numbers)
- ❖ **Schematic:**



when  $S=00$ ,  $R = A+B$   
when  $S=01$ ,  $R = A-B$   
when  $S=10$ ,  $R = A \& B$   
when  $S=11$ ,  $R = A | B$

# Simple ALU Schematic

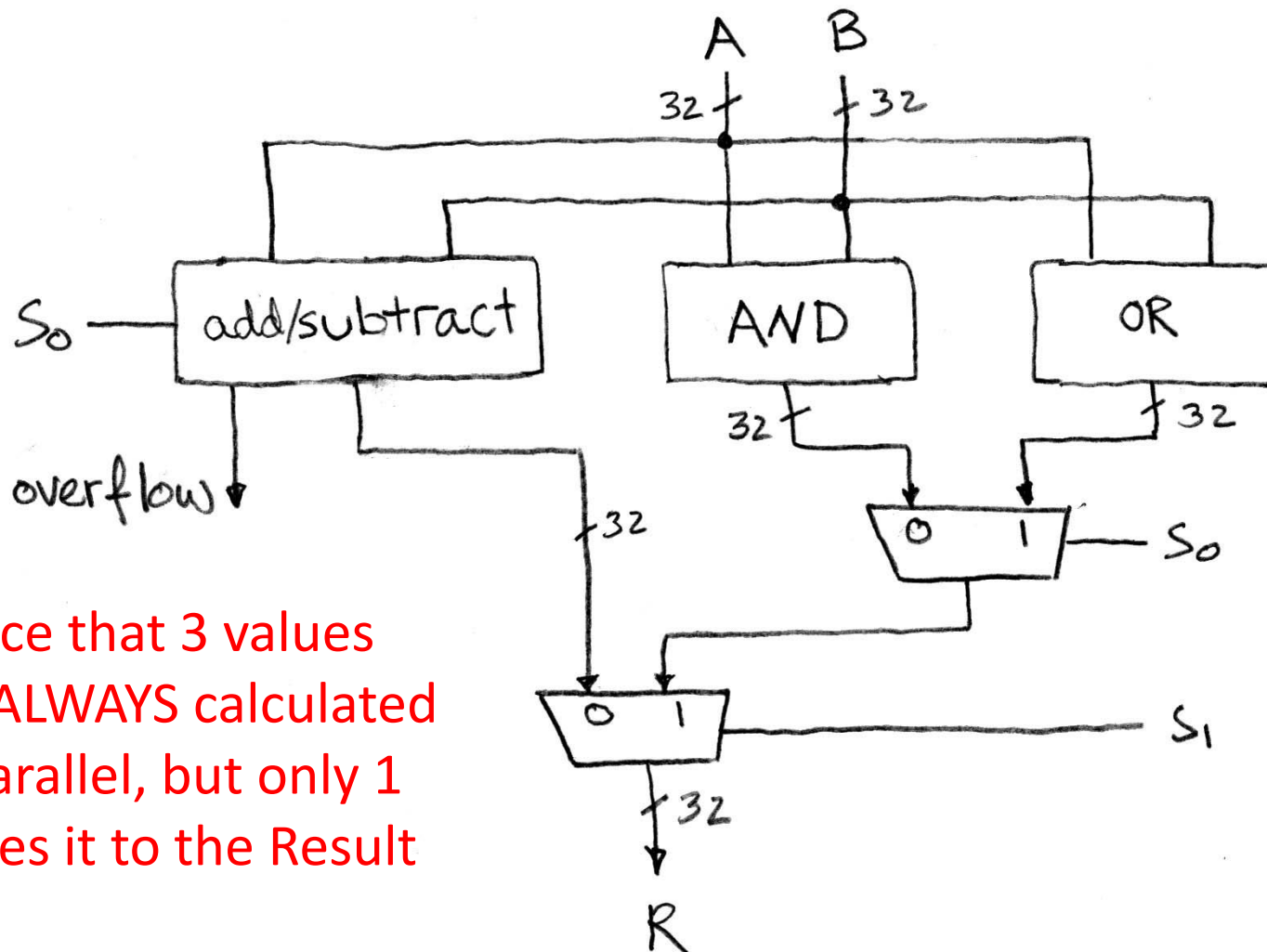

Notice that 3 values  
are ALWAYS calculated  
in parallel, but only 1  
makes it to the Result

# 1-bit Adders in Verilog

- ❖ What's wrong with this?
  - Truncation!

```
module halfadd1 (s, a, b);  
  output logic s;  
  input  logic a, b;  
  
  always_comb begin  
    s = a + b;  
  end  
endmodule
```

- ❖ Fixed:
  - Use of {sig, ..., sig}  
for *concatenation*

```
module halfadd2 (c, s, a, b);  
  output logic c, s;  
  input  logic a, b;  
  
  always_comb begin  
    {c, s} = a + b;  
  end  
endmodule
```



# Ripple-Carry Adder in Verilog

```
module fulladd (cout, s, cin, a, b);  
  output logic cout, s;  
  input  logic cin, a, b;  
  
  always_comb begin  
    {cout, s} = cin + a + b;  
  end  
endmodule
```

## ❖ Chain full adders?

```
module add2 (cout, s, cin, a, b);  
  output logic cout; output logic [1:0] s;  
  input  logic cin;  input  logic [1:0] a, b;  
  logic  c1;  
  
  fulladd b1 (cout, s[1], c1, a[1], b[1]);  
  fulladd b0 (c1, s[0], cin, a[0], b[0]);  
endmodule
```

# Add/Sub in Verilog (parameterized)

## ❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic          OF, CF;
  output logic [N-1:0] S;
  input  logic          sub;
  input  logic [N-1:0] A, B;
  logic  [N-1:0] D;      // possibly flipped B
  logic          C2;     // second-to-last carry-out

  always_comb begin
    D = B ^ {N{sub}};    // replication operator
    {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
    {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
    OF = CF ^ C2;
  end
endmodule
```

- Here using OF = overflow flag, CF = carry flag
  - From condition flags in x86-64 processors

# Add/Sub in Verilog (parameterized)

```
module addN_testbench ();
  parameter N = 4;
  logic      sub;
  logic [N-1:0] A, B;
  logic      OF, CF;
  logic [N-1:0] S;

  addN #(.N(N)) dut (.OF, .CF, .S, .sub, .A, .B);

  initial begin
    #100; sub = 0; A = 4'b0101; B = 4'b0010; // 5 + 2
    #100; sub = 0; A = 4'b1101; B = 4'b1011; // -3 + -5
    #100; sub = 0; A = 4'b0101; B = 4'b0011; // 5 + 3
    #100; sub = 0; A = 4'b1001; B = 4'b1110; // -7 + -2
    #100; sub = 1; A = 4'b0101; B = 4'b1110; // 5 - (-2)
    #100; sub = 1; A = 4'b1101; B = 4'b0101; // -3 - 5
    #100; sub = 1; A = 4'b0101; B = 4'b1101; // 5 - (-3)
    #100; sub = 1; A = 4'b1001; B = 4'b0010; // -7 - 2
    #100;
  end
endmodule
```