

# Intro to Digital Design

## Project Tips, Memory

**Instructor:** Justin Hsia

**Teaching Assistants:**

Caitlyn Rawlings

Emilio Alcantara

Naoto Uemura

Donovan Clay

Joy Jung

# Relevant Course Information

## ❖ Lab 8 – Project

- 2 weeks to work on it – don't wait to start!
  - Reports due Friday, March 8 @ 11:59 pm
  - Lab 8 check-in due next week during demo slot
  - Demos can be scheduled outside of the lab hours by making a *private* post on Ed Discussion
- 8 suggested projects, or get your own approved
  - **Most use LED breakout board – included in your lab kit**
  - Not all are worth the same number of points (“full credit” is 150)
  - Think carefully about what you want to tackle  
(*e.g.*, complex FSM, LED board, multiple “clock speeds”)
- Bonus points for adding cool features and early finish
  - Up to 20 points for extra features; up to 10 points for early finish

# Practice




❖ Implement a **counter** that goes through the state sequence

000 → 001 → 011 → 010 → 110 → 111 → 101 → 100 → 000 → ...

- Include an Enable signal to count
- Include a Reset signal (to 000)

P <sub>2</sub>	P <sub>1</sub>	P <sub>0</sub>	N <sub>2</sub>	N <sub>1</sub>	N <sub>0</sub>
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

   - $N_2 = P_2 P_0 + P_1 \overline{P_0}$
- $N_1 = \overline{P_2} P_0 + P_1 \overline{P_0}$
- $N_0 = \overline{P_2} \overline{P_1} + P_2 P_1$



# Outline

- ❖ **Project Tips**
  - “Multiple clocks”
  - Verilog generate
  - SystemVerilog Arrays
- ❖ Computer Components
  - Memory/RAM

# Comparator (Multibit)

- ❖ Equality ( $A == B$ )
  - XNOR corresponding bits of A and B, then AND together
  - NOR all bits of  $A-B$
- ❖ Comparator ( $A < B$ ,  $A == B$ ,  $A > B$ )
  - $A < B$ : MSB of  $A-B$
  - $A == B$ : NOR of all bits of  $A-B$
  - $A > B$ : NOT of MSB of  $A-B$

# “Multiple Clocks” Via Counters

- ❖ The `clock_divider` module is a 32-bit up counter
  - All output bits update at same time ( $t_{C2Q}$ )
  - Output bits get us powers of 2 differences in speed
- ❖ Still want to use *single* clock for all state elements
  - We will instead control actions using the Enable signal
- ❖ Use comparator on a counter as Enable signal
  - May need to feedback into Reset signal on counter

# Advanced Verilog: generate

- ❖ Condense your code using loops and conditionals
  - Often used with `assign` and module instantiation
- ❖ Details:
  - Loop variables must be declared as `genvar` outside of `generate` statement
  - Block statements (`for/if`) *must* have `begin` and `end` and be labeled

```
genvar <loop_var>;

generate
  for(<init>;<cond>;<update>) begin : <label>
    // do something with loop_var
  end
endgenerate
```

# Add/Sub in Verilog (parameterized)

## ❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic          OF, CF;
  output logic [N-1:0] S;
  input  logic          sub;
  input  logic [N-1:0] A, B;
  logic  [N-1:0] D;      // possibly flipped B
  logic          C2;     // second-to-last carry-out

  always_comb begin
    D = B ^ {N{sub}}; // replication operator
    {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
    {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
    OF = CF ^ C2;
  end
endmodule
```



# Add/Sub in Verilog (generate)

- ❖ Generate produces N fulladd modules

```
module addNgen #(parameter N=32) (OF, CF, S, sub, A, B);  
    output logic OF, CF;           // overflow and carry flags  
    output logic [N-1:0] S;       // sum output bus  
    input  logic sub;             // subtract signal  
    input  logic [N-1:0] A, B;    // input busses  
    logic [N:0] C;                // carry signals between modules
```

- ❖ Reminder: `module fulladd (cout, s, cin, a, b);`

# SystemVerilog Arrays


- ❖ A *bus* is known as a *vector* or **packed array**
  - e.g., **logic** [31:0] divided\_clocks;
  - Can only be made of single bit datatypes
- ❖ “Regular” array syntax is known as an **unpacked array**
  - e.g., **logic** an\_unpacked\_array[4:0];
  - Can be made of any datatype
- ❖ **Multidimensional arrays** can be combinations of packed and unpacked dimensions
  - e.g., **logic** [3:0] two\_D\_array[4:0];
  - Accessed left to right, starting with unpacked dimensions

# Outline

- ❖ Project Tips
  - “Multiple clocks”
  - Verilog generate
  - SystemVerilog Arrays
- ❖ **Computer Components**
  - **Memory/RAM**
 
# Five Components of a Computer

- ❖ Components a computer needs to work:
  - Control
  - Datapath
  - Memory
  - Input
  - Output




# Executing an Instruction

- ❖ Depends on ISA, but generally:
    - Instruction Fetch
    - Instruction Decode
    - Data Fetch
    - Computation
    - Store Result
  
  - ❖ Basic Datapath Components (idealized)
    - Register File
    - Memory Management Unit
    - Arithmetic Logic Unit (ALU)
    - Routing Elements
- } Next lecture
- } Today
- } Previous two lectures
 
# Storage Element: Idealized Memory

- ❖ Memory (idealized)
  - One input bus: **DataIn**
  - One output bus: **DataOut**
  - In reality, often combined



- ❖ Memory access:
  - Read: Data at **Address** placed on **DataOut**
  - Write: If **WriteEnable** = 1, **DataIn** written to **Address**
- ❖ For N addresses, need **Address** input to be  $(\log_2 N)$ -bits wide
- ❖ Clock (**CLK**) is a factor ONLY during write operation

# 8x4 RAM



WriteEnable

In3

In2

In1

In0

 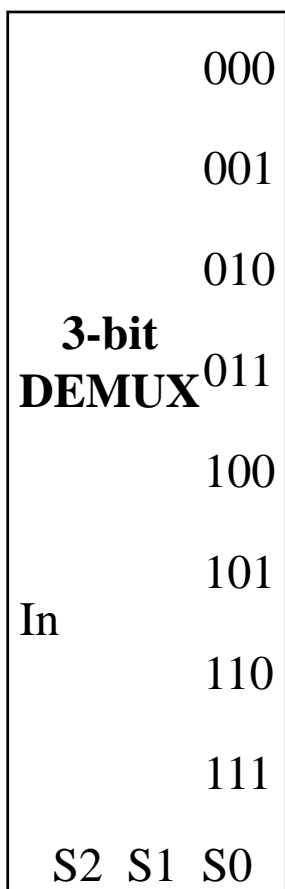

A2  
A1  
A0

Out3


Out2

Out1

Out0
 
# RAM Cell

- ❖ Requirements:
  - Store one bit of data
  - Change data based on input when row is selected
- ❖ Just a controlled register!
  - No need to Reset
  - Use RowSelect as Enable





# Verilog Memories

```
module memory16x8 (data_out, data_in, addr, write, clk);

    output logic [7:0] data_out;
    input  logic [7:0] data_in;
    input  logic [3:0] addr;
    input  logic      write, clk;

    logic      [7:0] mem [15:0]; // array of vectors

    assign data_out = mem[addr];

    always @(posedge clk)
        if (write)
            mem[addr] <= data_in;

endmodule
```