

# CSE 369 QUIZ 1

Name: \_\_\_\_\_

UWNetID: \_\_\_\_\_

**Please do not turn the page until 10:30.**

## Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	
(2) K-map	5	
(3) Waveforms & Verilog	11	
<b>Total:</b>	<b>24</b>	

**Question 1:** Combinational Logic Gates [8 pts]

 - (A) Write out a Boolean expression for the circuit diagram below. No need to simplify. [2 pts]



- (B) Find a minimal implementation of the function below using only **2-input NOR gates**. [6 pts]

$$F = \overline{\overline{A}\overline{B}(C + D)}$$

**Question 2:** Karnaugh Maps [5 pts]


Find the *minimum sum-of-products solution* for the K-map shown below.

		A			
		0	0	0	X
C	1	1	1	X	1
	1	1	X	1	0
	X	0	0	0	0
		X	0	0	0
		B			
		D			

### Question 3: Waveforms & Verilog [11 pts]

For both parts below, consider the following desired truth table and the Verilog simulated testbench waveforms shown below.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

- (A) Identify the time interval(s) where the testbench output does not match the desired functionality. Each horizontal tick represents 5 time units. [3 pts]
- (B) If we know that X and Y are outputs of 2-input logic gates, complete the module Mystery below based on the testbench output. [8 pts]

```

module Mystery (F, A, B, C);
    output F;
    input  A, B, C;
    wire  X, Y;

    _____
    _____

    and G3 (F, X, Y);
endmodule

```