

CSE 369 QUIZ 1

Name: Perry_Perfect

UWNetID: perfect

Please do not turn the page until 11:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	8
(2) K-map	5	5
(3) Waveforms & Verilog	11	11
Total:	24	24

Question 1: Combinational Logic Gates [8 pts]

 
- (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and $\bar{}$ (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts] $F = \overline{(A + C)} \cdot A(B + C)$



$X = \overline{(A + C)} = (A + C)$ [0.5 pt]
 $Y = B + C$ [0.5 pt]
 $Z = \overline{AY}$ [0.5 pt]
 $F = XZ$ [0.5 pt]

- (B) Find a minimal implementation of the function below using only **2-input NAND gates**. We will only accept circuit diagrams. [6 pts]


$F = (\bar{A} + \bar{B})\bar{C} + D$

 

- [2 pt] Valid gate conversion from expression
 [2 pt] DeMorgan's applications (either in expression or gates)
 [2 pt] Conversion of extra NOTs to NANDs

 Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.



$= \bar{B}\bar{D} + BC + \bar{A}BD$

- [2 pt] X choices
 [1 pt each] correct term/grouping
 [-0.5 pt each] smaller grouping used
 [-0.5 pt each] extra grouping included

Question 3: Waveforms & Verilog [11 pts]

- (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module Mystery below. [5 pt]


For both X and Y:

[1 pt] Correct input signals

[1 pt] Correct gate used

Overall:

[1 pt] Correct Verilog syntax

 

```

module Mystery (F, A, B, C);
    output F;
    input A, B, C;
    wire X, Y;

    and G1 (X, A, B); or assign X = A & B;

    nor G2 (Y, B, C); or assign Y = ~(B | C);

    xnor G3 (F, X, Y);

endmodule
    
```

- (B) We only have the 2-input logic gates at right available to us. Given the logic delays shown, draw out the circuit diagram of the *fastest* implementation of the Verilog statement below. [6 pts]

XOR	NAND	NOR
6 ns	8 ns	12 ns

Hint: Build a truth table first.

```

assign F = ~A & (A ^ B);
    
```

A	B	A^B	F
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$F = \bar{A}B$

