

# CSE 369 QUIZ 1

Name: \_\_\_\_\_

UWNetID: \_\_\_\_\_

**Please do not turn the page until 11:40.**

## Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is open book and open notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- You have 20 minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	
(2) K-map	5	
(3) Waveforms & Verilog	11	
<b>Total:</b>	<b>24</b>	

**Question 1: Combinational Logic Gates [8 pts]**

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and  $\bar{\phantom{x}}$  (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]



- (B) Find a minimal implementation of the function below using only **2-input NAND gates**. *We will only accept circuit diagrams.* [6 pts]

$$F = (\overline{\overline{A + B}}) + \bar{C}D$$


**Question 2: Karnaugh Maps [5 pts]**

Find the *minimum sum-of-products solution* for the K-map shown below.

		A				
		X	0	0	0	
		0	1	0	X	
		0	X	1	0	
		1	1	X	1	
C		B				D

**Question 3: Waveforms & Verilog [11 pts]**

 - (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module `Mystery` below. [8 pt]



```

module Mystery (F, A, B, C);
    output logic F;
    input logic A, B, C;
    logic X, Y;

    _____

    _____

    nand G3 (F, X, Y);
endmodule

```

- (B) Given the Verilog module `Circuit` below, assume the logic delays shown. If the values of inputs A and B first become known at  $t = 0$  and output F is unknown at  $t = 0$ , at what time will you know the value of F? [3 pts]

XOR	NOR	NOT
20 ns	8 ns	4 ns

```

module Circuit (F, A, B);
    output logic F;
    input logic A, B;

    assign F = ~(~(A | ~B) | (A ^ B));
endmodule

```

$t =$