

CSE 369 QUIZ 1

Name: Molly Model

Student ID
Number: 1234567

Please do not turn the page until 2:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 (+5) minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	8
(2) K-map	5	5
(3) Waveforms & Verilog	13	13
Total:	26	26

Question 1: Combinational Logic Gates [8 pts]

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and $\bar{}$ (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]




$$F = (\overline{A \cdot B + B}) \cdot (A + \overline{C})$$

- $X = \overline{A \cdot B}$ [0.5 pt]
- $Y = \overline{X + B}$ [0.5 pt]
- $Z = A + \overline{C}$ [0.5 pt]
- $F = Y \cdot Z$ [0.5 pt]

- (B) Find a minimal implementation of the function below using only **2-input NOR gates**. *We will only accept circuit diagrams.* [6 pts]


$$F = (A + B)(\overline{CD})$$

 

- [2 pt] Valid gate conversion from expression
- [2 pt] DeMorgan's applications (either in expression or gates)
- [2 pt] Conversion of extra NOTs to NORs

 Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.




$$= B\overline{D} + \overline{A}\overline{B}C + A\overline{C}\overline{D}$$

or + $A\overline{B}\overline{C}$

- [2 pt] X choices
- [1 pt each] correct term/grouping
- [-0.5 pt each] smaller grouping used
- [-0.5 pt each] extra grouping included

Question 3: Waveforms & Verilog [13 pts]

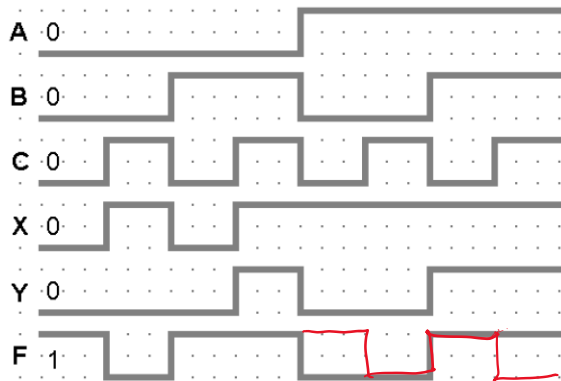- (A) Consider the Verilog simulated test bench waveforms shown. Assume all delays are set to 0. If we know that X and Y are outputs of 2-input logic gates, complete the module Mystery below. [7 pts]



```

module Mystery (F, A, B, C);
    output logic F;
    input logic A, B, C;
    logic X, Y;

    or G1 (X, A, C);
    // or assign X = A | C;

    and G2 (Y, B, X);
    // or assign Y = B & X;

    xnor G3 (F, X, Y);
endmodule

```

The following table will be used for both Part B and Part C:

A	B	C	F	Match?	Tested?
0	0	0	1	Y	Y
0	0	1	0	Y	Y
0	1	0	1	Y	Y
0	1	1	1	Y	N
1	0	0	1	N	Y
1	0	1	0	Y	Y
1	1	0	1	Y	Y
1	1	1	0	N	Y

- (B) The F column shows the intended/desired functionality of the signal F. Complete the Match? column with Y/N to identify whether the waveform above matches the desired functionality. [2 pts]

- (C) A test bench for the Mystery module (with inputs A, B, C) is shown on the right. Complete the Tested? column with Y/N to verify which combinations are currently being tested. [4 pts]

```

module Mystery_tb ();
    logic F, A, B, C;

    initial begin
        A = 1; B = 1; C = 1; #10; XXX
        C = 0; #10; 100
        B = 0; C = 1; #10; 101
        A = 1; #10; 101
        C = 0; #10; 100
        A = 0; C = 1; #10; 001
        C = 0; #10; 000
        B = 1; #10; 010
    end
endmodule

```