

CSE 369 QUIZ 1

Name: Perry_Perfect

UWNetID: perfect

Please do not turn the page until 10:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	8
(2) K-map	5	5
(3) Waveforms & Verilog	11	11
Total:	24	24

Question 1: Combinational Logic Gates [8 pts]

 
- (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and $\bar{}$ (NOT). [2 pts] $F = (\overline{AB + C})(B + \bar{C})$



$X = \overline{AB}$ [0.5 pt]
 $Y = \overline{B + C}$ [0.5 pt]
 $Z = B + \bar{C}$ [0.5 pt]
 $F = YZ$ [0.5 pt]

- (B) Find a minimal implementation of the function below using only **2-input NAND** gates. [6 pts]


$$F = AB + (\overline{C + D})$$

 

- [2 pt] Valid gate conversion from expression
 [2 pt] DeMorgan's applications (either in expression or gate)
 [2 pt] Conversion of extra NOTs to NANDs

 Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.



$$\overline{A}\overline{B} + \overline{B}C + \overline{B}\overline{D}$$

$$= \overline{B}(\overline{A} + C + \overline{D})$$

- [2 pt] X choices: 1, 0, 0, 1
 [1 pt each] correct term/grouping
 [-0.5 pt each] smaller grouping used

Question 3: Waveforms & Verilog [11 pts]


- (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module Mystery below. [8 pt]

For both X and Y:

[2 pt] Correct input signals

[1 pt] Correct gate used

[1 pt] Correct Verilog syntax

 

```

module Mystery (F, A, B, C);
    output F;
    input A, B, C;
    wire X, Y;

    nand G1 (X, A, C); or assign X = ~(A & C);

    or G2 (Y, B, C); or assign Y = B | C;


    and G3 (F, X, Y);
endmodule
    
```

- (B) Given the Verilog module Circuit below, assume that all gates (only 1- and 2-input) have a delay of 30 ns. If the values of inputs A and B first become known at $t = 0$ and output F is unknown at $t = 0$, at what time does F first become known? [3 pts]

```

module Circuit (F, A, B);
    output F;
    input A, B;

    assign F = (~A & B) | (A ^ B);
endmodule
    
```

 

$t = 90 \text{ ns}$