

CSE 369 QUIZ 1

Name: _____

UWNetID: _____

Please do not turn the page until 10:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	
(2) K-map	5	
(3) Waveforms & Verilog	11	
Total:	24	

Question 1: Combinational Logic Gates [8 pts]

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and ¬ (NOT). [2 pts]



- (B) Find a minimal implementation of the function below using only **2-input NAND gates**. [6 pts]

$$F = AB + (\overline{C + D})$$


Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.

		A					
		—	—	—	—		
C		X	0	0	1		D
		1	0	X	0		
		1	X	0	1		
		1	0	0	X		
		B					
		—	—	—	—		

Question 3: Waveforms & Verilog [11 pts]

 - (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module `Mystery` below. [8 pt]



```

module Mystery (F, A, B, C);
    output F;
    input A, B, C;
    wire X, Y;

    _____
    _____

    and G3 (F, X, Y);
endmodule

```

- (B) Given the Verilog module `Circuit` below, assume that all gates (only 1- and 2-input) have a delay of 30 ns. If the values of inputs A and B first become known at $t = 0$ and output F is unknown at $t = 0$, at what time does F first become known? [3 pts]

```

module Circuit (F, A, B);
    output F;
    input A, B;

    assign F = (~A & B) | (A ^ B);

endmodule

```

t =