

# CSE 369 QUIZ 1

**Name:** \_\_\_\_\_  
**Student ID**  
**Number:** \_\_\_\_\_

**Please do not turn the page until 11:30.**

## Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	
(2) K-map	5	
(3) Waveforms & Verilog	11	
<b>Total:</b>	<b>24</b>	

**Question 1: Combinational Logic Gates [8 pts]**

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and  $\bar{\phantom{x}}$  (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]



- (B) Find a minimal implementation of the function below using only **2-input NOR gates**. We will only accept circuit diagrams. [6 pts]

$$F = \overline{(A + B)\overline{\overline{CD}}}$$


**Question 2: Karnaugh Maps [5 pts]**

Find the *minimum sum-of-products solution* for the K-map shown below.

		A				
		<div style="border-top: 1px solid black; width: 100%;"></div>				
X	0	0	0	0		
1	1	1	1	X		D
X	1	0	1	1		
0	0	0	0	X		
		<div style="border-top: 1px solid black; width: 100%;"></div>				
		B				

**Question 3: Waveforms & Verilog [11 pts]**

 - (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module `Mystery` below. [7 pt]



```

module Mystery (F, A, B, C);
    output F;
    input A, B, C;
    wire X, Y;

    _____

    _____

    and G3 (F, X, Y);
endmodule

```

- (B) The snippet below is from a Verilog testbench. Draw out the waveforms. [4 pts]

```

logic [1:0] S;
initial begin
    S = 2'b00; #30; S[1] = 1; #10; S = S | 2'b01; #40;
    S = {S[0] ^ S[1], S[0] & S[1]}; #40;
end

```

