

CSE 369 QUIZ 1

Name: Molly Model

Student ID
Number: 1234567

Please do not turn the page until 12:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 (+5) minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	8
(2) K-map	5	5
(3) Waveforms & Verilog	10	10
Total:	23	23

Question 1: Combinational Logic Gates [8 pts]

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and $\bar{}$ (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]



$$F = \overline{(\overline{A \cdot B}) + (\overline{C} \cdot (B + C))}$$

$$X = \overline{A \cdot B} \quad [0.5 \text{ pt}]$$

$$Y = B + C \quad [0.5 \text{ pt}]$$

$$Z = \overline{C} \cdot Y \quad [0.5 \text{ pt}]$$

$$F = \overline{X + Z} \quad [0.5 \text{ pt}]$$


- (B) Find a minimal implementation of the function below using only **2-input NAND gates**. *We will only accept circuit diagrams.* [6 pts]

$$F = \overline{(\overline{A + B})\overline{C}}$$

[2 pt] Valid gate conversion from expression


[2 pt] DeMorgan's applications (in expression or gates)

[2 pt] Conversion of extra NOTs to NANDs

 

 Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.



$$= BD + AC + \overline{B}\overline{D}$$

[2 pt] X choices


[1pt each] Correct term / grouping

[-0.5pt each] Smaller grouping used

[-0.5pt each] Extra grouping included

Question 3: Waveforms & Verilog [10 pts]

 - (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module `Mystery` below. [7 pts]



```

module Mystery (F, A, B, C);
    output logic F;
    input  logic A, B, C;
    logic      X, Y;

    or  G1 (X, B, C);
    // or assign X = B | C;

    xor G2 (Y, A, C);
    // or assign Y = A ^ C;

    nand G3 (F, X, Y);
endmodule

```

For both X and Y:

[2 pt] Correct input signals

[1pt] Correct gate uses

Overall:

[1 pt] Correct Verilog syntax

- (B) For the Verilog module `FastOrSlow`, assume the logic delays shown. If the values of A and B first become known at $t = 0$ and output F is unknown at $t = 0$, at what time is F first guaranteed to become known? *Remember to include units. The correct time is all that is required, but an incorrect answer can receive partial credit for correctly drawing the circuit diagram.* [3 pt]


NOT	AND	OR
10 ns	25 ns	20 ns

```

module FastOrSlow (F, A, B);
    output logic F;
    input  logic A, B;
    logic      W, X, Y, Z;

    and  G1 (W, A, B);
    not  G2 (X, B);
    or   G3 (Y, A, X);
    and  G4 (Z, W, Y);
    not  G5 (F, Z);
endmodule

```

 

$t = 65 \text{ ns}$