

CSE 369 QUIZ 1

Name: Molly Model

Student ID
Number: 1234567

Please do not turn the page until 12:30.

Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 (+5) minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	8
(2) K-map	5	5
(3) Waveforms & Verilog	13	13
Total:	26	26

Question 1: Combinational Logic Gates [8 pts]

 - (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and $\bar{}$ (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]



$$F = \overline{(A + C) \cdot B + B \cdot C}$$

$$X = A + C \quad [0.5 \text{ pt}]$$


$$Y = X \cdot \bar{B} \quad [0.5 \text{ pt}]$$

$$Z = \bar{B} \cdot C \quad [0.5 \text{ pt}]$$

$$F = \overline{Y + Z} \quad [0.5 \text{ pt}]$$

 - (B) Find a minimal implementation of the function below using only **2-input NAND gates**. *We will only accept circuit diagrams.* [6 pts]

$$F = \overline{AB} + \overline{(\bar{C} + D)}$$




[2 pt] Valid gate conversion from expression

[2 pt] DeMorgan's applications (either in expression or gates)

[2 pt] Conversion of extra NOTs to NORs

 Question 2: Karnaugh Maps [5 pts]

Find the *minimum sum-of-products solution* for the K-map shown below.



$$= \bar{C}\bar{D} + \bar{A}C + BCD$$

[2 pt] X choices


[1 pt each] correct term/grouping

[-0.5 pt each] smaller grouping used

[-0.5 pt each] extra grouping included

Question 3: Waveforms & Verilog [13 pts]

 - (A) Consider the Verilog simulated testbench waveforms shown. Assume all delays are set to 0. If we know that X and Y are outputs of 2-input logic gates, complete the module Mystery below. [7 pts]



```

module Mystery (F, A, B, C);
    output logic F;
    input  logic A, B, C;
    logic      X, Y;

    nor G1 (X, B, C);
    // or assign X = ~(B | C);

    xor G2 (Y, A, X);
    // or assign Y = A ^ X;

    and   G3 (F, X, Y);
endmodule

```

- (B) A testbench for the Mystery module (with inputs A, B, C) is shown below. Which input combinations are NOT currently being tested? You may not need all of the blanks. [3 pts]

```

module Mystery_tb ();
    logic F, A, B, C;

    initial begin

        A = 0; B = 0; C = 0; #10; // XXX
        C = 1; #10; // 001
        B = 1; #10; // 011
        A = 1; #10; // 111
        C = 0; #10; // 110
        A = 0; C = 1; #10; // 011
        C = 0; #10; // 010
        B = 0; #10; // 000

    end
endmodule

```

Missing combinations:

1. {A, B, C} = 3'b100;
2. {A, B, C} = 3'b101;
3. {A, B, C} = 3'b___;
4. {A, B, C} = 3'b___;

- (C) Complete the SystemVerilog code below that creates a bus called my_bus that is a collection of various DE1-SoC inputs and outputs. Specifically, it should contain the first (*i.e.*, 0th) of each of SW, KEY, LEDR, and HEX in that order from most significant to least significant.

Hint: How many bits in a HEX display? [3 pt]

```

_logic [9:0]_ my_bus;

assign my_bus = _{ SW[0], KEY[0], LEDR[0], HEX0 }_____;

```