

CSE 369 QUIZ 3

Name: Molly Model

UWNetID: model

Please do not turn the page until 11:30.

Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put a box around final answers.
- The quiz is open book and open notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- You have 40 minutes to complete this quiz.

Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Counters	12	12
(2) Shift Registers	9	9
(3) Polynomials	11	11
Total:	32	32

Question 1: Counters [12 pts]

Implement a counter that goes through the following state sequence: **000** → **010** → **011** → **101** → **000** → ... using a *minimal number of 2-input logic gates*.

(A) Complete the truth table below. [3 pts]. [-0.25 pt per error]

PS ₂	PS ₁	PS ₀	NS ₂	NS ₁	NS ₀
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	X	X	X
1	0	1	0	0	0
1	1	0	X	X	X
1	1	1	X	X	X

(B) Complete the K-maps below and find the *minimum sum-of-products solutions*. [6 pts]

NS ₂	00	01	11	10
0	0	0	X	X
1	X	1	X	0

NS ₁	00	01	11	10
0	1	1	X	X
1	X	0	X	0

NS ₀	00	01	11	10
0	0	1	X	X
1	X	1	X	0

$$NS_2 = \overline{PS_2}PS_0 \text{ OR } NS_2 = PS_1PS_0$$


$$NS_1 = \overline{PS_0}$$

$$NS_0 = PS_1$$

[1 pt per K-map] Filled in correctly [1 pt per expression] Grouping


(C) Draw your minimal logic circuit. [3 pts]

[1 pt per circuit]

 


 Question 2: Shift Registers [9 pts]

We are using a 3-bit LFSR as a pseudo-random number generator, but we only have a 2-input XNOR gate available. Assume we start in state 000.



 (A) Draw out the full state transition diagram (i.e. include ALL states) for this LFSR below: [4 pts]



[0.5 pt per transition] Correct states/transitions

[-0.25 pt] No reset signal

(B) What is/are the sink state(s) of this LFSR? [1 pt]

Sinks(s): 111

(C) Complete the Verilog implementation below. [4 pts]

```

module LFSR (Q, enable, reset, clk);
  input  logic enable, reset, clk;
  output logic [2:0] Q;

  always_ff @(posedge clk)
  if (reset)
    Q <= ___3'b000___;
  else if (enable)
    Q <= { _~(Q[1] ^ Q[0])_, ___Q[2]___, ___Q[1]___ };

endmodule

```

Question 3: Polynomials [11 pts]

A third degree polynomial or a cubic function is a function of the form $F_3 = a_0 + a_1x + a_2x^2 + a_3x^3$.


Hint: Horner's method rewrites a polynomial as:

$$F_n = a_0 + x(a_1 + x(a_2 + x(a_3 + \dots + x(a_{n-1} + xa_n) \dots)))$$

The coefficients and x are n bits wide. Assume $t_{ADD} = 50$ ps, $t_{MULT} = 100$ ps, $t_{C2Q} = 30$ ps. The following logic blocks will be needed (w is the width of the bus):



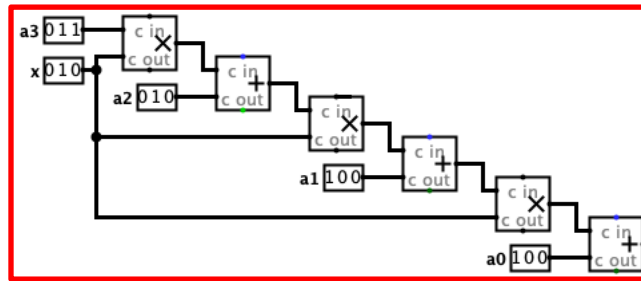
- (A) Implement a *minimal* combinational logic circuit using only adders and multipliers that computes a cubic polynomial of n bit numbers. [6 pts] [1 pt per logic block]



- (B) What is the delay through your combinational logic circuit? [1pt]

___450___ ps

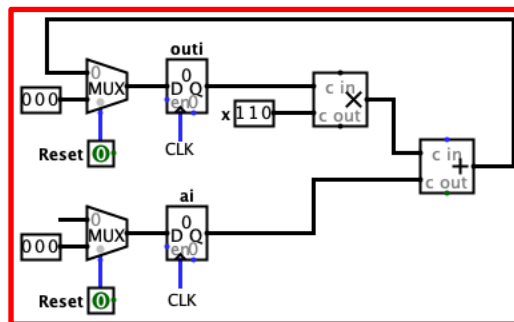- (C) Implement a *minimal* sequential logic circuit that computes a cubic polynomial. Assume that an n bit coefficient is available every clock cycle and that your registers start at 0. You can specify the order that the coefficients arrive. Again, you may only use adders and multipliers in addition to the 2 registers shown. Note: the 2 registers have a reset line to set them to 0. [3 pts] [2 pts] adder, [1 pt] mult



- (D) What is the delay through the critical path of your sequential logic circuit? [1pt]

___180___ ps