

# CSE 369 QUIZ 3

Name: \_\_\_\_\_ **SOLUTIONS** \_\_\_\_\_  
Student ID Number: \_\_\_\_\_ **123456789** \_\_\_\_\_

**Please do not turn the page until 11:30.**

## Instructions

- This quiz contains 7 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 60 minutes to complete this quiz.

## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Lightning Round	16	
(2) Analysis & Design	15	
(3) Module Design	15	
<b>Total:</b>	<b>46</b>	

### Question 1: Lightning Round [16 pts]

- (A) True or False: The number of rows in a truth table depends only on the number of inputs to the logic function. [1 pts]

True

- (B) Name one of the 2-input “universal” logic gates discussed in class. [1 pts]

NAND or NOR

- (C) A K-map is used to perform logic simplification and generates what type of two-level Boolean expression? [1 pts]

Sum of Products

- (D) True or False: The input of a positive edge-triggered DFF must remain stable from the positive edge of the clock through the CLK-to-Q delay. [1 pts]

False

- (E) True or False: In a Synchronous Digital System (SDS), we only need to know the setup time, hold time, and CLK-to-Q delay constants to ensure correct behavior. [1 pts]

False

- (F) True or False: In a circuit where all inputs and outputs are registered, the *critical path* is the path with the longest delay between any two registers in the circuit. [1 pts]

True

- (G) True or False: A synchronous reset signal causes the value of the register to be reset when the reset signal is asserted. [1 pts]

False

- (H) Sequential logic (e.g., registers) timing must not violate the setup and hold time constraints within a clock period. Write out the inequality used to verify the hold and setup time constraints. [2 pts]

$$t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$$

(I) Finite State Machines (FSMs), as studied in this class (Mealy machines) are defined by what three items? [3 pts]

- **A set of states,  $S$**
- **An initial state,  $S_0$**
- **A transition function that maps from the current input and current state to the next state and output**

(J) How many state bits are required to represent a state machine with  $S$  states? [1 pts]

**ceiling( $\log_2(S)$ )**

(K) What computational building block or routing element can be used to implement arbitrary N-input logic functions? [1 pts]

**Mux / multiplexor**

(L) An LFSR (Linear Feedback Shift Register) often uses a two-input logic gate to produce the feedback input in the shift register. How does the choice of logic gate and its input bits affect the output sequence of the LFSR? [2 pts]


**Sub-optimal choice results in an LFSR that produces a shorter and/or less random output sequence.**

## Question 2: Analysis & Design - TMR [15 pts]


*Triple Modular Redundancy (TMR)* is a common technique for making a circuit fault tolerant. A TMR-based circuit performs the same computation in three identical and independent circuits before outputting a result that is agreed upon by at least two of the three circuits (i.e., the majority result).

 **Part 1** What is the minimum clock period achievable by the non-TMR circuit below? The Inputs and Results blocks are n-bit registers. [3 pts]

Assume  $t_{setup} = 10\text{ ns}$ ,  $t_{hold} = 5\text{ ns}$ ,  $t_{c2Q} = 8\text{ ns}$ , and  $t_{ALU} = 50\text{ ns}$ .



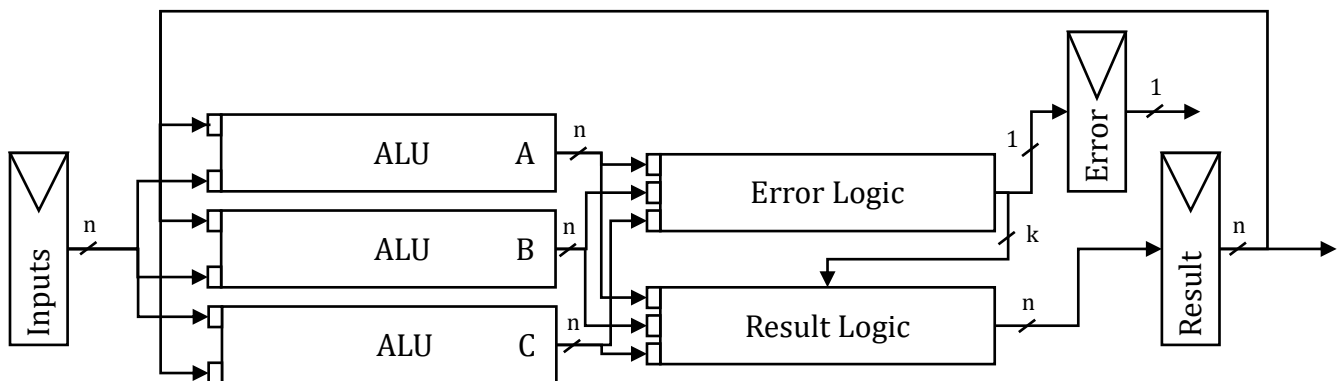**Part 2** The circuit diagram below shows the circuit above with TMR added. The Error Logic block takes n-bit ALU results A, B, and C as inputs and produces two outputs: a 1-bit Error signal that is captured by a register and a k-bit signal that is sent to the Result Logic block. The Result Logic block takes the k-bit signal from the Error Logic block and ALU results A, B, and C as inputs and produces the n-bit Result signal that is captured into a register.



What is the minimum clock period achievable by the TMR circuit above? The Inputs and Results blocks are registers. [4 pts]

Assume  $t_{setup} = 10\text{ ns}$ ,  $t_{hold} = 5\text{ ns}$ ,  $t_{c2Q} = 8\text{ ns}$ ,  $t_{ALU} = 50\text{ ns}$ ,  $t_{Error} = 12\text{ ns}$ ,  $t_{Result} = 15\text{ ns}$ .



$$t_{c2Q} + t_{ALU} + t_{Error} + t_{Result} + t_s$$

$$= 8 + 50 + 12 + 15 + 10 = 95$$

95 ns

 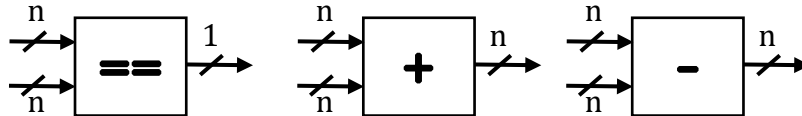**Part 3** The TMR-based design in Part 2 has an Error Logic block to detect a failure in one of the ALUs. The block takes ALU results A, B, and C as inputs and outputs a **1-bit Error signal**, which has a value of 1 if the result of any ALU does not match the result of any other ALU. Assume the ALUs produce **n-bit** results. **Implement the Error Logic block's Error Bit functionality from the TMR circuit in Part 2 (draw the circuit diagram).** [8 pts]

You can freely use 2:1 muxes, 1:2 demuxes, 2- or 3-input logic gates, the constants **0** and **1**, and the following logic blocks:



### Question 3: Module Design – Up/Down Counter [15 pts]

An n-bit Up/Down Counter is a counter that supports both increment and decrement operations.

The Up/Down Counter has the following interface:

- **up** (input, 1-bit): increments counter by 1 when raised
- **down** (input, 1-bit): decrements counter by 1 when raised
- **count** (output, n-bits): current value of counter
- **clock** (input): clock signal for sequential logic
- **reset** (input, 1-bit): synchronous reset, resets counter to 0 when raised

**reset** has priority over **up** and **down**, and the **up** and **down** signals may be raised at the same time.

**Part 1** Complete the following table describing the functionality of the Up/Down Counter. **next count** is the next value of the counter. The current count is given by the variable C. You may use the values 0, 1, and X (logical don't care), along with the variable C in expressions in the table. [5 pts]

*Note:* There may be more rows than are required to fully specify the functionality.

count	reset	up	down	next count
C	1	X	X	0
C	0	0	0	C
C	0	0	1	C-1
C	0	1	0	C+1
C	0	1	1	C
C				
C				
C				

**Part 2 Implement the Up/Down Counter described above (draw the circuit diagram).** You can freely use 4:1 and 2:1 muxes, 1:2 and 1:4 demuxes, 2-input logic gates, the constants **0** and **1**, and the logic blocks given below. The Reg block is a collection of **n** 1-bit DFF's that share the same clock and collectively hold an n-bit vector. *Clearly label all five of the module's interface signals in your circuit diagram.* [10 pts]

