

# CSE 369 QUIZ 3

Name:   Perry\_Perfect  

UWNetID:   1234567  

**Please do not turn the page until 10:30.**

## Instructions

- This quiz contains 4 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 35 minutes to complete this quiz.

## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

| Question             | Points    | Score     |
|----------------------|-----------|-----------|
| (1) Counters         | 12        | 12        |
| (2) Shift Registers  | 11        | 11        |
| (3) Routing Elements | 9         | 9         |
| <b>Total:</b>        | <b>32</b> | <b>32</b> |

### Question 1: Counters [12 pts]

Implement a counter that goes through the following state sequence: **000** → **111** → **110** → **101** → **001** → 000 → ... using a *minimal number of 2-input logic gates*.

| PS <sub>2</sub> | PS <sub>1</sub> | PS <sub>0</sub> | NS <sub>2</sub> | NS <sub>1</sub> | NS <sub>0</sub> |
|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|
| 0               | 0               | 0               | 1               | 1               | 1               |
| 0               | 0               | 1               | 0               | 0               | 0               |
| 0               | 1               | 0               | X               | X               | X               |
| 0               | 1               | 1               | X               | X               | X               |
|                 | 0               | 0               | X               | X               | X               |
| 1               | 0               | 1               | 0               | 0               | 1               |
| 1               | 1               | 0               | 1               | 0               | 1               |
| 1               | 1               | 1               | 1               | 1               | 0               |

PS<sub>2</sub> / PS<sub>1</sub> PS<sub>0</sub>

| NS <sub>2</sub> | 00 | 01 | 11 | 10 |
|-----------------|----|----|----|----|
| 0               | 1  | X  | 1  | X  |
| 1               | 0  | X  | 1  | 0  |

$$NS_2 = \overline{PS_0} + PS_1$$



| NS <sub>1</sub> | 00 | 01 | 11 | 10 |
|-----------------|----|----|----|----|
| 0               | 1  | X  | 0  | X  |
| 1               | 0  | X  | 1  | 0  |

$$NS_1 = PS_0 \text{ xnor } PS_1$$

most credit given for  $NS_1 = PS_0 PS_1 + \overline{PS_0} \overline{PS_1}$

| NS <sub>0</sub> | 00 | 01 | 11 | 10 |
|-----------------|----|----|----|----|
| 0               | 1  | X  | 1  | X  |
| 1               | 0  | X  | 0  | 1  |
 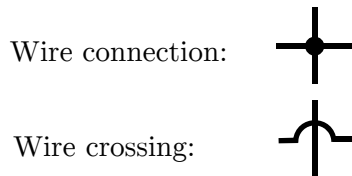
$$NS_0 = \overline{PS_0} + PS_2 \overline{PS_1}$$



## Question 2: Shift Registers [11 pts]

We have a 4-bit linear feedback shift register (LFSR) that goes through the following state sequence: 0000 → 0001 → 0010 → 0101 → 1011 → ...

- (A) Circle one: This LFSR is shifting bits to the **LEFT** / **RIGHT**. [1 pt]
- (B) The bit that is shifted in is a function of two of the LFSR bits. We number the bits starting from 0 increasing from right to left (like standard binary). What is the name of the gate being used and which two bits are its inputs? [6 pt]

|       |                               |
|-------|-------------------------------|
| Gate: | <b>XNOR</b>                   |
| Bits: | <b>__2__</b> and <b>__0__</b> |

From the first transition, we see that we are shifting left (shifting in on the right) and that  $\text{gate}(0,0) = 1$ . The second transition tells us that  $\text{gate}(0,1) = 0$  and that one of the bits is bit 0 (far right). All of the named two-input gates are associative, so  $\text{gate}(1,0) = \text{gate}(0,1) = 0$ . The third transition narrows the options for the 2<sup>nd</sup> tap to bit 3 or bit 2. The fourth transition indicates that  $\text{gate}(1,1) = 1$  and the 2<sup>nd</sup> tap must be bit 2. Looking at the truth table, the gate is actually XNOR.

- (C) Complete the Verilog code below to implement this LFSR. Feel free to use “`state[i] ? state[j]`” to indicate the correct answer to part B. [4 pt]

```
module LFSR (state, shift, reset, clk);
  output reg [3:0] state;
  input          shift, reset, clk;

  always @(posedge clk) begin
    if ( _reset_ )
      state <= _4'b0000_;
    else if ( _shift_ )
      state <= _ { state[2:0], state[i] ? state[j] } _;
  end
endmodule
```


### Question 3: Routing Elements [9 pts]

Implement a circuit that computes the **factorial function**  $n! = n \cdot (n-1)!$ . Note that it will take  $n$  clock cycles to compute  $n!$  and we will let it run infinitely (*no stop condition*).

**Note 1:** Both registers (after a Reset) start with value 0. Make sure that your circuit doesn't get stuck at the value 0. **Hint:** what's the title of this problem?

**Note 2:** Make sure that your  $n$  and  $n!$  bus values line up properly (other than  $0!$  and  $0$ ).

 Assume you can freely use gates and routing elements discussed in class plus the constants **0** and **1** and the following logic blocks:



**Other working alternatives exist:**

- Instead of the MUX, use an adder with the output of the comparator (though in reality we would need a zero-extender to match bit widths).

