

CSE 369 QUIZ 3

Name: Perry_Perfect

UWNetID: perfect

Please do not turn the page until 10:40.

Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put your final answers in the boxes and blanks provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 35 minutes to complete this quiz.

Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Building Blocks	12	12
(2) Shift Registers	9	9
(3) Filter	11	11
Total:	32	32

Question 1: Building Blocks [12 pts]

In Lab 5, one landing light sequence (left-to-right) was **100** → **010** → **001** → 100 → ...
 Implement this sequence as a **counter** with **Reset** and **Enable** signals using a *minimal number of logic gates plus routing elements* discussed in class. Reset to the **100** state.

- Make sure you label the corresponding selector bits for ports of routing elements.
- Assume the clock inputs are connected properly for you.

PS ₂	PS ₁	PS ₀	NS ₂	NS ₁	NS ₀
0	0	0	X	X	X
0	0	1	1	0	0
0	1	0	0	0	1
0	1	1	X	X	X
1	0	0	0	1	0
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	X	X	X

Handwritten Karnaugh maps for NS bits:

NS₂ (P₁P₀):

	00	01	11	10
0	X	1	X	0
1	0	X	X	X

NS₁ (P₂):


	00	01	11	10
0	X	0	X	0
1	1	X	X	X

NS₀ (P₂):

	00	01	11	10
0	X	0	X	1
1	0	X	X	X

Handwritten equations:
 NS₂ = PS₀
 NS₁ = PS₂
 NS₀ = PS₁


Reset	Enable	PS
0	0	PS
0	1	NS
1	0	100
1	1	100

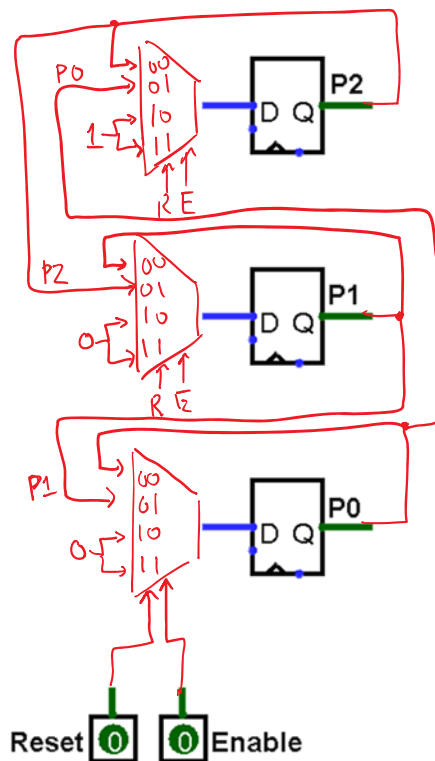

Question 2: Shift Registers [9 pts]

- (A) We are designing a 3-bit LFSR to use as a pseudo-random number generator, but we only have a 2-input NAND gate available. Assuming we start in state **000**, which state bit (q_2 or q_1) should we connect along with q_0 to the NAND gate in order to get the longest possible cycle? What is the length of the cycle we end up in? [5 pt]

a	b	NAND
0	0	1
1	0	1
1	1	0

 

Bits:	<u>q1</u> and q0
Cycle length:	5

bits 2 & 0: 000 → 100 → 110 → 111 → 011 → 101 → 010

bits 1 & 0: 000 → 100 → 110 → 111 → 011 → 001

- (B) The Verilog code below is supposed to implement an *enabled* version of the LFSR above with bits q_2 and q_1 connected to the NAND gate. Find errors in the code and rewrite the offending lines in the boxes. [4 pt]

```

module LFSR (Q, enable, reset, clk);
  input      enable, reset, clk;
  output [2:0] Q;

  always_ff @(posedge clk)
    if ( reset )
      Q <= 3'b000;
    else if ( enable )
      Q = { ~(Q[2] ^ Q[1]), Q[2], Q[0] };

endmodule



```

- | |
|--|
| 1) output reg [2:0] Q; |
| 2) Q <= { ~(Q[2] & Q[1]), Q[2], Q[1]}; |

Question 3: Filter [11 pts]

A **boxcar** (or moving average) **filter** computes the average of the last k samples and can be used to smooth out sudden input spikes (*i.e.* a low-pass filter).

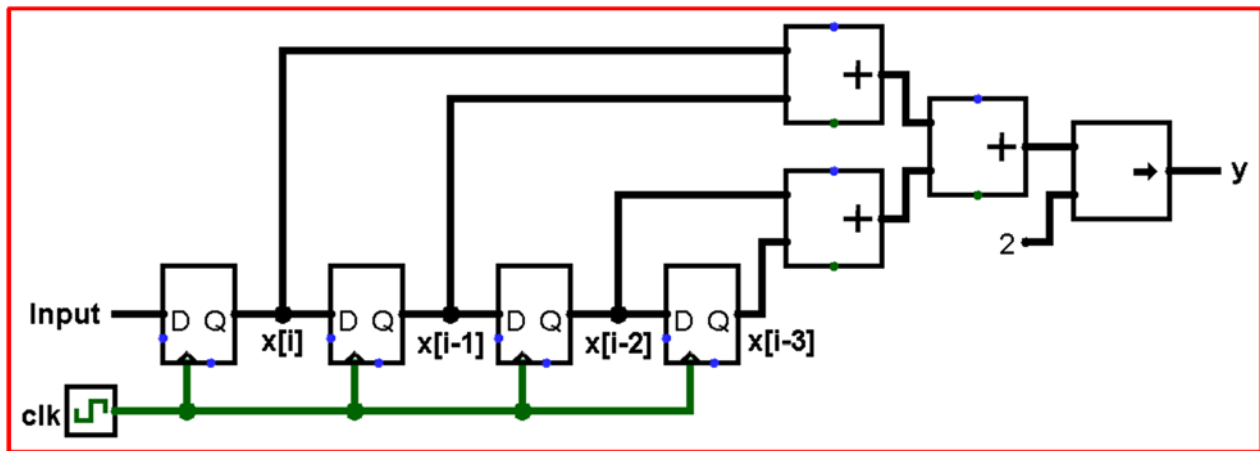 - (A) Draw a circuit below that computes the moving average of the last 4 inputs, *i.e.* $k = 4$ $y_i = (x_i + x_{i-1} + x_{i-2} + x_{i-3}) / 4$, for a signal x , where x_{i-1} is the value of x_i from the previous clock cycle and so on. The given register is there for synchronization; you should *not* connect anything directly to Input. You can freely use registers, constants, and the following logic blocks: [8 pts]



An alternative solution would be to shift all signals first before summing them together (6 logic blocks total).

- (B) Let $t = 0$ be a rising edge of the clock with the signal x_0 on the Input bus. If the clock period is 100 ps, $t_{C2Q} = 10$ ps, $t_{add} = 20$ ps, and $t_{shift} = 5$ ps, at what time will y_3 be computed (*i.e.* at what time will y_3 's correct value first be known)? *Include units!* [3 pts]

$t_{y_3} = 355 \text{ ps}$

It takes 3 clock cycles *after* $t = 0$ for x_0 to appear on the output of the last register (the bus $x[i-3]$ in the diagram above). After 3 clock triggers, it then takes $t_{C2Q} + 2 * t_{add} + t_{shift}$ for y_3 to be computed. So in total: $3 * t_{period} + t_{C2Q} + 2 * t_{add} + t_{shift} = 355$ ps.

Note: The alternative solution described in part A results in the same answer.

Note: If you had an incorrect solution in part A, then you were given credit based on your solution, as long as it had at least 3 additional registers.