

CSE 369 QUIZ 3

Name: _____

UWNetID: _____

Please do not turn the page until 10:40.

Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put your final answers in the boxes and blanks provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 35 minutes to complete this quiz.

Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Building Blocks	12	
(2) Shift Registers	9	
(3) Filter	11	
Total:	32	

Question 1: Building Blocks [12 pts]

In Lab 5, one landing light sequence (left-to-right) was **100** → **010** → **001** → 100 → ...
 Implement this sequence as a **counter** with **Reset** and **Enable** signals using a *minimal number* of logic gates plus routing elements discussed in class. Reset to the **100** state.

- Make sure you label the corresponding selector bits for ports of routing elements.
- Assume the clock inputs are connected properly for you.

PS ₂	PS ₁	PS ₀	NS ₂	NS ₁	NS ₀
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

NS₂ 00 01 11 10




0				
1				

NS₁ 00 01 11 10

0				
1				


NS₀ 00 01 11 10

0				
1				

   

Question 2: Shift Registers [9 pts]

 - (A) We are designing a 3-bit LFSR to use as a pseudo-random number generator, but we only have a 2-input NAND gate available. Assuming we start in state **000**, which state bit (q_2 or q_1) should we connect along with q_0 to the NAND gate in order to get the longest possible cycle? What is the length of the cycle we end up in? [5 pt]



Bits:

Cycle length:

--

- (B) The Verilog code below is supposed to implement an *enabled* version of the LFSR above with bits q_2 and q_1 connected to the NAND gate. Find errors in the code and rewrite the offending lines in the boxes. [4 pt]

```

module LFSR (Q, enable, reset, clk);
  input      enable, reset, clk;
  output [2:0] Q;

  always_ff @(posedge clk)
    if ( reset )
      Q <= 3'b000;
    else if ( enable )
      Q = { ~(Q[2] ^ Q[1]), Q[2], Q[0] };

endmodule



```

1)	
2)	

Question 3: Filter [11 pts]

A **boxcar** (or moving average) **filter** computes the average of the last k samples and can be used to smooth out sudden input spikes (*i.e.* a low-pass filter).

  - (A) Draw a circuit below that computes the moving average of the last 4 inputs, *i.e.* $k = 4$ and $\mathbf{y}_i = (\mathbf{x}_i + \mathbf{x}_{i-1} + \mathbf{x}_{i-2} + \mathbf{x}_{i-3}) / 4$, for a signal \mathbf{x} , where \mathbf{x}_{i-1} is the value of \mathbf{x}_i from the previous clock cycle and so on. The given register is there for synchronization; you should *not* connect anything directly to Input. You can freely use registers, constants, and the following logic blocks: [8 pts]



- (B) Let $t = 0$ be a rising edge of the clock with the signal \mathbf{x}_0 on the Input bus. If the clock period is 100 ps, $t_{C2Q} = 10$ ps, $t_{add} = 20$ ps, and $t_{shift} = 5$ ps, at what time will \mathbf{y}_3 be computed (*i.e.* at what time will \mathbf{y}_3 's correct value first be known)? *Include units!* [3 pts]

$t_{y3} =$