

CSE 369 QUIZ 3

Name: _____

UWNetID: _____

Please do not turn the page until 11:40.

Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put your final answers in the boxes and blanks provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 50 minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Decoders	12	
(2) Shift Registers	10	
(3) Luhn Algorithm	12	
Total:	34	

 Question 1: Decoders [12 pts]

We are building a small **keypad-to-7seg decoder circuit** in two parts. The keypad is 4 buttons arranged in a square. The signals C_1 , C_0 , R_1 , and R_0 are high (1) only if a button in the corresponding column or row is being pushed. The 2-bit bus K (K_1 , K_0) represents which key is recognized (in binary). The Valid signal (V) is high when at least one key is being pressed.




(A) Complete the truth table. We give priority to C_1 and R_1 . [4 pt]

R_1	R_0	C_1	C_0	V	K_1	K_0
0	0	0	0	0		
0	0	0	1	0		
0	0	1	0	0		
0	0	1	1	0		
0	1	0	0	0		
0	1	0	1	1		
0	1	1	0	1		
0	1	1	1	1		
1	0	0	0	0		
1	0	0	1	1		
1	0	1	0	1		
1	0	1	1	1		
1	1	0	0	0		
1	1	0	1	1		
1	1	1	0	1		
1	1	1	1	1		


(B) In the space below, solve for the minimal logical expression (using 2-input gates) for V . [4 pt]

(C) For the 7seg signal numbering and outputs shown above (lit/black = 1), draw the minimal logic for S_4 in terms of V , K_1 , and K_0 . All signals should be off when $V = 0$. [4 pt]

 

 Question 2: Shift Registers [10 pts]

We are using a 3-bit LFSR as a pseudo-random number generator by connecting q_1 and q_0 to a 2-input NOR gate. Assume we start in state **011**.




- (A) Circle one: This LFSR (look at Q) is shifting bits to the **LEFT** / **RIGHT**. [1 pt]
- (B) How many distinct states do we end up visiting? What is the length of the cycle we end up in? [4 pt]

States visited:

Cycle length:

- (C) Modify the LFSR to add **Enable** and **Load** signals and draw the circuit diagram below using *logic gates* and *routing elements* discussed in class. Give priority to Load. [5 pt]
- Make sure you label the corresponding selector bits for ports of routing elements.
 - Assume the clock inputs are connected properly for you.

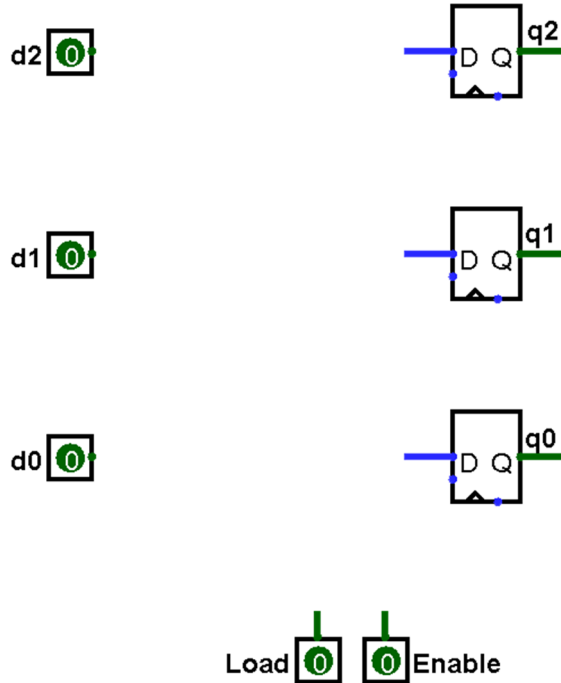

Question 3: Luhn Algorithm [12 pts]

The Luhn algorithm is a “mod 10” formula used for validation of decimal numbers (like credit cards) that uses a “check digit” in the rightmost position. The validation algorithm is as follows:


1. From right to left, double every *second* digit.
2. Sum all of the *digits*.
3. The number is valid if the sum % 10 = 0, invalid otherwise.

Example:

Digits:	$d_3 = 9$	$d_2 = 7$	$d_1 = 6$	check = 1
Double every other:	18	7	12	1
Sum digits:	9	7	3	1

= 20, so 9761 is *valid* ✓

 Here we will implement a Luhn verifier for 4-digit numbers. You can freely add **registers**, **constants**, and the following **logic blocks** (with specified combinational delays):



- (A) Using these parts, complete the *fastest* 4-digit Luhn verification circuit below. Assume the clock inputs are connected properly for you. [7 pts]



- (B) What is the minimum value of the bus width n for this circuit? [2 pt]

$n_{\text{min}} =$

- (C) Assume $t_{\text{hold}} = 10 \text{ ps}$, $t_{\text{setup}} = 40 \text{ ps}$, $t_{\text{C2Q}} = 70 \text{ ps}$ and $t_{\text{comparator}} = 55 \text{ ps}$. How long after a clock trigger does your circuit from Part A take to compute the final value of Valid? [3 pt]

ps